
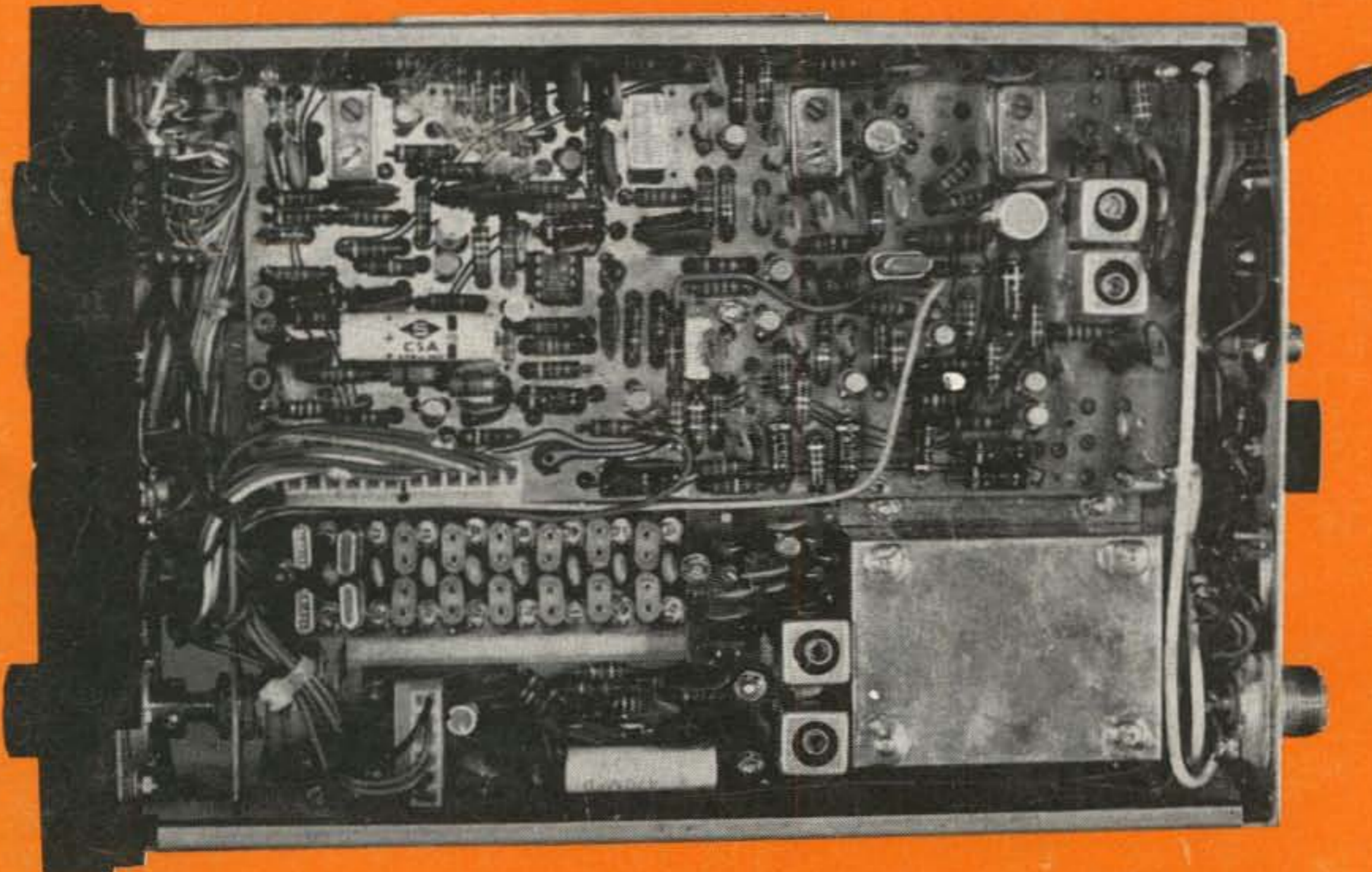


73

magazine for radio amateurs

\$1.00
JUNE 1974

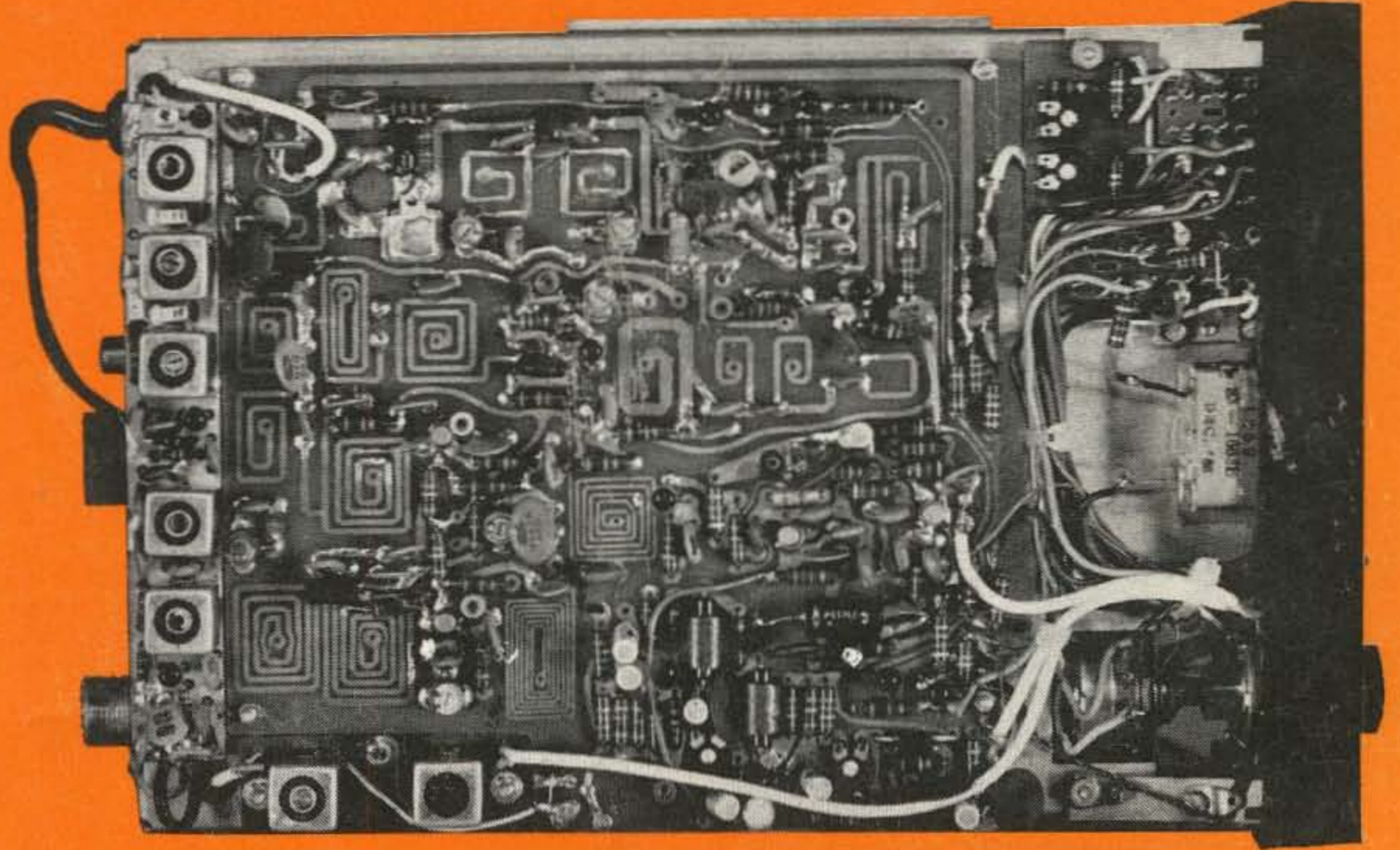

new

HUSTLER[®]

the real performer! specifically for repeater

...or any TWO-METER FIXED STATION OPERATION

With **6** db—
db—
db—

- Gain compared to ½ wave dipole
- FCC accepted for repeater application
- Based on EIA Standard RS-329

mechanical

- Vertical element—117" long, 1-1/8" telescopic to 3/8" OD high strength aluminum
- Radials—four, 21" x 3/16" OD aluminum rod
- Connector—SO-239
- Wind load—26 pounds at 100 mph.
- Wind survival—100 mph.
- Completely self-supporting
- Mounting—fits vertical pipe up to 1-3/4" OD


The gain you gain—you gain transmitting and receiving—get both with Hustler!

Available from
all distributors
who recognize the best!

electrical

- 6 db. gain over ½ wave dipole
- Omnidirectional radiation pattern
- Maximum radiation—at horizon
- 50 ohm feed impedance
- Field adjustable—140-150 MHz
- SWR at resonance—1.2:1 measured at antenna
- Bandwidth—6 MHz for 2:1 or better SWR
- Power—one kilowatt FM
- Feed—Shunt with D.C. grounding
- Radiator—5/8 wave lower section, ¼ wave phasing, 5/8 wave upper section

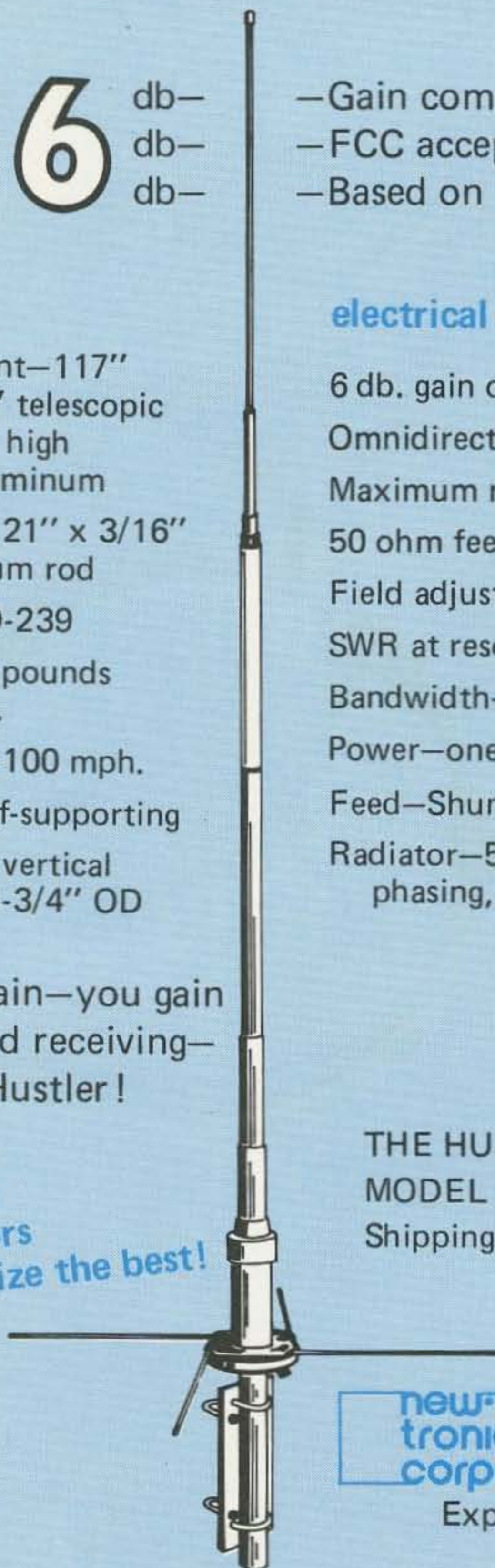THE HUSTLER MASTER GAINER
MODEL G6-144-A
Shipping Wt.: 6.8 lbs. Price: \$52.95



new
tronics
corporation

15800 commerce park drive,
brook park, ohio 44142

Exporter: Roburn Agencies, Inc.,
New York, N.Y.

73

magazine for radio amateurs

165 JUNE 1974

FEATURES

- 2 Never Say Die W2NSD/1
- 4 SSTV Scene
- 6 Letters
- 8 Social Events
- 9 50 MHz
- 10 Repeater Update
- 12 Caveat Emptor
- 13 Looking West
- 14 New Products
- 74 Schematic of the Month
- 76 Amsat
- 76 Traveling Ham
- 77 Circuits — Circuits

EDITORIAL STAFF

Wayne Green W2NSD/1
Yvette Grimes WA8ULU/1

ASSOCIATES

Gus M. Browning W4BPD
Tom DiBiase WB8KZD
Terry Fox WB4JFI
Mike Frye WB8LBP
Dave Ingram K4TWJ
Joe Kasser G3ZCZ/W3
Bill Pasternak WA2HVK/6
Jonathan Tara WB8DBN
Bill Turner WA0ABI

PRODUCTION

Lenore DeLiguori
Lyman DeLiguori
Biff Mahoney
Lynn Panciera-Fraser
Bob Sawyer
David Subka
Barbara Walker

ADVERTISING

Bud Sunkel WA9HLP/1

BUSINESS

Knud E. Keller KV4GG/1

CIRCULATION

Barbara Block
Dorothy Gibson

TRANSPORTATION

Bill Barry
Marshall Raymond

DRAFTING

T. M. Graham W8FKW
Bill Morello
Wayne Peeler K4MVW

CONTENTS

- 17 **Poor Man's Quad** W6SUN
The Adventures of George, The Antenna Maker.
- 27 **Reconciling the Long Squared Quad** W4KAE
Developing a new type antenna.
- 33 **Antenna Load Indicator** W5JJ
Whoops, there goes another swisher!
- 37 **Matching** WB2PAP
The poor little match girl and her coathanger.
- 45 **Remotely Tunable Antenna Coupler** W2EEY
Watch out, Johnson.
- 51 **A Practical Ground System for 160** W6FPO
Makes a difference!
- 55 **Wide-Range Antenna Tuner** VE1TG
For wide range antennas.
- 59 **Old Antennas and New Baluns** W2EEY
Build a double zepp.
- 63 **A Multiband Ground Plane** WA8IYL
10-40 meters.
- 65 **Mod Quad for Frustrated Cliff Dwellers** WN3QBK
The old hidden antenna game.

COVER: The new TPL-220 transceiver — shown at Dayton — has a tunable receiver in addition to crystal FM channels so you can tune the whole band. More and more 220 gear is being made available. Perhaps, with the 220 CB deal a dying, the manufacturers will help us get the band going for amateurs?

73 Magazine is published monthly by 73, Inc., Peterborough, New Hampshire 03458. Subscription rates are \$7 for one year in North America and U.S. Zip Code areas overseas, \$8 per year elsewhere. Two years \$12 and \$13 overseas. Three years, \$15, and \$16 overseas. Second class postage paid at Peterborough, New Hampshire 03458. Phone: During office hours 603-924-3873, other times there is a tape recorder for messages on 603-924-3883. Microfilm edition of 73 available from University Microfilms, Ann Arbor MI 48106. Magnetic tapes available from Science for the Blind, 332 Rock Hill Rd., Bala Cynwyd PA 19004. Entire contents copyright 1974 by 73 Inc., Peterborough, NH 03458.



NEVER SAY DIE

...de W2NSD/I

EDITORIAL BY WAYNE GREEN

GREEN VS IRS

While my complaints about the IRS in the past issues of 73 have been raised mostly on the basis of what they have done to a lot of other people and what powers they have, as well as how this can affect you and what you might do about it, the fact is that the IRS has been working diligently on me — and with some success.

Samuelson said in his interview in *Playboy* (whether you like the pictures or not, it is one of the few magazines powerful enough to be able to speak out against the IRS) that the IRS can, if it wants, convict anyone of criminal fraud on the basis of their tax returns. I can testify that he was not exaggerating.

Readers who dislike my carping, pushing and shoving the ARRL, the FCC and other such seemingly immovable objects, while taking delight in my problems, will ask why I should air my personal troubles in the magazine and thus offend them. The answer is simple — what happened to me was no more personal than polio or cancer — it can (and does) happen to anyone. It *is* something to be concerned about.

Readers who are able to look at the long run — the things that I have helped to get changed down through the years as a result of my needling and bitching — know that I am not without some effect, in spite of my irritating way of going about things. In my defense on this I would point out that no one in history who has tried to change things was very popular — not to draw a comparison, but look what they did to Christ. There have been a lot of martyrs in history, but this editorial happened to be written on Easter Sunday and the thought was fresh in mind.

ON TRIAL

The indictment which was handed down by a grand jury said that I was accused of knowingly having the tax returns for 73 Magazine and myself prepared falsely for the years of 1966-67-68. Since this was completely untrue, it seemed like a problem that would eventually get cleared up when light could be shed on it.

Three years of tax returns for 73, three for me, came to six counts on the indictment — plus six more counts

for my signing the returns — that little line on the bottom which says under penalty of perjury — a total of twelve counts.

Those of you who have watched the Perry Mason series are familiar with the thinking of the prosecution — they want a conviction, whether the accused is guilty or not and they get furious when Perry is able to show that the accused is innocent. The actual innocence of their victim is of no consequence, only their need for a conviction is paramount.

What you don't see in Perry Mason is the back stage maneuvering of the government to win the case. They try to hide as much of their case as they can so the defendant will have a minimum of opportunity to prepare to argue or counter the evidence or testimony. In our case they had a list of over 200 witnesses which they withheld as long as they could to make sure that there was no possible way to do much about it. Their use of out of date addresses for many of the witnesses was an added obstacle.

Since they only used about a dozen of these 200 plus witnesses, it is rather obvious that this was an attempt to hide the real witnesses among a crowd of pseudo-witnesses to prevent any defense being worked up.

Even with all this I didn't worry exceedingly about the situation because I was sure that justice would be done, that the facts would have to come out in court. They did, but they were so obscured by trivia and massive amounts of irrelevant things, that they got lost in the shuffle.

Would you go into court as a defendant, knowing you are up against the very best lawyers the government can afford, brought in from Washington to do a job on you, and with you defended by a lawyer who has never tried a case before? You would if you were in my place and found that the mere indictment had cut off your credit so you had no money to pay an experienced trial lawyer — not even enough to have a second lawyer just sit and help with the paperwork during the trial.

Just as an added hurdle, let's make your lawyer an accountant with a small one-man office and a bunch of clients who need their tax returns prepared during the first three and a half months of the year — and let's

put that trial at the worst possible time during that work period. Thus, he will not only have to work all day in court defending you, but will then have to work nights on his regular business instead of preparing for the next day's court action.

Would *you* expect a fair trial?

THE PROBLEMS

For the last twenty years I have had my tax returns prepared by accountants. I know only enough about taxes to know that there is no way for anyone but an expert to understand them, so I turn to professionals. My "professional" (General Business Services) for the years 1966-67 let me down and the IRS jumped in with glee to take advantage of the situation.

During those years I had little to do with the financial end of the magazine. We had a business manager and he took care of all that. I depended on the accountant to make sure that any personal expenses paid by the magazine would be charged to me and all checks spent were clearly marked as to their purpose to simplify this. Nothing was hidden or obscured. Starting with some of these expenses which the accountant did not properly allocate, and then adding an unbelievable number of "disallowed" expenses, the IRS built up a formidable figure for taxes. Each disallowed expense counted twice, of course, once as unreported income for me personally and once as unreported income for the magazine, so this doubled each disallowed expense.

What sort of items did the IRS disallow? In my office they disallowed my desk, a chest, the paintings on the walls, the chairs, tables, lamps. They disallowed the decorations in the reception room, the table and chairs in the lunchroom, and many other pieces of office furniture — lamps — tables — chairs. Then add to that the expenses on trips to hamfests and conventions where I have given talks and sold subscriptions — total disallowance of DXpedition expenses — cameras — books and magazines for research — all car repairs, licensing, purchase costs, even for cars used strictly by the magazine — ad sales trips — interview trips for new editors — entertainment of visiting hams, advertisers and dignitaries — and you end up with a formidable list — times two.

The trial lasted almost a month and during that time there was never one word of testimony that I falsified my records, that I hid anything, that I tried to deceive the accountants, that there was any double bookkeeping, or anything that I did was wrong. The accountants all testified that I did not try to influence them when it came to

business vs personal expenses and that I accepted their decision without complaint.

Some of the expenses involved were indeed personal — many were in what the accountants call the gray area — where accountants and the IRS get together and haggle — and many were very clearly and obviously business expenses. It should be mentioned that the IRS did not make any effort to even find out what most of the disallowed expenses were. They went by what was written on the check and asked few questions. And some of the disallowed expenses were things which had been allowed by an IRS audit in a previous year!

My lawyer pointed out that if he could get one businessman on the jury we would have no problem. No way. The jury was mostly retired people, housewives and a couple of blue collar workers. They were as lost as I was during all of the obscure accounting and tax talk and they ended up voting, I suspect, on the basis of the closing statement of the prosecutor, which was masterful. My lawyer took a few minutes to point out that there had not been a shred of evidence produced during the long trial that I was guilty of anything except hiring a lousy accountant. The prosecutor took well over an hour to dwell on the indictment and the massive amount of disallowed expenses.

It didn't help a lot that I managed to get the flu half way through the trial and had to sit there day after day, with a fever of 102 or so, shivering with chills, unable to really be aware of what was happening. In ten days I lost 15 pounds and was so weak I could just barely walk — this, of course, was when I was called upon to testify. I have little recollection of it.

In retrospect I understand how foolish I was to trust the IRS. I thought that if I was honest with them that we could solve the few problems we had with the taxes. I didn't realize that they are desperate for goats to parade at tax time to frighten taxpayers into compliance. My case was complex enough to be made to order for them. I should never have cooperated with them — shown them our records — for I'm now convinced that they were interested in a fraud conviction right from the first and pretended to be interested in a civil audit just to pick out items which might convince a jury.

WHAT NEXT?

The decision of the court is not yet known in the case, so it is still premature to say that I have been convicted of tax evasion. Whether I am convicted or not I will do every-

thing I can to help keep other people from getting into the same position. I now know personally that it can indeed happen to anyone.

You are undoubtedly familiar with the frustration of being accused of something you didn't do. It is infuriating. You want to do something about it when someone lies or distorts things, yet under the trial system you have to sit there and grind your teeth. I'd love to publish the transcript of the trial, but that is over 3000 pages! No wonder the jury fell asleep. Unless the court stops me, I do want to cover the essential points of the trial — the story developed by the IRS — and the story they so successfully covered up. Knowing that most juries work on the "where there's smoke there must be fire" principle, the IRS generated an almost impenetrable smoke screen.

If the court does convict me we will appeal and try to do better next time. In view of the total lack of evidence that I did anything wrong, it is possible that there will be no conviction.

DO YOU WRITE

If there is anyone out there who has been working with Novices a lot and has an understanding of what information they need — and who is able to write coherently — there is a possibility that a relatively short Novice column in 73 might be well received. Any takers?

There is also a rather continuing need for research articles for 73 — things that you might suppose would be done by the 73 staff — if there were that much of a 73 staff. About once a year or perhaps every other year the readers would like to have a survey of the equipment available for a particular band or a particular mode. For instance, an article on all of the 220 MHz gear available, including any specific accessories. Or one on 12vdc power supplies. Or one on 6m ham gear. 450 gear. Test equipment for the ham shack. Two meters would have to be split up a bit — hand units — mobile and fixed station units — power amplifiers — antennas. Low band sideband gear. 160m gear. You get the picture. It means getting the latest information from manufacturers, pictures, making up charts of comparison, and providing a brief review of each unit. . .etc. It pays.

TO CB OR NOT TO CB

A call from a friendly eastern FCC inspector explained some of the working of his organization. When calling on licensed CBers he has the authority to levy a fine on them for breaking the rules. When the CBer is unlicensed he can just warn them and then, if they continue, go to a U.S. magistrate, file a complaint of violation of the Communications Act and apply

for a search, seizure and arrest warrant. He can then get a U.S. marshall to accompany him and to execute the warrant.

Amateurs who have CB neighbors who are operating illegally must wrestle with their conscience about calling the FCC. Is it better to turn in an illegal operator and perhaps get rid of a lot of local TVI and bad will towards amateurs, or just keep quiet and thus be a party to the law-breaking? Silence is assent. If you don't do anything about it, you are guilty.

MORE NEWS REPORTS NEEDED

Radio amateurs have been performing emergency services in recent months as never before. While it is important to see that news of this service reaches your local papers, always remember that other amateurs will want to know what you've done too, so be sure to either send a copy of the news clipping to 73 or send in a brief writeup of the service to the magazine. Pictures of the people involved are also helpful, if they are available or can be taken, either in group or solo. The deadline for newspaper material is the 15th of the month.

While some congressmen may get to see your newspaper articles, most of them won't. Only 73 sends copies of important amateur news from the newspages to congress. The FCC will get to see them this way too.

Long, detailed articles on emergency service normally should go to QST, while briefer reports should be aimed at 73.

HOTLINE COOKING

The HOTLINE, a ham newsletter sent out by first class mail every other Friday, is drawing bravos from all over. It covers all the late breaking news — the latest FCC reports — the hamfest news — contest news — jobs open in the industry — DX late news — new equipment announced — new books — propagation flash — repeater update — so why wait two months for these items to reach you through 73 Magazine. Get the inside scoop while it is still news. It'll make your contacts a lot more interesting. All this for only \$8 per year sent first class — and that reaches most places as fast as airmail — and some places it reaches faster.

NEW FCC FORM

Repeater groups who have been asking about their license applications have been receiving a new FCC form from Walker. This form announces that they've lost the application, so please do it again.

W2NSD/1

SSTV SCENE

Dave Ingram K4TWJ
Rte. 11, Box 499, Eastwood Vil. 50N
Birmingham AL 35210

This year's Slow Scan contest appeared a fine success, and I'm sure all of you enjoyed it. As of this writing date, I have tallied U.S. results, (see Chart 1) and am standing by for world results from Franco 11LCF. I understand some of the U.S. stations sent their logs directly to Franco (rather than either sending me a copy, or having me forward them to Franco, as I mentioned in the January column) so the final tally was from received information.

Don Miller W9NTP, was the winner with a rather impressive score which included WAC on SSTV. Next was Bob WA7MOV, and Connie WA1NXR, both who are quite active on Slow Scan. Although everyone agreed conditions were anything but optimum, it's interesting to note East Coast stations reported fair openings into (primarily) Europe, while West Coast stations reported fair openings into (primarily) the South Pacific and Asia area. "Centrally located" stations appeared to have the advantage of catching both areas. Like most contests, this one also had its points of interest. WB4ECE reported "being tied up with business 'phone calls most of the time." K9BTU had his Ham-M Rotor give up, leaving the beam stuck on Europe, plus taking time out to attend a wedding. WA1NXR operated the contest without AGC action on her TR-4 (Boy, I bet that was good on the ears!) only to have the rig go out completely right after the contest. Quite a few of the gang reported falling asleep at their rig during the wee AM hours. AhAh...the pleasures of the chase. Our thanks to all for your comments and pictures. Naturally next year will be even better!

Slow Scan on 2m appears to be growing in popularity, probably because it is handy in checking ideas and circuits with others under "closed circuit" conditions. (Just watch deviation — present regs call for this to be low). In some circumstances this could prove advantageous. One could "show" a problem to another local SSTVer, even while driving to work. That's as simple as remembering to grab the cassette unit on your way out. Newcomers could check out and get familiar with Slow Scan gear by taping these QRM free pictures also. (Again, just a cassette recorder in the car is all that's necessary.) No "tuning for proper syncing" is required on

UNITED STATES RESULTS 4TH SSTV CONTEST

CALL	QSOs	CONTINENTS	BAND/ COUNTRIES	TOTAL POINTS
W9NTP	82	6	42	9348
WA7QBV	43	3	56	5334
WA1NXR	44	4	31	3608
WB4ECE	43	4	33	2279
WA1KYW	33	4	21	2046
K9BTU	16	3	10	560

FM. In fact, a simple PLL circuit could be built which would energize the recorder while Slow Scan was being received, thus a "no hands" operation could be accomplished. I have found a two cartridge system works best...one for recording and one for transmitting. The "Program" is recorded on both "sides" (directions) of one cartridge, so I needn't worry about rewinding. Then, when receiving SSTV, I just swap cartridges. I also often use my car's 8 track stereo tape deck for Slow Scan. One of my "home recorded tapes" has a SSTV ID on one track's left channel output and a SSTV program on the right channel output. Simple switching circuits are used to also feed this (through a small attenuator) to the 2m rig. Incidentally, I might mention here although good results can be obtained by just holding a mike near a speaker, (watch the volume) a better way would be to connect the audio through a .005 μ F capacitor to the deviation pot. This bypasses the first audio stages that usually incorporate limiters that could clip the signal. This also is a much better way to connect a touchtone pad into a 2m rig, as it's more stable and reliable (and more convenient). I accomplished this on my TR-22 (yes, R.L. Drake agrees it's the better way) by disconnecting the speaker positive leads from the earphone jack, taping them and sticking them back beside the jack. Then "quick soldering" a small lead to the actual wiper on the deviation pot, running this lead to the earphone jack completes the modification. Plugging either a touchtone pad, cassette or 8 track player into this

jack (watch that level) gives double capability. I can even talk low into the mike during SSTV transmission for mixed audio and video. Slow Scan transmissions on 2m can be kept very short since there is no QRM. A single frame can be spliced into a tape loop and replayed indefinitely. And if you would like a good antenna for SSTV especially try the New-Tronics CGT-144 — 5.2dB gain job. It really helps me from the car. I feel SSTV on 2m is good for experimenting (watch that deviation!) but would defeat its basic purpose (that of long distance



K9BTU Transmission

TV communication) if used for 20m style QSOs. 440 MHz Fast Scan would be better suited for that purpose. However, pulse modulation SSTV for moonbounce might be a worthwhile consideration. (Let's see you beat that 262dB path loss!)

Ralph ZL2AAV, should have received his Robot monitor by now, so watch for him around 14.230 kHz. He has some interesting taped programs that show active volcanoes, crater lakes and ski slopes in his area. In fact, Ralph has been quite busy on a sampling camera that might be working by now. Bill XW8DO, reports being back on 2m and looking for SSTV QSOs mainly on Tuesday and Wednesdays (approx. 1400 GMT) and Saturdays (around 0100 GMT). Joseph WA2ZDF/CP1, is busy finishing his new 'MXV monitor and should be on 20m soon, at least with some taped programs while he builds a plumbicon camera.

Next month I plan to have world results of the Slow Scan contest, a recap of the Dayton bash, and much more. 'Till then,




The K9BTU SSTV Setup

K4TWJ

ANATOMY OF A GREAT 2-METER RADIO

sr-c 826MA

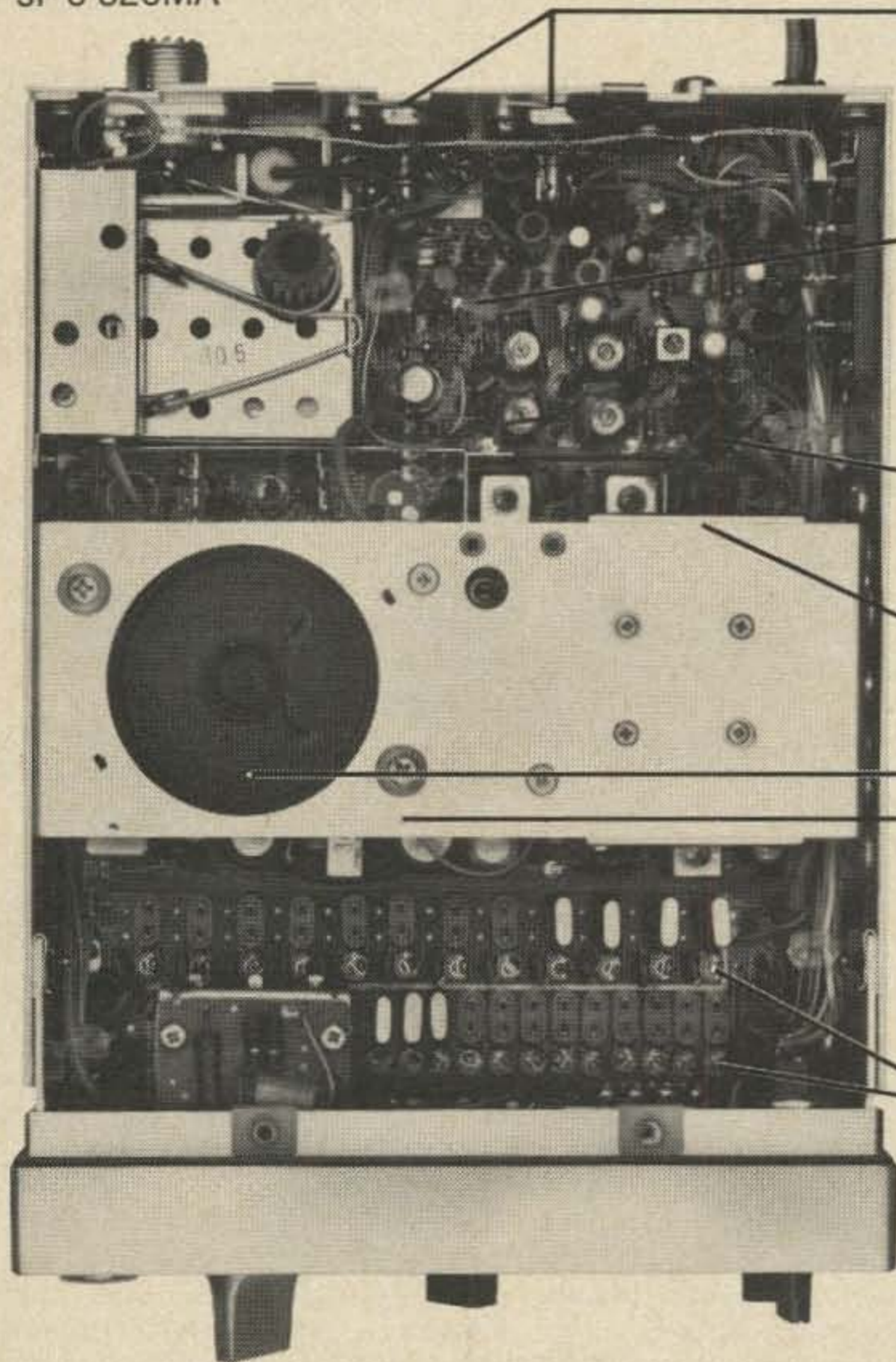

Rear panel test jacks for complete Tx and Rx metering and discriminator output for crystal netting; Input for external tone burst and Touchtone®; Provision for external speaker.

Conservative 10 Watt transmitter with an effective IDC circuit to maintain narrow band deviation (± 5 KHz) for today's repeaters; Automatic current Control and final protection against high VSWR.

Provision for front panel selectable "Private Channel" tone coded squelch (CTCSS) on both receive and transmit.

Triple tuned receiver "Helical Resonators" for maximum intermodulation interference rejection.

Built-in speaker.

The heart of a quality radio—a commercial grade receiver featuring Front-end MOS-FETS and a highly selective 9 section ceramic I.F. filter—necessary for today's active 2 Meter band; Reserve audio for noisy environments.

Individual "Netting" capacitors on both Tx and Rx crystals; 12 channel provision with popular channels 94/94, 34/94, 16/76 and 52/52 included; Easy access to crystal deck through "snap-open" trap door.

Touchtone®—trademark of A.T.&T. Co.

ASTROPOINT = TOTAL PERFORMANCE

STANDARD's "ASTROPOINT" system gives the no compromise performance for the active amateur, unlike the claims made by the "cheapies." Don't be misled by gimmicks or gadgets—it's what's inside that counts. Reliable, solid state circuitry and Glass-Epoxy

PC boards used throughout, backed by our 6 month warranty. **INSIST ON TOTAL PERFORMANCE—INSIST ON STANDARD.**

The 826MA comes complete with microphone, mounting brackets, 4 channels and line filter.

For detailed information on the 826MA, the complete Standard line and the name of your nearest dealer write:

 **Standard
Communications**

213/835-3134 • 639 North Marine Avenue, Wilmington, California 90744

ou goons don't ever proof
loasy man...
bunch of rocks...
you ignored my comments in
I insist that you print ev

LETTERS

COUNSEL FOR THE TAXPAYER

Internal Revenue Service officials have assured congress that IRS employees do their best to comply with the letter and spirit of the Freedom of Information Act, now in its eighth year of operation. Do they?

No. I'm sorry to report that they're still flaunting the law despite repeated warnings from Capitol Hill. Eloquent proof is found in the results of a recent survey of nine IRS district offices. The inquiry was made by representatives of Freedom, a journal of national circulation published by the Church of Scientology.

Reverend Kenneth J. Whitman, Freedom's editor, authorized the survey after examining instructions that all IRS employees are supposed to be following. They're contained in an IRS manual supplement entitled "Release of IRS and Other Telephone Directories to the Public."

This manual was distributed by the IRS national office to all IRS district offices. In accordance with the Fol Act, it clearly states that IRS district telephone directories are to be made available to the public on request.

Certainly there's nothing hush-hush about a mere list of employees, with their office telephone numbers. I keep one in my desk that covers the entire IRS national office, as well as other listings. This directory can be obtained at nominal cost from the Superintendent of Documents, Government Printing Office, Washington, D.C. 20402.

Yet Freedom representatives were allowed a look-see at district office directories in only three out of nine cities: St. Paul, Detroit and Portland OR. They were summarily turned down in Los Angeles, Honolulu, San Francisco, St. Louis, Boston and Austin TX, after receiving the third degree in each office.

Whitman said the results lend great weight to the charge, frequently heard, that IRS operates like a secret police organization.

Portland was the most cooperative office. But even there, the inquirer was interrogated before being allowed a peek at the directory.

Apparently it was only by luck that the Freedom requester was successful in St. Paul. The IRS employee who handed over the directory said, "Here you go. Monday is my last day anyway."

Freedom got a chilly reception in San Francisco. An IRS public servant said, "I wouldn't know why you would want a directory except to

spread propaganda." IRS spends millions of tax dollars every year to spread its own propaganda from the Atlantic to the Pacific.

When turned down in Austin, the Freedom representative asked if there was any way to get a directory. Answer: "No."

Freedom pollsters really got the run-around in Los Angeles and Honolulu. The inquirer in L.A. was told that he'd have to write to the district director and state exactly why he wanted to see a directory!

In Honolulu, an IRS official said the directory wasn't available to the general public. It was only for inter-office use, he said. The Freedom man was asked what company he was with, who he represented, what he wanted to use the directory for and how he came to know there was such a telephone book.

Reverent Whitman's conclusion: If you want to know how IRS really operates, watch what it does, not what it says it does.

E. Edward Stephens
Third Floor
815 King St.
Alexandria VA 22314

IRS - BAH!

I am in complete agreement with you on your stance on the blood-sucking Infernal Revenue Service.

You want to do away with the income tax? It is a very simple matter, according to the Constitution of the United States, which has been used as toilet paper up till now by the Nixon administration. The First Amendment to the Constitution says: "Congress shall make no law respecting an establishment of religion. . ." Yet, the church in this country is free from the burden of paying its fair share of taxes. It does business in this country via owning railroads, buildings, houses and bingo halls. It makes hundreds of millions of dollars per year. It has billions of dollars in real estate and priceless jewelry and gems. All untaxed! If this is constitutional then I am the Statue of Liberty.

In Mr. Green's editorial, in the April issue, he states, "The IRS has no right to see your records, cancelled checks, etc. without a court order. . ." I am very sorry to say, Mr. Green, that the Nixon court (formerly the Supreme Court), has just this week, declared constitutional, the 'right' of the government to examine any and all financial transactions, checks written, etc. without a court order. All banks must now keep a micro-

filmed record of all activity in your bank accounts, and make them available at the government's request. Of course, the stooges appointed to the high bench by Nixon, voted for this.

Name Withheld
Flushing NY 11352

HOW TO MAKE \$100

Received the April copy of 73 this evening. Could hardly wait for dinner to be over so I could get started reading. Imagine my surprise when I read the article entitled "The New Breed On 2 Meter FM."

No foolin Wayne, the same thing happened to me about 2 weeks ago. I drove into a service station to have my car serviced. Naturally the attendant noticed my call sign in the back window and the bumper mounted antenna. Some one had told him there was a 2m repeater hookup nationwide, and he has a licensed brother in Oregon. The attendant knows the code but not the theory. If he had a license he figured he could talk to his brother.

When I told him I got an advanced license about three years ago he says, you ought to be pretty good, and if I would take the exam for him, he would give me \$100.

Boy oh boy!

George A. Lewis W7SBZ
Mesa AZ 85202

RECTANGULAR PEG IN A ROUND HOLE

Do you sometimes want to chassis mount an IC in a round can? Here's my solution: Use the bottom side of a tube socket as a round terminal strip on which to mount the IC. No large hole is made in the chassis; only those for the mounting screws. Flat wafer type sockets work best. For example, suppose you want to mount an 8-pin, TO-5 IC. I suggest a 7-pin, miniature socket. Obviously you will have one pin left over on the IC. Look at the IC diagram - almost always at least one pin is a "no connection." Make that the "extra" pin. Cut the lead short or at least make sure it doesn't touch anything.

There is one fly in this ointment. Some ICs are unstable with leads this long. However, the popular self-compensated operational amplifiers (such as a 741C) are completely stable. Try to keep all output wires from getting close to the + or non-invert input.

The IC can be soldered in either right side up or upside down (looking at the bottom of the tube socket), but make damned sure you know which pin is which. If an octal socket is used, the upside down way will mean that the IC will fit neatly into the hole in the middle of the socket! However, be careful here as some ICs have power supply connections to the can - the IC might touch the chassis through the hole and short out.

Clyde E. Wade, Jr.
Little Rock AK 72205

MORE RECEIVER INFORMATION RECEIVED

Thank you for publishing "How The Communications Receiver Began," March 1974. Truly a refreshing look at the great beginnings of radio communications, with most of the contributions by active "hams."

Concerning National Company and the justly famous HRO. Two names deserve special mention: James Millen W1HRX and Dana Bacon W1BZR. The precise division of labor at National is a bit unclear, but I know that Millen was by training a mechanical engineer and was responsible for the National line of "Velvet Vernier" dials and also the entire PW series used on HRO and other receivers.

Rumor once had it that Millen vacated National to form a company in his own name because someone insisted that the HRO be redesigned into a prettier radio, with band-switching and a direct-reading dial. The HRO continued unchanged!

The correct name is McMurdo Silver — not McCurdo Silver! I believe that McMurdo Silver won international competitions with his receiver designs a number of times, and that his sets were chosen for use on Arctic expeditions as being the best available.

A final addendum: Hallicrafter DD-1, a real brute of a receiver! This was a dual-diversity receiver consisting essentially of two separate SX-28's connected to independent antennas with automatic sampling to choose the stronger signal and feed it to the common audio system.

B. van Sutphin
St. Petersburg FL 33701

TAPE GREAT STUDY GUIDE GREAT

Fantastic! Both the code tape and the Extra Class study guide!! The tape enabled us to bring our code speed to 22 WPM in short order, while the guide...well, it was just about the most lucid text I've ever read. It has been said that good writing is transparent; that is, with good writing, the reader never stops to think, "Now, isn't that a cute way of presenting this or that." But the guide IS well written and many times I found myself stopping to observe how well a particular point was made, or how something that I really never had a good feeling for was suddenly crystal clear! That I passed the Extra Class exam today on the first go around is due in no small way to the tape and guide you supplied!

Ted Cohen
Alexandria VA 22308

WRETCHED SUCCESS

A pleasant surprise to see wretched Coward writing again in 73. I had wondered where he was hiding out. Seriously, the warning about "license consultants" was well taken. All I can say is nix on that type of activity!

J. R. Johnson WA5RON
Austin TX 78751

\$9 — OUTRAGEOUS

While Wayne Green is hassling with the FCC perhaps he could shame them into reducing the fee for re-application for the Ham license. I think nine bucks is outrageous, when I was a lad in the early teens (years on the calendar that is) it cost nothing for a ticket and Uncle Sam issued the ham and commercial call books for a very nominal sum, a buck I recollect. Now we are supporting a bureaucracy which is not doing the job.

Christopher Noble Ex/W6HEC
Comdr. USN Ret.
Durham NC 27707

CIRCUIT CORRECTION

Your feature column on Circuits is great — provides the experimenter with many useful ideas. But the one circuit shown on page 34 of the April 1974 issue scares the H--- out of me and it is no April fools joke either. Of course I am referring to the line operated audio power amplifier.

As it is shown, the common side of the input can be riding directly connected to the hot side of the AC power line. And this condition is true as long as the unit is plugged in, whether or not the power switch is on or off. The only way to use this with safety would be through an isolation transformer. It could be used with a three terminal plug and making sure that the grounded side of the AC line is the one connected to the common return line of the circuit. But even this is risky unless the user checks the outlet he uses to make sure the electrician didn't make the wrong connection in the outlet box.

Harley Gabrielson K6DS
La Mesa CA 92041

DQ

Re: *Sexton's Laws* (March 1974). Mr. Sexton neglected to mention the means of estimating the complexity of any amateur project. This is the DQ, or "dammit quotient," and it indicates the number of dammits required to complete a project. The more complicated the project, the higher the DQ.

Full credit for discovering this handy measuring unit must go to my husband, Bill Hood W2FEZ, who employed it for years before becoming fully aware of its utilitarian potential.

Barbara Hood
Albion NY 14411

INFORMATION PLEASE?

I live in a small cottage in an industrial park. The back of my house is up against a large concrete-steel reinforced building. Lots of electrical QRN and high powerlines all over. I can't have an outside antenna, so I must use an indoor one. If anyone has any suggestions or designs I'd appreciate hearing about them.

P. Cook WA7CSK
Phone: 762-0358
218½ S. Findlay St.
Seattle WA 98108

TWA SERVES?

I haven't noticed any answer to the "TWA Serves" and "What am I Eating?" published a few issues ago. My wife says the "TWA Serves" is a type of Coffee Creamer and "What am I eating?" is another brand of the same thing. (Right...ed.)

This is just another example of today's advanced technology. If that makes you wonder what you are eating, look up what our convenient "processed" cheese is made of. A very good book which covers this field is "Consumer Beware" by Beatrice Trum Hunter. But if you read it, beware — you may want to stop eating things you accept as everyday food.

Happy reading and EATING.

Bob MacArthur
Penticton BC Canada

XU1AA

WHERE OH WHERE!

I have received the following note from Bill Spencer KA6WS, relative to problems with the lost XU1AA logs. Bill offers the following aid:

"All USA and other stations working with XU1AA who was MC on prearranged skeds with XU1AA, be advised that the logs of XU1AA for June through September 1973, have been lost. When, and only when, KA6WS acted as MC he maintained a copy of the logs. To obtain a QSL, send complete QSO information and SASE to: Bill Spencer KA6WS, P.O. Box 128 MCAS (H), F.P.O., Seattle WA 98772.

Bill is not acting as the general QSL manager for XU1AA, he is only offering to confirm those QSO's for people who checked in through him for an XU1AA QSO.

Ed Moody W3GID
Furlong PA

AUTHOR HINTS

Many times your construction articles appear to be "just what the doctor ordered." Regretfully, some projects meet an untimely end. Why? Because:

(1) The author has access to a line of experimental or limited run devices from a "friend" employed by the manufacturer.

(2) The particular project involves a key device with a \$40 price tag and said project needs six of them.


I would like to see all authors make note of limited availability devices and include a cost estimate based on major components (Tubes, ICs, diodes, transistors, etc.,).

Tom Valosin WB2KLD
Middleburgh NY 12122

NOVICE NET

Is there anyone that could tell me if there is a net in any of the novice bands? Thank you!

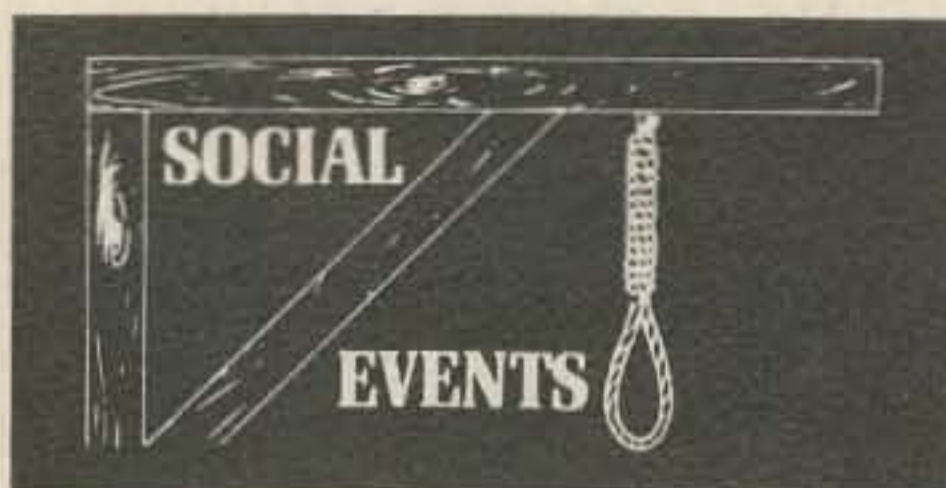Joel Craig WN6WKQ
308 Shamrock Dr.
Ventura CA 93003



PENN-CENTRAL HAMFEST

The Williamsport and Milton Club's 11th Annual Penn-Central Hamfest will be held Sunday, June 2, at the Union Township Volunteer Firegrounds on Route 15 in Winfield PA. Indoor and outdoor facilities for contests, auction, and fleamarket. Starting at noon, gate registration \$3, free parking. Talk-in on 3940, 146.52, and 146.94. More information available from Clair Yeagle WA3QXI, 714 N. Main, Watsonstown PA or call (717) 538-9292.

MISSOURI SINGLES

The Missouri Single Side Band Net will have their annual picnic at Memorial Park in Jefferson City MO, Sunday June 9. A covered dish dinner will be served at 12:30. Coffee, ice tea and soft drinks will be provided by the net. Door prizes given. All amateurs, their families and friends are invited.

POMONA FEST

The Tri-County Amateur Radio Association will hold a field day celebration on June 23 and 24, at the Water Department Filtration Plant in Claremont CA. General Dynamics ARC and our club will join forces.

On August 4th, we will have our hamfest picnic at Westmont Park in Pomona CA. Drawings for prizes and gifts. For more information contact: John Goodreau, P.O. Box 142, Pomona CA 91769.

SEE YOU IN DES MOINES

2nd Annual Des Moines Hawkeye Hamfest will be held on Sunday, June 16, 1974, at the Iowa State Fairgrounds. Plenty of free parking. Fleamarket, covered display booths available, small charge; open arena, no charge. Dealer displays, prizes, and expanded XYL activities. Saturday night auto races and camping-extra. Registration \$1.50 advance/\$2.00 at gate. Write Des Moines Radio Amateur Association, Box 88, Des Moines IA 50301.

EGYPTIAN BASH

The Egyptian Radio Club Inc., will hold its annual HAMFEST on Sunday, June 9, 1974 at the picnic grounds, 700 Chouteau Slough Road, Granite City IL. Something for everyone — prizes — games for the children — food at the club house — parking for swaps, etc.

ROCKY ARRL FEST

The 1974 ARRL Rocky Mountain Regional Convention will be held June 7, 8, and 9, at the Ramada Inn in Pueblo CO. Pre-registration fee is \$6, at the door \$7. Meals, accommodations and camper/trailer hook-ups will be available for the three days of the convention at special reduced rates. Sunday afternoon banquet with speakers from industry and the Amateur Radio Field. For additional information write: Convention Committee, P. O. Box 92, Pueblo CO 81002.

SSB IN MISSOURI

The Missouri Single Side Band Net will have their annual picnic at Memorial Park in Jefferson City MO, Sunday June 9, 1974. A covered dish dinner will be served at 12:30. Coffee, ice tea and soft drinks will be provided by the net. Door prizes given. All amateurs, their families and friends are invited.

6M — WOW!

The 6m club of Chicago, Inc., will hold its 17th Annual Hamfest Sunday, June 9, 1974, Southwest of Chicago at Santa Fe Park, 91st and Wolf Road, Willow Springs IL, swap row — picnic grounds — plenty of parking space — refreshments. Advance registration \$1.50 — at the gate \$2.00. For more information or advance tickets contact: Val Hellwig K9ZWU, 3420 South 60th Court, Cicero IL 60650.

FLUSHING FESTIVITIES

The Hall of Science Radio Club will hold its annual Fleamarket/Auction/Picnic at the Hall of Science, 111th St. and 48th Ave., Flushing Meadow Park, Queens, on Saturday, June 8, from 10:00AM to 4:00PM. Fleamarket setup 9:00-10:00AM. Admission \$1. Sellers \$2. No commission. Free parking. An auction service available with 10% fee. Rain date is Saturday, June 15. Zoo, Childrens' Farm, Golf, Boating, Art Museum, Science Museum, etc., adjacent. For more information call/write: 212-699-9400 or Box 1032, Flushing NY 11352.

MONTREAL '74

The 1974 Montreal Hamfest will be held August 4, at the MacDonald College Farm, Ste Anne de Bellevue. Prizes, giant fleamarket, technical sessions, family fun — \$2.50/Adult. For more information contact: VE2RM, Box 201, Pointe Claire-Dorval, Quebec H9R 4N9.

FUN IN KANSAS

The Central Kansas ARC sponsored Hamfest will be held June 2. For more information contact: Charles R. Svoboda W0LQK, 225 West 9th, Chapman KS 67431.

MILWAUKEE FEST (Bastille Day Celebration)

South Milwaukee Amateur Radio Club 4th annual Southeastern Wisconsin Swapfest will be held Saturday, July 13, 1974 at Shepard Park (American Legion Post 434), 9327 South Shepard Avenue, Oak Creek WI. Activities begin at 7:00AM and will run to 5:00PM or later. Parking, picnic area, hot and cold sandwiches and liquid refreshments will be available on the grounds. Admission is \$1.00 and includes a "Happy Hour" with free beverages. Prizes will be awarded. Talk-in on 146.94MHz. More details available from: So. Milwaukee Amateur Radio Club, S.F. Schreiter W9AKF, Secretary, 104 Brookdale Drive, South Milwaukee WI 53172.

INTERNATIONAL HAMFEST

The 11th Annual International Hamfest will be held July 13 and 14, at the Canadian Pavilion in the International Peace Garden between Dunseith ND, and Boissevain, Manitoba. Camping excellent. Party — Contest — Prizes — Meetings. For information contact: Ken Larson

"INDY" 14

(Another Bastille Day Bash)

The Greater Indianapolis Hamfest will be held on Sunday July 14, 1974 at the Marion County Fair grounds on the South East side of Indianapolis at the junction of Interstates 465 and 74. All events including the giant flea market will be under roof. Thirteen area amateur radio clubs combine to bring central Indiana an outstanding convention of technical forums, commercial displays and fellowship. Complete food facilities. Free coffee and donuts in the morning. Gates open at 6:00AM. \$2.00 at the gate entitles the bearer to hourly and main prize drawings. There will be a presale ticket drawing for a Genave transceiver. The main prizes consist of an impressive array of low band and 2m Drake gear. There is a good restaurant on the grounds. Free prizes for the kiddies and a full schedule of women's activities.

GRAND EVENT

The Grand Rapids Swap and Shop will be held Saturday, September 21, 1974 at the Hudsonville Fairgrounds, M-21 at 40th Street, three blocks west of the Hudsonville traffic light. Admission is \$1.75 at the gate, no charge for tables or trunk sales. Talk-in on .16/.76 and 146.94. For more information contact: Grand Rapids Amateur Radio Association, Inc., P.O. Box 1333, Grand Rapids MI 49501.

TURKEY RUN

The 27th Annual Turkey Run Hamfest and VHF Picnic, sponsored by the Wabash Valley ARA, Inc., will be held Sunday, July 28, at Turkey Run State Park near Rockville, Indiana. Don't miss the Midwest's finest fleamarket. Fun for the whole family: XYL Bingo and fleamarket; food and refreshments, camping facilities, and park recreation for the kids. First Prize: Genave GTX-10, Second Prize: Regency HRT-2, Third Prize: Drake WV-4 VHF Wattmeter; plus many more. Activities begin at 9:00 AM with free coffee and doughnuts. Talk-in 146.94 by W9UUU/9. For details, send SASE to WVARA Hamfest, Box 81, Terre Haute IN 47808.

GLACIER FEST

On the weekend of July 20 and 21, 1974 the WATERTON GLACIER INTERNATIONAL HAMFEST will be held in the beautiful Waterton Lakes National Park. For more information contact: John A. Fyke VE6AIV.

IRVINGTON HAMFEST

The Irvington Radio Amateur Club will hold its annual hamfest on Sunday June 2, 1974, 1-6 PM, at the Irvington PAL Building, 285 Union Ave., Irvington NJ. Admission - 50¢ in advance, \$1 at the door. Table rental - \$2.50. Refreshments will be available. Door prize!! For more information and advance tickets contact WA2PWZ, 9 Barbara St., Newark NJ 07105.

SRRC HMFST

The SRRC Hamfest will take place June 2, at a new sight - the Bureau County Fairgrounds, Princeton IL (It has formerly been held in Ottawa IL). Easy access Rtes. 80 - 6 - 29 - 34. Advance registration \$1.50 before May 20, \$2 at the gate. For more information write: G. E. Keith W9QLZ/W9MKS, RFD #1, Box 171, Oglesby IL 61348.

MELBOURNE HERE I COME

The 9th annual Melbourne Hamfest is September 7-8. All air conditioned, \$1.50 at door. Tables \$2/day. PCARS, P.O. Box 1004, Melbourne FL 32901.

NINTH SWAPFEST

The ninth annual Northwest Texas Emergency Net Picnic & Swapfest will be held at the City Park in Levelland, Texas on Sunday, August 11, 1974. Bring your own picnic basket. Free registration begins at 0900. Lunch at 1300. Swapping all day. This event is for the entire family. Mobile talk in frequency is the net frequency 3950kHz and 28/88, 34/94 on 2m.

MOBILEERS BASH

The Maryland Mobileers ARC Hamfest is June 16, Father's Day, at Anne Arundel Community College, Arnold MD, at 10:00AM - rain or shine. Talk-in on 10/70 and 146.94. Games, refreshments, contests and an auction are planned. Top awards: 2m transceiver and an electronic calculator. Registration \$2, tailgating \$2. Free parking, but plan car pools to save precious petrol. For further information contact: Ted Redick K3UPU, 2 Acton Place, Annapolis MD 21401. Telephone: 301-269-5577.

ZERO-BEATERS A.R.C. HAMFEST

August 4, 1974, Washington MO City Park. It starts at 10AM CDST, Auction at 11AM. Attendance prizes and other goodies. Auction, free bingo for XYL, cake walk, candy scramble - gigantic traders row. For Hamfest information and tickets write or contact Zero-Beaters ARC, Box 24, Dutzow MO 63342.

50 MHz BAND

*Bill Turner WA0ABI
Five Chestnut Court
St. Peters MO 63376*

From Maine WA1EXN reports a March 21st Aurora during which 2s and 4s were worked. Art comments that not many stations were active. April 4th brought a repeat with better signals and 2-3-4-8 and 9 land represented. The high point of the month was working WA2OAF and giving ham state number 50. Ed had been looking for Maine for 14 years from his New Jersey QTH. Art says he spent the winter building test equipment, reworking the rig and "slumming" on 40m.

From the far Northeast to the far Northwest and WA7ECY, Oregon, who reports a dead February except for a short opening to Phoenix on the 28th during which K7PXI, K7VYL and WA7VIS were worked with Q5 signals peaking S7 to 8. March was a similar situation with an opening the 29th to WA7FPO Phoenix and WB6RAM, Barstow. Scott says he and K7ZCB are tentatively planning a DXpedition to Idaho over a weekend sometime this summer to operate 6 and 2m SSB. More details are promised as they develop.

From Texas, Ray K5ZMS/5, says, "16 March... Today it gets interesting. At 2055CUT I started hearing strong FM signals and carriers at a number of frequencies below 50.1 from the Southeast - Spanish speak-

ing types. Evidently the MUF shot up this high very quickly from the high 40s for a short period of time. This lasted about a half hour. After a number of calls I heard nothing and it subsided. March 17th worked W4LZW, SC, for QSO #5000 on 6m then worked Alabama, Mississippi and several in Tennessee. March 22nd weak opening to Georgia, Kentucky and North Carolina, conditions unstable, few on. March 27th open to Florida." Ray also says SMIRK now has 89 members in 16 states and 5 countries and is still growing daily.

The New Jersey chapter of the National Awards Hunters Club is sponsoring a "1st Annual 6m QSO Party" from 0000CUT June 1st to 2359CUT June 8th. The exchange is to be RST, ARRL Section and if you are a NAHC member. Scoring is one point for stations in your section, two for stations outside your section and three points for stations outside the continental 48. Multiply your total score by the number of sections plus add one point for each NAHC member worked. Any mode is acceptable with the exception of repeater contacts. Certificates will be awarded to the top scorer in each section. Mail logs to NAHC Contest, c/o Vince Del Giudice, P.O. Box 91, Franklin Lakes NJ 07417 by July 31st.

JM Communications, 101 1/2 Washington St., Venice CA 90291, has announced a linear version of their Model 6100 6m amplifier. The 6100 previously advertised is intended for FM use and is capable of 100 to 145 Watts output with inputs of 15 to 25 Watts. The Model 6100L produces 120 Watts PEP output when used in conjunction in an exciter delivering 10 or so Watts. AM operation is also possible with 40 Watts of carrier being developed when driven by a typical (Communicator III) AM rig. Both amplifiers operate from a 12V supply, feature Silicon balanced emitter transistors, solid state automatic antenna switching, reverse polarity protection, broadband (no tuning) circuitry, plus provision for remote ON-OFF and relative output metering. Both are 10.48cm x 22.86cm x 8.89cm (4 1/8" x 9" x 3 1/2"), come complete with cables, manual, final test sheet and a one year warrantee. The 6100L is switchable from class C to linear operation. The 6100 is \$199.95, the 6100L is \$219.25 postpaid. A modification kit, the LAK-6100 at \$19.95, is available for 6100 owners who would like to convert to linear operation. Solid state has finally fully arrived for the 6m operator. Owners of SBE SB-50s, Gonset Sidewinders or the new Regency and Genave FM rigs will have a ball running this kind of power.

WA0ABI

73 REPEATER ATLAS REGISTRATION

REPEATER CALL (WR only)		FORMER CALL		LOCATION (City)		STATE
INPUTS	OUTPUTS	TT Wh TB PL	FM AM RTTY	AUTO PATCH	ERP	USEFUL RANGE (RADIUS)
		Hz				
		Hz				
		Hz				
		Hz				
EQUIPMENT						ANTENNAS & HEIGHT <input type="checkbox"/> SPLIT SITE <input type="checkbox"/> DIPLEXER
REPEATER GROUP/SPONSOR						
TRUSTEE			ID-TYPE OR MFR.			
<input type="checkbox"/> I certify that I have received no outside assistance while completing this form.						
DATE	SOURCE (NAME/CALL)	SPECIAL OR EMERGENCY FUNCTIONS				



CA	WR6ADZ	Pacifica	T1.8	6.25-6.85
CA	WR6ADY	Pise Look		
CA	WR6ADY	Pise Lookout	T1.95	6.25-6.85
CA	WR6AEA	Woodside	T2.1	6.25-6.85
CA	WR6ADZ	Pacifica	T1.8	6.25-6.85
CO	WR8ADO	Castle Rock		6.07-6.67
FL	WB4QER	Panama City		6.10-6.70
GA	WR4AGD	Augusta		6.34-6.94
				7.90-7.30
GA	WR4AEW	Valdosta		6.16-6.76
IN	WR9ADA	La Porte		6.01-6.61
MD	WR3ACR	Baltimore		7.63-7.03
MI	WR8ADA	Flint		6.31-6.91
MS	WR5ADC	Gautier		6.28-6.88
NC	WR4AGC	Durham		6.22-6.82
NJ	WB2AHF	Vineland		6.055-6.655
NM	WR5ABV	Capitan Mountain		6.34-6.94
NM	WA5YTK	DELETE		
OH	WR8ABS	Middletown		6.01-6.61
OK	WR5ACB	Oklahoma City		6.22-6.82
				52.680-52.525
WA	WR7ACB	Chehalis	T1.95	7.66-7.06
WA	WR7ADB	Marysville		CLOSED
CANADA				
Manitoba	VE4BDN	Brandon		6.34-6.94

UPDATES NEEDED

QSL CONTEST


Sailing, sailing, over the... Your editor spent many wakeful nights this month trying to pick a QSL Contest Winner. There were so many excellent entries that reaching a decision was extremely difficult. However, this card sent in by Russell Butterworth WA6TJS/mm, had that special something that set it apart from all the others. Perhaps it's the lure of the sea that tugs in all of us. Nevertheless, congratulations Mr. Butterworth and your boat, the Spucomba.

Is your card something special. Does it arouse oohs and ahs from visiting hams. If so, you have a chance to win a one-year subscription to 73. Send your winning entry to 73 Magazine, Peterborough NH 03458.




WA6TJS

MM

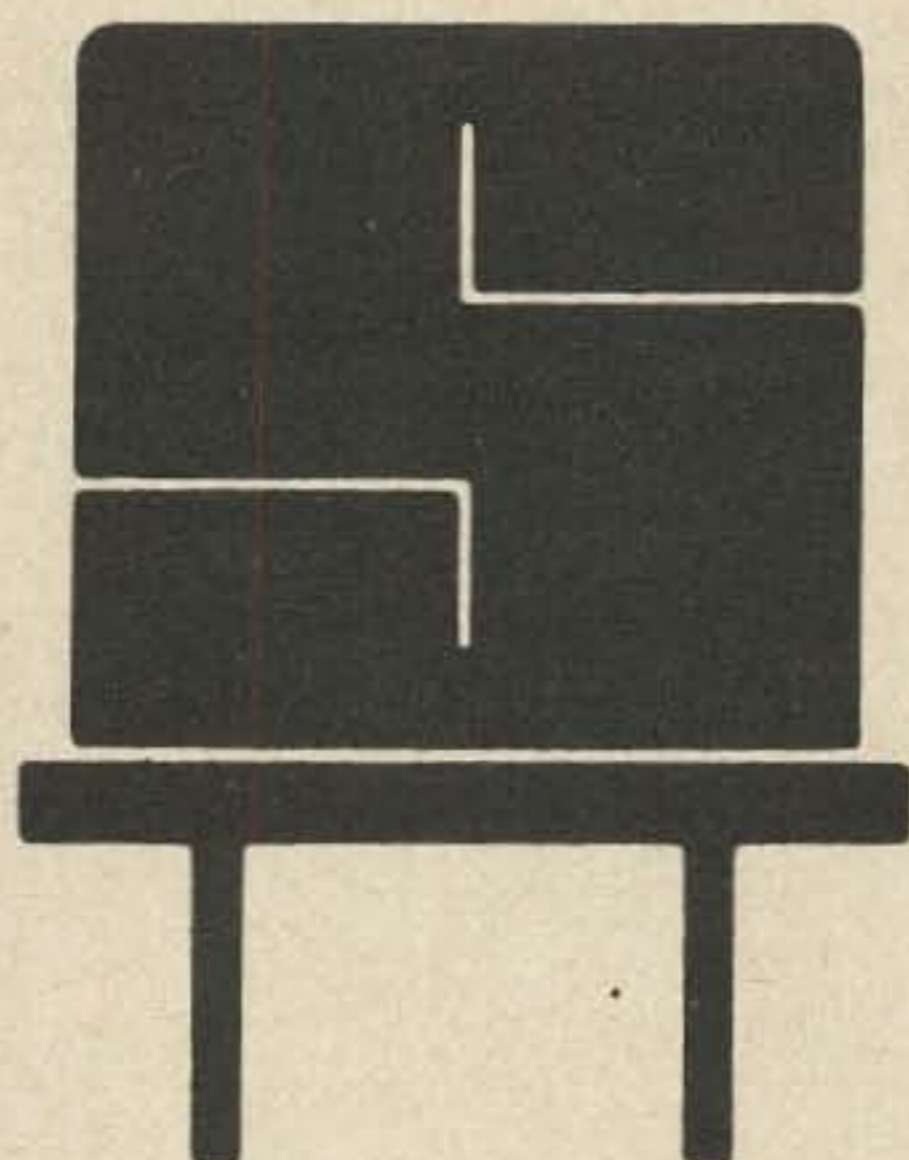


REPEATER OWNERS

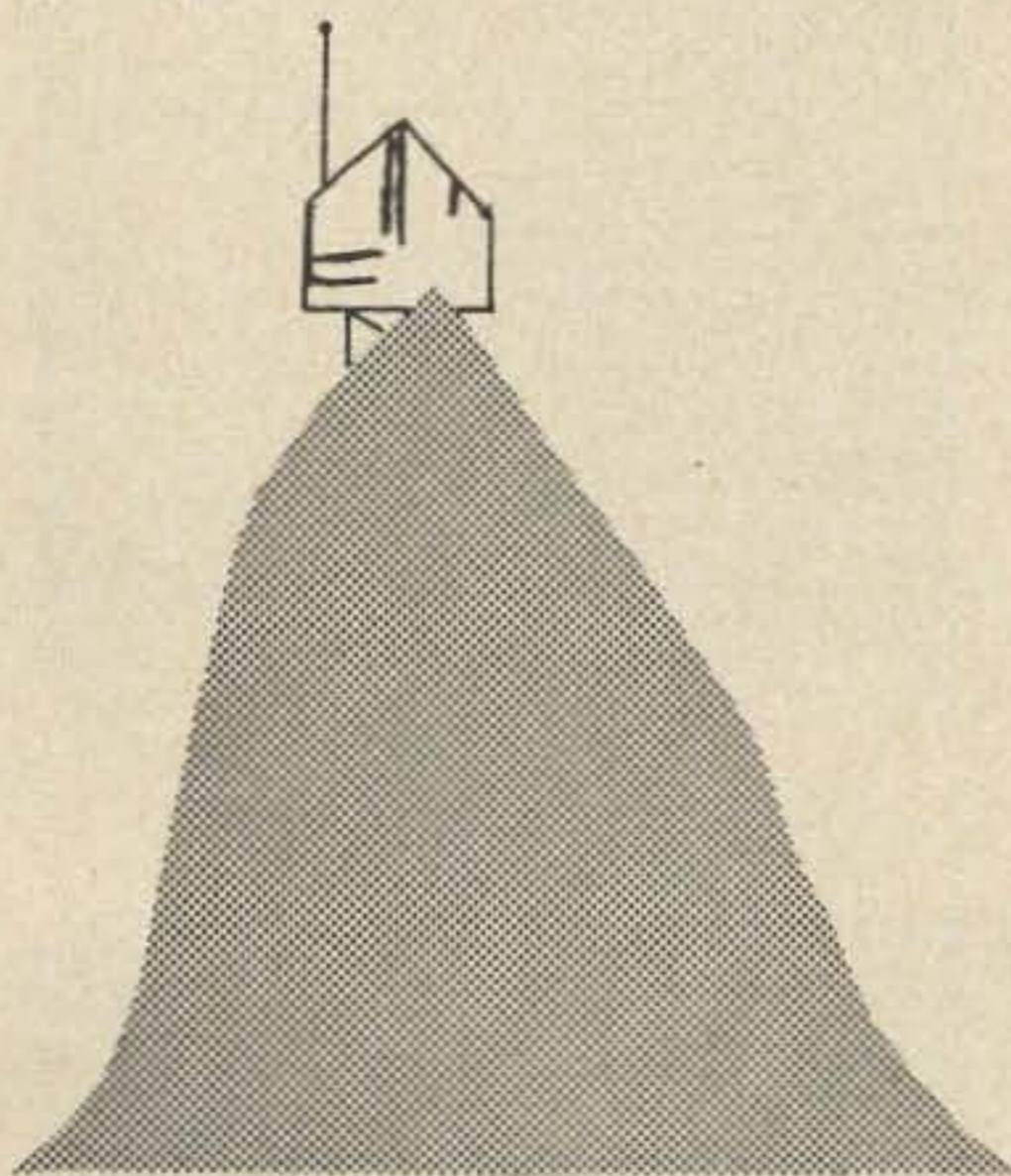Don't Take Chances. SENTRY offers custom made crystals made exactly to your specifications. When it comes to crystals for your repeater, BUY THE BEST - SENTRY.



REPEATER USERS

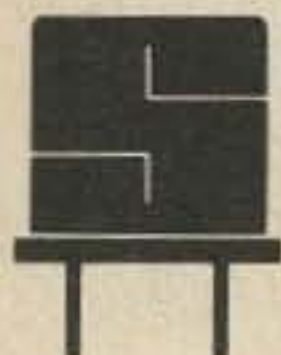If you want reliable access to the repeaters in your area, you want and need SENTRY CRYSTALS. SENTRY CRYSTALS are custom made for your rig. We don't stock a large quantity of crystals for a certain frequency and hope you can tweak them to frequency in your rig. We do offer FAST service on crystals made especially for you and your rig. If you want reliable, on-frequency operation, INSIST ON SENTRY.



SENTRY MANUFACTURING COMPANY
Crystal Park, Chickasha, Oklahoma 73018

PHONE: (405) 224-6780

TWX-910-830-6425

Caveat Emptor?

Price — \$2 per 25 words for non-commercial ads; \$10 per 25 words for business ventures. No display ads or agency discount. Include your check with order.

Deadline for ads is the 1st of the month two months prior to publication. For example: January 1st is the deadline for the March issue which will be mailed on the 10th of February.

Type copy. Phrase and punctuate exactly as you wish it to appear. No all-capital ads.

We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.

For \$1 extra we can maintain a reply box for you.

We cannot check into each advertiser, so Caveat Emptor . . .

THE 27th ANNUAL Turkey Run Hamfest and VHF Picnic, sponsored by the Wabash Valley ARA, Inc., will be held Sunday, July 28, at Turkey Run State Park near Rockville, Indiana. Don't miss the Midwest's finest fleamarket. Fun for the whole family: XYL Bingo and fleamarket; food and refreshments, camping facilities, and park recreation for the kids. First Prize: Genave GTX-10, Second Prize: Regency HRT-2, Third Prize: Drake WV-4 VHF Wattmeter; plus many more. Activities begin at 9:00 AM with free coffee and doughnuts. Talk-in 146.94 by W9UUU/9. For details, send SASE to WVARA Hamfest, Box 81, Terre Haute IN 47808.

AUTOMATIC TELEPHONE Answering Computer. The best available. List \$239.95. I have two new and still in boxes for \$150.00 each. Warranty is still good. First check takes one or both. WB8CTA, 1000 Moore Road, Conway MI 49722.

U.S. GOVERNMENT Topography Maps in six colors are available for most areas in U.S. Send \$2.00 and latitude & longitude for each map. Write: Maps, 274 Mainzer, W. St. Paul MN 55118.

TELETYPE EQUIPMENT For Sale: Models 14, 15, 19, 28, 32, 33. TD's, Reperfs, KSR's, ASR's. Parts or complete machines. Write needs and send SASE for complete listing and prices. Larry Pflieger, 10615 W. Ridge Rd., Apt. 54, Hales Corners WI 53130.

SALE-TEST EQUIPMENT: Heath TV Alignment Sweep Generator IG-52 \$35.00; Pyramid Capacitor/Resistance Meter, 10 pf-2000mf-25megohm \$30.00; Dumont Electronic Switch/Square Wave Generator \$15.00; Heath Color Bar/Dot Generator CD-1 \$20.00; Heath VTVM V-7A \$19.00. All good working condition. Add approx. postage. Michael Windolph, 3140 Meramec, St. Louis MO 63118.

EQUIPMENT FROM 73

The following list of gear, unless otherwise noted, consists of brand new equipment purchased for testing purposes only. Some have been tested, some remain unopened in original cartons. We are offering this gear at a considerable discount on a first-come-first-served basis. Please send Money Orders or Certified Checks only to 73 Magazine, Peterborough NH 03458.

MITS 908M Calculator w/p.s./case (\$143) new	\$ 100
Logiclocks (\$120 new) 3/4" numbers - 6 figs	\$ 75
Heath 1B-101 counter (\$170) - 5 figs	\$ 140
Vanguard Scaler - by 10 - to 200 MHz (\$120)	\$ 75
Clegg 21 220 MHz xcvr - new (\$300)	\$ 235
Regency 16ch scanner TME-H-LMU (\$300) - new	\$ 245
SBE Scanvision, complete, like new (\$900)	\$ 500
Robot Monitor - new (\$295)	\$ 240
Pickering CW keyboard KB-1 (\$265) - tested	\$ 175
Heath HW-202 - brand new (\$180)	\$ 165
Heath HA-2022 amplifier - new (\$70) - built	\$ 65
Gladding 8ch scanner - Cheyenne - brand new (\$150)	\$ 99
Gladding Hi-Scan - 8ch scanner - tested (\$180)	\$ 99
Genave GTX-2 - used (\$250)	\$ 180
Motorola KW 2m amplifier - used	\$ 350
Heath IC-2009 calculator - brand new (\$92)	\$ 88
SBE-450 xcvr - new (\$450)	\$ 299
Standard 1400 2m 22ch xcvr 10w (\$550) - used	\$ 250
Heath HWA-202-1 power supply - new - built (\$30)	\$ 25
Signal One CX7-A - tested - perfect - like new - fantastic	\$1990
Kenwood Twins - Tested - like new (\$900)	\$ 750
Standard 146 2m HT - used (\$289)	\$ 190
Fannon intercom - exc - 6 ch master - (\$60) tested	\$ 35
Icom IC-80 450 MHz xcvr - brand new (\$375)	\$ 275
Concord TV camera MTC-15 ch5-6 output - tested (\$500)	\$ 250
Concord video monitor VM-12 - tested (\$400)	\$ 250
Concord all channel TV tuner Dem-911 (\$600)	\$ 250
Concord VTR - like new - fantastic (\$400)	\$ 300
Bell & Howell 2966 VTR - like new - excellent (\$995)	\$ 350
Bell & Howell 2965 portable VTR - new (\$1595)	\$ 475
Batteries for B&H 2965 - like new (\$36)	\$ 25
Vanguard 2m preamplifier - used (\$25)	\$ 15
Regency 450 MHz scanner - (\$280) - like new	\$ 140
Vantronics PA-50 2m amp (\$110) - brand new - 10w in 50 wout	\$ 75
RP tone burst gen - 5 freq - TB-5 - exc (\$37.50)	\$ 25
Electro-Voice 717 noise cancelling ceramic mike - new (\$13)	\$ 10
Hitachi stereo cassette recorder - exc - (\$120)	\$ 75
Hitachi AM-FM cassette recorder - exc - (\$90)	\$ 50
Turner mike - noise can NC350DM - brand new	\$ 30
Vanguard com 144-146/14-15 MHz -407 - new (\$50)	\$ 40
Antenna Spec rubber ducky antennas HM-4 2m	\$ 4
SWR meter - exc (\$25) KW	\$ 12
Test Labs - 10 in 1 - SE-400 (\$25) as is	\$ 10
Concord stereo recorder-changer - 12 cassettes (\$240) brand new	\$ 135
VTR Monitor - exc - Hitachi (\$225)	\$ 125
Radio Shack Code cassette - new (\$6)	\$ 4
Regency HR-5 (\$240) six meter 10w xcvr 12ch	\$ 199
Standard SR-C826M (\$360) 2m 10w xcvr 12 ch	\$ 299
Regency HR-220 (\$239) 220 MHz 10w 12 ch	\$ 199
Regency ACT-RBH/L Scr (\$160) VHF/UHF 8ch scr receiver	\$ 136
Standard SR-C826MA (\$398) Latest model 10w 12ch 2m xcvr	\$ 339
Regency HR-2MS (\$319) 2m 15w xcvr with 8ch scanner	\$ 269
Icom IC-22 (\$289) 10w 22ch 2m xcvr	\$ 245
SBE SB-450TRC (\$180) 450 MHz transverter	\$ 149
SBE SB-1PA (\$190) 10w in 40w out power amplifier 2m	\$ 159
Pace 10-4H (\$80) Scanner VHF 4 channel	\$ 69
Regency Pocket scanner 4 channel ACT-P4H (\$120)	\$ 99
Cobra 220 MHz Transceiver 10w 12ch (\$300)	\$ 255
Amphenol RG-8/U Polyfoam 100' with PL-259 connectors (\$24)	\$ 19
Icom IC-21 (\$359) demo unit - perfect shape 10w 22ch ac/dc	\$ 299
Standard 14U 2m 22ch superfantastic rig, VOX (\$510) demo	\$ 499

All Prices fob: UPS collect.
73 Magazine - Peterborough NH 03458

THE ORIGINAL FM Hamfest Sunday August 4, 1974, near Angola IN. Free flea market, entertainment for ladies and kids. Picnic grounds, campsites, boating, food, soft drinks, available rain or shine. For information contact: Fort Wayne Repeater Assoc. Box 6022, Fort Wayne IN 46806.

TECH MANUALS for govt. surplus gear - \$6.50 each: R-390/URR, R-220/URR, URM-25D, CV-591A/URR, CV-278/GR, TRM-1, TS-382D/U, TS-497B/URR, TT-63A/FGC, URM-32. W3IHD, 7218 Roanne Drive WA DC 20021.

COLLECTORS ITEM, Nazi Kwea German Wehrmacht WW-II Receiver, magnesium alloy chassis, working condition, spare tubes. Freq range LW-BC-SW with crystal calibrator. Requires 2 volt filament, 90V plate. WT, 100 pounds FOB Dartmouth, N.S. Best offer over \$400.00. Contact Jim Murphy VE1PV, 100 Joffre Street, Dartmouth, Nova Scotia.

FREE CRYSTALS with the purchase of any 2m FM radio. Write for our deal on the rig of your choice. Factory-authorized dealers for Regency, Drake, Icom, Kenwood, Tempo, Alpha, Genave, Swan, Clegg, Ten-Tec, Standard, Midland, Telex, Halli-crafters, Galaxy, Sony, Hy-Gain, CushCraft, Mosley and Hustler. For the best deal around on HF or VHF gear, see us first or see us last, but see us before you buy. Write or call us today for our low quote and become one of the many happy and satisfied customers of Hoosier Electronics, R.R. 25, Box 403, Terre Haute IN 47802. 812-894-2397.

FLEA MARKET/AUCTION/PICNIC! Hall of Science Radio Club annual event Saturday June 8 10am-4pm Flushing Meadow Park Queens, 111th St. 48th Ave. Rain date June 15. Admission \$1.00 - sellers \$2.00 no commissions. Auction service at 10% fee. Free parking. Zoo, Children's Farm, golf, boating museums adjacent. Info 212-699-9400 or write Box 1032, Flushing NY 11352.

DANVILLE HAMFEST at Douglas Park in Danville IL on September 1, 1974. Take Bowman Avenue Exit off I-74 and follow the signs. Prizes will include a low-band rig and VHF gear, antennas, electronic keyer, watt-meters, SWR bridges, and many others. Camping and motel accomodations nearby. Food and plenty of parking available. Huge flea market and commercial displays. Tickets are \$2 or three for \$5. Advance tickets available from Dave WA9PDS, Dolan Rd., Catlin IL 61817. Send check or M.O. and SASE. Talk-in on 22/82 and 94 simplex.

NE555V: \$1.10, 8038 Waveform Generator: \$6.95, 1103 (1024 Bit Ram): \$4.50, DG200BA Analog Switch: \$3.25, 2N6084 RF PWR: \$10.50, 74181 Alu: \$3.75, Catalog: 10¢. ELECTRONIC DISCOUNT SALES, 138 N. 81st St., Mesa AZ 85207.

G.E. MASTR 100W highband RPT or base station, RPT panel, perfect cond \$400.00. G.E. Mastr 60W mobil high band U.H.S. RX 8 freq, 6 inc. \$375.00. G.E. Port-a-mobil high band 10W 94 16-76 with charger \$250.00. Jim Maloney, 2670 Tierra Cir., Winter Park FL 32789, Ph. 305-678-0244 after 8PM.

KLM AND MADISON ELECTRONICS present the finest in VHF antennas. 144-148MHz, 7-element to 16-element; 9-element \$31.95; 14-element \$45.95; 16-element \$49.95; 220MHz; 420-450MHz, 14-element \$19.95; 27-element \$41.95; write literature. All prices FOB Houston. Free flyer. Madison Electronics, 1508 McKinney, Houston TX 77002. 713-224-2668; Nite 713-497-5683.

MIX PLEASURE with pleasure at the Hamburg International Hamfest on September 21. For information contact Lin Brownell WB2HCL, 210 Buffalo, Hamburg NY 14075.

WANTED: HT200 2 meters, any condition. State price and condition. Ron Dierkens WA6QVE, 3367 Ellington Dr., Altadena CA 91001.



Bill Pasternak WA2HVK/6
14725 Titus St. #4
Panorama City CA 91402

Guess by now you may have gotten the idea that Sharon and I are very happy and proud to be a part of the "Southland." I am also quite proud of an amateur organization out here that some two and a half years ago begot itself into existence and in short order straightened out the mess that was the Southern California FM scene. True, like any other part of the nation we too have our problems from time to time, but the Southern California Repeater Association has never run away from any of them. Quite the contrary, they have faced any and all situations with a willingness and objectivity that is unsurpassed. While not everyone is always happy with their decisions, the record is proof positive that the majority of the FM populous has benefitted from what they have done and will continue to do. On March 24, SCRA held a meeting and this time I was able to attend and see the SCRA in operation for myself.

Aside from the election of Dick Flanagan W6OLD, as their 1974 chairperson, the most important announcement made was that of the FCC granting the WR6ABB repeater "Special Temporary Authority" referred to as STA for development and implementation of a fully automatic remote control system for the machine. Thanks to the hard work of Dick McKay K6VGP, outgoing SCRA chairperson and Fred Deeg K6AEH, the trustee of WR6ABB, permission has been granted for the *Palisades Amateur Radio Club* to utilize the repeater input channel as a secondary control frequency and designate certain individuals that the club selects to control WR6ABB via this system. The STA stipulated that the existing wire-line control system was to remain as primary control system and that the secondary, on-channel system was

SB-102 FOR SALE. Excellent condition. Prefer Dallas-Fort Worth area buyer. Must deliver in person. Call or write 817-293-2128, 6920 Stonewall, Fort Worth TX 76119.

DRAKE 2B, all crystals, manual, calibrator, excellent \$160 plus shipping. John Skubick, 1040 Meadowbrook, Warren OH 44484.

FOR SALE: NCX-5 MK11 Digital, 200W, 10-80 SSB, CW, AM transceiver with matching NCXA power supply-speaker and manual. \$350.00 Jim W1VYB 617-922-3850.

GIVE your voltmeter a memory. Don't look the other way with meter probe in the works. Details free. Dan WN8RJZ Box 423A, Owosso MI 48867.

only to be used when a designated control operator was within reach. Moreover, it was stipulated that all regular users of the machine would be considered to be "Official Repeater Observers" and put upon them the responsibility of immediately notifying either a primary or secondary control operator in the event of malfunction or misuse of the repeater. According to Fred, the system will be in operation in the near future. If this experiment runs well, and there is little reason to doubt it will, a petition for rule-making will be presented to the FCC by the SCRA when the STA expires in mid-September. However, both P.A.R.C. and SCRA are determined to go by the book in this matter, and knowing both groups as well as I do, I can assure the FCC that they will get an accurate report on the outcome of this authorized experiment, as they have requested in the STA. It is my sincere hope that we here in the Southland can lead the way in easing the control restrictions that all repeaters now must operate under.

One of the major problems that we face here is the overcrowded conditions that exist on 2m within the 146-148MHz spectrum. Even with all standard repeater allocations filled and one machine sharing a 1MHz plus special split with simplex there are not enough channel pairs to go around. Yet, the SCRA continually receives requests for channel allocations from new groups that want their own 2m machine. To that end, a resolution was adopted to study the feasibility of issuing split-split or tertiary channel allocations in this area. For those of you unfamiliar with the term split-split it means putting new repeaters halfway between already existing machines. As you may know from past writings, I was personally involved in such a project back in NY about three years ago and from personal experience I can attest to the fact that it can be done. In fact, the job should be much easier today owing to the many improvements in the receiver selectivity of today's newer transceivers. Add to this the type of terrain we have, i.e., mountain vs valley, and I can see successful doubling of the available number of available allocations. The SCRA Tech

Committee was delegated to study the matter and make recommendations on the matter at the next meeting and LW will keep you informed of the outcome.

Finally, a new concept in amateur repeaters is being born in Phoenix AZ. The sponsors of WR7ABT call it a "Full Service" amateur repeater and the first of its kind anywhere in the U.S. By using a number of tape recorders and touchtone control, and being very careful in providing program material that will not violate the Commission rule prohibiting broadcasting, WR7ABT will soon provide its users with such diverse material as multi-speed code practice, assistance in correcting FM problems, location and time of radio club meetings and other information that will be of benefit to their amateur community. One innovation that they are incorporating I think is of top benefit. How many times have you been in QSO only to have another ham break for a signal or deviation report. One of WR7ABT's new services should eliminate this. An operator will be able to access a tape recorder via the repeater, make a 10 second test transmission and then play him or herself back for a first-hand look (or hear) of the way they sound. Now that one I really like and if I ever put up a machine again that's one idea I will be sure to incorporate. LW wishes Phoenix good luck with their "second generation" machine.

I usually close with a little aside or comment, but this time I will answer a question; an important one to me. Many times I have been asked why I write a monthly column. It's not for money or glory, but rather it's because I sincerely believe in the following, "Congress shall make no law respecting an establishment of religion, or prohibiting the free exercise thereof; or abridging the freedom of speech or of the press; or the right of the people to peaceably assemble, and to petition the government for a redress of grievances." If perchance you didn't recognize it, you have just read the First Amendment to the Constitution of the United States of America. To that ideal and to the betterment of amateur radio I devote this column.

WA2HVK/6

NEW PRODUCTS



73 TESTS THE IC-230

ICOM has come up with a two meter transceiver which has set many manufacturers to burning the mid-night oil in their labs. It has 66 channels of synthesized operation, and that covers all of the standardized FM channels from 146.0 to 148.0 — the dial readout is for the receiver and the transmitter can be switched to send 600 kHz higher or lower, as well as on the same channel for direct (simplex) communications. It is exceptionally versatile.

The receiver, which is the most important aspect of any transceiver, is a beaut. Mr. Inoue and his engineers went for every dB they could with this one, always being careful not to forget the probales of intermod, overload, and other discouraging miseries we've had with more than one of the other rigs on the market.

The receiver is dual conversion. Single conversion is on the horizon, but we haven't tried a receiver using it that was quite as good as a well designed double conversion job. They'll be along, you may be sure, as the scientists cram more and more transistors into those IC chips. The 230 has an FET front end and high-Q helicalized cavity resonators to keep out the garbage. By keeping the gain in the i-f the Icom gang got rid of a lot of the overload problems. They made up for it with a six stage i-f amplifier. The two local oscillators are zener regulated for stability.

The transmitter puts out at least ten watts and is also zener regulated in the oscillator. It is load protected in case your antenna falls off or gets shorted, and the low pass filter in the output will be appreciated by television viewers you drive past.

Now, outside of all the technical data on the unit, how does it work? Is it easy to change channels while driving?

The rig, being very small, mounts just about anywhere in a car. We put it on the side of the transmission hump next to my knee, facing up. It didn't take a half hour to get into

place, even for a mechanical klutz. This puts the controls in easy reach of the hand, including the upper-lower offset switch for the transmitter which is on the top of the unit instead of the front panel. You have to get at this one when you move to the 147 MHz channels unless you make a small modification to put that function on the 146-147 MHz segment switch — and this is a very simple mod.

There are two knobs for switching channels, one for the hundreds of kHz, and one for the 30-kHz jumps. With this simple system you can switch from one repeater to another without even looking at the rig — which is excellent for driving. You just count the switch positions as you turn the knob. This is particularly handy for someone like Wayne who has to put on his glasses for the simplest of reading. It's a bore having to put your glasses on in the car just to change a repeater channel.

The 66 channels makes it so you can use most of the repeaters on the air today. If you do much traveling you'll appreciate having every standard channel in the rig. How many crystals would that take? If you wanted them all it would take 132 crystals, and at \$4 each that would come to \$528. You could get by for half that because most of us don't need the reverse pair crystals, but that is still a bundle.

The ICOM will put you on the reverse pair, if you want. This is almost imperative these days when you are flying so you won't lift every repeater for three hundred miles around every time you talk. It's also useful when you are close by the other op and can get him better on the repeater input frequency than the output. It happens.

If you hook another 230 owner you can use any of the simplex channels for fairly private contacts. Or even a locally unused repeater input or output channel.


The ICOM 230 has worked without a flaw all through the New Hampshire

winter, from about 20 below zero on up. It has always been right on channel on both transmit and receive, and it has always sounded superb. It is one of the few ham rigs that works well on top of the local mountain. Most of them have trouble with the several commercial repeaters up there, or even miseries from ham repeaters on adjacent channels. One well known rig loses sensitivity and cross modulates when the next channel lower is coming through strongly. Another very well known rig is totally useless on the mountain — everything comes through.

About the only drawback of the IC-230 is that it doesn't get the splinter repeaters, but even that can be corrected by changing a crystal, if you've got splinters in your area.

Bravo ICOM 230.

PUSH-PULL AMPLIFIER APPLICATION NOTE

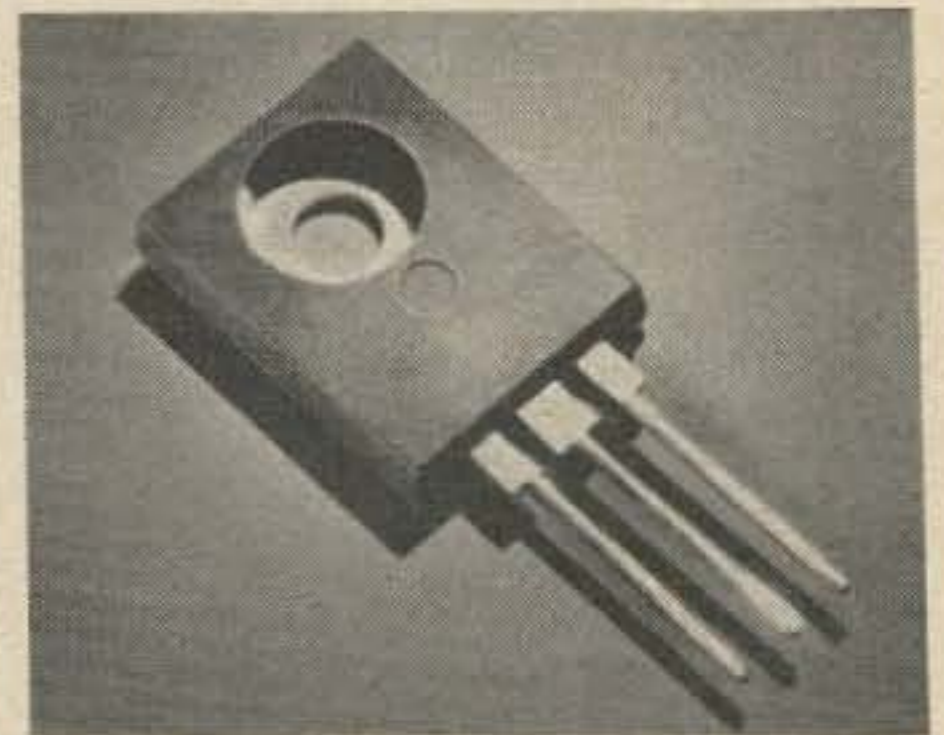

The advantages and design of broadband push-pull amplifiers are described in an application note available from TRW Semiconductors. The 8-page application note discusses, in particular, 60 and 120W 225-400MHz push-pull amplifiers using TRW J02000, J02005 transistors.


The application note describes the basic concept of the push-pull approach and compares it with conventional designs.

Schematic drawings present the complete electrical circuit for 60 or 120W push-pull amplifiers, and layouts for components, heat sinks and circuit board. The electrical circuit for a push-pull driver amplifier providing up to 30 watts output is also presented.

The application note includes specification ratings, electrical characteristics and package dimensions for TRW J02000 and J02005 rf Power Transistors. The units incorporate internal integrated circuits to reduce the effects of the reactive part of the input impedance to nearly zero. J02000/J02005 units are rated for 30/20 watts and 200-400 MHz.

Further information and a copy of the application note are available from Sales Manager, TRW Semiconductors, 14520 Aviation Blvd., Lawndale, CA 90260; phone (213) 679-4561.

REALISTIC TIMEKUBE RADIO

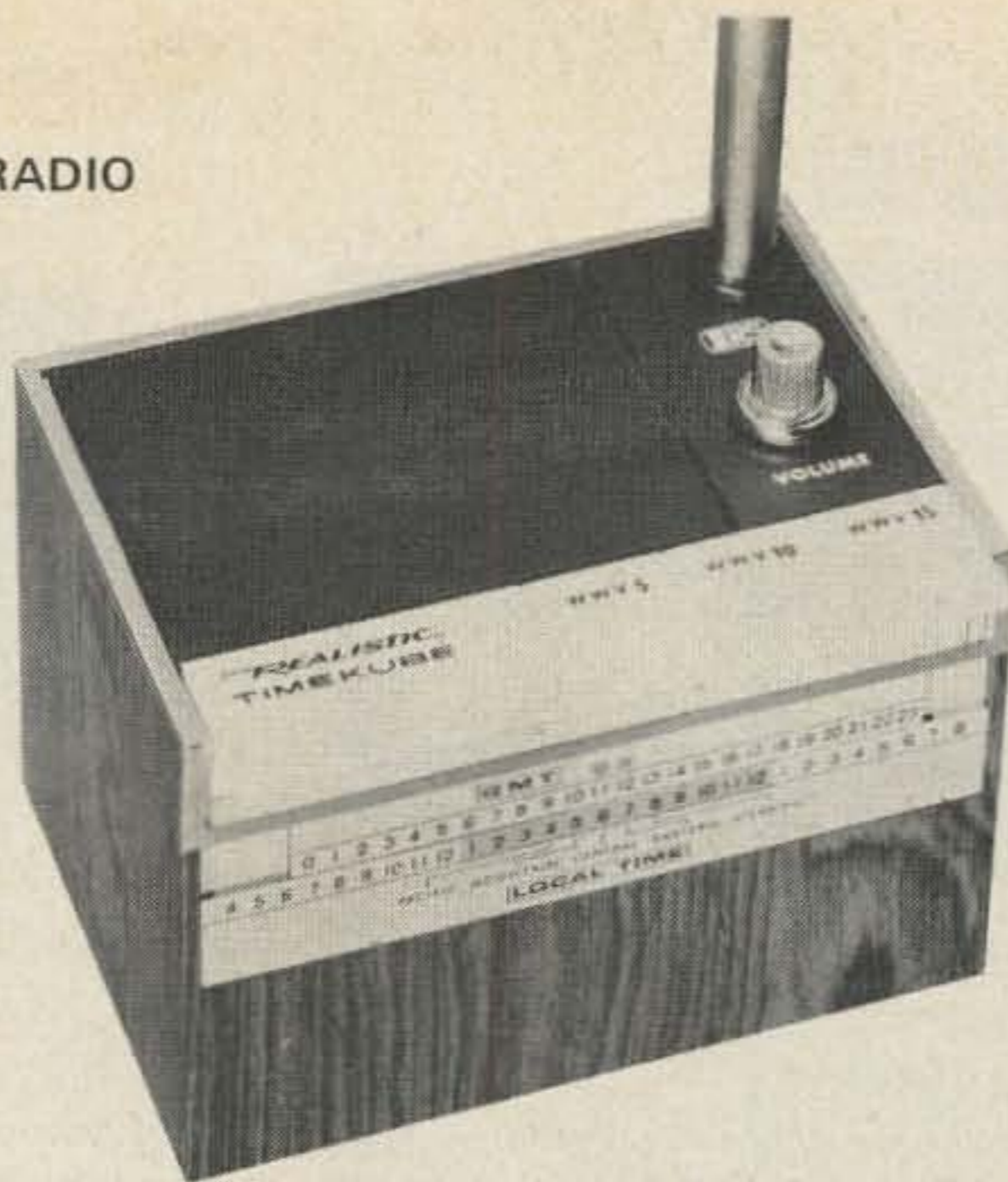

Even if you don't have time on your hands, now you can have it at your fingertips with the new Realistic Timecube (TM) radio from Radio Shack.

A sliding scale on the front of the Timecube allows instant conversion of UTC to local time. Pushbutton selection of three different WWV frequencies (5, 10 and 15 MHz) is said to assure optimum reception in all parts of the country at any time of the day or night. National Bureau of Standards time signals are controlled by an atomic clock which is accurate to within 20 billionths of a second per day, or within one second in 31,709 years!

Some of the additional data broadcast by WWV includes: geophysical alerts and summaries of geophysical events during the previous 24-hour period. "At sea" weather information is broadcast in three 45-minute segments four times in each 24-hour period.

The Realistic Timecube desk radio, in simulated rosewood case, 8.26cm x 11.75cm x 8.89cm (3¼ x 4-5/8 x 3½"), is priced at \$49.95. Operates on one 9V battery.

Realistic products are available from more than 2,500 Radio Shack stores.


McMOS DATA BOOK

Over 300 pages of product data, basic technology information, applications information, and product selector guides are included in the new "McMOS Integrated Circuits Data Book," from Motorola. Just off the presses, it is probably the most comprehensive product directory of complementary MOS circuits ever produced.

The McMOS product line cataloged in this new book includes complete data on 68 separate functions. These devices plus 12 new devices introduced in late 1973, (not included in the book) offer the system designer a choice of 80 logic functions. It is now possible to implement any type of digital system using McMOS circuits; therefore, presenting the design engineer with the same type of design flexibility in CMOS that before was possible only with bipolar logics such as MECL 10,000 and DTL/TTL from a logic design point of view.

Order your copy of the, "McMOS Integrated Circuits Data Book," by sending \$2.50 to: Technical Information Center, Motorola Semiconductor Products, Inc., P.O. Box 20924, Phoenix AZ 85036.

SUB-MINIATURE SENSOR

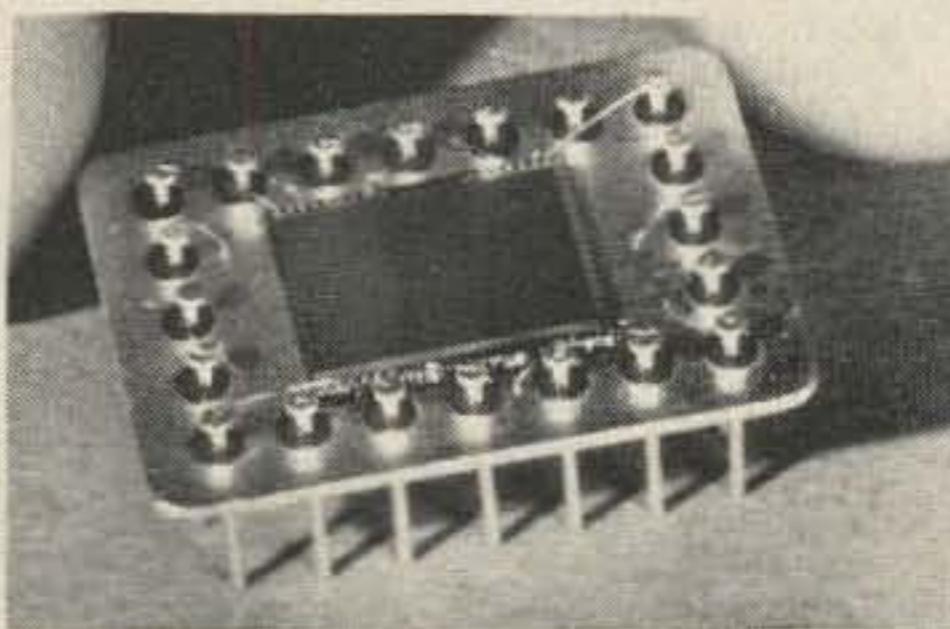

A miniature optical sensor no bigger than an adult's thumbnail has been developed by General Electric Company for use in hand-held or vest-pocket TV camera systems for a host of uses in business, industry, government and the home.

Making possible a tubeless TV camera no larger than a pack of cigarettes, the tiny solid-state sensor and essential circuitry is called a "CID Module" (Charge Injection Device) and converts optical images to electrical video signals.

With decided advantages over tube and other solid-state imagers, GE's CID Module brings into sharp focus the possibility of completely new imaging and sensing systems in the foreseeable future. Such systems in-


clude home video, industrial control, TV cameras, security systems, auto safety, supermarket checkout and numerous other applications for systems' manufacturers and users.

The dynamic range of the CID module — approximately 500:1 — provides broad gray shade or tonal rendition exceeding the performance of conventional image tube cameras.

Matrix readout of the CID sensor provides several inherent advantages over existing solid-state technologies. Total area of the CID device is used for sensing, thereby providing higher sensitivity than devices requiring transfer and storage in their readout technique. "Random access capability," also provides a valuable characteristic for applications such as low bandwidth communications and guidance systems.

The tiny 100 x 100 image sensor by GE's Optoelectronic Systems Operation, here, is only 1/4-inches long X 3/8-inches wide and consists of a two-dimensional array of 10,000 charged storage image sites. For more information write: *General Electric, 2100 Gardiner Lane, Louisville KY 440205.*

HIGH POWER PLASTIC TRANSISTOR SERIES

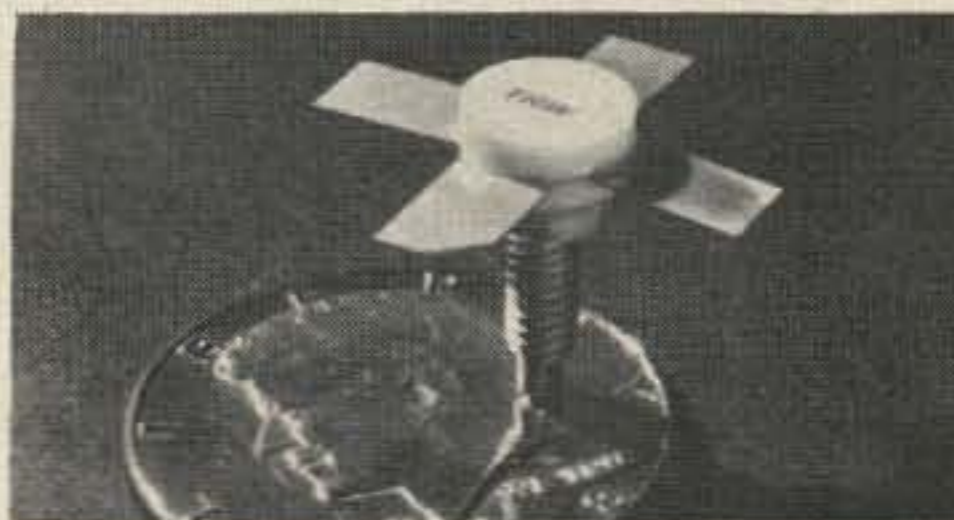


Motorola's new 2N6497, 2N6498 and 2N6499 silicon NPN power transistors have dissipation ratings of 80W Pd' made possible by a significantly better plastic package. Motorola's type 199 plastic package design eliminates mechanical mounting stress while providing improved heat transfer characteristics, and convenience and cost savings in mounting.

These devices are rated at 5A dc continuous collector current 10 Amperes peak, and have a Gain-Bandwidth product of 5 MHz. Well suited for inverter and ignition system applications as well as general purpose use, this series is priced 15 to 25% below comparable metal parts.

The 2N6497, 2N6498, 2N6499 are rated at 250, 300 and 350 Vdc VCEO respectively, and priced at \$1.55, \$1.85 and \$2.75 in 100-999 lots. Convenient mounting hardware for this series is also available from Motorola.

For further information please contact the *Technical Information Center, Motorola Semiconductor Products, Inc., Box 20924, Phoenix AZ 85036.*

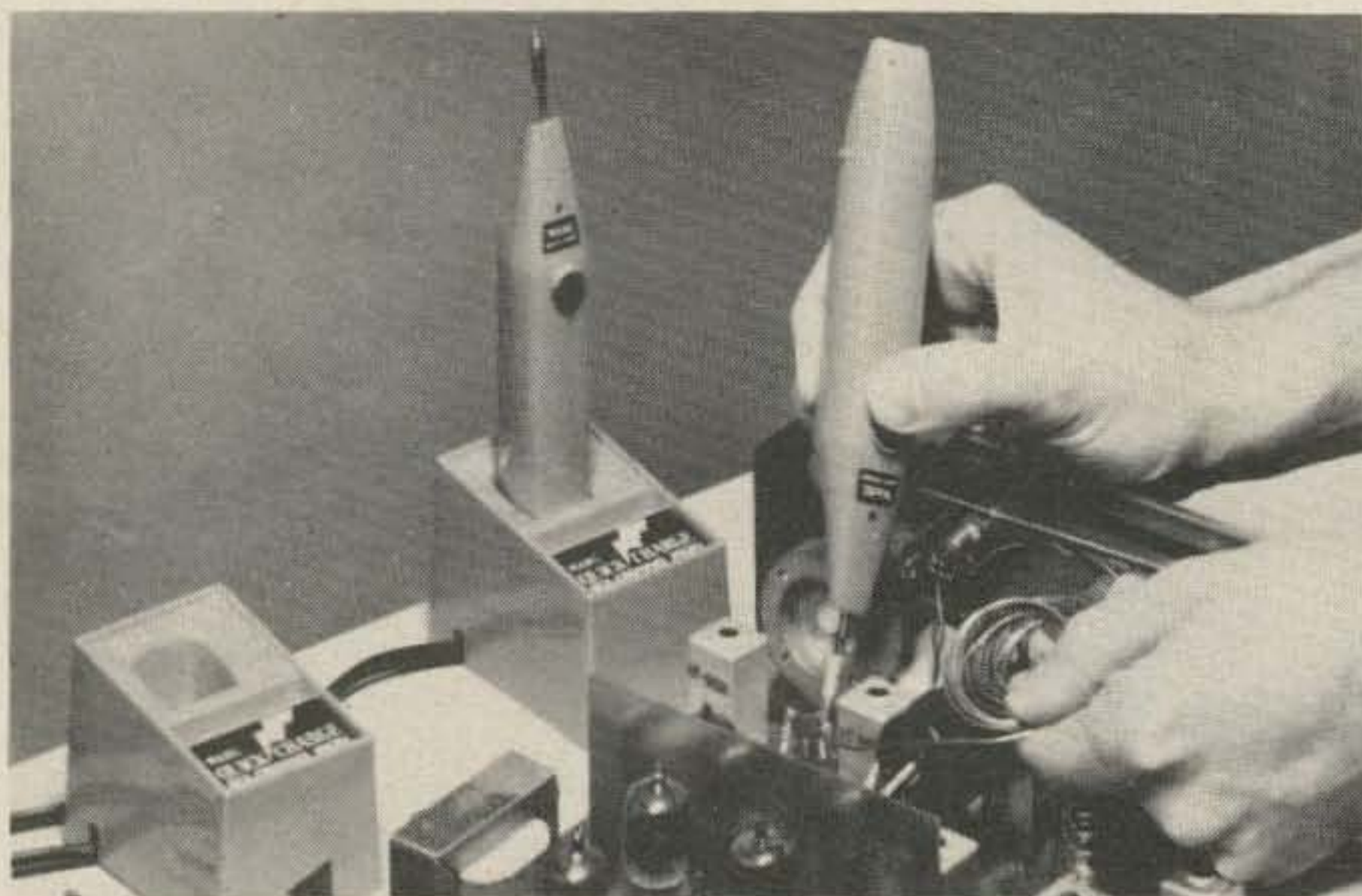QUICK CHARGE CORDLESS ISO-TIP SOLDERING IRON



Wahl eliminated the cord from the soldering iron quite some time ago with its 'Iso-Tip' Cordless Soldering Iron. But now it's cordless for even a greater percentage of the time with the new, orange, "Quick Charge" Iso-Tip.

This decrease in recharging time is due to the "Quick Charge" iron's special premium quality long-life nickel cadmium batteries. These batteries are designed for charging at high rates for longer periods of time without deterioration and will outlast standard batteries.

The new lower base stand (with slot for spare tip) will return a partially discharged battery to full capacity in an hour or two. And a completely discharged battery can be fully recharged and used again in about 4 hours, giving tip performance equivalent to up to 50W and over 700° temperature.

The "Quick Charge" has the same low voltage and special isolated-tip construction as the original 'Iso-Tip' which eliminates electrical leakage and the need for grounding, reducing and the risk of heat damage to sensitive components. The tip is easily replaceable with any of the 4 completely different tip sizes from heavy duty to

fine. The manufacturer *does* caution against interchanging a 'standard' Iso-Tip and a "Quick Charge" stand, however, as the units are not interchangeable.

Pressing the button gives you soldering heat in 5 seconds plus a built-in work light on the working area. Pilot light, too. And an exclusive "lock off" switch to prevent accidental heating of the tip.

The unit is designed for good "feel" and balance — only 8 inches long with tip and weighs just 6 ounces. The "Quick Charge" carries enough power to make up to 125 electronic joints (or more) per charge. And it automatically begins recharging when replaced in its stand. No wires to connect; no "positioning" of the iron in its stand. And it can't overcharge itself.

Model 7700 "Quick Charge" kit consists of Cordless "Quick Charge" Soldering Iron; Separate Recharging Stand; One #7545 Fine Tip; One #7546 Heavy Duty Tip; and an instruction booklet.

For further information contact your local electronic dealer or *Noel Wallen at the Wahl Clipper Corporation, 2902 Locust Street, Sterling, Illinois 61081. Phone: 815-625-6525.*

SIMULTANEOUS READ/WRITE MEMORY

A high performance 16-bit Multiport Register File capable of reading 4-bits and/or writing 2-bits at the same time has been introduced by Motorola. Designated the MC10143L, this MECL random access memory is an excellent example of a large scale integrated (LSI) device produced in the very fast MECL 10,000 series logic family. This versatile memory unit has a complexity equivalent to 110 gates. Access time to any four bits is 10 nanoseconds while simultaneously writing in new data.

The ECL outputs of the MC10143

are capable of driving transmission lines directly eliminating translator delay times. Outputs of the MC10143 can be wire ORed together or several register files can be combined on a bus line. On chip decoders and write amplifiers reduced the number of external components required to use the MC10143.

For further information contact: *Technical Information Center, Motorola Inc., Semiconductor Products Division, P.O. Box 20924, Phoenix AZ 85036.*

HV POWER SUPPLY



The James Millen Manufacturing Co., Inc. is pleased to announce the addition of the new #90202-D Plug-in Module High Voltage Power Supply for use with small Cathode Ray Display Systems. The #90202-D supplements the other Millen plug-in modules.

The Millen #90202-D High Voltage Power Supply is designed to provide up to 1400V high-voltage dc accelerating potential and filament-heating power for small and medium size cathode ray tube indicators. The high voltage is rectified by a semiconductor bridge, producing a 120Hz ripple frequency which is filtered by a 2-stage RC filter. With a 1.1mA external dc load, the ripple voltage is less than 1.5V rms and increasing the dc output current to 3.0mA increases the ripple voltage to less than 3V rms. With the 1.1mA dc output current, the voltage provided is 1350V ac input. Since this power supply unit is not regulated or stabilized, the output voltage is proportional to the input voltage. It is possible to adjust the output voltage within reasonable limits, by varying the load current, such as by choosing high, or low, values of voltage divider resistors for the focusing and brightness control network.

The #90202-D High-Voltage Power Supply is designed for continuous service under suitable conditions where adequate ventilation is provided. Momentary short-circuits will not destroy the circuit elements internally mounted, but continued short circuits may burn out some of the over-loaded components. Hence, it is desirable to use a fuse which will prevent burn-out conditions from becoming established.

A feature of the circuit allows grounding of either the (+) or (-) terminal of the dc high voltage. The 6.3V, 0.6A filament winding is insulated to stand the full dc output voltage, with the filament connected to either the positive or negative high voltage terminal. For more information contact *James Millen Manufacturing Company, Inc., 150 Exchange Street, Malden MA 02148.*

POOR MAN'S QUAD

(If you aren't poor when you start, you will be.)

Thanks very much for the QSO, Fred. I'd like to talk with you more, but I must QRT now. I've been on for over an hour and I do have some things to do, so 73's and hope to meet you again. This is FG7XL signing off and clear and leaving the air."

The soft French accent of Monique's voice slipped permanently away, leaving only background static, punctuated by a few calls from the diehards who never can bring themselves to believe that anyone could have the temerity to turn a receiver off, just because they had politely and firmly announced that this was their intention.

Soon only the static filled the speaker of my Drake 2-B. I sat slumped in the chair, conjugating obscenities in every tense I could think of. Oh, how I wanted that first contact with Guadalupe Island! Monique had been on ten meters for over an hour. Her signal had gradually slipped as band conditions changed. As the signal faded, I had grown more and more desperate, employing every technique my slim resources could muster. My left hand vibrated with anticipation as I waited for the crucial sign-overs. Only nanoseconds could have elapsed before I had turned the transmit switch on the HT-37 and blurted out my call sign. Somehow there was always some jerk in the middle of *his* call letters when I

started mine. I tried tail-ending. The cacaphony of calls stopped momentarily and I jumped in like sly old Rennie the Fox. Back on receive. Another station is calling her with a 20 over 9 signal and capping it off by having the gall (or is it de Gaulle) to call in *French*. Naturally, she was delighted to talk to *him*.

I sat there for fifteen minutes, gradually slipping into a state of torpor, which is my equivalent for deep thought. It had been less than three months since I had been back on the air after an absence of fifteen years. I had been a ham for over twenty-five years, and there were Novices who had logged more operating time than I.

My return had been a joy after all the years of intending to get back on the air and not quite making it. I operated 75 phone to start. Having three quarters of an acre of land eliminated any antenna space problems. The 75 meter dipole was up fifty feet and gave good east-west transmission. A friend had given me a Mosley trap vertical for the other bands. He was the comptroller where I had worked and he had temporarily become interested in becoming a ham. He had purchased a brand new Drake 2-B and the Mosley vertical. He installed the vertical on his roof without any radials, and then compounded that oversight by shorting out the RG-58U at the base of the vertical. He

SCANVISION

ready to operate SSTV monitor with built-in cassette tape recorder

SBE SCANVISION is conservative—reliable—has picture-proved circuitry—is all solid state except for scope tube in monitor and the videocon camera pickup tube. Equipment fully meets all accepted SSTV standards.

SB-1MTV, monitor.

SB-1CTV, camera
complete w/11.9, 35 mm lens.

WRITE FOR BROCHURE



LINEAR SYSTEMS, INC.
220 Airport Blvd. Watsonville, CA 95076

Now—a high quality slow-scan monitor so complete that the non-engineer radio amateur can connect it to his receiver and start enjoying SSTV in minutes! The pleasure and excitement potential of SSTV can best be realized when a tape recorder is part of the system. So—**exclusive**—a cassette tape recorder is built-in—wired—matched for correct levels and impedances—ready to go. Now, tape incoming pics for future viewing. Or pre-tape self and family, station scenes, call letters for later transmission (of course, “live” pics from the camera can be transmitted directly).

was disappointed with the performance of his receiver for some reason and quickly lost interest. Subsequently I bought the Drake for two shares of stock in a glamorous defense conglomerate and \$25 cash. Some time later I accepted employment with said conglomerate and their stock promptly dropped to one-third of its former price. I maintained this was the sheerest coincidence, but my friend never lets our occasional lunch pass without a hurt reference to the stock deal. My rejoinder is that I sold him the stock, I didn't tell him to *keep* it.

Shortly after I had returned to the air I worked XE1CCW in Mexico City. Gus was putting in a tremendous signal. He said he was using a vertical on top of a flat-roofed home. The vertical was mounted on a 4 ft cement pillar and had 64 radials! He had put 16 radials for each of the four bands and they sloped down to the roof, making about a 110 degree angle to the mast. Gus reported very low SWR and high signal-to-noise ratio on all bands.

My home is one of those long, low, California ranch types with a cedar shake roof of moderate pitch. It was totally

unsuited for a duplication of XE1CWW's installation. Naturally, I attempted to duplicate his antenna.

Unfortunately I didn't have the right kind of wire. A quick calculation of the length required indicated that I would need to refinance the home to pay for No. 12 copper. Refusing to give up on that basis I found a large roll of No. 32 PE wire I had surplus from some warehouse.

Gus had said the more radials the better, so I cut twenty for each of the four bands. I made an eight inch circle of No. 12 copper and began to solder one end of the eighty wires to the circle. It takes a while to solder eighty wires. I had conceived the result to look like the spokes of a wheel. I dragged the entire mess up to the roof where I was confronted with a simple problem. The house is 107 ft long, but only 30 ft wide. The ten and fifteen meter radials wouldn't have posed any problem, *if* I could have unsnarled them from what had somehow become an extended Gordian knot. I stood on the roof grasping one end of this unplanned cable, looking as though I were

Six for less than Five!

Six channels at \$239 = \$39.83 per channel.

Five channels at \$289 = \$57.80 per channel . . .

(think about it)

2m FM Transceiver

only \$239⁰⁰

(Amateur Net)

SMALL — 8 7/8 x 1 7/8 x 2 7/8"

SIX CHANNELS! Six crystals are supplied. 94/94,
34/94, 16/76

LIGHT WEIGHT! Only 1 lb. 4 oz.

HIGH POWER — 2 watts output (draws 15 mA on
receive, 410 mA on transmit)

LOW INTERMOD — operates near transmitters without
interference.



accessories

12 Watt Amplifier


Includes steel case to hold
the 1402. Plugs into cigar-
ette lighter!

\$99⁰⁰

- Battery Charger, Model 14 BC \$29.95
- Speaker - Mike - SMI \$24.00
- Leather Case for belt - LCL \$12.00

SPEC SHEETS — write Wilson for complete info on the
finest hand transceiver on the market.

DEALERS — Call us about handling the Wilson Walkie-
Talkies (commercial version available too), the Wilson
beams, and other products.

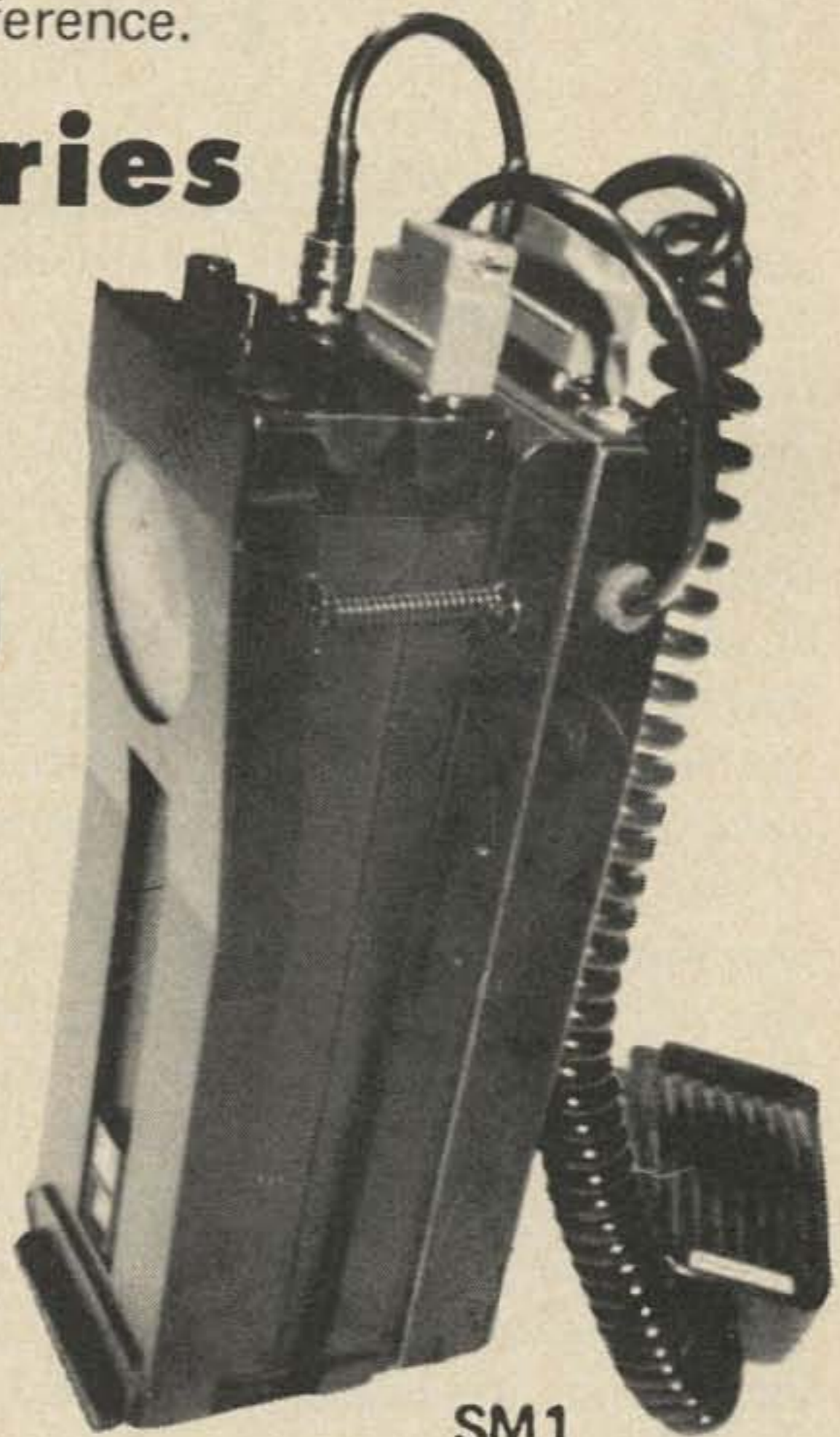

SM1

WILSON ELECTRONICS

Box 794, Henderson NV 89015 (702) 451-5791/6650

TRANSISTORS

2N3905 High speed PNP, house numbered	5/\$1.00
MJE 1093 PNP DARLINGTON, 70W, 80V	\$2.25
JAN2222A high speed NPN switch	\$.39
MPF 120 dual gate MOS FET	\$.75
MFE 2000 VHF/UHF N channel JFET	\$.75
MFE 20001 VHF/UHF N channel JFET	\$.80

8038C VCO WAVEFORM GENERATOR

New, factory parts. Full specs
\$5.75 ea., 2 for \$10.50, 10 for \$50.00

MM5314 CLOCK CHIP

with full specs \$9.50

7 SEGMENT LED READOUTS, MAN-1 Size.

RED - \$2.75 each, 6/\$15.00
GREEN - \$4.95 each, 6/\$24.00

FM MULTIPLEXER ADAPTOR

Solid State, new, with hook-up diagrams \$5.25

MC 1455(555) TIMER

New \$1.65

DTL SALES

930 Dual 4-input NAND GATE
946 Quad 2-input NAND GATE
962 Triple 3-input NAND GATE

\$.25 each, 10/\$1.75, 100/\$15.00
ANY MIX


TTL SALE

New - House numbered SN7400, SN7402, SN7410, SN7430
\$.25 each, 10/\$2.00, 100/\$17.50
ANY MIX

VISIT OUR NEW RETAIL STORE -

6522 N. 43rd AVENUE
GLENDALE ARIZONA

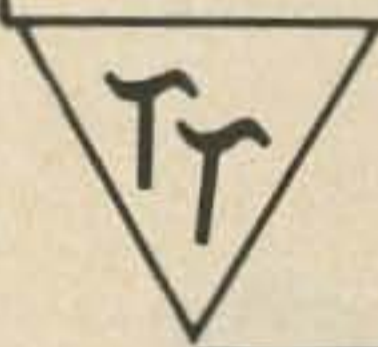ALL ORDERS POSTPAID - PLEASE ADD INSURANCE
MINIMUM ORDER - \$5 U.S./\$15 FOREIGN
LATEST LISTS - 10¢ stamp



TRI-tek, inc.

P.O. BOX 14206, DEPT 7
PHOENIX, ARIZONA 85063

posing for the cover of one of the old Bell Telephone books.

Several hours later and only minutes away from a total nervous collapse, I gave up trying to sort out the radials and just laid them on the roof and tried to spread them around in some semblance of a circular pattern. The forty meter radials dangled over the front and rear of the house. I climbed down and went inside for a drink or two.

When I emerged an hour later the sun was just dipping into the west. We were having one of those gorgeous California sunsets. The sky glowed red. It was beautiful. I turned and looked at my house. Every little curled and twisted piece of No. 32 wire had captured a glint of sunset. It looked as though a giant spider had squatted over the place and disgorged a year's supply of metallic spider web.

"Oh, what the hell," I thought, "it didn't cost anything, and I only blew one weekend." Eventually most of the forty meter radials got pruned off with hedge shears. It was this peerless contribution to the art of communications that had unsuccessfully

transmitted my pleas for recognition to Monique.

I got up from the chair and walked outside. I glared at the Mosley. There must be a better way. I quickly brushed aside the obvious, a cram course at the Berlitz School of Languages so I could call anyone in *their* native tongue.

How about those guys who always seemed to get through in spite of the pileup? They said they were using QUAD antennas. That's it. I will build a QUAD antenna and then I also will get through any pileup with my barefoot HT-37.

I got Bill Orr's book, *All About Quads*, and poured over it until the pages were dog-eared. It was the only definitive information available. I began to dream of the DX I would work with my quad. At that time I was working for a major space firm fifty miles from the QTH, so I had at least two and a half hours of driving time each day to devote to thinking about quads. I spent ten hours a day thinking about quads.

After stopping at several rug emporiums I found that rugs no longer came rolled on bamboo poles but on cardboard tubes. I called an outfit that made rattan furniture. I got a quick answer. "We don't have no bamboo for no goddammed antennas!" I surmised I had just joined a large group of Los Angeles hams looking for bamboo.

Thwarted? Not on your life! Why not just buy a ready-made quad kit from one of the several outfits on the market? *Buy?* I shrank back from that notion like Dracula from a crucifix. There must be a way.

One day at work, while I was supposed to be concerned with some business proposal, it came to me. A sudden inspiration. All great ideas are inspirations, born of that magic amalgam of insight and sheer genius. I could hardly wait for the coming weekend. My idea? Simplicity itself! Just make the spreaders out of plastic pipe easily and cheaply obtainable at the local building supply house.

I began to expand on the concept during the next two days and nights. (When I'm in a creative mood time becomes meaningless.) I would use 3/4 in. pipe for the first ten feet and a reducing coupler down to 1/2 in. pipe for the remaining three feet. I had laid a lot

of plastic pipe in the lawns and had no trouble gluing it together with solvent. I plunged on. Cross couplers would be used to insure a perfect X. For a simple two element quad I would only need 80 ft of 3/4 in. pipe and 24 ft of 1/2 in. pipe, 8 couplers, 2 cross couplers and a can of solvent.

You must realize that with us creative types the thought is father to the deed, and I was waiting outside Builders' Emporium for opening hour Saturday morning. Naturally the clod who runs the hardware section leaped to the conclusion that I was embarked on a sprinkler job and offered to show me the new pop-up heads. I favored him with a patronizing smile and allowed as how my purchases were destined for a use far above such mundane matters as lawn watering.

I struggled through the cash register line clutching my lengths of plastic pipe with all of the protective zeal of a missionary carrying the native Chief's first born son toward the baptismal waters. The bill was just under \$15. What a wonderful thing the human brain is! To think I had conceived this idea and was about to witness its birth. I rushed home and laid the pipe out in the back yard.

With glue can and hacksaw I quickly assembled the eight spreaders. The next step was childishly simple. I inserted the ends of the 3/4 in. pipe into the cross fittings and cemented them in place. My two quad sections were finished! Less than an hour had elapsed!

I decided to transport the sections over to the driveway where I would attach them to the 30 in. squares of plywood with C clamps. I stooped down and raised the center section waist high. The four ends remained imperturbably on the ground. A hint of disaster began to penetrate. I raised the center to the top of my head. Oh, no! I raised it as high as I could reach. The ends just cleared the ground. I stood there looking like I was holding the framework of a giant parasol. As soon as I began to walk my creation began an undulating motion. I tried to damp its oscillation by changing the cadence of my step. This required a rapid change of rhythm since the damn thing was really responsive. I was in the midst of this inadvertent boo-ga-loo when I noticed my neighbors staring thoughtfully in my direc-

Model PD 301 is a 300 MHz prescaler designed to extend the range of your counter 10 times. This prescaler has a built-in preamp with a sensitivity of better than 50 mV at 150 MHz, 100 mV at 260 MHz, and 175 mV at 300 MHz. The 95H90 scaler is rated at typical 320 MHz. To insure enough drive for all counters, a post amp. was built-in.

The prescaler has a self-contained power supply regulated at plus-minus .08%. The PD 301 is supplied without power supply if desired (input 50 ohms) (output Hi Z). The PD 301 has been tested on the following counters: Heath Kit 1B101 — Heath Scientific 105 — Monsanto 105A — Miida — Regency — Beckman — Hewlett — Packard 524B — and many home builds. In short, to this date we do not know of any counter that the PD 301 has failed to work well with. All prescalers are shipped in a 4" x 4" x 1 1/2" cabinet all wired and tested.



PD 301 with Power Supply **\$55.50**

Pd 301 without Power Supply **\$50.50**

Shipped day order is received

Include \$1.50 for postage/insurance

Write for Catalog

K - ENTERPRISES

1401 NORTH TUCKER • SHAWNEE, OKLAHOMA 74801

**We're
overwhelmed!
...but not surprised by your acceptance of
the new
TS-520**



**WE KNEW THIS NO-COMPROMISE, DO EVERYTHING, GO EVERYWHERE
TRANSCEIVER WOULD BE POPULAR. NOW WE ARE DELIVERING THEM IN
RECORD NUMBERS. PLEASE BE PATIENT...WE HAVE ONE FOR YOU.**

Here are 30 special reasons you will want to own a TS-520. After you have operated one, you will doubtless give us 30 more why you're glad you own one.

- | | | |
|--|---|---|
| <ol style="list-style-type: none"> 1. Built-in AC power supply 2. Built-in 12 volt DC power supply 3. Built-in VOX with adjustable gain, delay and anti VOX 4. 1 KHz dial readout 5. Ultra stable FET linear VFO 6. Built-in noise blanker 7. Built-in RIT circuit and RIT indicator light 8. 8 pole crystal filter 9. Built-in 25 KHz crystal oscillator 10. Provisions for optional CW filter 11. Break-in CW with sidetone 12. Completely solid state except final section. Compact, low current, | <ol style="list-style-type: none"> 13. Built-in cooling fan 14. Accessory external VFO & accessory external speaker 15. Built-in speaker 16. Modern styling & functional design. Modular construction. 17. Amplified ALC 18. TUNE position increases tube life 19. Maximum TVI protection 20. Built-in fixed channel operation (4 channels) with indicator light 21. Provisions for use with a VHF transverter | <ol style="list-style-type: none"> 22. Full metering 23. Selectable SSB 24. Selectable AGC operation for different modes 25. VFO indicator light 26. Built-in selectable ALC action for speech processing 27. Carrying handle 28. Rugged 6146 type final tubes 29. Internal cross-channel operation. 30. Push button WWV reception |
|--|---|---|

**Proven Kenwood quality
and reliability**

The price..\$629.00
subject to change without notice.

Accessories: External VFO-(VFO-520), External speaker - (SP-520), CW Filter - (CW-520)

**Available from
Kenwood dealers
throughout the U.S.**

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

tion. They have tended to view my behavior as a little strange for some time, and this latest exhibition did nothing to shake their confidence in the opinion that I was a prime candidate for the local laughing academy just north of here.

I'll admit it. I was undone. I laid the whole thing down on the driveway and sat in the sun, gently flexing my fingers along the back of my neck. Sometimes I get these damn headaches . . .

At times like these, ham radio can be such a help. I went inside and fired up the rig on fifteen. A WØ in Milwaukee came back to my CQ. After the amenities, I described my plight in lucid terms. He immediately had the perfect solution! "Yes, sir," he said, "just cap the ends, fill it up with water and freeze the whole thing. It'll be just as rigid as you want. Ha, ha, ha," he cackled insanely, vastly amused at his cleverness. I complained of sudden QSB and signed off.

After a few days I went out and disassembled the whole thing. The plastic pipe is lying on the ground in the far end of the back yard. It can be had for a very reasonable price. It has been there for three years.

Subscribing to some idiotic ethic that postulates that adversity is meant to strengthen character, I resumed brooding about how to put up an inexpensive quad.

In no time at all it became evident to me that I should have chosen material with more strength, say like one-inch wooden doweling. In order to insure success I decided to fiberglass the doweling. Better to spend a little extra and be sure. I asked some of the boating types at work about fiberglassing and was assured it was a relatively simple operation.

Naturally, I was crouched by the door of Builders' Emporium on Saturday morning, money in hand, awaiting opening hour.

The only problem with the doweling was length. The longest pieces they had were eleven feet, two feet too short. This was only a temporary setback. My fevered brain devised an on-the-spot fix. I picked out eight pieces of 3/4 in. doweling. I would simply drill out the ends of the 1 in. doweling about eight inches and insert the 3/4 in. dowel and glue them together.

Congratulating myself on my obvious problem-solving ability, I proceeded to the section containing materials for fiberglassing. Horror! The prices! The boating types had forgotten to tell me I could have gold plated the poles for less money. A further complication — Builders' didn't have the glass cloth in rolls. I wanted the materials right then, not later. I bought two large squares of glass cloth and the cans of resin and setting agent. I forgot to buy solvent for cleaning up the resin. This time the bill was more imposing — \$15.40 for the lumber and \$18.85 for the fiberglass junk. Heck, with tax, it was only a little over \$35, and that's still a long way from the \$59.95 most quad kits are advertised for.

I rushed home with my newest purchases, imbued with new enthusiasm, a blend of overconfidence and plain ignorance.

I glanced at the directions for fiberglassing. Admittedly, it was raining out and the temperature was in the low 60's, but who wants to split hairs over little things like that?

I laid out the big squares of glass cloth and began cutting strips for rolling onto the doweling. No one had told me that glass cloth has such a tendency to unravel. In short order the family room looked as if Florence Nightingale had held a bandage-wrapping rally for the Crimean War. I decided it would be better if I conducted the actual wrapping operation out on the porch even though the weather was miserable.

I had less trouble drilling the ends of the 1 in. doweling to accept the 3/4 in. doweling than I had expected. (I was beginning to develop a paranoid expectation of trouble at every step.) Realizing that I had weakened the walls of the doweling with the drilling, I wrapped the outside with copper wire (No. 32 PE of course) and wrapped electrical tape over the wire. The result would have pleased a Watusi tribesman. It looked like a thirteen and a half foot spear.

I laid one of the spears between two chairs and began the fiberglassing operation. The trouble was that the three foot strips of glass cloth tended to come loose before I could overlay the next strip and get it started. I had liberally doused the spear with



Write: Box 864-S
Council, Bluffs, Ia. 51501
Phone: (712)323-0142
Al McMillan - W0JJK
Tues/Sat, Noon/5PM



HAM II Regular ~~\$149.95~~

H. I. SPECIAL \$129.95

CD44 Regular ~~\$99.95~~

H. I. SPECIAL \$89.95

THE HEAVY DUTY - HAM-11... 98 BALL BEARINGS, STEEL GEARS, POSITIVE LOCKING BRAKE... (29 LB).

THE STANDARD DUTY - CD44... 50 BALL BEARINGS, STEEL GEARS, FRICTION BRAKE... (22 LB).

CONTINUING THE TRADITION OF THE HEAVY-DUTY CAST ALUMINUM, IN-LINE ROTORS, SUPPORTING BIG VERTICAL LOADS ON TWO SIX INCH RACES & BALL BEARINGS. BOTH MODELS HAVE A HUSKY 800 IN/LB TURNING TORQUE... THE STRIKING NEW CONTROL BOX HAS A FRONT PANEL CALIBRATION CONTROL WITH SEPARATE ON/OFF CONTROL FOR CONTINUOUS METER INDICATION AND INDIVIDUAL SNAP ACTION SWITCHES FOR EACH DIRECTION ROTATION. NORTH CENTER.

resin before starting. The whole operation wasn't going well. The resin got all over my hands and arms. Bits of the glass cloth started to adhere to the resin. I began to panic. More cloth. More resin. The spear was beginning to look lumpy in places. I abandoned all pretence at competence. Resin was puddling on the concrete floor beneath the spear. The resin on my hands, arms and clothing was beginning to congeal. More cloth came off on me. I felt like an old W. C. Fields movie, trying to peel cloth off of one hand only to have it stick on the other hand. I also felt like an ass.

My teenagers chose this moment to arrive home with some friends. "Hey you guys, look, it's the MUMMY." They all peered at me. "I think it's FRANKENSTEIN," said the youngest. "You're both wrong," the eldest said flatly, "can't you see the neighbors have tarred and feathered the Old Man while we were gone? I told you they would get him sooner or later." They beat a hasty retreat. There's a certain look I get at these times.

I made one right decision. The other seven poles would remain unfiberglassed. It was raining anyway, so I couldn't go much further. Back down to Builders' Emporium and the purchase of some epoxy paint. Expensive as hell, but the paint man said it would withstand anything. Only another \$5.15 which beats trying to fiberglass the poles anyway.

While the epoxy paint was drying, I zipped back down to Builders' Emporium (I'm well known there) and picked up two three inch end bells, a three inch threaded T, and a twelve inch threaded pipe. Then over to the lumber section where I got more doweling to fit into the pipe sections. I forced a five foot section of doweling through the T joint and jammed an end bell on either end. Another section of doweling was stuck into the bottom of the T joint to make a mast. The end bells would be bolted to some aluminum plates and the spreaders attached to the plates with C clamps.

The pipe fittings were expensive and the doweling wasn't cheap either. The bill came to \$13.71, but the end was in sight.

I was forced to wait for the next weekend to assemble my masterpiece, since it was January and too dark to work by the time I got home.

Saturday I strung the wires for the three bands on each of the sections. I had been advised by competent engineering talent at the space factory where I labored that some of the hams had successfully fed all three elements with a single 52Ω coax by bringing the three driven elements together at a single feedpoint. This seemed so simple I wondered how it could work. It was simple. It didn't work. I tried resonating with my grid dipper, but I kept getting sharp dips all over the place and finally abandoned this brief attempt at the scientific approach. I copped out and used three different coax cables, one for each band.

I had started another project, an "inexpensive" home-built tower (more about *that* some other time) and decided I would use the first twenty foot section to test my quad.

I rounded up my teenagers, all four, and we hoisted the assembled quad up on the tower. I stood back to admire my handi-

ROBOT



Slow Scan TV Equipment Line.

① MODEL 70A SSTV MONITOR

Displays amateur standard pictures from any SSTV audio source: station receiver, tape, camera. Six inch (diagonal) display.

Front panel controls for easy station operation. Connectors for receiver, transmitter, microphone, tape, waveform monitor. LED tuning indicator.

All solid state except cathode ray tube.

\$295

② MODEL 80A SSTV CAMERA

Generates amateur standard SSTV pictures and fast scan video for viewfinders. Ample sensitivity in ordinary room light. Controls for contrast, brightness, vidicon beam, SSTV signal level, black/white video reversal and 1/4, 1/2, full frame selection.

All solid state except vidicon. All station cabling included; requires suitable C-mount lens.

\$295

③ MODEL 61 VIEWFINDER

Displays Model 80A or 80 Camera's fast-scan video on six inch (diagonal) display to simplify setting camera focus and field of view before and during transmission. All solid state except cathode ray tube; cabling to camera fast-scan output included.

\$239

④ LENSES

Lens	Focal Length mm	Min. f stops (All 22 max)	Min. Focus (in inches)	Price
A	12.5	1.9	10	\$ 59
B	25	1.9	24	\$ 29
E	25	1.4	6	\$ 65
F	50	1.9	42	\$ 55
G	150	3.2	96	\$ 89
H	20-80	2.5	60	\$220

⑤ VIEWING HOOD

Two piece detachable hood. Fits monitor bezel to block outside light.

\$25

CALIBRATION TAPES

Three inch reel or cassette tape recording aids setting monitors and cameras to SSTV standards.

Cassette **\$4**

Reel **\$3**



All Robot equipment carries a one-year warranty. Four easy ways to purchase: cash, C.O.D., Master Charge, BankAmericard

ROBOT RESEARCH INC. 7591 Convoy Court, San Diego, CA 92111 Phone 714 279-9430

work. Alas! The weight of the No. 12 wire was too much for the 3/4 in. doweling. The whole quad appeared to suffer from advanced arthritis. Although the ten and fifteen meter sections attached to the 1 in. doweling were reasonably taut, the twenty meter section caused the 3/4 in. doweling to bend over at an awkward angle. The twenty meter section just wasn't going to hack it. I got up on a ladder with a saw and methodically cut the spreaders just above the fifteen meter attachment. The boom wasn't too tight in the end bells and so I was able to spin the spreaders around until all eight were cut down.

Standing amid the wreckage of tangled wire and stumps of wood, I could feel that funny headache in the back of my neck coming on. There was nothing more I could do that evening. I went inside and fixed some drinks. I drank all of the drinks.

The next morning I decided I might as well try out the remaining two bands. I hooked them up and turned on the rig. I could hardly believe my ears. I switched over to the Mosley vertical. The signal was S-5. I switched back to the quad. The meter read S-9 plus 10 dB. Fantastic! I swung the quad around. The signal started dropping. It was down to 40 dB off the side. Out of sight! I was so excited I forgot about breakfast and lunch. I was working one station after another, first on ten and then on fifteen. By early evening I was gracefully acknowledging S-9 reports from Japan. One JA gave me an S-8, and I immediately decided he must have inferior receiving equipment.

This was only the beginning of a long line of quad antennas in the three years that have passed since that lovely Sunday morning in January.

I found that the big end plates had a windmill effect, and I had steel straps welded to the end bells, which proved strong enough to support the spreaders with much less wind resistance. Also I found that I really needed some matching device between the coax and the driven element. A gamma match worked out quite well.

I began a long series of experiments with element spacing for the individual bands. My peerless engineering had limited me to ten and fifteen, but I was able to satisfy myself

that the quad is one hell of an antenna when it is tuned up properly. Generally speaking, if you have a low SWR and are getting at least 20 dB front-to-back, you are in good shape. It is possible to get a higher front-to-back at some sacrifice in bandwidth. My present quad is a three-element job with no tuning stubs. I cut the reflector 5% longer and the director 5% shorter than the driven element and strung them up as closed loops without any tuning stubs. So far, after a week's testing, it seems to be working out pretty well, 25 dB over S-9 in Tokyo and 40 over in Guayaquil, Ecuador.

I suffered through a few further reverses. The wind blew the tower down and broke one spreader, which I quickly replaced. One day at work I got a phone call from the youngest harmonic who plaintively relayed the information that my daughter's horse had got loose, tripped over the guy wires and the tower was down again, this time with two broken spreaders. Small matter! Now I knew I had a working antenna, and I accepted these trivial happenings with equanimity, not even the hint of those headaches.


Honesty requires me to admit that by the end of the year I purchased the \$59.95 kit from Polyquad. This finally got me on twenty. Incidentally, I ran a series of tests while the quad was mounted on a twelve foot four-by-four. The twenty meter section barely cleared the ground. In both Europe and Africa I was only 5 dB under K6SHA who is about two miles away. Since Casey was running 2 KW PEP to a four-element Yagi 60 feet up and I was barefoot with the HT-37, he should have been at least 10 dB louder on power factor alone. Remember, my quad is barely off the ground.

I gave the original quad antenna to W6UOD and his son, Steve WB6UHE. It was really a minor investment anyway. Only cost me \$68 or so, which any way you figure it is only a few dollars more than those store-bought kits. I don't care to discuss those headaches or the liquor bill. As the new generation would say, "It isn't relevant."

That 54 ft all-wood white tower though... but, as I said earlier, that's another story.

...W6SUN

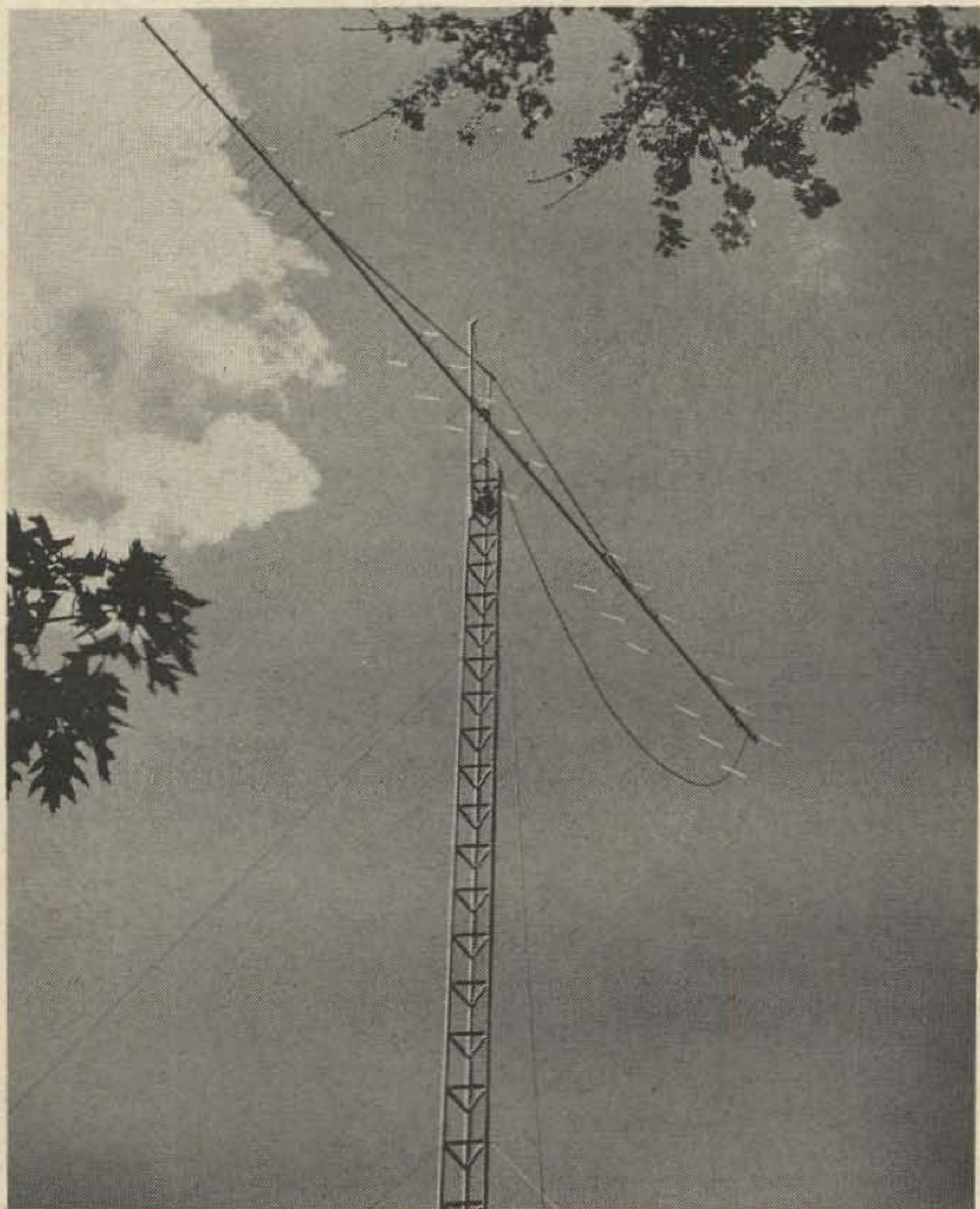Ralph W. Campbell W4KAE
405 Granite Circle
Lexington KY 40503



RECONCILING

THE LONG

SQUARED


QUAD

Referring to the August 1969 issue of 73 Magazine: The article beginning on page-101 was the first full length composition I ever had printed. Although another paper was carefully rewritten for a non-paying journal, a nice check from the Editor spurred my research and experimentation which resulted in the final issuance of Patent No. 3,491,361. This was the birth of the Long Circular Quad, as we know it today.

Original work was performed with the diagonal-square or "diamond shape" parasitic-element quad; however, this approach was abandoned for the circular loops. The round model was tested free and the gain and performance properties were just about as expected, except for normalized frequency being somewhat lower than the array was cut for.

This article tells about *new* research on the older - diamond - model; and if it doesn't herald a new breakthrough in antenna design, at least it spells out the danger

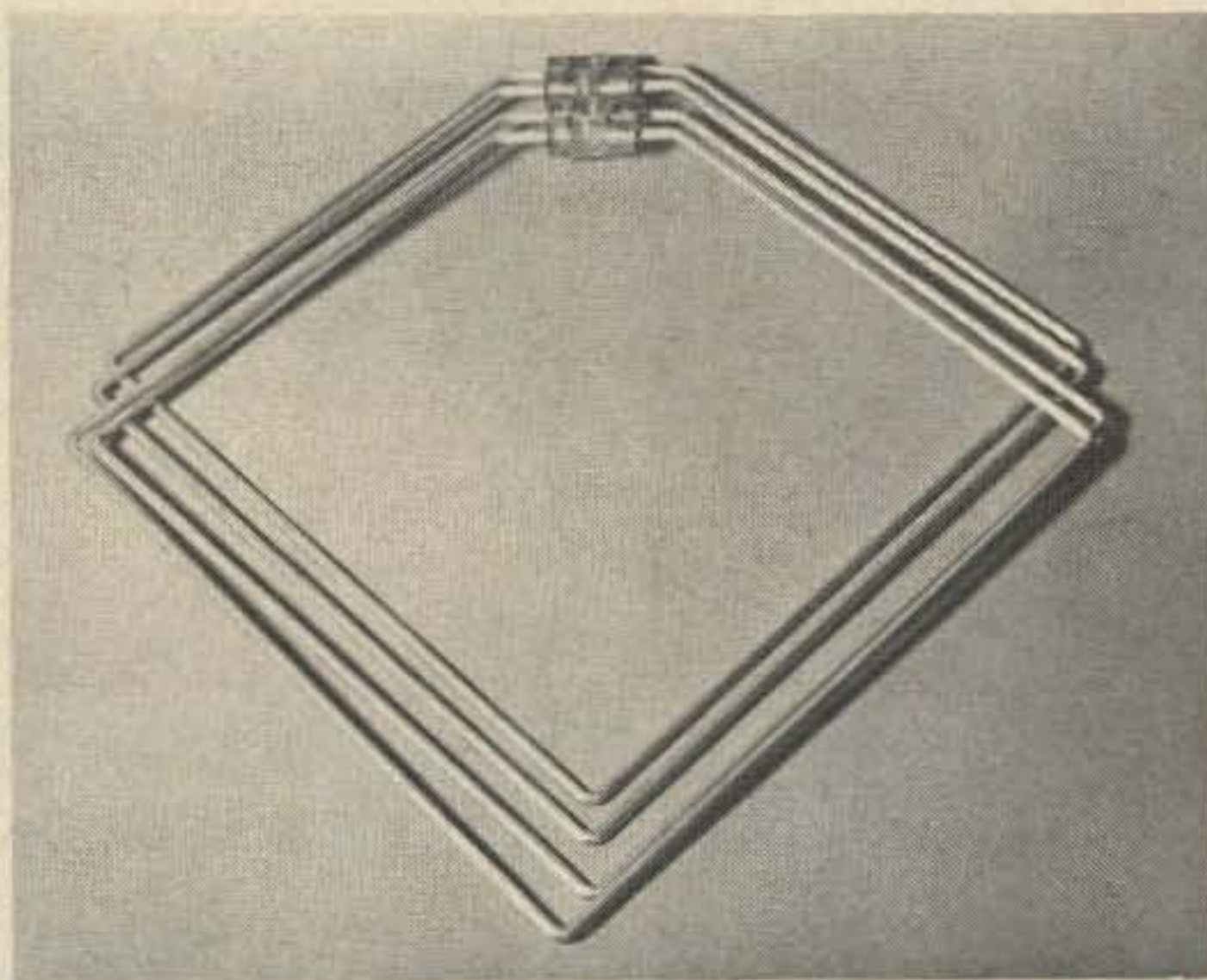zones to be avoided. The L.C.Q. theory has therefore been more firmly established, using *circular* elements. From our experiment comes two new ideas: 1. The function



Hand-made casting-resin plastic insulators installed upon 5/16 in. solid aluminum rod stock. This work, which included aluminum welding at a local sheet metal shop, was performed "free" because shop was supplied with TV samples!

The Ultimate F.M. Transceiver

Here it is, the FMer's dream, a fully synthesized transceiver that'll cover the entire two meter band, PLUS a built-in scanning receiver that'll locate any repeater frequency in your area that's in use.

And get a load of these other features that make the ultimate rig:

- Operates on FM, AM or Modulated CW
- Built-in DC and AC power supplies
- Frequency Range of 143.5 to 148.5 MHz in 5 KHz increments
- Autoscan in 5 KHz steps across entire band, with adjustable speed and frequency limits.
- Synthesizer flexibility that offers choice of 600 KHz up or down, 1 Meg up or down, simplex, frequency split, or any nonstandard split (programmable) all from a single function switch.
- Receiver Sensitivity of 0.35 Mv for 12 db SINAD on FM
- Dual power output of 20 watts or 5 watts across entire band
- Adjacent channel rejection (30 KHz) 100 db minimum
- Image spurious and intermodulation (EIA) 80 db minimum
- 10 pole, 13 KHz crystal filter
- Receiver Superhet, single conversion
- Frequency stability of 0.0005%
- Built-in tone burst and PL encoders and decoders
- Built-in touch tone pad
- Full LED Digital readout
- Built-in S Meter also serves as VSWR bridge, power output meter, battery indicator, deviation indicator and discriminator meter.
- Audio output 4 watts @ 10% THD
- Speaker built-in to left side of cabinet for maximum mobile reception
- Headphone jack for noise-free mobile operation
- Independent selectable priority channel
- Built-in Auto CQ
- Temperature range from -20° to 170° Fahrenheit
- Size: 4" H x 8" W x 10" D Weight: 10 pounds
- One million channels (1000 Rec. x 1000 Trans.)



\$995.00

A \$100 deposit will insure early delivery and guarantee price

**You owe it to yourself to go first class. Try an EBC 144 —
You deserve it !**



**emergency
beacon corp.**

15 II River Street
New Rochelle NY 10801

(914) 235-9400

AMATEUR PRODUCTS DIVISION




Nine dram bottles used in preparation of large size insulator molding. Greased rod stock, cut to proper length, is held in bottles with modeling clay and an epoxy blob from the bottom. Valspar Casting Resin No. 8880 was then poured in. When dry, glass was cracked off carefully.

of the parasitic groups is compared to standard waveguide/mode concepts; 2. Constant-phase boom length, with regard to the number of discrete directors in any given group, is explained.

Curiously, the 18 dBi we were claiming for the original array resulted in 13 dBr, for an over-the-dipole comparison, when improvements were made. A separate article on the 11 Element L.C.Q. is in the files of 73 Magazine; and this is the antenna depicted on the August cover. The 11 Element L.C.Q. exceeds performance for a 215B long john (15 element) Yagi by a full 3 dBr. All models of the L.C.Q. in print can be scaled for higher UHF frequencies, but it is of prime importance to maintain proper circumference to wire-diameter ratios. On 432 MHz, my conclusion is that a 4 ft. reflecting screen may be needed to offset increased stray radiation behind the driven reflector, for the same gain figures as on VHF.

Theory

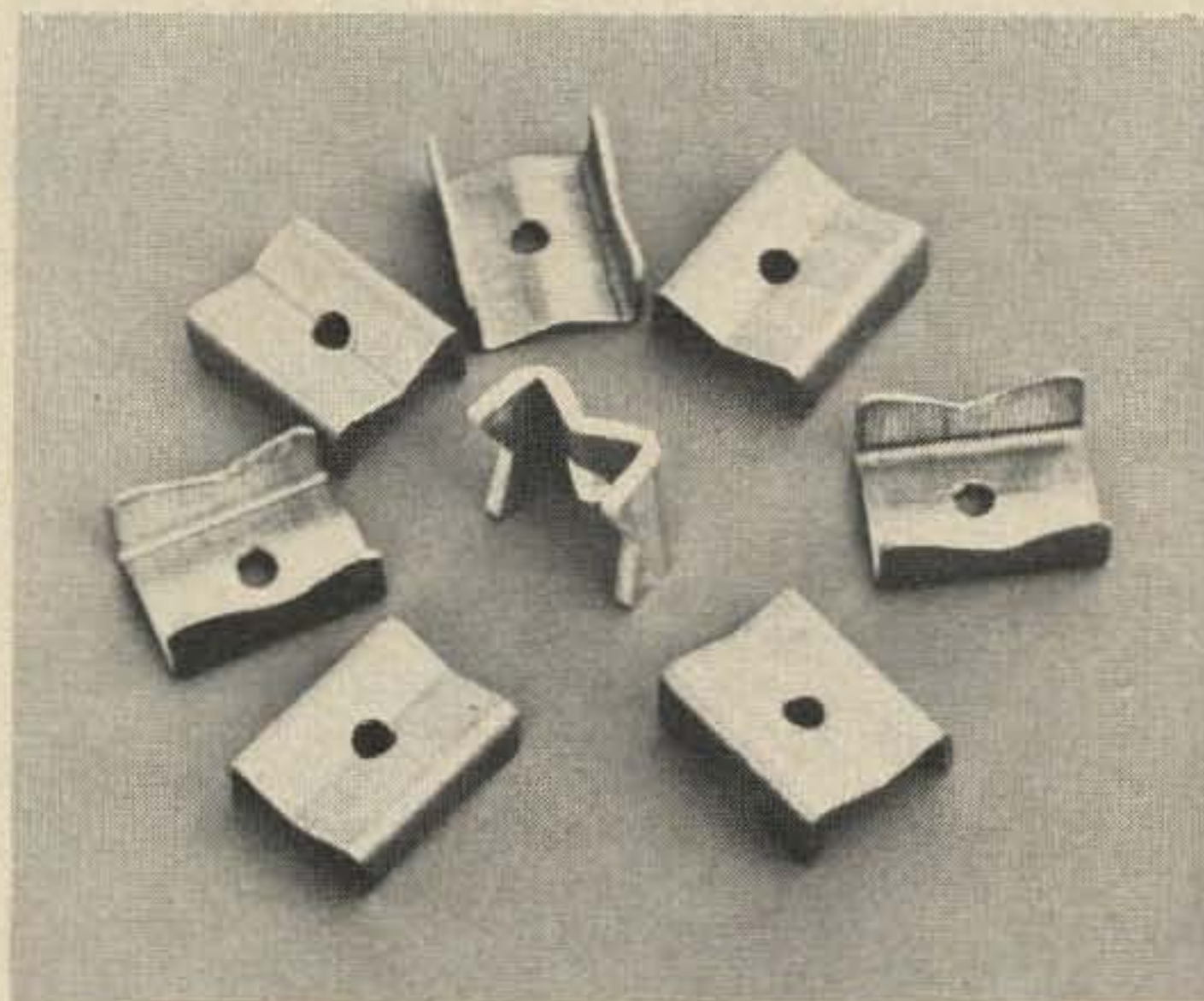For a long time vertex-fed diamond-shaped elements have been used on the HF bands. There was apparently no difference between this type mount for quads, or for the kind with a square-side parallel to earth. This is for truly parasitic discrete elements, and not for driven parasitic groups. However, from my experiments on VHF, it is



Parent-part of mounting hardware is shown in center of this photo. Note I had the seven additional parts manufactured by a local sheet metal shop; after being flatly refused help from a well-known antenna manufacturer! Parts are plastic insulator-to-boom clamps.

clear in my mind that an E-vector to H-vector cancellation can occur as noticed here, which must reconcile, especially in light of the fact that for both parallel and diamond configurations, the feed point is classically correct (i.e., feed connections made to the middle of a lower parallel member, or at the six o'clock vertex of the diamond-shape, for desired E-vector polarization to be horizontal).

For the VHF experiment, it seems that we've got a waveguide-type mode propagation similar to the TM (transverse magnetic) field pattern for Long Squared Quad versus the TE (transverse electric) for the L.C.Q. Subscripts are normally used below the TM or TE letters; however, since I cannot accurately define which mode is which, I am content to mention only that the TE field appears replaced by the TM field. If you consult MIT's Principals of Radar, or NAVSHIPS No.900,018, a simple breakdown is illustrated. With this apparent mode-shift, keeping the feedpoint the same obviously results in cancellation — which was noticed!

Mode considerations for discrete element parasitic quads (not groups) is not treated because there is no common-driven energy to be propagated. For the LCQ it is proper to think of this array as having properties of an irradiated slot-structure, or like several mag-

FM YOUR GONSET

(for your Clegg 22'er, Poly-Comm 2, PC-62, Johnson 6N2, Aerotron 500, HA-460, TX-62 or VHF-1)

- New! Plug-in modulator puts the Communicator transmitter on FM.
- No modification or rewiring on your Communicator. Just plug into mike jack and crystal socket.
- Compact self-contained modulator measures 4" x 3" x 1½".



- Works with Communicator I, II, III, IV and GC-105, and other rigs listed.
- FM at a tenth the cost of a new rig.
- Frequency adjust for netting built in.
- \$34.50 postpaid U.S.A. \$36.50 for PC-2, PC-62, HA-460. Specify transmitter model. California residents add 5% sales tax. (HC-6/U crystal and 9 volt transistor battery not supplied.)
- Send for free descriptive brochure.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

KITS



Encoder \$8.95

Sub-Audible tone

Decoder \$9.95



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass epoxy PCB's & silicon xstrs throughout.
- Any reeds, except special dual coil types may be used: Motorola, G.E., RCA, S.D.L., Bramco, etc.
- All are powered by 12 vdc.
- Use on any tone frequency 67 Hz to 250 Hz
- Small size 1.5 x 4 x .75"
- All parts included except reed and reed socket
- Postpaid - Calif. residents add 5% sales tax

COMMUNICATIONS SPECIALISTS
P.O. Box 153 Brea CA 92621

30 Hz Selectivity!



"... a must for anyone using an inexpensive receiver or a sideband transceiver on our crowded CW bands."


(73 Magazine test report)

Our Q-BOX audio filter features: Bandwidth CONTINUOUSLY VARIABLE from 30 Hz (almost 100x sharper than most xcvrs!) to 2 kHz. Active filter (no coils). No insertion loss. Not a breadboard. Ready to plug into ANY rcvr/xcvr. Drives phones or ext. spkr. amp. Full instructions. In use worldwide. Plug one into your receiver today! . . . Only \$17.95 + \$1 shipping in U.S. (Add Sales Tax in Cal.) 10 day moneyback guarantee. SEND FOR FREE LITERATURE AND TEST REPORTS.

AUTEK research
Box 1494L, Canoga Park, California 91304

netic dipoles stacked end-to-end on a single boom. It is worth remembering that a vertical magnetic-slot antenna radiates a horizontally polarized E-vector.

Constant-phase boom theory is another concept derived from our work. Basically, this theory says that an increasing number of parasitic, strapped circular elements may be added (up to about 7 per group) as long as there's the same spacing (boom length) as there are quarter-wavelengths between the discrete elements in the next group ahead. Seven discrete elements have 6 ninety-degree intervals, so the previous group boom

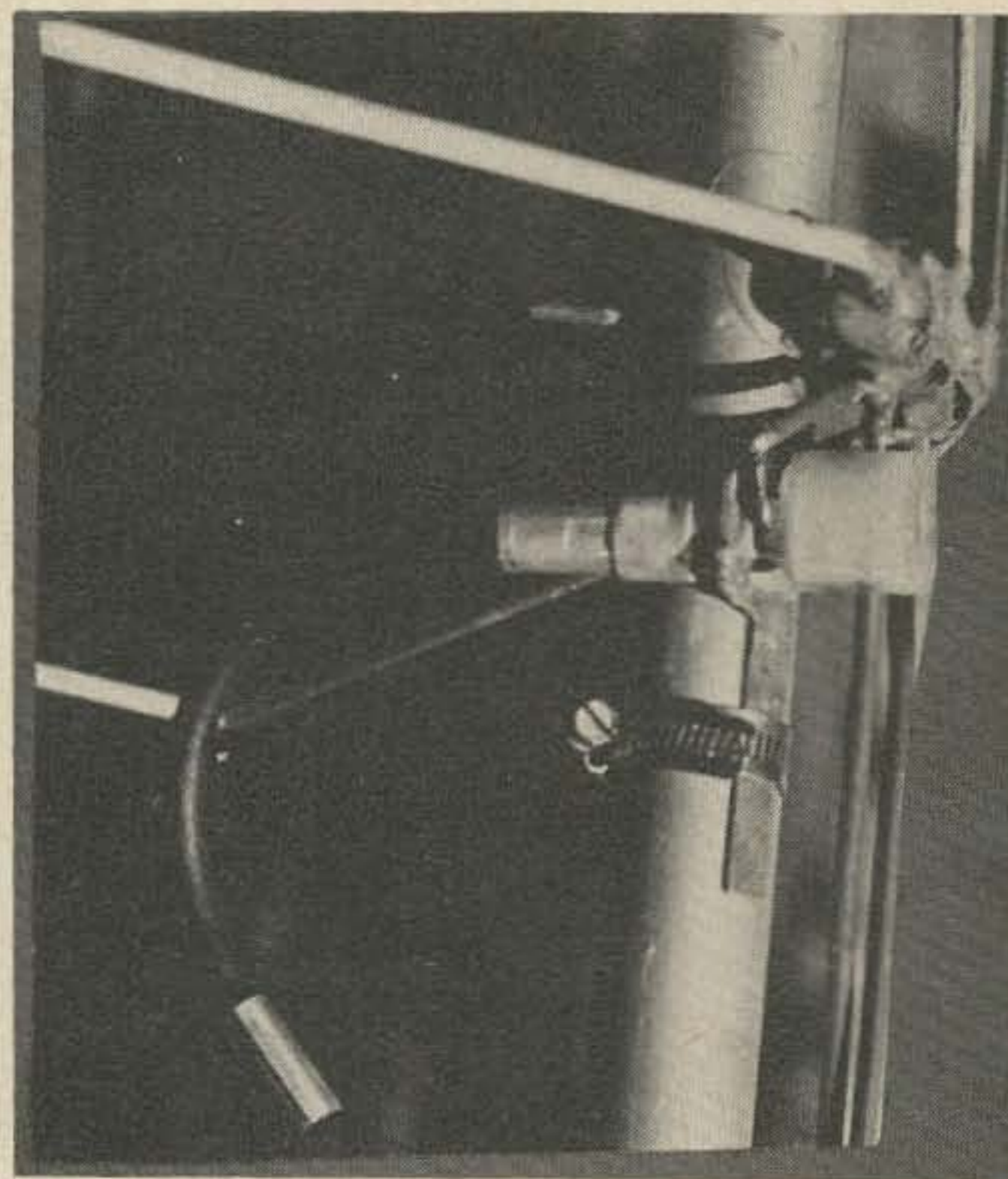

Close-up view of the rugged ferrite balun, constructed for the square quad. Although complete balance of the driven diamond-shaped squares was obtained, as well as energy propagated along the structure, cancellation or cross polarization occurred.

spacing must be 540 electrical degrees, etc. To initiate another group on-the-boom requires an increase, on a per-group basis, of 90 electrical degrees so that array will become proportionately longer as more elements are added. Thus, the next group out from the 7 element one will contain 8 elements at 630 electrical degrees from the last element mounted. Since more than 7 elements could theoretically result in unwanted side-lobes, you can content yourself with a total of 24 elements VHF or 25

elements UHF, with use of a passive reflector. This concept is more fully explained in Patent No. 3,491,361. I will make patent copies available for \$1.00 each, should anyone desire a copy of this document.

Construction

A great deal of time was spent in constructing the array shown in photograph No. 1. Other photos show how I handmade my own insulators from glass 9 dram pill bottles, with a finished closeup of this work. The 5/16 in. aluminum elements were fluxlessly welded, because of inferior quality of the material supplied.

Conclusion

Sometimes the best results in independent research come from failure. The array under discussion was just that, by amateur standards. Out of two months construction time (to get "weird" parts by mail) plus four months more in evaluation, new theories were developed which are protected in my patent; however, we don't mind if hams use these arrays for non-commercial purposes.

In retrospect it is impossible to get much more gain from the diamond-shaped quad with discrete parasitic elements, for anything you might build with more than 8 elements (see Fig. 1, page 101 of August 1969 73 Magazine) unless you use circular loops and strapping. Horizontally square, strapped elements will work fair - I think - but the mode may be wrong. Our patent was allowed over the Wells' case, where interference was encountered, so we know our way works best!

Although not mentioned earlier, I recommend HF users of cubical-quad antennas to try the diagonal-square type of array in preference to the horizontally-square. I think Kirk Electronics, and Particularly Hy-Gain's new "Hy-Quad" array are top-of-the-line. Always check the match with the antenna mounted no closer than 1/8 wavelength above ground, on the lowest frequency (usually 20 meters) for unity SWR - AT THE ANTENNA TERMINALS. The advantage of the diamond shape on HF is probably a lowered angle of radiation. Don't strap those elements!

...W4KAE

GATEWAY ELECTRONICS


8123-25 PAGE BOULEVARD
ST. LOUIS, MISSOURI 63130
(314) 427-6116

THUMBWHEEL SWITCHES


STANDARD SIZE - 0.5 x 2.125 x 1.78
10 position decimal **\$3.00**
10 position BCD & compl. **\$4.00**
End Plates (per pair) **\$1.45**

MINIATURE SIZE - 0.312 x 1.3 x 1.3

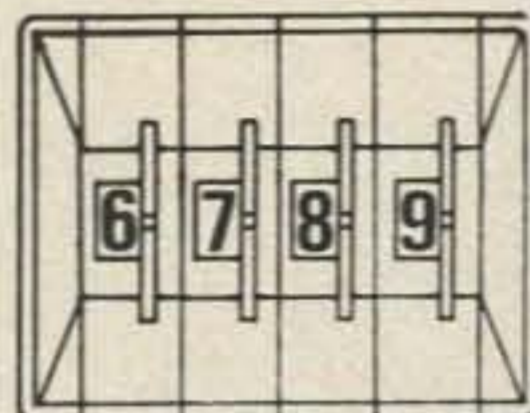10 position decimal **\$2.50**
10 pos. BCD & comp. **\$4.00**
10 pos. BCD only **\$2.75**
End Plates (per pair) **\$1.00**
Divider Plates **\$1.25**
Blank Body **\$.30**



L.E.D. - MAN 1 or DL707 TYPE -
NEW \$2.75

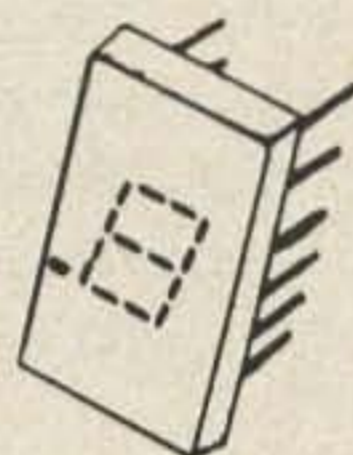

DL62 - (large MAN 1) 0.6
inch - **NEW \$3.95**

DL33B-3 - Triple 7 seg-
ment, for calculators **\$2.95**

L.E.D. INDICATORS -

RED OR CLEAR **35¢ 3/\$1.00**
YELLOW or GREEN **60¢**

12 VOLT REGULATED POWER SUPPLY - 1.5 amp-adjustable from 9 to 14 volts. Small, solid state. Ship wt. 4 lbs.
\$6.00

12 BUTTON TOUCH TONE PAD -
NEW - MANF. by W.E. w/diagram
ship wt. 1 lb **\$19.50**

200 PRV - 25 AMP diode bridge
\$2.00

20 KV - .6 AMP diode (two 10 KV
diodes in a single package) **\$2.00**

30 KV - 1.2 AMP diode (two 15 KV
diodes in a single package) **\$2.50**

EQUIPMENT COOLING FAN - 115V
AC - 3" diameter - w/mounting
bracket - 3 lbs. **\$3.50**

*\$5 Minimum Order. Visit us when in St. Louis.
Please include sufficient postage.*



Juge Electronics has spent 10 years now building a reputation for customer service. In the past two years, this reputation has spread far and wide, and we've had a few growing pains, but we feel we've cured them, and can still deliver what we advertise . . . better than ever.

Amateur Radio is our profession, not a sideline. We maintain a large inventory, which is now computerized to minimize backorder problems (we do have them when our suppliers just can't deliver), and keep our shop well stocked to maintain your radio after the sale. Our computer will also furnish you a used gear list which is current as of the previous day's business . . . not a "padded" list of "what it will cost if we happen to have it when you order."

We maintain telex links with almost all major factories to speed orders, service, and answers to your questions. Your letters are answered normally the day they arrive (we admit to and apologize for some delays recently while our computer was being put into operation), whether you are buying or just asking for some advice or help. We don't publish a catalog . . . just haven't had time to do that and give our kind of personalized service. Your questions about equipment will be answered candidly — if we think an item "isn't up to snuff", we'll say so, because we want you completely satisfied, or we'd rather not sell you.

We will check your gear prior to shipment if you request . . . just a little added insurance that you won't know the frustration of getting a brand-new radio which doesn't work. We can finance through General Electric Credit or Swan's Credit plan, with 10% down. And we'll tell you the truth about any backorders. If it's going to be 6 months, we'll say so, not string you along. You'll find our service after the sale is excellent too.

Now obviously this type of operation is expensive to run, and this is the only way we're geared to operate. If you're looking for the last dollar of trade-in or the lowest rock-bottom price, writing us is probably a waste of your time and ours. We frankly can't compete with the non-servicing of small inventory dealers. But if you feel that spending several hundred dollars with a company entitles you to the consideration of being dealt with honestly and quickly, and being helped with questions or problems, and treated like a valued friend . . . and you don't mind spending a few extra dollars to get these things, then write us today . . . *you should be a Juge customer !!!*

ED JUGE ELECTRONICS, INC.

**3850 S. FREEWAY
FT. WORTH TX 76110**

**11181 HARRY HINES BLVD.
DALLAS TX 75229**

Closed Sun. & Mon.

ANTENNA LOAD INDICATOR

Here's an easy way to get your antenna to accept a load — naturally.

You want your antenna to take a load from your transmitter, but there's only one frequency at which it will accept that load naturally and with no undue urging. What is that frequency?

You can find that frequency with an antenna noise bridge invented by Ted Hart. You'll need an even multiple of half waves in your feedline if the indications are to be meaningful. The same limitation applies to a grid-dip meter coupled to a loop at the transmitter end of the feedline. If you want to do it the hard way, you can plot a curve with an SWR meter . . . and still have the probability that the curve really is distorted by feedline length factors.

If one rocks back on one's haunches and considers the situation, what you're really concerned with is the antenna's ability to accept power. Once it accepts that power, it'll radiate it, less that very small portion that'll go out in the form of heat waves because of ohmic losses. Now, it's axiomatic that a reactive termination will not accept a load. So the point at which the antenna accepts maximum power is the point where its resistance (resistance, not impedance, not reactance) most nearly matches the feedline's impedance. you hope that its resistance is almost all radiation resistance, with a very minimum of ohmic resistance, but that's neither here nor there; you built that ratio into your


antenna initially, and this is no time to be worrying about it.

Now that you've bought the acceptance-of-power concept, you next consider how you're going to judge it. Here's where you want to keep it simple, keep it basic. What, you ask yourself, is the most simple form of rf power generator for the frequency I want to use? You can't get any more simple than a Hartley! So build one. Use a tube big enough to put out a couple of watts so you'll not have to squint too much to detect that rf power. Of course, if you're dead set on going modern, there's nothing wrong with using a big and husky transistor.

How to detect that rf power? Still keeping it simple, you take a dial light bulb or a flashlight bulb and a single turn of insulated wire. Put them in a series circuit. Loosely couple it to the coil of the Hartley oscillator. Couple it closely enough to get a fair degree of light, keeping in mind that you can determine changes in that amount of light better when it's not at full brilliancy.

Now couple the antenna feedline loosely to the Hartley's coil, using another single turn of insulated wire. Tune the oscillator slowly. When it hits the frequency at which the antenna accepts a load (takes power out of the oscillator), the light will dim. Read the oscillator's frequency with your receiver. That's all. You've finished the job.

. . . W5JJ

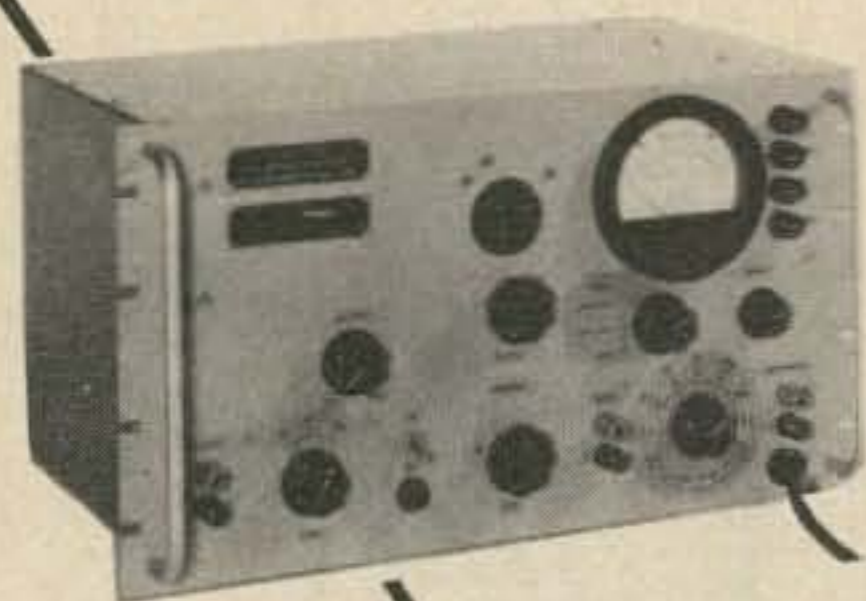

DISTORTION ANALYZER measures noise as small as $100\mu\text{V}$ from 20 Hz to 20 KHz. Distortion as low as 0.1% can be measured on this equivalent to the HP 330B analyzer. Measurements of audio distortion, voltage level, power output, gain, noise and hum level, audio signal frequency and total distortion of AM, rf, carrier. Military units in excellent condition.


MODEL TS-723\$125.00

ANY HOBBYIST WILL LOVE TO TINKER WITH THIS TELEMETRY RECEIVER. Operation at any frequency can be accomplished by use of an inexpensive solid state converter ahead of the receiver.

THE NEMS-CLARKE 1401 is a late model 215 to 260 MHz receiver with a crystal controlled 1st injection oscillator, variable 2nd oscillator ± 150 KHz and selectable 100/500 KHz IF bandwidth.



**NEMS-CLARKE 1401
\$95.00**

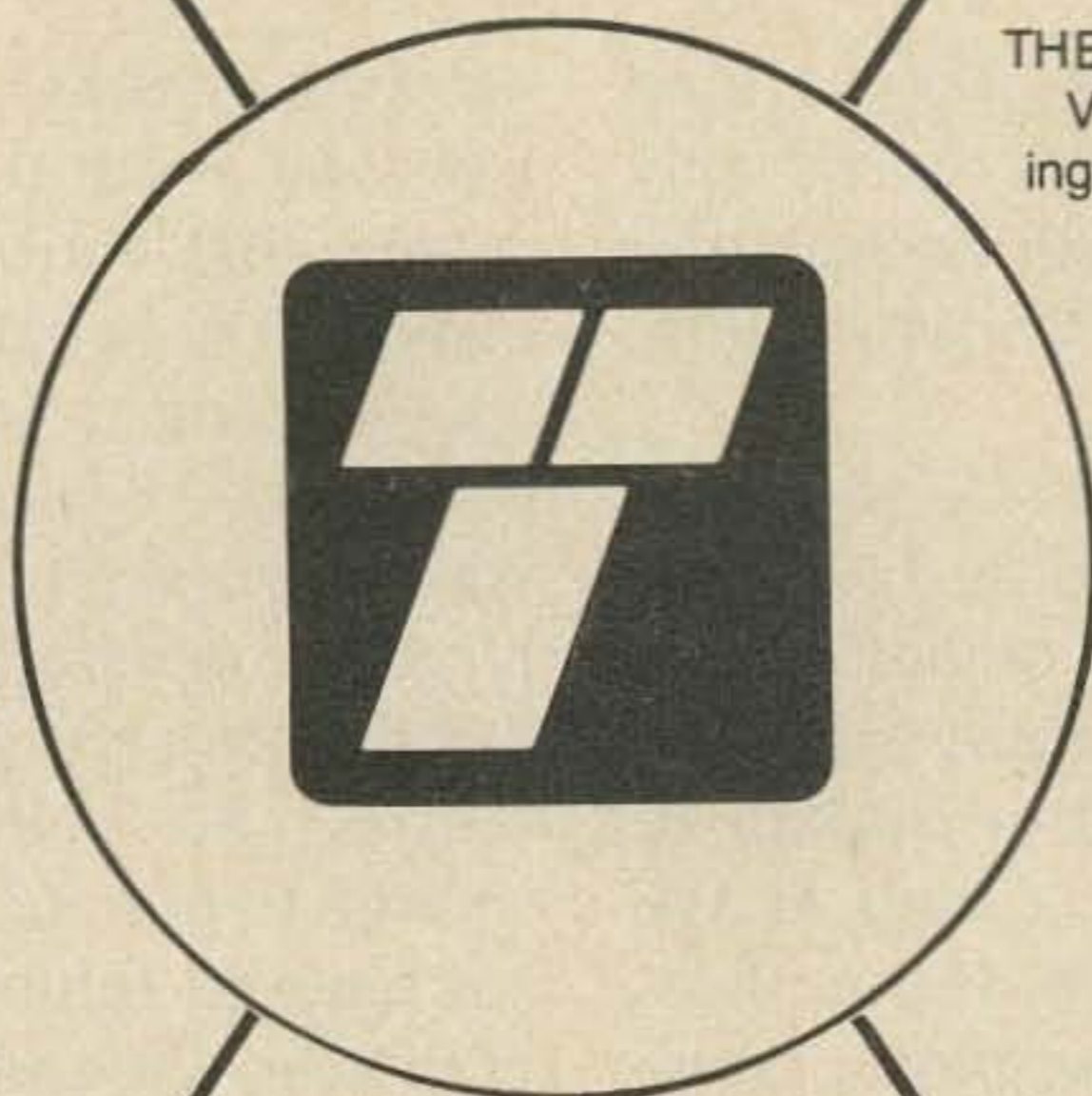

THE BARGAIN HUNTER'S SPECIAL VTVM features 1mV to 100V readings over a range from 10 Hz to 150 KHz with better than 2% accuracy anywhere on the scale. 0.5 megohm input impedance.



**BALLANTINE 300 VTVM
\$29.50**

OTHER BALLANTINE UNITS INCLUDE:

MODEL 305 Peak Reading VTVM measures 1mV to 1000V P or P-P from 5 Hz to 500 KHz..... **\$95.00**


MODEL 310A Video VTVM measures $100\mu\text{V}$ to 100V from 10 Hz to 6 MHz $\pm 2\%$ **\$75.00**

CAUTION: THESE INSTRUMENTS ARE SOLD AS-IS. WHILE EVERY ATTEMPT IS MADE TO ASSURE COMPLETENESS AND TO DELIVER AN OPERATIONAL INSTRUMENT, THERE IS NO WARRANTY IMPLIED OR STATED EXCEPT: "YOU MAY EXAMINE THE UNIT FOR TEN DAYS AND, IF YOU ARE NOT SATISFIED, YOU MAY RETURN FOR FULL CREDIT PAYING ONLY THE FREIGHT CHARGES". EVERY TECO INSTRUMENT IS CONSIDERED TO BE A GENUINE BARGAIN, BUT THE BUYER SHOULD HAVE ACCESS TO COMPETENT TECHNICAL TALENTS TO MAKE THE PURCHASE PRACTICAL.

SEND FOR THE LATEST "BARGAIN HUNTER" BROCHURE - IT'S FREE!

THE FAULT-LOCATING WHEATSTONE BRIDGE with multiplying values of 1/1000, 1/100, 1/10, 1/9, 1/4, 1/1, 10/1, 100/1 for resistance measurements and for Varley Loop Tests; also settings of M1000, M100 and M10 for ratios in Murray Loop Tests. 4-decade rheostats. With overall accuracy exceeding $\pm 0.05\%$. A great buy — some with metal and some with wooden cases.

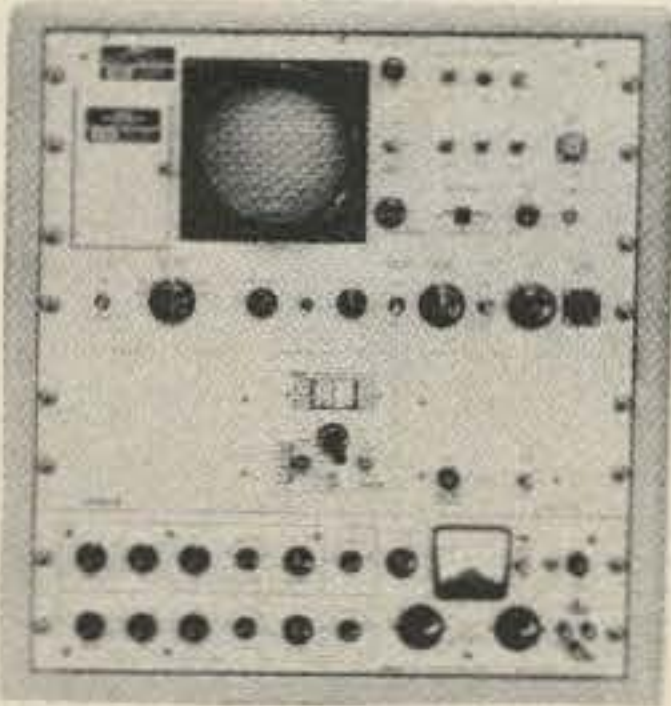SINGLE
SIDE BAND
SPECTRUM
ANALYZER
2-40 MHz




MILITARY ZM-4B/U
\$75.00




A comprehensive communications systems analyzer with five preset sweep widths and continuously variable control. $3\mu\text{V}$ sensitivity and switch selectable 50 or 600 ohm input impedance. Resolution from 10 Hz to 3 KHz, internal markers and many features.

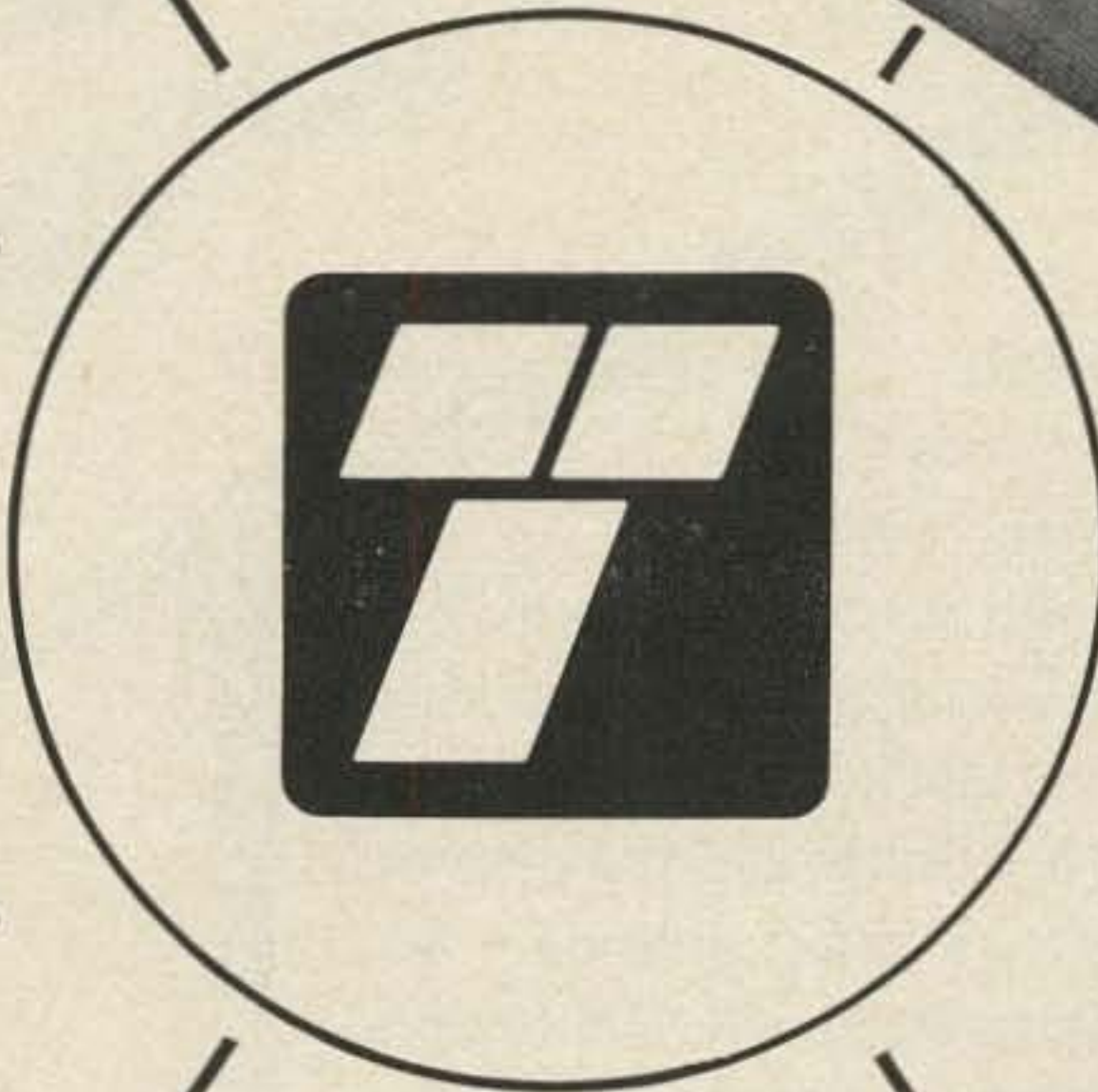SINGER (PANORAMIC) MODEL
SSB-3b
\$1295.00



A bargain hunter's delight. The HP 233A checks carrier current systems and much more. This fine oscillator generates 3 watts output into 600 ohms over the frequency band of 50 Hz to 500 KHz making possible tests over 100 to 200 mile loops. A second output of 6V into 600 ohms can be used simultaneously for other tests. New price exceeds \$700.00

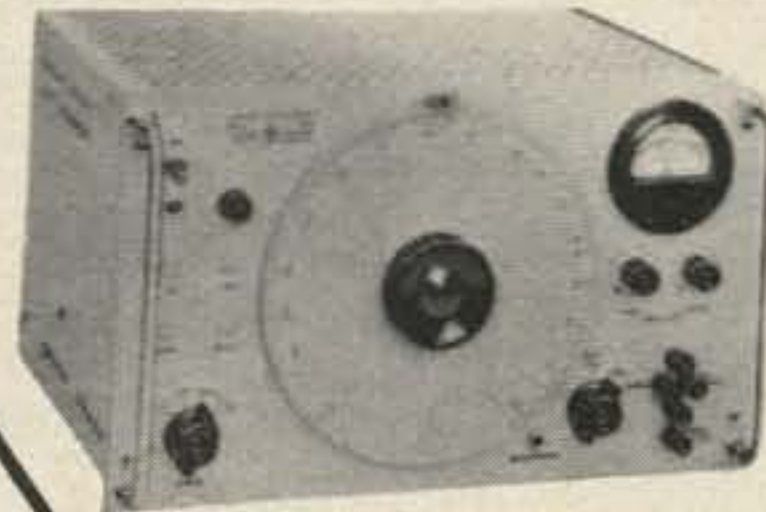

HP 233A
CARRIER TEST
OSCILLATOR
\$75.00

- | | |
|--|---------|
| TEKTRONIC 53/54C dual trace plug-in for use with 530, 540 and 550 series oscilloscopes | \$95.00 |
| TEKTRONIX 53/54K Fast-rise plug-in with 30 MHz bandwidth and 50mV sensitivity | \$50.00 |
| TEKTRONIX G Wide-band DC differential plug-in with 0.05V/cm sensitivity and DC to 20 MHz frequency range | \$65.00 |
| TEKTRONIX H Wide-band high-gain DC plug-in with 0.005V/cm sensitivity and 15 MHz frequency | \$75.00 |
| TEKTRONIX L Fast-rise high-gain plug-in with 0.005V/cm sensitivity and 24 MHz bandwidth | \$65.00 |



TECO a subsidiary of Tucker Electronics Co.
SURPLUS TEST EQUIPMENT FOR BARGAIN HUNTERS
P.O. BOX 1050-A 322 KIRBY ST. GARLAND, TX. 75040
214-348-8800

GET TO THE FASTOP!

NOW YOU CAN CHANGE, ADJUST OR JUST PLAIN WORK ON YOUR ANTENNA AND NEVER LEAVE THE GROUND!

ROHN manufactures towers that are designed and engineered to do specific jobs and that is why we have the FOLD-OVER TOWER . . . designed for the amateur. When you need to "get at" your antenna just turn the handle and there it is. Like other ROHN big communication towers, they're hot dip galvanized **after** fabrication to provide a maintenance free, long lived and attractive installation. ROHN towers are known and used throughout the world . . . for almost a quarter century . . . in most every type of operation. You'll be in good company. Why not check with your distributor today?



ROHN MANUFACTURING

®

DIVISION OF



P.O. Box 2000 / Peoria, Ill. 61601

MATCHING

Here are several methods for making everything match everything else.

Impedance-Matching" is a phrase that haunts the electronics student. He may ask half a dozen people before he gets any kind of explanation of what it means, let alone what it implies. And the explanation may be simply that "all impedances have to be matched to each other," which is occasionally correct, but more often wrong. He may even be told that it takes higher mathematics to explain, which is completely in error. Lower mathematics will do nicely.

This concept is not taught to beginners at all, though I think it should be, since it is an important part of how things work. I myself taught it to my Novice classes, to the amused surprise of my sponsors.

Let me point out at once that the effects of mismatch in impedances can be seen by man, woman and child in the family television receiver. The antenna has a 300Ω impedance, and it is connected to a flat ribbon line of 300Ω impedance, and the other end of this line is connected to the TV set which also has a 300Ω input impedance. All matched; that is the way it is supposed to be. But let us assume that the TV set input impedance is actually 600Ω instead of 300Ω for some reason — mistuning, trouble or whatever. Now the signal from the antenna enters the line, goes all the way to the TV

set, and *most* of it enters and makes a picture. But the mismatch reflects a small part of the signal back up the line all the way to the antenna. Now the antenna is not a perfect match either; it should be, but in practice it can't be. Most of the reflected signal goes into the antenna and is radiated back to the transmitter and good riddance, I don't know a better place for it. But a small fraction is reflected from the antenna mismatch down the transmission line again to the receiver, where most of it goes in.

But the reflected signal, or echo, is late. Meanwhile, the scan on the face of the tube has moved a little, as it should, to pick up the next part of the picture. And here comes a late reflection of something already printed, which prints on top of the signal that should be received at this time to form a "ghost." This image is faint, but annoying, especially if it happens to be an extra face. Everyone has seen this. You have too — remember?

There is a very simple trick that often — not invariably — remedies this trouble. Take a palm-sized piece of aluminum foil from the kitchen and wrap it around the ribbon lead near the set, like a flat napkin ring. Watch the picture while you slide this gadget slowly

top quality... top value... fm by tempo

Tempo's Commercial Line VHF transceivers offer commercial performance at amateur prices. Compare these transceivers with any other available. Compare their performance, their quality of construction, their ease of maintenance, and then compare prices. Your choice will have to be Tempo.



TEMPO/fmh

So much for so little! 2 watt VHF/FM hand held. 6 Channel capability, solid state, 12 VDC, 144-148 MHz (any two MHz), includes 1 pair of crystals, built-in charging terminals for ni-cad cells, S-meter, battery level meter, telescoping whip antenna, internal speaker & microphone. \$199.00



TEMPO/CL 146


The CL-146 offers operation on the 146 MHz amateur band. The price includes a microphone power cord, mounting bracket and one pair of crystals. A full line of accessories is also available.

- 12 channel capability
- 13 watts or a power savings 3 watts
- All solid state, 12 VDC
- 144 to 148 MHz (any two MHz without retuning)
- Supplied with one pair of crystals
- RF output meter, S-meter, receiver detector meter
- Provisions for external oscillator
- Monitor feature
- Audio output at front panel
- Internal speaker
- The Price: \$299.00

TEMPO/CL 220



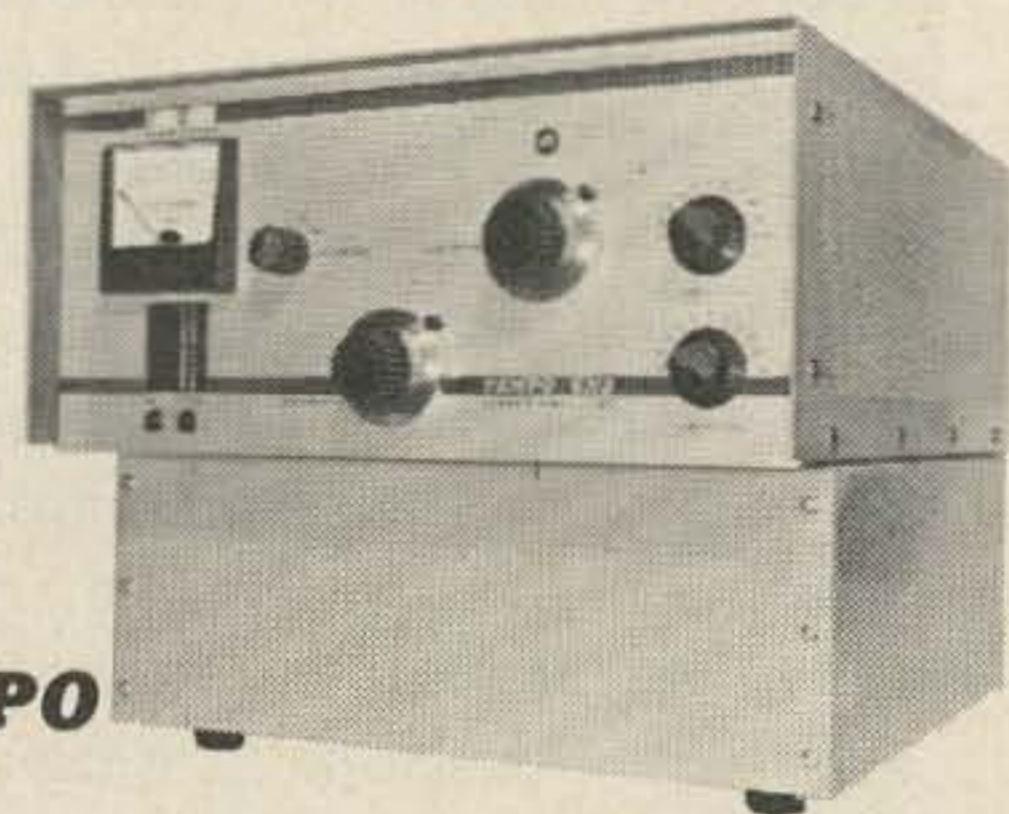As new as tomorrow! The superb CL-220 embodies the same general specifications as the CL-146, but operates in the frequency range of 220-225 MHz (any two MHz without retuning). At \$329.00 it is undoubtedly the best value available today.



TEMPO 6N2

The Tempo 6N2 meets the demand for a high power six meter and two meter power amplifier. Using a pair of Eimac 8874 tubes it provides 2000 watts PEP input on SSB and 1000 watts input on CW and FM. Completely self-contained in one small desk mount cabinet with internal solid state power supply, built in blower and RF relative power indicator. \$695.00

TEMPO VHF/UHF AMPLIFIERS

Tempo offers a broad line of FM power amplifiers. Rugged, dependable and all solid state. Outputs from 30 to 120 Watts.

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

AVAILABLE AT SELECT DEALERS THROUGHOUT THE U.S.

Prices subject to change without notice.

TABLE

RI	Rt	I	I ²	Pg	PI	Pt	E	K
10	20	.500	.250	2.50	2.50	5.00	5.00	50%
0	10	1.000	1.000	10.00	0	10.00	0	0
∞	∞	0	0	0	0	0	10.00	0
990	1.000	.01	.0001	.001	.0990	.100	9.900	99%
11	21	.476	.227	2.27	2.497	5.767	5.236	43.28%
9	19	.526	.277	2.77	2.493	5.263	4.734	47.61%

up and down the line, an inch or so at a time, until the "ghost" is exorcised.

A friend of mine who is a pretty good TV repairman, had a very odd case of trouble. He checked the antenna and transmission line, which he followed through the house wall and across a clothes closet and thence downstairs to the TV receiver. He couldn't figure out why the line had been strung across the empty closet, but an even greater mystery was that someone had hung an ordinary wire coat hanger on the ribbon line. He took it off as a matter of course, and went down to the receiver (see Fig. 1).

Here he soon found the trouble, which he fixed. Confidently, he turned the receiver on again, fully expecting it to work perfectly. He got a hazy picture of poor quality. He was trying to clear this up with just about every adjustment the set had, when the lady of the house came in to check on his progress.

She took one look at the picture and exclaimed, "Oh, somebody must've taken the coat hanger off!" and dashed upstairs. This was ridiculous, of course — there wasn't so much as a kink or crease in the line, and the connections were good. The line was all in one piece.

Suddenly the picture cleared up and the woman came back downstairs. He got his money and left. When I heard this story, I asked him: "And was that *all* she did? Put the coat hanger back on?"

"I was afraid to ask her. Who knows about things like that?"

Auto drivers see the effects also, especially in the winter when they start their cars. When they engage the starter switch, the battery is connected straight across the starter-motor. This is wound with copper bars instead of wire, and is as near to being a short circuit in an iron casing as you could ask. It develops over a horsepower to spin a big engine.

In cold weather, it doesn't exactly spin it — it groans and shudders and grinds, but it does turn over, slowly. The ignition doesn't work very well, since the voltage is too low.

And why is it low? Because roughly half the voltage is being dropped in the battery itself. This also means that *half the power* is being lost in the battery! Under these conditions, the transfer efficiency is only 50%. This is why a battery is rated, say, 100 amp-

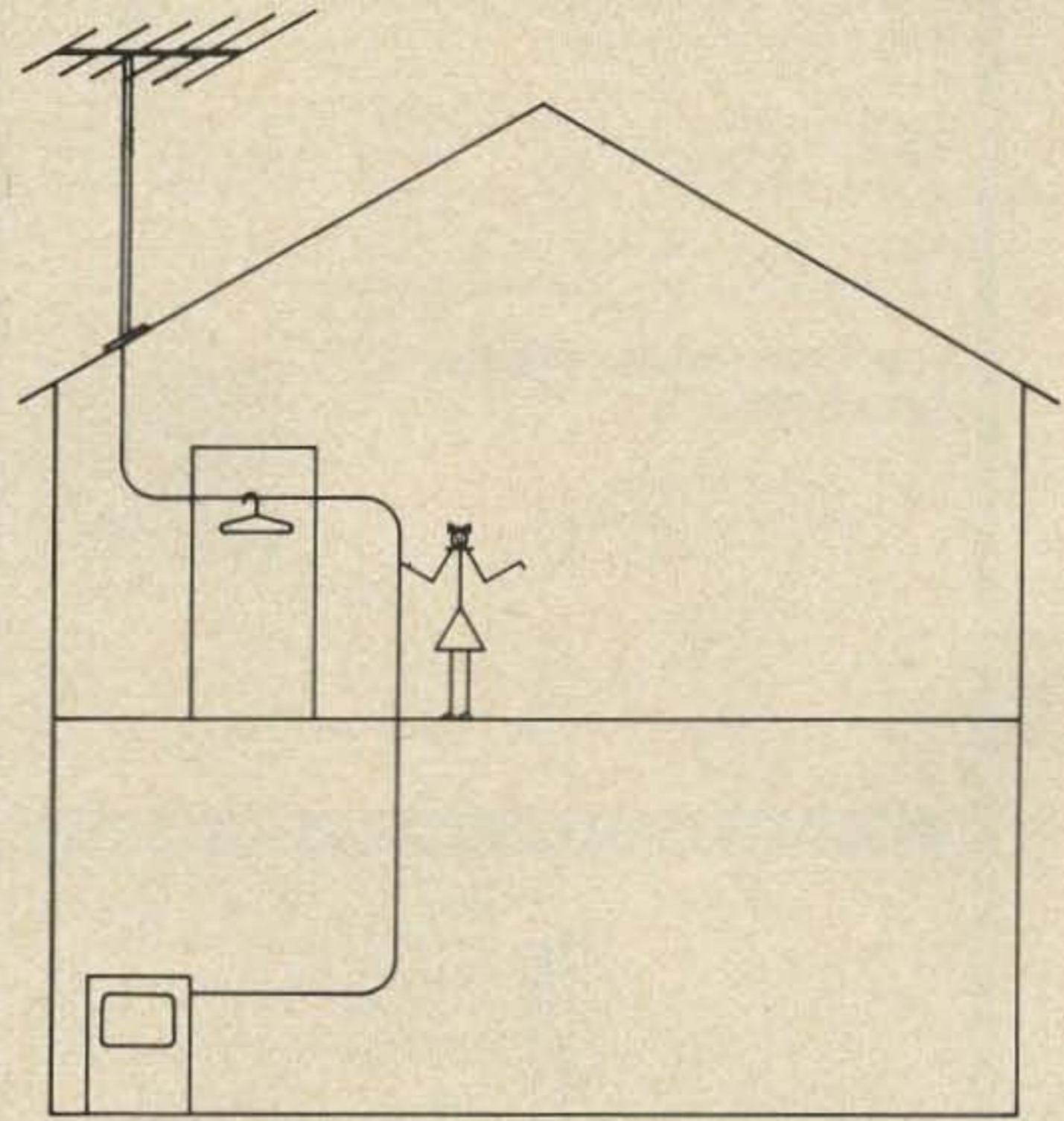


Fig. 1.

ere hours for a one ampere rate, and a great deal less for higher rates. The heat that is lost in the battery does do some good — in warming up the battery it speeds up the chemical reaction that produces the current and so gives a power boost when it is badly needed.

By this time, the heavy oil in the bearings and on cylinder walls has loosened a bit, and the engine turns easier. As the mechanical load lightens, the starter-motor turns faster. It generates more back-voltage to oppose the battery voltage, so that the current from the battery is less. Now the battery voltage goes

NES

NURMI ELECTRONIC SUPPLY

Department 49
1727 Donna Road • West Palm Beach, Florida 33401
PHONE — (305) 686-8553



HEP 170's
THE "DO EVERYTHING"
2 1/2 AMP, 1000 VOLT DIODE



Motorola is catching up on the backlog and we've got thousands of them back in stock. 10/\$2.50 — 100/\$20.00

RCA 40673's

THE MOST POPULAR DUAL GATE PROTECTED MOS FET around. Good to over 400 MHZ. We got 'em and you get 'em for only 5/\$6.00

RG-174/U

WE WENT THROUGH 20 MILES OF IT LAST TIME!

We are authorized Belden Distributors and new shipments have come in from the factory. Split a 500' spool with a friend and save \$\$\$\$\$

BELDEN NO. 8216 100'/\$5.25 — 500'/\$19.30

RF POWER TRANSISTORS

We did it again - All brand new with standard markings and most were manufactured this year. A major manufacturer dropped his RF power line and we bought his inventory.




2N5589	3 Watts Out	\$ 3.50	2N6080	4 Watts Out	5.00
2N5590	10 Watts Out	6.00	2N6082	25 Watts Out	10.00
2N5591	25 Watts Out	12.00	2N6084	40 Watts Out	15.00

All are Silicon NPN and power output ratings are good to 175 MHZ. Hurry! Some quantities are limited.


KEYSTONE PERF BOARD

G-10 Glass Epoxy
Perf Board 3/64" Thick.

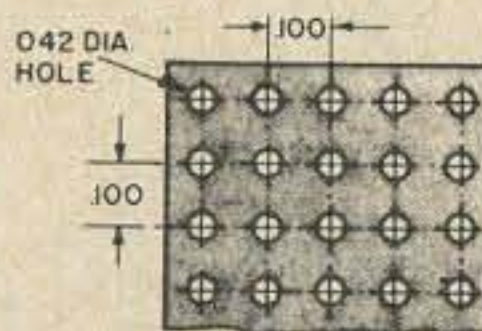


--UNCLAD--			--COPPER CLAD ONE SIDE--		
No.	Size (in.)	Price	No.	Size (in.)	Price
4229	2 x 4 1/2	\$.85	4238	2 x 4 1/2	\$1.35
4230	2 x 6	1.09	4239	2 x 6	1.85
4231	4 1/2 x 6	1.55	4240	4 1/2 x 6	3.20
4232	17 x 6	5.75	4241	17 x 6	6.70

PUSH-IN TERMINALS For .042 DIA. HOLES

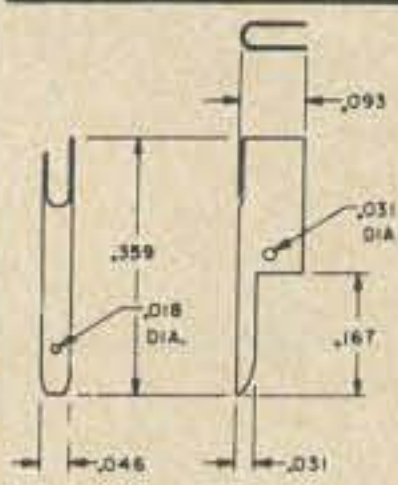

Cat. No. 1495 \$1.50/C
MATERIAL: .008 thick Beryllium Copper.
FINISH: Fused Tin Plate

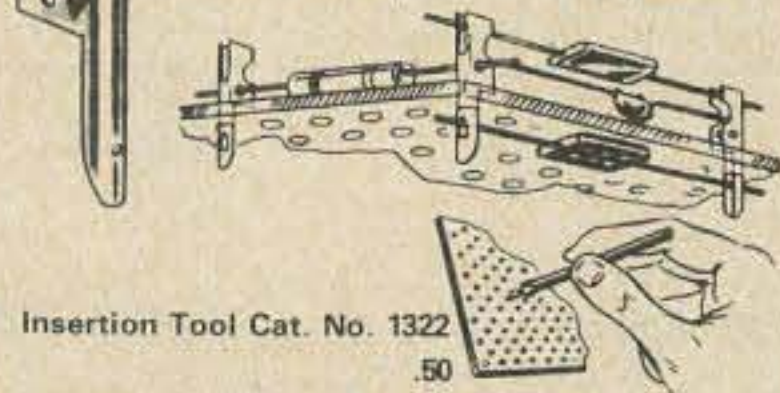The terminal is easily press-fit into a .042 dia. hole without staking or the base may be flared for permanent installations. Ideally designed for use in micro-circuitry to support components when space is at a premium.



RF RELAY



Designed to handle 200 watts to 450 MHZ. 12 VDC coil, DPDT. The nicest RF relay we have ever had. Only about 1-1/4" cube. Super low VSWR. Satisfaction guaranteed.

Only \$4.95 or 4/\$17.00

ARCO/EL Menco TRIMMERS

400 \$.55	421 \$.55	428 \$1.26	464 \$.69
402 .55	422 .55	429 1.26	465 .89
403 .67	423 .64	460 .37	466 .97
404 .81	424 .80	461 .32	467 1.04
405 1.01	425 .85	462 .52	468 1.20
406 1.04	426 1.01	463 .64	469 1.22
420 .58	427 1.12		



WE GUARANTEE WHAT WE SELL!!!!

We ship UPS whenever possible. Give street address. Include enough for postage, excess refunded in cash. Florida residents include 4% Tax.

up in consequence, and the ignition has enough for a nice hot spark and VAROOOM! — the engine starts.

The only thing that could be done about that 50% business would be to increase the size of the battery. If you made it ten times bigger, then the voltage would drop only a little. But think of hauling all that big battery around, and of the room it would take, and what it would cost. Obviously, the solution is too costly.

Some drivers trickle-charge their batteries each winter night. (I do.) This puts a few ampere hours into their batteries, but more important, it warms them a little, making more current available for morning starts.

An example of the opposite case is your local power company. What is the output impedance of those big generators, do you suppose? One thing is sure — the entire load impedance of a big city won't match it, because the impedance of the generator would be much, *much* lower. If the impedances were equal (matched) the big, expensive generating machines would burn up literally in seconds — they run warm as it is, but they don't dissipate more than a couple of percent of the power they produce.

When it comes to impedance matching, the local telephone company is the champion. They match anything and everything to cut reflections to an absolute minimum. This means lines, coils, repeaters, test instruments, subscribers' telephones, the whole works. Even here there are exceptions: the volume indicator meters which are used to check transmission levels in broadcast stations, recording studios and telephone offices. They are deliberately made high impedance so they won't load down the line under test and drain the signal, at the same time giving a false indication. And that is exactly the same reason your VOM is 20,000Ω per volt instead of a much cheaper 1,000Ω per volt resistance — accuracy and minimum drain.

From this point on, generalities won't do; let's try some of the "lower mathematics" I mentioned. Figure 2 shows a simple generator which may be a battery-charging generator, vacuum-tube oscillator, or almost anything that puts out current and has an

internal resistance of 10Ω . You can't get in behind this resistance in any fashion; this is what you get at the generator terminals. The voltage is a constant 10V inside the generator but the voltage you get outside depends on the load.

Suppose the load resistance matches the generator resistance (impedances are the same). Refer to the table: the top line shows this condition, and reads as follows:

R_l , the load resistance, is 10Ω . R_t is the total resistance in the circuit, 20Ω . I is the current in the circuit, .500A. $I \times I$ is this quantity squared, .250A. P_g is the power lost in the generator as heat, 2.5W. P_l is the useful power, the power in the load, also 2.5W. P_t is the sum of these two, the total power generated. E is the voltage across the line (generator terminals and the load, all the same point). K is the transfer efficiency, which you already know is 50%. This looks very low, and usually we want to do a lot better than this. Sometimes we can't, or other things are much more important, as in signal transmission.

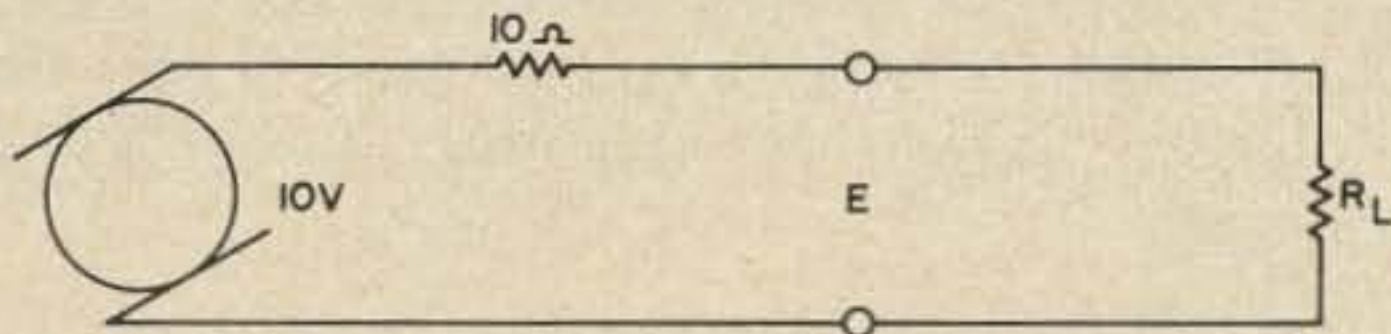


Fig. 2.

Look at line two. Here, the load is zero, a short circuit. The total resistance is only 10Ω the current 1A, the current-squared 1A, and all the power is lost as heat in the generator itself, 10W. The power transferred to the short circuit is zero because there is no resistance in it. The total power is, of course, that in the generator, 10W. The voltage across the short circuit is zero, and the transfer efficiency is also zero. Not hard, so far, just simple Ohm's law.


Now in line three we take the opposite extreme, or an open circuit. Load resistance, infinite. Total resistance, infinite. Current zero, current-squared zero, power lost in generator zero, power delivered to the load zero, total generated power zero, voltage equals the full 10V — no $I \times R$ drop. Transfer efficiency is zero too.

Here comes the lower mathematics — to make it easier, we'll use a load of 990Ω

CW FILTER



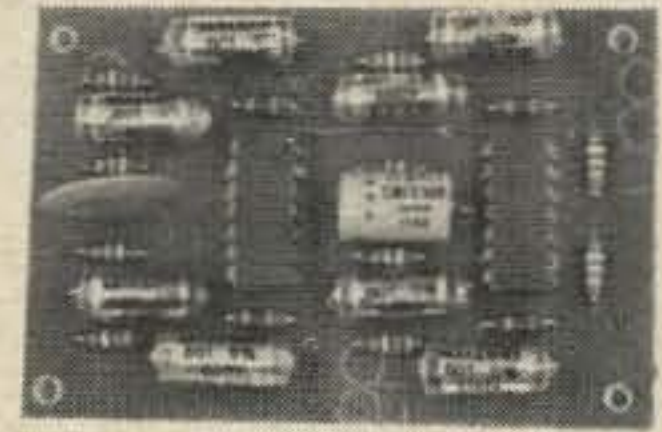New Model CWF-2BX—\$19.95.
Ready to use. Please include
\$1.00 postage



Model CWF-2—\$12.95, Kit.
\$14.95 Wired, tested, guaranteed.
Please include 55c postage

- Get Razor Sharp selectivity from any receiver or transceiver.
- Extremely high skirt rejection
- Drastically reduces all background noise.
- No audible ringing.
- No impedance matching.
- Ultra modern active filter design uses IC's for super high performance.

We have what we think is the finest CW filter available anywhere. The 80 Hz selectivity with its steep sided skirts will allow you to pick out one signal and eliminate all other QRM and QRN. Simply plug it into the phone jack or connect it to the speaker terminals of any receiver or transceiver and use headphones, small speaker, or speaker amplifier. Better yet, connect it between any audio stages to take advantage of the built in receiver audio amplifier.

Build the 2"x3" CWF-2 PC card into your receiver or get the self contained and ready to use CWF-2BX and plug in!

SPECIFICATIONS

BANDWIDTH: 80 Hz, 110 Hz, 180 Hz (Switch selectable)
SKIRT REJECTION: At least 60 db down 1 octave from center frequency for 80 Hz bandwidth
CENTER FREQUENCY: 750 Hz
INSERTION LOSS: None. Typical gain 1.2 at 180 Hz BW, 1.5 at 110 Hz BW, 2.4 at 80 Hz BW
INDIVIDUAL STAGE Q: 4 (minimizes ringing)
IMPEDANCE LEVELS: No impedance matching required
POWER REQUIRED: CWF-2 . . . 6 volts (2 ma.) to 30 volts (8 ma.); CWF-2BX . . . standard 9 volt transistor radio battery
DIMENSIONS: CWF-2 . . . 2"x3" PC board; CWF-2BX . . . 4"x3 1/4"x2 3/16" (black winkle steel top, white aluminum bottom, rubber feet)

TRY this fantastic CW filter. If you don't think it is the best you have ever used, ask for your money back. We will cheerfully refund it. These filters carry a full one year warranty.

Write for FREE brochures and magazine test reports. Other IC active filters available: CW mini filter (1 1/2"x2"), low pass, high pass, and wide bandpass filters. Audio amplifiers: 1/2, 1, 2 watts. Crystal calibrator.

MFJ ENTERPRISES

P. O. Box 494, Mississippi State, MS 39762



For FREQ. STABILITY

Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us.

CRYSTAL SPECIALS

- 2-METER FM for most Transceivers ea. \$3.75
144-148 MHz — .0025 Tol.
 - Frequency Standards
 - 100 KHz (HC 13/U) 4.50
 - 1000 KHz (HC 6/U) 4.50
 - Almost all CB Sets, Tr. or Rec. 2.50
(CB Synthesizer Crystal on request)
 - Any Amateur Band in FT-243 1.50
(80-meter, \$3.00 — 160-meter not avail.) 4/\$5.00
- For 1st class mail, add 20c per crystal. For Airmail, add 25c. Send check or money order. No dealers, please.



Division of Bob Whan
& Son Electronics, Inc
2400 Crystal Drive
Ft. Myers, Florida
33901

All Phones
(813) 936-2397

Send 10c for new catalog with 12 oscillator circuits and lists of frequencies in stock.

Atlas-180 ...No Repeater Required.



WITH THIS MOBILE RIG YOU CAN QSO all over the state, across the country, and even work intercontinental DX, right from the driver's seat, and without the aid of a repeater! Only a little bigger than a 2 meter FM rig, the Atlas-180 is an all-solid-state SSB-CW Transceiver that covers 4 bands, 20-40-80, and 160 meters, with a power input rating of 180 watts, and sells for only \$479. See your Atlas dealer for complete details, or write us for a brochure and dealer list.



ATLAS
RADIO INC.

5580B El Camino Real

Phone (714) 729-8985

Mail Address: P.O. Box A, Carlsbad, California 92008

which will simplify currents and such. Load 990Ω total resistance $1,000\Omega$, 10 mils (.01A), current squared $100\ \mu\text{A}$ or .0001A, power lost in the generator is only a milliwatt (whee!), power delivered to load nearly $1/10\text{W}$, total power is exactly $1/10\text{W}$, the voltage is up to 9.900V (only 0.1V lost in the generator) and the transfer efficiency, K, is a great big 99%. This is the kind of setup the power company has. They are not interested in maximum power transfer, but maximum transfer efficiency. For this reason they use big generators and run them conservatively. Line 1 is the telephone company case. They *must* have minimum reflections and the power transferred is important. The actual power involved is tiny, so they are happy with 50% transfer efficiency – it's a cheap price for what they accomplish.

Here comes the sticky part in line five. Here we use 11Ω load. Theory tells us we should transfer just a little less power from the generator to the load, and that the efficiency should be a little less. And so it proves; the current I is a little less, but the voltage E is a little more – how *about*

that? – won't they average out? – no, the delivered power is 2.497W for a K of 43.28%.

The last line tells the same story in different words; with a load of 9Ω , the current is higher and the voltage is lower, and the delivered power is 2.493W, with a K of 47.61%.

Mathematicians would sniff at proof like this – it really does take higher math to rigorously prove the proposition. But we all know instinctively that the power actually *does* peak at 10Ω , and that if you mismatch the load even the smallest amount, the delivered power drops off correspondingly, which is plenty good enough for our present purposes.

How good is your Ohm's law? Could you make up a table like this one to explain a different but similar case to someone else? Reading the values and agreeing with them is not quite the same as working them out. To thoroughly understand this impedance-matching (resistance-matching in this case, same thing) theorem you should be able to do all the pencil work too.

CHARGE IT
ON



CHARGE IT
ON



**CALL
FREE**



**CALL
FREE**

**TRADE
ON
NEW**

CALL

**TRADE
ON
USED**

Bill Du Bord, WØKF

(9 A.M. — 5 P.M. Central, Closed Sunday and Monday)

**FOR
A SQUARE DEAL
ON**

- **DRAKE**
- **TEMPO/ONE**
- **HALLICRAFTERS**
- **CLEGG**
- **STANDARD**
- **YAESU**
- **SWAN**
- **COLLINS**
- **KENWOOD**
- **REGENCY**

We carry all major brands and a large stock of used reconditioned equipment


SEND STAMP FOR USED LIST

HAM RADIO CENTER INC.


8342 OLIVE BL.

ST. LOUIS, MO 63132

NEW

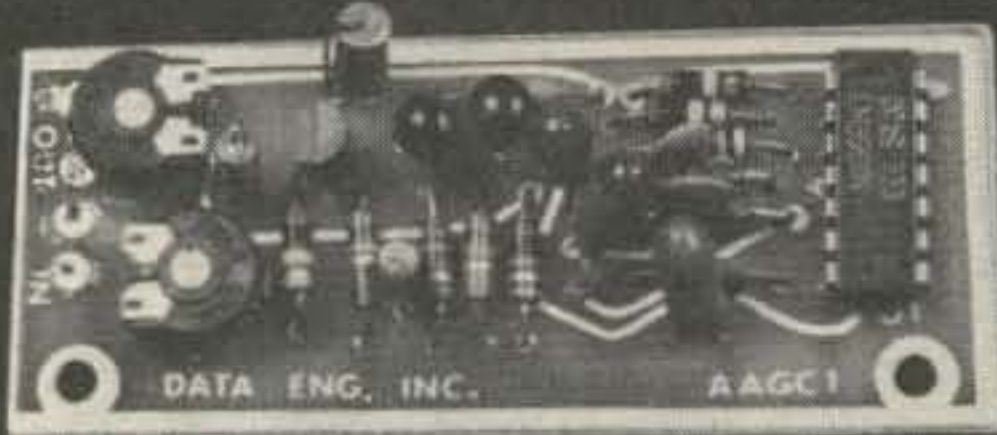

NEW

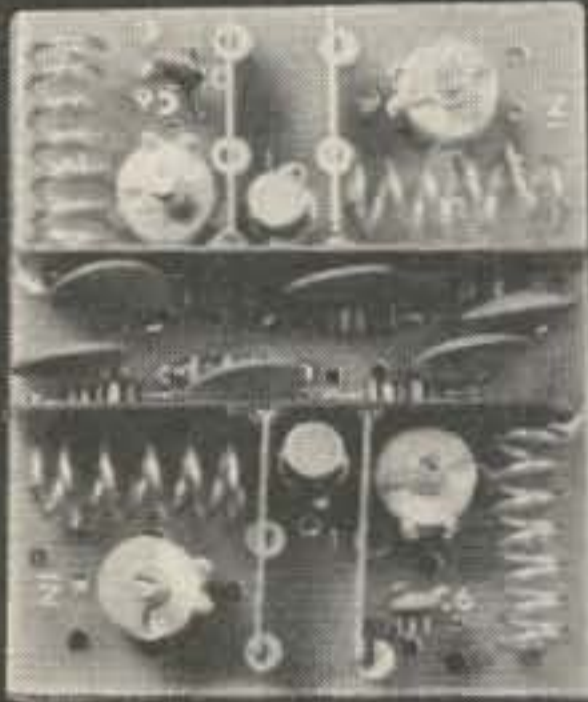

AUDIO AUTOMATIC GAIN CONTROL AMPLIFIER

Eliminate tone decoder problems due to input signal variations and other problems caused by weak, strong or varying signals. The AAGC-1 will take signal levels between 50 mV to 5 Volts and feed a clean rock stable signal to any decoder for perfect operation.

Shipping Weight 3 oz. **\$12.95 kit**
\$17.95 wired

DELUXE RECEIVER PREAMPS


Specially made for both OLD and NEW receivers. The smallest and most powerful single and dual stage preamps available.

BAND	STAGES	GAIN	NOISE FIGURE	KIT PRICE	WIRED PRICE
10 meter	Single	20 dB	2 dB	\$9.50	\$12.50
6 meter	Single	20 dB	2 dB	\$9.50	\$12.50
2 meter	Single	20 dB	2.5 dB	\$9.50	\$12.50
2 meter	Double	40 dB	2.5 dB	\$18.50	\$24.50
220 MHz	Single	17 dB	2.5 dB	\$9.50	\$12.50
220 MHz	Double	35 dB	2.5 dB	\$18.50	\$24.50
*440 MHz	Single	14 dB	3 dB	\$9.50	\$12.50
*440 MHz	Double	28 dB	3 dB	\$18.50	\$24.50

DATA ENGINEERING INC.



2212 PALMYRA RD. ALBANY, GA 31701

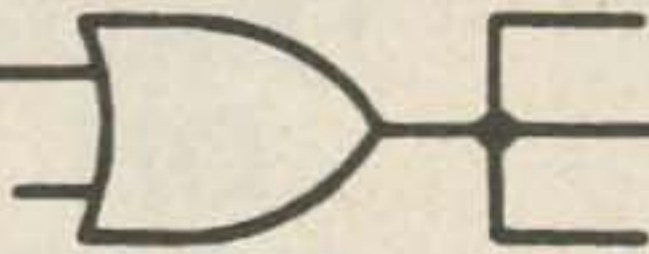

Please include sufficient postage for shipping

912-435-1764

I is easy – it is equal to R_t divided into 10, the generator voltage. Don't let this confuse you – the generator 10Ω and 10V are equal by coincidence. P_I is $I \times I$ times the load resistance. How do you get E? Ohm's law again; I times R_l will do it in one step. If K puzzles you, it is simply P_I divided by P_t and can be expressed as a decimal, or more impressively, as a percentage. Unfortunately, the only way to do arithmetic is to *do* it. Shortcuts are mostly longer, unless you are wholesaling, such as when you make up a table.

Another case of deliberate mismatching is employed in some filters. You don't know how much the filter is actually mismatched, of course. But the designers have discovered that if the mismatch is exactly the right amount, the cutoff points are much sharper, and it works better all around. So they specify the in and out impedances they want you to use, and you use them. It is not wise to deviate here if you expect results.

One last case: Sometimes an audio amplifier must work into a specified load for lowest distortion. Look up any big output

triode in your tube manual – you will find, under Class A conditions, that all output triodes work into a load impedance of twice their own plate impedance.

The reason is that as the load impedance is raised from equal to, to twice the plate impedance, the output delivered to the load goes down slowly, while the distortion goes down pretty rapidly. The two-to-one mismatch represents about the best compromise. At this value, the distortion is only about 5%. However, this is mostly even order stuff, which means that you can get rid of most of that by going to push-pull. But even single-ended amplifiers sounded pretty good, without reverse feedback or filtering or fooling around.

The pentodes had a lot more gain, which eliminated a stage and made the amplifiers simpler. Besides, they were the latest thing!

So this is the story of impedance matching and mismatching. If someone insists that impedances must always be matched evermore by Divine Law, be gentle with him. Why destroy his illusions? He won't believe you anyhow, unless he really wants to know.

...WB2PAP

REMOTELY TUNABLE DUAL - BAND ANTENNA COUPLER

John J. Schultz W2EEY/1
c/o RLC Inc.,
30 East 42nd St.
New York, New York 1004

Simplified and inexpensive motor-operated remote control of tuning and provision for remote reflected power monitoring are features of this coupler. The ideas presented can be applied to a variety of situations where remote control and band-switching of an antenna coupler unit is desired while utilizing only a single pair control cable for all remote control functions.

Instead of running resonant feedlines or the end of a voltage-feed antenna into the shack, it would generally be better to have the coupler used remotely located and controlled. In many instances, this would avoid most of the problems of rf in the shack and possibly permit a more optimum placement of the radiating portion of the antenna system. In apartment situations, it may also prevent TVI/BCI difficulties due to being able to use a coaxial transmission line to the remotely located coupler.

Many schemes have been developed for the remote control of antenna couplers. One can get involved with expensive motors, special relays, elaborate control circuits and the need for multi-conductor control cables. The coupler described, however, uses inexpensive components that really make it only slightly more expensive than a regular antenna coupler. The coupler is shown built for dual band operation, but the ideas used can be incorporated into more elaborate designs as required to fit a specific need.

Basic Scheme

The functional units comprising the coupler are shown in Fig. 1. The coupler itself contains a matching network with motor controlled tuning. The motor tuning is also arranged to provide a switching function. The reflected power sensor is simply half an in-line SWR meter. One could use an SWR meter located at the transmitter to

indicate the effect of tuning the coupler but a reflected power indication directly between the coupler and transmission line is much more accurate. It is also generally easier to use than a field-strength type indicator when tuning. The indicator voltage from the reflected power sensing unit and the dc control voltage for the motor are both transferred over a shielded 2 conductor cable which is completely independent of the transmission line. The motor itself is a dc

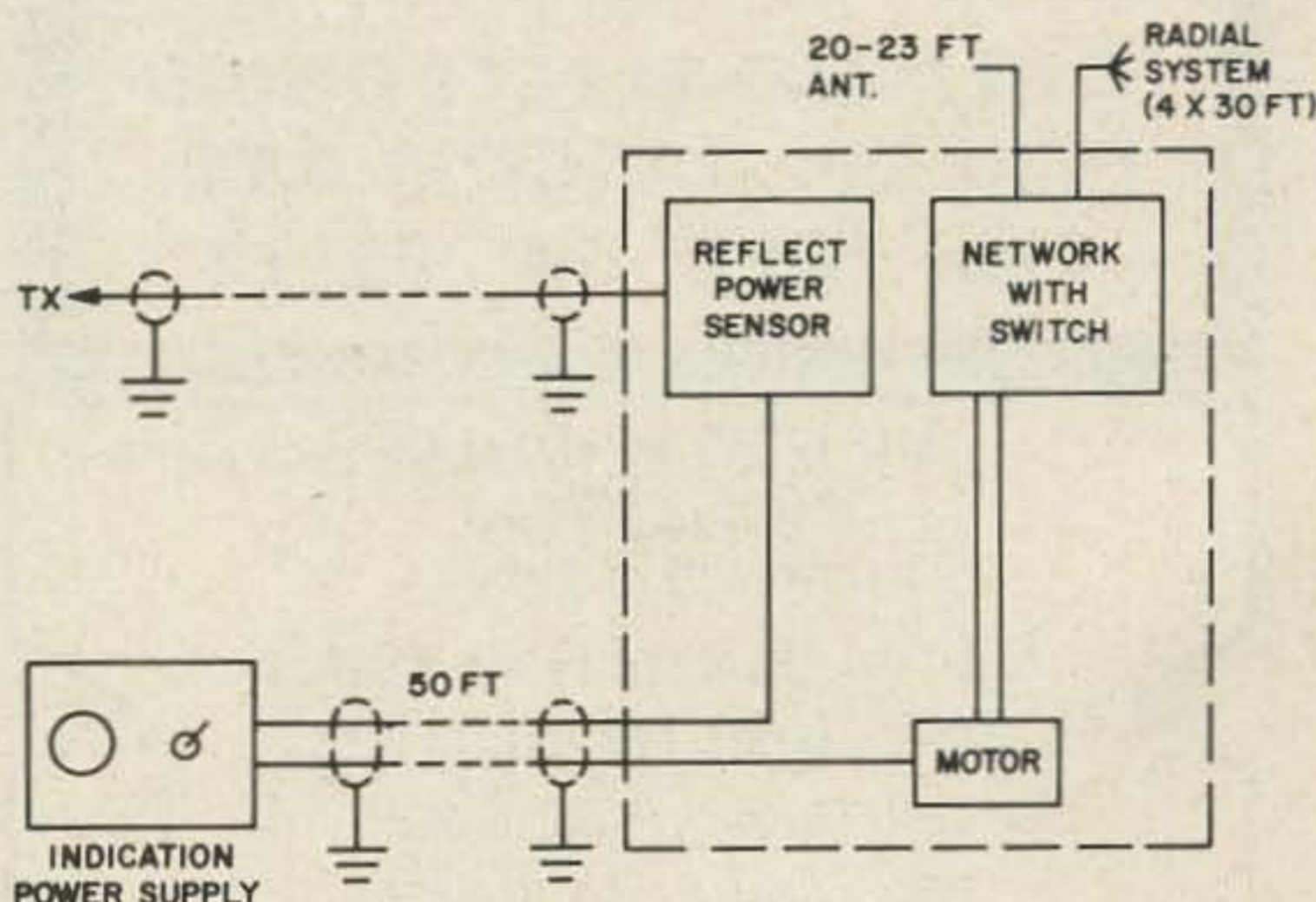



Fig. 1. Basic components of the dual-band remote antenna coupler system.

type and the direction of rotation is controlled simply by changing the polarity of the motor voltage supply.

Coupler Unit

The coupler unit circuit is shown in Fig. 2. The unit was designed for use with about a 20 foot rod antenna on 80 and 40 meters. As was mentioned before, the basic scheme shown can be used with many coupler arrangements. However, one should be sure first that the coupler will properly tune manually with a given antenna before any attempt is made to control it remotely.

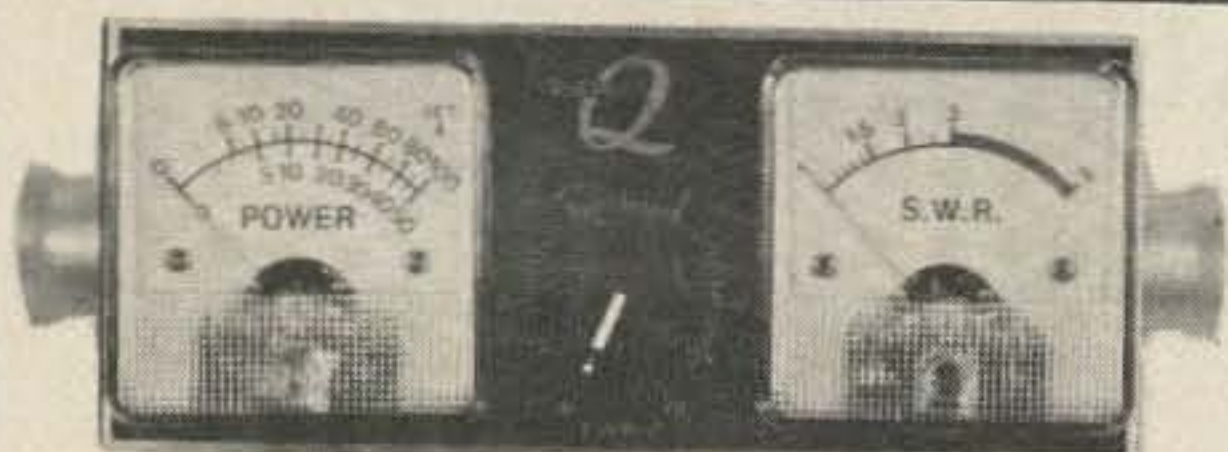As shown in Fig. 2, the transmission line is link coupled to the loading coil. On 80 meters the variable capacitor is used to



SWB-2 \$19.95
 SWR BRIDGE READS FORWARD & REFLECTED POWER
 SIMULTANEOUSLY 'EASY READ' METERS
 DUAL 100-MICROAMP METER MOVEMENTS
 LOW INSERTION LOSS SIZE 5X2X2
 MAY BE LEFT IN LINE UP TO 2,000 WATTS
 3 TO 150 MHZ
 ADD \$1.25 FOR POSTAGE

OUR BEST "HAM" BUY



QUEMENT ELECTRONICS
1000 SO. BASCOM AVE.
SAN JOSE, CA. 95128

CFP ENTERPRISES

866 Ridge Road
 Lansing, NY 14882

Central Upstate New York's
Mail-Order Headquarters
Specializing in Two-Meter FM
and Quality Used Gear

Office and Salesroom Hours by Appointment Only
 24-Hour Phone: 607-533-4297

Send SASE for Monthly Listing of:
Used Equipment and Bargain Goodies

Trade-ins accepted on both new and used equipment. Cash deals get prepaid shipping in the Continental USA plus a 15% discount on the items on our regular listing!!!!

COLUMBIA PAYS TOP \$\$\$!
We need these today - now!

- ★ SP-600 JX HAMMERLUND RECVRs
- ★ 618T COLLINS TRANSCEIVERS

P.S. We're also hungry for: Bendix, Collins, Tektronix, H-P, etc. lab equipment; late model military elec. for ground, sea, air; other good gear. We pay freight! Airmail cond. & \$\$-wanted today - NOW! We're desperate!

COLUMBIA ELECTRONIC SALES, INC.
 Box 9266-A; No. Hollywood, CA 91609
 Phone: (213) 764-9030

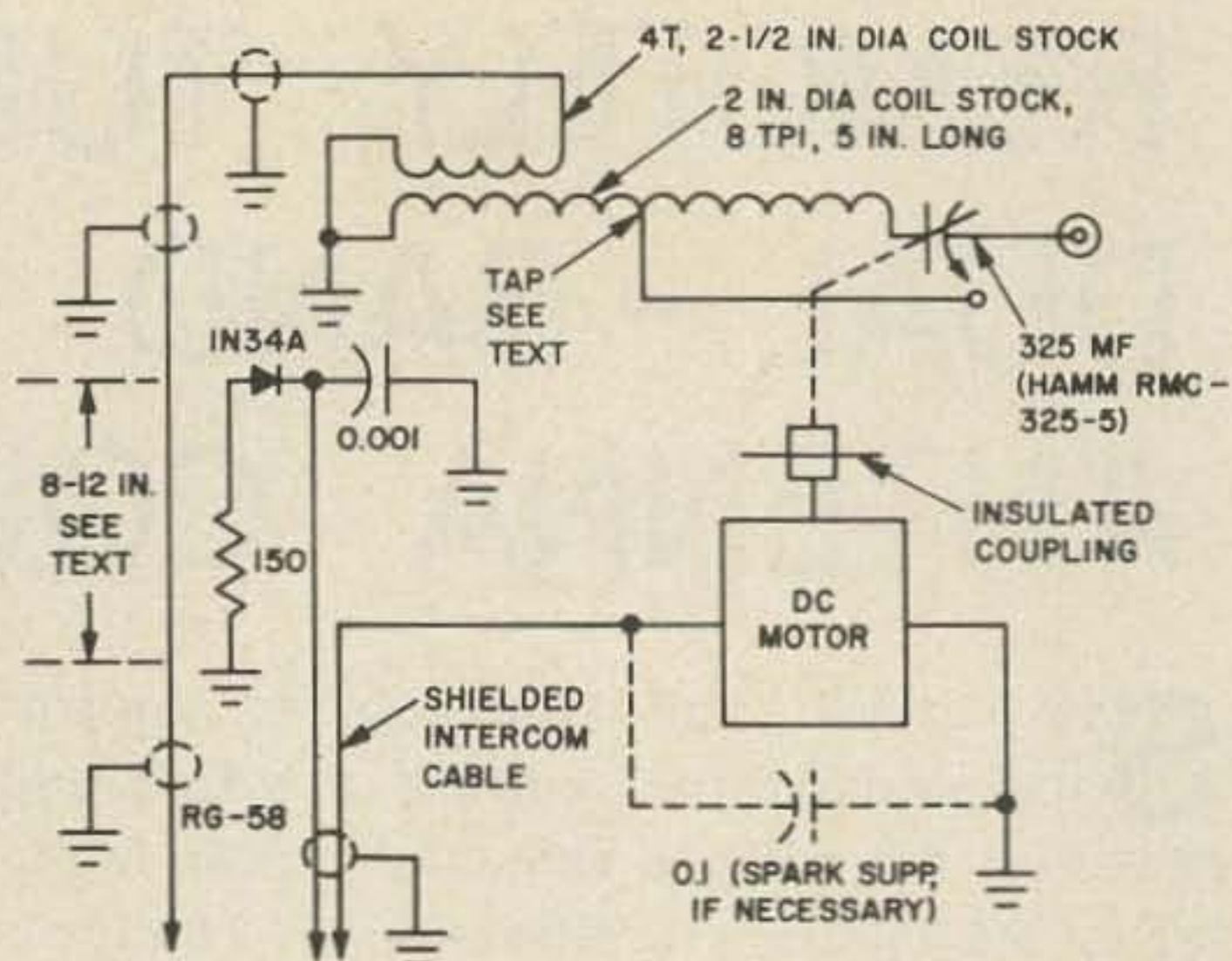


Fig. 2. Diagram of the remote antenna coupler.

allow tuning of the series resonant antenna/loading coil circuit across the band. For operation on 40 meters, the variable capacitor is placed on minimum capacitance. In this position, the rotor plate mates with a contact placed on the capacitor frame, and part of the loading coil is shorted out. The slower change in reactance across the 40 meter band allows operation over most of the band without the need for additional tuning. The dc motor is coupled to the capacitor by means of an insulated coupling.

The reflected power sensor is formed as part of the transmission line. The pickup


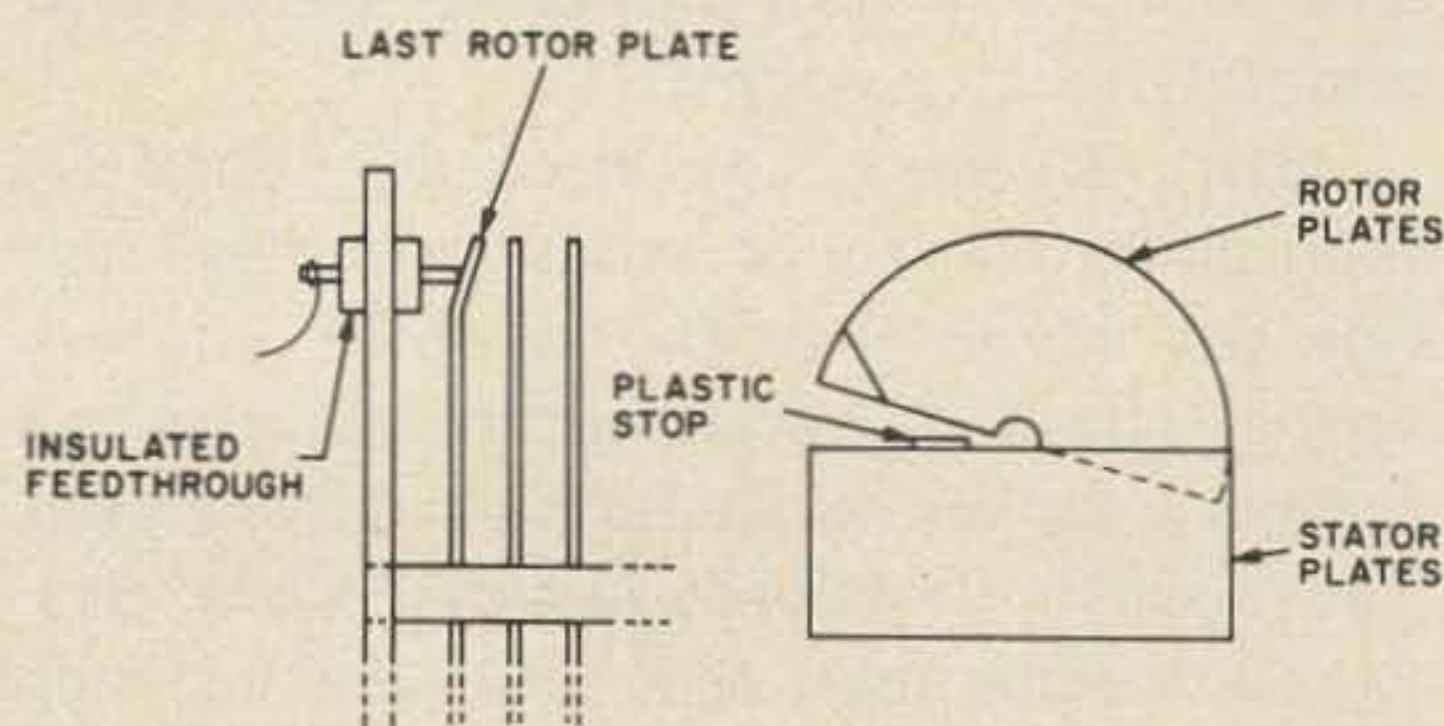


Fig. 3. Details of capacitor switch top view (A) and back view (B). Feedthrough is placed in capacitor back frame such that rotor plate makes contact with plates almost fully disengaged from stator plates.

link is made somewhat longer than usual in order to develop a reasonable current over the control cable back to the indicator unit in the shack. The unit is not designed to read the actual SWR, although this can be done if one calibrates the system initially with dummy load resistor simulating different SWRs. Assuming that the SWR was checked initially using a calibrated SWR meter, the

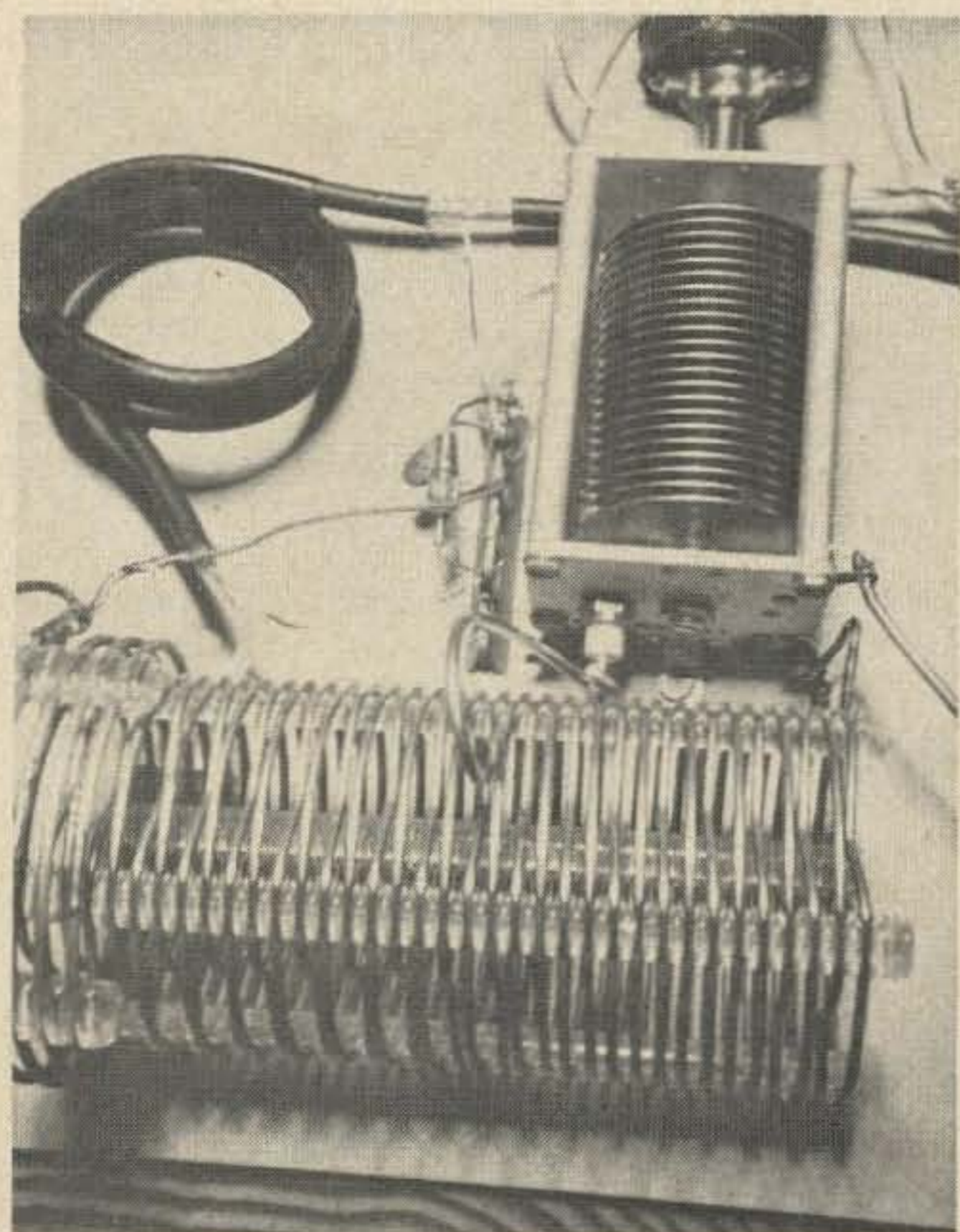reflected power indicator is only used to set the motor driven variable capacitor for minimum reflected power at any given operating frequency. If one does, however,



Remote Coupler Construction

The main coil is shown in the foreground with the link on the left. The feedthrough used for COR switching can partially be seen on the backframe of the variable capacitor. The coiled coax on the left forms the reflected power sensing unit with the components mounted on the terminal strip.

also use an SWR in the transmission line by the transmitter, there is a possibility of having a means available to continuously monitor the condition of the entire transmission line/antenna system. For any reference setting of the forward power indicator on the SWR meter by the transmitter, the same reference reading from the reflected power sensor in the coupler unit should be obtained as long as all components remain in good condition.

Coupler Unit Constructor

The photograph shows the general layout used for placement of the components on an approximate 8" square of wood which was placed in a slightly larger wooden enclosure. There is nothing critical about the construction as long as one keeps the variable capacitor insulated. A small metal enclosure

FREE IC

With Every \$10 Order*

- REDUCE YOUR PROJECT COSTS
- MONEY-BACK GUARANTEE
- 24-HOUR SHIPMENT
- ALL TESTED AND GUARANTEED
- LINEAR IC's:

709	Popular OP AMP (DIP/TO-5)	.39
723	Adjustable Voltage Regulator (DIP/TO-5)	.75
741	Freq. Compensated OP AMP (DIP/TO-5/MINI-DIP)	.45
747	Dual 741 OP AMP (DIP)	.95
LM305	Positive Voltage Regulator (TO-5)	1.25
MC1458	Dual 741 OP AMP (MINI-DIP)	.95
Assorted Linears-741/709/723, etc. (4)		2.00
- FET's

N-CHANNEL (LOW-NOISE):		
2N4416	TYPE RF Amplifier to 450 MHz (TO-72)	2/\$1.00
2N5486	TYPE RF Amp to 450 MHz (plastic TO-106)	3/\$1.00
2N5163	TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
2N4091	TYPE RF Amp & Switch (TO-106)	3/\$1.00
Assort. RF & GP FET's, 2N5163, 2N5486, etc. (8)		\$2.00
P-CHANNEL		
2N4360	TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
- TRANSISTORS

NPN:		
2N3563	TYPE RF Amp & OSC to 1GHz (TO-106)	6/\$1.00
2N3565	TYPE Gen. Purpose High Gain (TO-106)	6/\$1.00
2N3904	TYPE GP Amp & Sw to 100mA (TO-92)	6/\$1.00
Assort. NPN GP TYPES, 2N3565, 2N3641, etc. (15)		\$2.00
PNP:		
2N3638	TYPE Gen. Purpose Amp & Sw (TO-106)	4/\$1.00
- DIODES:

1N914	TYPE Gen. Purpose 100V/10mA	10/\$1.00
1N3600	TYPE Hi Speed SW 75V/200mA	6/\$1.00
1N4608	TYPE GP & SW 80V/400mA	6/\$1.00
RECTIFIER Stud Type 400V/5A		2/\$1.00
1N749	ZENER 4.3 Volt 400mW	4/\$1.00
1N753A	ZENER 6.2 Volt 400mW	4/\$1.00
1N755A	ZENER 7.5 Volt 400mW	4/\$1.00
1N757A	ZENER 9.1 Volt 400mW	4/\$1.00
1N758A	ZENER 10 Volt 400mW	4/\$1.00
1N965B	ZENER 15 Volt 400mW	4/\$1.00
1N968B	ZENER 20 Volt 400mW	4/\$1.00
VARACTOR 1-3W @ 432MHz 2-10pF		\$1.00

*MAIL NOW! With every order of \$10 or more, postmarked prior to 6/30/74, FREE IC of our choice included.

ORDER TODAY—All items subject to prior sale and prices subject to change without notice.

WRITE FOR FREE CATALOG offering hundreds of semi-conductors not listed here. Send 10¢ stamp.

TERMS: All orders prepaid. We pay postage. \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax.

ADVA

ELECTRONICS

BOX 4181-C, REDWOOD CITY, CA 94062
Tel. (415) 851-0455

WEIRNU IN ELECTRONICS AND CHARGING FAIR PRICES FOR GOOD DEVICES

Win up to \$500.00 in cash prizes. —we just bought 80,000 prime house marked devices at a low low price. But OOPS! Somebody goofed. We can't figure out what they are! All we know is that they are Fairchild ECL & that all of them are good. Sooooo we're gonna put all of you hams to work out there with an offer you can't refuse. \$100.00 to the first person sending us information leading to the arrest of our dismay; \$1 per type entry fee covers postage, handling & 5 units to experiment on. type A, type B, type C, type D, type E, try one type! try all types! but go go GOOO—

7400 series ^b Price Schedule

00	.30	41	1.50	95	1.25	165	3.00
01	.30	42	1.25	96	1.25	166	2.50
02	.30	45	1.25	100	9.99	170	4.25
03	.30	46	2.00	107	.60	173	2.50
04	.30	47	2.00	121	.75	174	3.25
05	.30	48	2.00	122	.90	175	3.50
06	.50	50	.30	123	1.25	176	1.00
07	.70	51	.30	125	.75	177	1.00
08	.30	53	.30	126	.75	180	1.25
09	.30	54	.30	132	4.25	181	6.25
10	.30	60	.30	141	4.50	182	1.25
11	.30	70	.40	145	1.75	184	3.25
12	.70	72	.45	150	3.25	185	3.50
13	1.00	73	.60	151	1.25	190	4.50
16	.70	74	.60	152	4.50	191	5.00
17	.70	75	1.50	153	1.50	192	2.25
20	.30	76	.60	154	2.00	193	2.50
23	.50	83	1.25	155	1.50	194	2.50
25	.50	85	1.50	156	1.50	195	1.25
26	.50	86	.50	157	1.50	196	2.50
27	.80	88	5.00	158	4.50	197	2.50
30	.30	89	4.00	160	2.00	198	4.25
32	.40	90	1.50	161	2.00	199	4.25
37	.50	91	1.50	162	2.00		
38	.60	92	1.25	163	2.00		
40	.30	93	1.25	164	3.00		

Linear Price Schedule

National*

LM301	T05 or mini	.50
LM302	T05	1.00
LM304	T05	1.50
LM305	T05	1.50
LM307	T05 or mini	.50
LM308	T05	1.25
LM309	T03	2.00
LM311	T05 or mini	1.25
LM320	-5.2V T03	2.25
	-12V T03	2.75
	-15V T03	2.25
LM380	Dip	2.00
LM381	Dip	2.50
LM382	Dip	2.50
LM3900	Dip	1.50
LM709	T05 or Dip	.50
LM710	Dip	.50
LM711	Dip	.50
LM723	T05 or Dip	1.00
LM741	T05 or Dip	.50
LM747	T05 or Dip	1.00

*or equivalent

Dual peripheral drivers

75450	.80
75451	.60
75452	.60
75453	.60
75454	1.00

Memories

MM5260	9.25
1101	3.25
1103 ^a	8.75
7489	4.00
8223	7.50
8225	4.25
74200	12.00

Signetics*

550	Dip	1.25
555	mini	1.50
560	Dip	3.00
561	Dip	3.00
562	Dip	3.00
565	T05 or Dip	3.25
566	mini	3.25
567	mini	3.25

74H00 series

H00	.50
H01	.60
H04	.60
H05	.80
H08	.60
H10	.60
H11	.60
H20	.60
H30	.60
H40	.60
H50	.60
H51	.60
H72	.80
H73	.90
H74	.90
H76	.90
H78	.90
H106	2.00

74L00 series

L00	.50
L02	.50
L03	.50
L04	.50
L06	.90
L10	.50
L20	.50
L30	.50
L51	.50
L71	.75
L73	.80
L74	.90
L78	.90
L85	2.00
L86	.75
L90	2.00
L93	2.00
L95	1.75

74S00 series

S00	.80
S03	.80
S04	.80
S10	.80
S11	.80
S15	1.00
S16	1.00
S20	.80
S22	1.00
S64	1.00
S65	1.00
S74	2.00
S153	3.00

odd devices at low low prices . . .

8160	6-bit comparator	3.00
85L12	LP gated dual J-K ff	1.00
8613	quad gated D ff	1.00
86L93	pin forpin 7493	1.00
8810	quad TTL/MOS interface gate	.75
8812	14V open collector hex inverter	.75
8833	line driver	1.00
8853	dual retrigger. reset one shot	2.00
8880	Sperry decoder/driver	1.50
SP380	bus receiver	.50

(spec sheets free with order)

Notes . . .

a. even the factory can't test the 1103 properly, so, if you get a bad one please bear with us, send it back for immediate replacement.

b. 7400 series parts available at 25% of list untested. No guarantee! 10 pcs/type min. order.

Request Orders

We sell many items not listed, & can obtain many not kept in stock. If you need any odd or hard to find ICs, odds are we can get them. Please write.

—spec sheets .25¢ each
 —our complete catalog \$2.00, free with order of \$100.
 —Calif residents add 6% sales tax
 —add \$1 postage on orders under \$10

WEIRNU
 Box 1307
 Colton, CA 92324
 ph # (714) 882-5387
 (ask for FANNIE!)

Satisfaction guaranteed. All items except as noted have been precision tested by the latest equipment. We're so certain you'll keep coming back once you've tried our quality that we make this amazing first order offer: BUY \$100.00 worth of merchandise, choose \$100.00 worth free.

could be used just as well by placing the capacitor or standoff insulators. The motor shaft is connected to the capacitor by an insulated coupling which fortunately mated the 1/4" capacitor shaft and the approximate 1/8" motor shaft. Actually, a small piece of dowel with appropriate size holes drilled in each end and the use of epoxy cement will work just as well. The motor used was a "junk box" item which works on 12V dc and with internal gearing, and the friction provided by the capacitor results in a very slow tuning rate. Surplus and hobbyist outlets are sources for suitable motors.

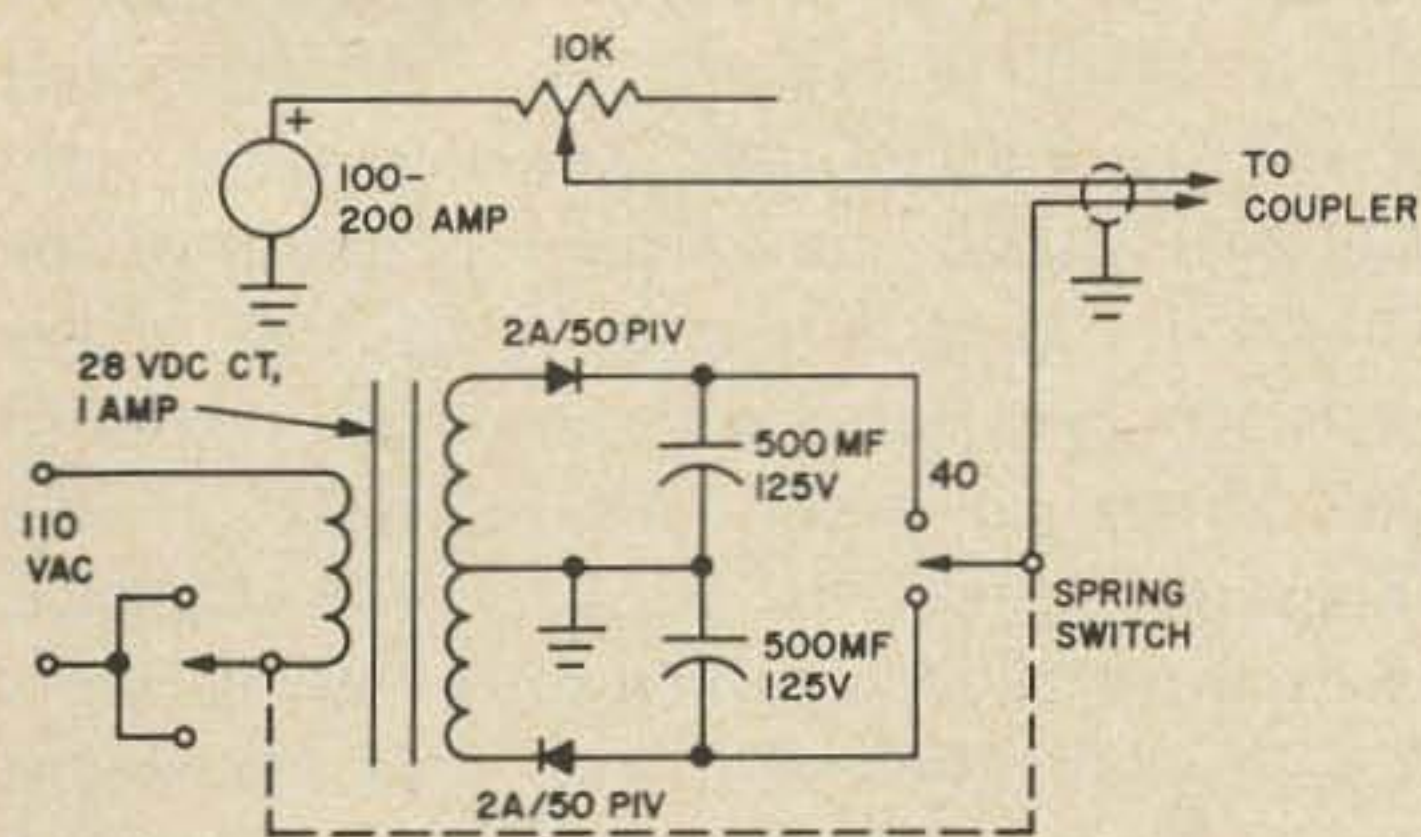


Fig. 4. Diagram of indicator/power supply unit. Batteries may also be used to power most small dc motors.

Almost any intermittent duty 12–24V dc type that has been geared down to 50 rpm or less will work.

The rotor plate on the capacitor nearest the back frame of the capacitor is bent slightly, as shown in Fig. 3, to form a sliding switch contact with one end of a chassis feed-through insulator mounted on the capacitor back-frame. A miniature chassis type feed-through such as USECO no. 1432 is used. Any small piece of plastic may be used as a stop to prevent further rotation of the rotor plates once the switch is engaged by placing it across the stator plates on the same side as the switch (see Fig. 3). Epoxy cement should be used to secure the top.

The reflected power sensor is constructed by carefully slitting the jacket away for about 8–12" at the end of the coaxial cable to be connected to the link. A length of #20 enamelled wire is then manipulated under the shield, the ends being connected as shown in Fig. 2. The jacket is then replaced

SCELBI COMPUTER CONSULTING, INC.

ANNOUNCES

THE TOTALLY NEW AND THE VERY FIRST

MINI-COMPUTER

DESIGNED FOR THE ELECTRONIC/COMPUTER HOBBYIST!

Kit prices for the new SCELBI-8H mini-computer start as low as \$440.00!

Write or phone for detailed literature.

SCELBI COMPUTER CONSULTING, INC.

125 Edgefield Avenue
Milford, Connecticut 06460
Phone: (203) 874-1573

WANTED

MILITARY SURPLUS ELECTRONIC EQUIPMENT. WE NEED RT-750/ARC-34C, RT-742/ARC-51BX, RT-698/ARC-102, RT-823/ARC-131, RT-857/ARC-134, RT-859/APX-72, 618T, GRC-106, VRC-12, VRC-24, URC-9, ANTENNA COUPLERS CU-1658A, CU-1669A, 490T-1, C-6287/ARC-51BX CONTROL BOXES, ALSO EQUIPMENT WITH APM, ARM, ASM AND USM PREFIXES. TOP DOLLAR PAID OR TRADE FOR NEW AMATEUR GEAR. WRITE OR PHONE (704) 524-7519, BILL SLEP, SLEP ELECTRONICS COMPANY, P.O. BOX 100, OTTO, NORTH CAROLINA 28763.

FM Schematic Digest

A COLLECTION OF

MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes covering 1947-1960

136 pages 11½" x 17" ppd \$6.50

S. Wolf

Box 535

Lexington, MA 02173

— WE GOT 'EM —

CLEGG, COLLINS, DRAKE, SWAN, YAESU, TEN-TEC, and many more in stock. See us first for quick, courteous service. Est. 1928 — MASTERCHARGE — BANKAMERICARD W4WL

FRECK RADIO & SUPPLY CO.

40 Biltmore Avenue

P.O. Box 7287

Asheville NC 28807

Telephone: 704-254-9551

and the length of cable coiled together, if necessary, for compactness to fit the enclosure. The few components for the sensor are assembled on a terminal strip.

Indicator Unit

The indicator units contain only a microammeter and potentiometer as a reflected power indicator and a dual polarity source for the tuning motor. Batteries may be used for the latter function, although a small ac supply is shown in Fig. 4. Some overvoltage from the supply must be available in order to account for the drop in the control cable.

Adjustment and Operation

As was mentioned before, one should be sure first that a coupler operates properly manually before an attempt is made to remotely control the unit. In the case of the unit described, the numbers of turns in the

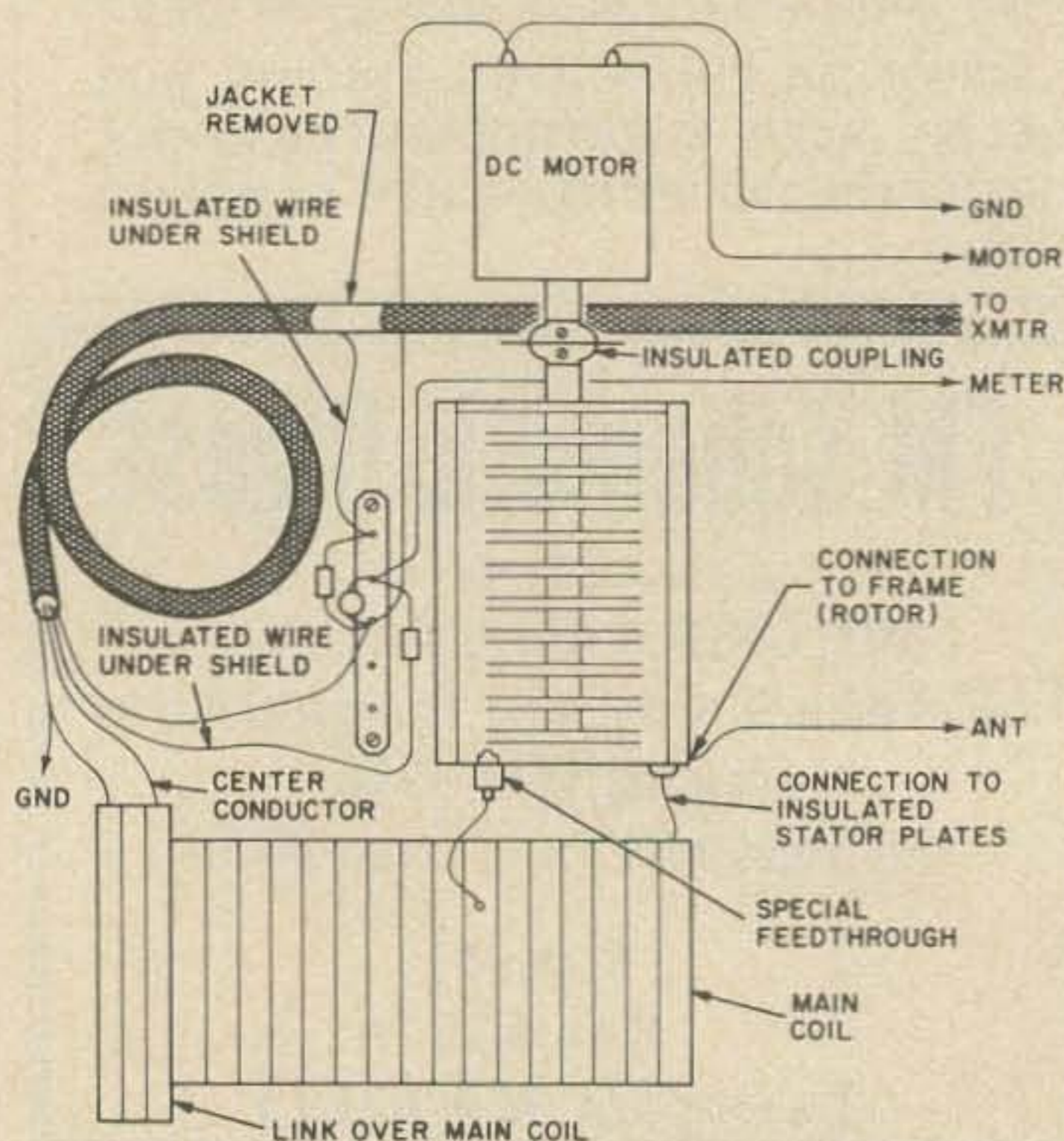


Fig. 5. Sketch of parts layout for dual band coupler.

main coil was established by trimming the coil on 80 meters and checking the frequency range of operation possible and the variable capacitor. On 40 meters, the capacitor switch was engaged and the coil top on the main coil established. These tests were done with a conventional SWR connected in the transmission line immediately before the coupler which was mounted in its operating position. Simultaneously, operation of the reflected power sensor was checked to see

that minimum output from it corresponded to minimum reflected power indication on the conventional SWR meter. Operation of the motor should be checked with a length of cable equal to that actually used for the control cable. This is necessary to insure that the voltage drop in the cable is not enough to affect motor torque.

Operation of the unit is not complicated, but it does require a little practice since its simple design does not provide for automatic motor cutoff or signalling of motor position. By observing the speed of motor rotation, one can learn to anticipate when a complete revolution has been made. One position of the control switch on the indicator unit should be marked "40" (or something similar) to indicate one extreme position of the capacitor. Then if one loses an idea of the capacitor position, one can always return to this reference point. Alternatively, if one doesn't require the idea of the capacitor switch for bandswitching purposes, it can be used to activate a pilot lamp over the control line. This might in some cases prevent holding the motor against its stop for a prolonged period and drawing excessive current which could possibly damage the motor. A motor with an internal clutch arrangement can, of course, also be used to prevent this possibility.

In general, there is no great problem when tuning an antenna with a transmitter since the reflected power indication at resonance is clear. This is not the case if one uses an antenna only for receiving. Under fading conditions, it is often very difficult to determine proper resonance of a remote tuner by observing a received signal level.

Summary

The coupler shown was used with low power equipment — up to about 100/150 watts. For higher power levels, an increase in the coil wire size, the insulation path between the motor and capacitor shafts and the spacing of the capacitor plates will probably be necessary. The latter, meaning a larger capacitor, will probably also require a heavier motor. Nonetheless, the basic construction can be modified as necessary for any power level.

...W2EEY

A PRACTICAL GROUND SYSTEM FOR 160

Ground systems for 160 may be anything from a simple cold water pipe "connection" to an elaborate system of buried copper radials, second in performance only to a salt water marsh. For obvious reasons, such an ideal ground is impractical for most of us, so this poses the question of how good can a "make do" ground system really be? This problem came up while experimenting with a vertical antenna for 160, which is a quarter wave radiator normally working against ground.

First we needed something with which to compare our ground system. Since we had no "ideal" ground system available, it was decided to compare the antenna current when working against ground to the current obtained when working the antenna against a single wire counterpoise. The radiation pattern was of no concern — only the antenna current was measured at the same point in the antenna for both conditions.

First the antenna was grid dipped, using a cold water pipe ground. The resonant frequency was noted and a single horizontal wire was adjusted in length until the antenna resonated at the same frequency as with the ground connection; in the writer's case, 1990 kHz.

The transmitter was next loaded into the antenna first using the counterpoise and

then using the cold water pipe with the following results:

	ANT. I
COUNTERPOISE	1.3A
WATER PIPE GROUND	0.5A

Care was taken to keep the final plate load the same for both conditions. From the above it is obvious that our ground is wasting a lot of rf.

A multiple ground system was tried next. This consisted of three 8 foot ground rods spaced approximately ten feet apart and two cold water pipe connections also spaced ten feet apart. The results were as follows:

GROUND SYSTEM	ANT. I
1 water pipe	0.5A
2 water pipes	0.7A
each ground rod	0.6A
2 ground rods	0.85A
3 ground rods	0.95A
combining grounds	1.15A

This compares very favorably with the antenna current obtained with the counterpoise and it can be assumed that the ground system is just about as good as the counterpoise wire as far as losses are concerned.

The soil at this location is largely decomposed granite — not particularly low resistance without benefit of rock salt or copper sulphate treatment. After the above experiment, we decided against treating the soil and, much to our surprise, the antenna current varied only about 10% from wet to dry seasons. The two ground lead configurations used are shown in Fig. 1. As a matter of passing interest, configuration (a) resonated the antenna 75 kHz lower in frequency than configuration (b). Configuration (b) was finally decided upon at this station, since it was assumed that less "antenna effect" was present because of the higher resonant frequency.

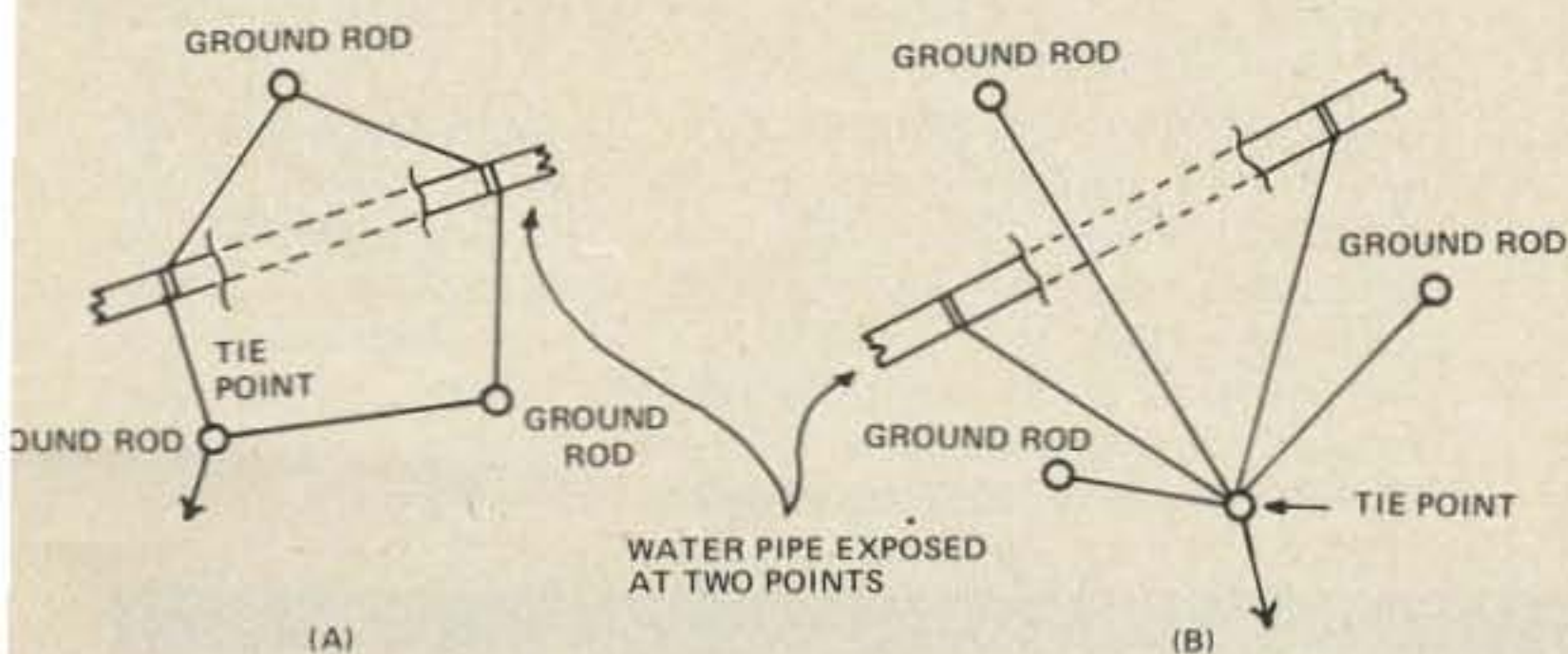


Fig. 1. Ground lead configurations. With a given antenna, (a) results in a lower frequency than (b).

...W6FPO

TWO GREATS for GREAT TWO METERS

FROM ICOM.....of course



IC-21...24 channel capability, with 7 channels supplied. It's MOSFET front end provides better than .4uv sensitivity at 20 db quieting. 5 helical filters virtually eliminate intermodulation. Built in AC and DC power supplies. Modular construction, of course. Many other features make the **IC-21** a great two meter transceiver.

IC-230...67 channels with 30KHz separation for simplex operation from 146.01 to 147.99MHz, synthesized with INOUE'S unique Phase Locked Loop (PLL) system. One switch puts you up or down 600 KHz for use with repeaters. Modular construction makes service a snap, if it's ever needed.

Helical filters, MOSFET front end, and an Automatic Protection Circuit, for the final transistors, are only some of the outstanding features of the **IC-230**. It's the great synthesized two meter radio today, and will still be tomorrow!

The **IC-3PA** is a regulated DC power supply for all the INOUE mobile transceivers. Use it with your **IC-230** for base operation. It's completely regulated, and gives you an indication of it's operating condition; normal, low voltage, excessive current, or if the protection circuit is working. These are shown through the use of eye catching indicator lamps. There is also a built in speaker in the cabinet.



ICOM

INOUE COMM.EQUIP.CORP.
3-8 Kamikurazukuri-cho
Higashi Sumiyoshi-ku
Osaka, Japan

ICOM WEST, INC.
Suite 232-Bldg. II
300·120th Ave. N.E.
Bellevue, Wash, 98005
(206)454-2470

Distributed by:

ICOM EAST
Div ACS, Inc.
Box 331
Richardson, Tex. 75080
(214)235-0479

Get the entire Inoue ICOM family at one of the dealers listed below:

ALABAMA

Wolfe Electronics
Box 358
Foley, AL. 36530

ARKANSAS

Gavin Electronic
516 Ridgeway
Little Rock, ARK. 72205

ARIZONA

Ell Dee Enterprises
12612 N. 28th Drive
Suite 3
Phoenix, AZ. 85029

CALIFORNIA

Buddy Sales
Reseda, CA.

Buddy Sales
Ventura, CA.

CDS Electronics & Hobbies Unltd.
235 Mitchell Drive
Atwater, CA. 95301

Communications Headquarters, Inc.
930 W. Washington Street
San Diego, CA. 92103

Gary Radio, Inc.
8199 Clairemont Mesa Blvd.
San Diego, CA. 92111

Ham Radio Outlet
Burlingame, CA.

Henry Radio Company
11240 W. Olympic Blvd.
Los Angeles, CA. 90064

Henry Radio Company
931 N. Euclid Avenue
Anaheim, CA. 92801

M-Tron
Oakland, CA.

Quement Electronics
San Jose, CA.

R. Donald Hall & Son
Riverside, CA.

Selectronics
1709 Markston Road
Sacramento, CA. 95825

Sequoia Stereo
773-8th Street
Arcadia, CA. 95521

Sichel Equipment Co.
245 E. Harris Avenue
S. San Francisco, CA. 94080

Teletronics
San Jose, CA.

Webster Radio
Fresno, CA.

Westcom Engineering Co.
Box 1020
Escondido, CA. 92025

COLORADO

C.W. Electronics Sales Co.
1401 Blake Street
Denver, CO. 80202

LEC Electronics
P.O. Box 7515
Pueblo West, CO. 81007

CONNECTICUT

Marcus Communications
134 E. Center Street
Manchester, CN. 06040

FLORIDA

Amateur Electronic Supply
621 Commonwealth
Orlando, FL. 32803

Amateur Radio Center, Inc.
2805 N.E. 2nd Avenue
Miami, FL. 33137

Amateur Wholesale Electronics
8817 S.W. 129th Terrace
Miami, FL. 33165

Tony's Radio
1159 N.W. 46th Avenue
Lauderhill, FL. 33313

GEORGIA

Bright Electronics
Box 256
Loganville, GA. 30249

IDAHO

Ross Distributing Co.
Preston, ID.

United Electronics Wholesale
Twin Falls, ID.

ILLINOIS

Erickson Communications
3501 Jarvis
Skokie, ILL. 60076

Klaus Radio, Inc.
8400 N. Pioneer Parkway
Peoria, ILL. 61614

Spectronics, Inc.
1009 Garfield
Oak Park, ILL. 60304

INDIANA

Hoosier Electronics, Inc.
Rt. 25, Box 403
Terre Haute, IND. 46608

Story Electronic
441 Walnut
Wabash, IND. 46992

LOUISIANA

Preston Electronics
611 Highland Drive
Houma, LA. 70360

MAINE

Yorks Radio
Court & Main
Houlton, Maine 04730

MARYLAND

CQM Electronics
900 Crain Hwy. SW
Glen Burnie, MD. 21061

MICHIGAN

Audio Land
36633 S. Gratiot
Mt. Clemens, MI. 48043

Electronic Distributors, Inc.
1960 Peck Street
Muskegon, MI. 49441

MISSOURI

Ham Radio Center
8342 Olive Street
St. Louis, MO. 63132

MONTANA

Conley Radio Supply
Billings, MT. 59101

Electric City Radio Supply
Great Falls, MT.

NEVADA

Wilson Electronics
Henderson, NV. 89105

NEW HAMPSHIRE

Craig Radio
29 Sherburne Avenue
Portsmouth, N.H. 03801

NEW MEXICO

Robert Foster
Box 198 - Star Rt.
Tijeras, NM. 87059

NEW YORK

Adirondak Radio Supply
185 W. Main Street
Amsterdam, N.Y. 12010

Barry Electronics
512 Broadway
New York, N.Y. 10012

OHIO

Amateur Electronic Supply
17929 Euclid
Cleveland, OH. 44112

Queen City Electronics
1583 McMakin Avenue
Cincinnati, OH. 45231

OREGON

Portland Radio Supply
Portland, OR. 97205

PENNSYLVANIA

Electronic Exchange
311 E. Walnut Street
N. Wales, PA. 19454

Hamtronics
4033 Brownsville Road
Trevose, PA. 19047

Kass Electronics, Inc.
2502 Township Road
Drexel Hill, PA. 19026

SOUTH DAKOTA

Accessory Specialist
Rt.1, Box 13
Rapid City, S.D. 57701

Burghardt Amateur Center
P.O. Box 73
Watertown, S.D. 57201

TEXAS

Bellaire Electronic Supply
5204 Bellaire Blvd.
Bellaire, TX. 77401

Douglas Electronics
1118 South Staples
Corpus Christi, TX. 78404

Electronic Center, Inc.
2929 N. Haskell
Dallas, TX. 75204

Howard Radio
4235 N. First
Abilene, TX. 79603

Juge Electronics
3850 S. Frwy.
Ft. Worth, TX. 76110

Texas Technical Products
Rt. 2 Box 324-D
San Antonio, TX. 78228

Trimble Electronics
1918 Mary Ellen
Pampa, TX. 79065

Yucca Associates
7606 Boeing Suite E
El Paso, TX. 79925

UTAH

Utah FM Sales
Salt Lake City, UT. 84117

VIRGINIA

Northern Va. Communications
729 N. Edison
Arlington, VA. 22203

Williams Radio Sales
113 Grandin Ct.
Danville, VA. 24541

WASHINGTON

ABC Communications
Seattle, WA. 98155

ABC Communications
Everett, WA. 98200

Columbia Communications, Inc.
Kennewick, WA.

GDS Electronics
Spokane, WA. 99208

HCI Electronics, Inc.
Spokane, WA.

Progress Electronics
Longview, WA. 98632

Radio Supply Co.
Seattle, WA.

Seattle Radio Supply
Seattle, WA.

WISCONSIN

Amateur Electronic Supply
4828 Fond Du Lac Avenue
Milwaukee, WI. 53216

WYOMING

Rule Communications
Laramie, WY.

*IF YOUR DEALER DOESN'T STOCK ICOM EQUIPMENT,
LET THE ICOM DISTRIBUTOR FOR YOUR REGION KNOW.*

2 METER FM HEADQUARTERS

Only STANDARD
 sells more STANDARDS
 than ERICKSON!

and here's
 ANOTHER
 ERICKSON
 SPECIAL

SRC-826 MA



A better BEST BUY than ever

OUR DEAL:

826 MA list	\$398.00
+ 16 extra xtals	80.00
Package list price	\$478.00
You pay only	\$359.00
YOU'VE SAVED	\$119.00

YOU GET Standard's 826MA, the best 12-channel 10-watt solid state rig on the market, factory set up on four channels plus crystal coupons for eight more channels (16 of Standard's lifetime Astropoint crystals!) of your choice; with helical-resonator front end receiver, built in provision for tone-coded squelch, rear panel test point/monitor/control sockets — all in one compact, reliable package — at a GIANT \$119 ERICKSON saving !!

Shipping prepaid for cashier's check or MO.

Handheld Special

SRC-146A with:

- Deluxe basecharger
- "Stubby" antenna
- Leather case
- Ni-cads
- 94/94, 34/94 and one other channel of your choice

List Price	\$369.00
Our Price	\$319.00
YOU SAVE	\$50.00 !!

Another Best Buy from Erickson



Make ERICKSON your headquarters for all your FM needs

SEND QSL FOR COMPLETE SPECIFICATIONS

ERICKSON COMMUNICATIONS

3501 W. Jarvis, Skokie, IL 60076 (312) 677-2161

WIDE-RANGE ANTENNA TUNER

George Cousins VE1TG
R.R. 2 Box 18
Lower Sackville, N.S., Canada

Most modern ham rigs are designed with single-ended outputs for direct connection to coax-fed antennas, but there are still many cases where a good wide-range antenna tuner can be very valuable. The most obvious are:

1. To couple the transmitter to any one of the wide variety of antennas which require high impedance feedlines, such as V-beams, rhombics, Lazy H's, Zepps, folded dipoles, etc. This is especially important when the QTH will not allow the erection of several antennas, and the use of a wire antenna and tuner will permit multiband operation.
2. In moderate to severe cases of TVI, where the high harmonic attenuation of the tuner will be of considerable assistance.
3. To permit optimum coupling between the antenna feedline and the

receiver, an advantage which seems to get little attention.

The tuner can be built in a variety of ways, using circuits which have proved to be reliable over the years. However, to be as useful as possible, the tuner should be capable of either series or parallel tuning, and should be continuously useful over the entire 3-30 MHz range. All controls should be operated from the front panel, and no bandswitching, coil changing, or coil tapping should be required. The tuner to be described satisfies these requirements, and is also a neat, good-looking addition to any station. This particular model was built by Bill Shearman, VE1AX, for use of both amateur and commercial marine frequencies.

The general circuit arrangement is known as a "Z-match" and has been well

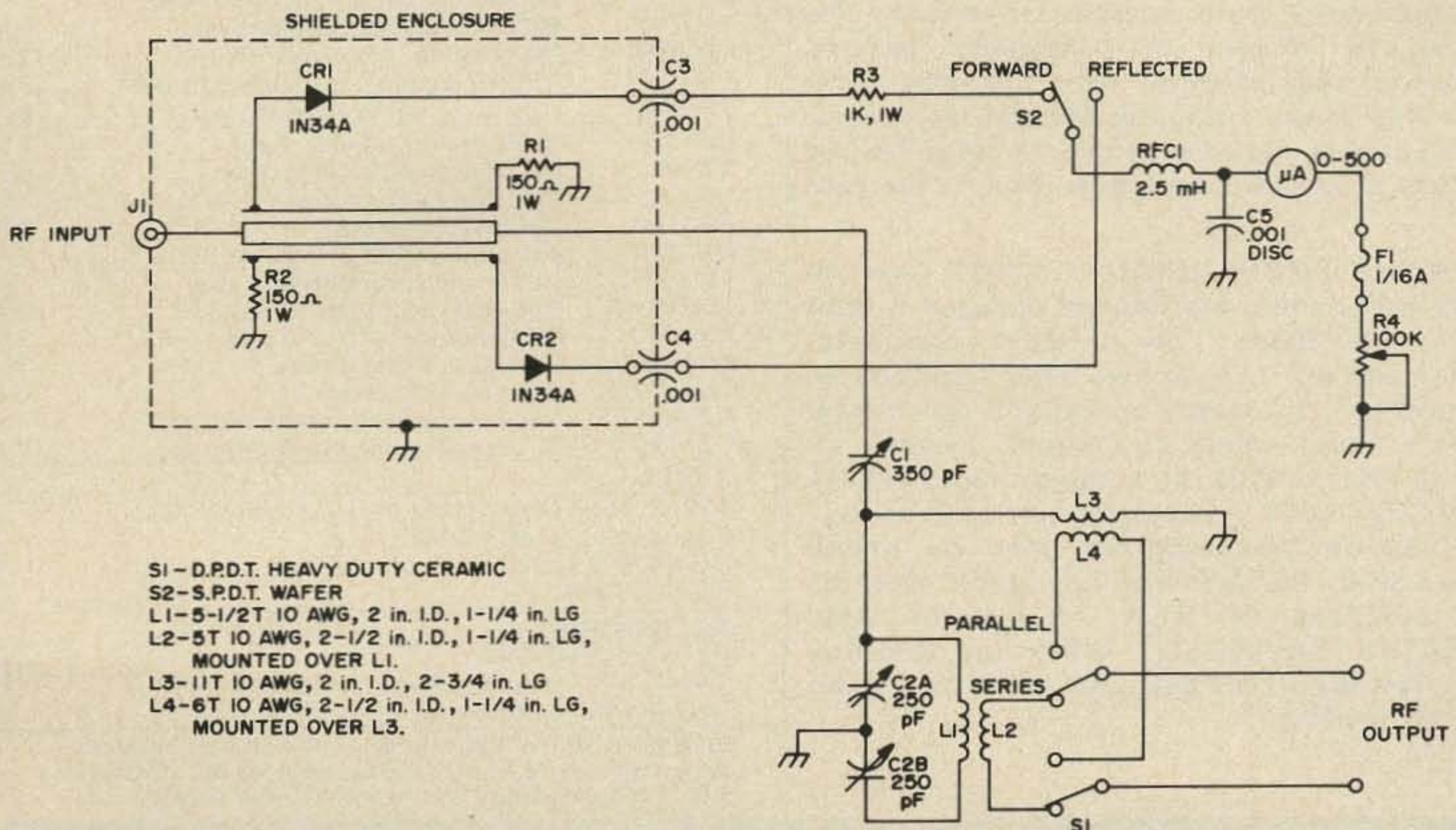


Fig. 1. Overall schematic of the tuner.

save \$50 to \$500

on a "design-it-yourself" antenna package from Henry Radio. Simply put together the package you want . . . consisting of an antenna, a rotator, a tower, 100 feet of rotator control cable and 100 feet of coax cable. We will quote you a money saving price that's sure to please. Thousands have benefited from this program since it was started five years ago. You can also!



For many years Henry Radio has been providing a beam-antenna tower program for amateurs who wanted an efficient but economical package. Thousands have benefited from this offer in the past. Now Henry Radio has restyled and updated its program to allow the amateur to design his own package at savings even greater than in the past!

WHY BUY FROM HENRY RADIO? Over 40 years experience. No finance charges if paid with-in 90 days. Low interest contracts- 8%/yr add on (14% annual rate) - as long as 24 months 10% down or trade-in down payments. Good used equipment. Nearly all makes and models of amateur radio equipment. Our used equipment carries a 15 day trial, 90 day warranty and may be traded back within 90 days for full credit towards the purchase of NEW equipment. Also **GREATER SAVINGS!!!** Write for information. We export all over the world so inquiries are invited.

ANTENNAS		
	TH2 Mk3 . . . 2 element, 3-band beam	109.95
	TH3 Jr. . . . 3 element, 3-band beam	119.95
HYGAIN	DB10-15A . . 10 and 15 meter beam	129.95
	HyQuad . . . 2 element, 3-band Quad	169.95
	203BA 3 element, 20 meter beam	149.95
	TH3 Mk3 . . . 3 element, 3-band beam	169.95
	204BA 4 element, 20 meter beam	169.95
	TH6 DXX . . . 6 element, 3-band beam	199.95
MINI	B-24 2 element, 4-band beam	62.95
	RK-3 Third element for B-24	36.95
	HQ-1 Hybrid 4-band Quad	79.95
MOSLEY	TA-32 Jr . . . 2 element, 3-band, Low power	73.15
	TA-33 Jr . . . 3 element, 3-band, Low power	115.30
	TA-32 2 element, 3-band beam	103.00
	MP-33 3 element, 3-band, medium power	111.95
	TA-33 3 element, 3-band beam	164.95
	CL-33 3 element, 3-band beam	176.90
	TA-36 6 element, 3-band beam	213.10
	CL-36 6 element, 3-band beam	216.45
	CL-20 5 element, 20 meter beam	306.00
SWAN	TB-2A 2 element, 3-band beam	119.95
	TB-3HA Heavy duty TB-3A	159.95
	TB-4HA Heavy duty, 4 element, 3-band beam	189.95
	MB-40H 2 element, 40 meter beam	179.95
WILSON	M510 5 element, 10 meter beam	130.00
	DB-32 3E/20M, 2E/15M beam	157.00
	M-420 4 element, 20 meter beam	187.00
	M-615 6 element, 15 meter beam	163.00
	M-240 2 element, 40 meter beam	297.00
	DB-65 6E/15M, 5E/20M beam	257.00
	DB-54 5E/20M, 4E/15M beam	299.00
	M-620 6 element, 20 meter beam	387.00
	DB-52 5E/20M, 2E/40M beam	520.00
ROTATORS		
	CDR AR-22R Rotator	44.95
	CDR CD-44 Rotator	89.95
	CDR HAM-II Rotator	149.95
	HyGain 400 Rotator	229.95
TOWERS		
	Free Standing Aluminum Towers	
ASCOM	7-40 7 square foot load, 40 foot tower	252.00
	7-50 7 square foot load, 50 foot tower	362.00
	9-60 9 square foot load, 60 foot tower	561.00
	12-40 12 square foot load, 40 foot tower	332.00
	15-50 15 square foot load, 50 foot tower	532.00
TRIEX	MW-35 35' Self supporting, crank-up tower	224.00
	W-51 51' free standing, crank-up tower	591.00
	TM-240 40' crank-up sky needle tower	672.00
	TM-358 58' crank-up sky needle tower	1186.00
	LM-470D . . . 70' Self supporting, crank-up tower	2297.50
	TM-370 70' motorized sky needle tower	2848.00
TRISTAO	MM-40 40' crank-up tubular tower	219.95
	MB-10 Optional free standing base	55.95
	MF-50 Optional raising fixture	69.95
	MRB-80 Optional rotor base	129.95
	MA-490 49' crank-up tubular tower	411.10
	MAF-40 Optional raising fixture	134.95
	MARB-40 . . . Optional rotor base	281.80
	MA-660 66' crank-up tubular tower	1218.95
	MAF-60 Optional raising fixture	159.95
	MARB-66 . . . Optional rotor base	545.95
	CZ-454-FS . . 54' free standing crank-up tower	534.95
	CZ-471-FS . . 71' free standing crank-up tower	1043.95
CABLE		
	4 conductor rotator cable (AR-22R only)10/ft
	8 conductor rotator cable25/ft
	RG-58 A/U Coax07/ft
	RG-8/U Coax25/ft
ACCESSORIES		
	HyGain BN-86 Balun	15.95
	Triex TB-2 Thrust Bearing	24.75
	Unadilla W2AU Balun	12.95

Literature on the above items is available on request. All prices will be quoted FOB Los Angeles, California. All prices are subject to change without notice.

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
 931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
 Butler, Missouri 64730 816/679-3127

known for many years. Two coils are used in conjunction with a split-stator capacitor to cover two frequency ranges at the same time. This allows a smooth transition from series to parallel tuning and no bandswitch is required. An SWR bridge is incorporated, and is in the input line at all times, making tuneup a simple matter.

The tuner is built on a 10 x 17 x 3 in. chassis, with an 8½ x 19 in. front panel. Depending upon the power range of the station transmitter, smaller components could be used and thus reduce the size of the chassis. However, the unit shown will safely handle more than the legal limit on all bands and modes.

A close study of the photos and schematics will reveal most of the construction features. The input coaxial line is first routed through the small shielded enclosure used for the rf components of the SWR bridge. This will be described later. From this enclosure, the line is connected to the variable coupling capacitor C1, which must be insulated from the chassis and panel. A small vernier dial drives this capacitor through an insulated coupling and provides smooth control. (To aid in setting the tuner to the proper tuning point during rapid band changing, calibrated vernier dials are used on both capacitors along with a tuning chart on the front panel.)

The main tuning capacitor, C2A and C2B, is mounted parallel to C1, but *not* insulated from the chassis. A heavy-duty, two-pole, two-position ceramic switch (S1) is mounted on the front panel directly under the two large feedthrough insulators. The two coils are mounted at right angles to each other between C2 and S1 and are supported by their own leads. Commercial air-wound coil stock was used in this model, which made this method of mounting quite feasible. However, homebrew coils should be wound on ceramic forms and firmly mounted.

The SWR bridge is built in two sections, one containing the rf pickup, diodes, and matching resistors, and enclosed in the metal shell at the rear of the chassis, underneath. A small piece of terminal board holds the components associated

with the meter, and the meter itself is mounted on the front panel, flanked by the sensitivity control R4 and the FORWARD-REFLECTED switch (S2).

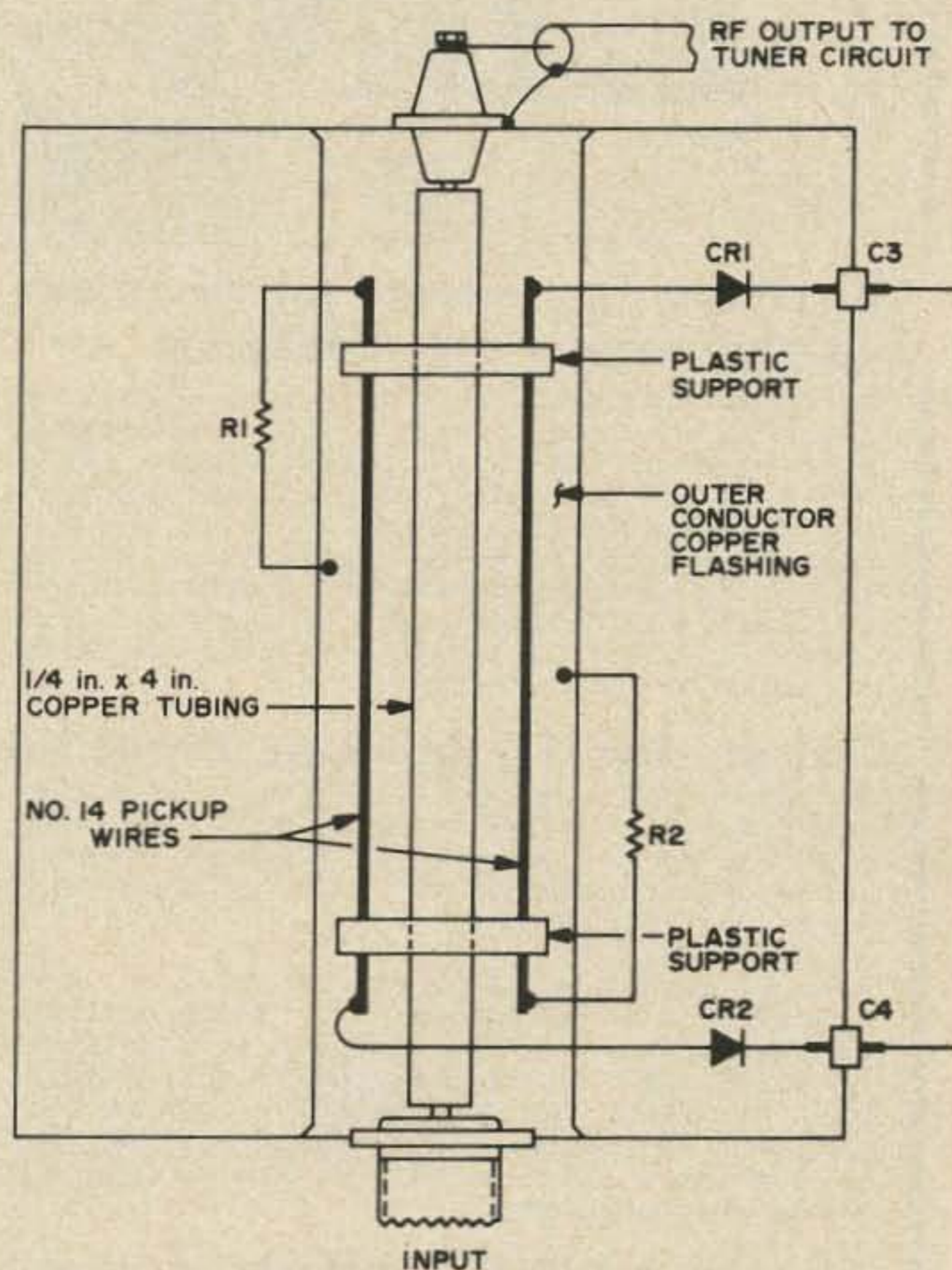


Fig. 2. Construction of the SWR bridge. See text for details.

The construction of the rf section of the bridge can be seen from Fig. 2. The inner line conductor is a 4 in. length of ¼ in. copper tubing. The outer line conductor is a flat piece of copper flashing mounted under the tubing and secured to small mounting bolts at each end of the enclosure. Small square pieces of Plexiglas are used to separate the two conductors, with the tubing being inserted in holes drilled in the center of the squares. Small holes are drilled in the outer edges of the squares to hold the two pieces of 14-gage copper wire used for coupling the rf to the diodes. A matching resistor is connected to one end of each pickup wire, and a diode is connected to the opposite end. The resistors are connected to the outer copper conductor, but the diodes are connected to the two small feedthrough capacitors mounted on the wall of the enclosure. Small shielded wires run from these capacitors to the terminal board, then via

NEW AND DIFFERENT!!



The all new T_{doc} manual for electronics experimenters and hobbyists ---

More than two years in the making, T_{doc} has gathered the most practical and usable data from industry, the U. S. Patent Office, DOD, NASA, NTIS (National Technical Information Service) and others. Jam-packed with all the data needed by the hobby experimenter at the bench. From theory refresher to applications diagrams, device characteristics, tables and formulas, charts and graphs -- hundreds upon hundreds of illustrations.

A High-Density Modular Document

No wasted space or words. Separate sections are removable in loose-leaf fashion -- books within a book -- mounted in a rugged binder, big enough to hold other T_{doc} publications -- or your own notes.

Just by way of example, the section on hand soldering was boiled-down from the practices of the American Welding Society -- Committee on Soldering and Brazing; NASA, USN, solder manufacturers, the Bell Telephone System and others. The section contains everything you need to know about solder, fluxes, soldering tools and techniques.

There are over 100,000 words covering theory and application of semiconductor devices -- diodes, transistors, the SCR/TRIAC, digital and linear integrated circuits, operational amplifiers, voltage regulators, counters and decoders, and much, much more.

Sections also treat the vacuum tube and CRT, capacitors and electrostatic devices, relays and switches, electromechanical devices and mechanical movements, energy sources, cable and wire, ++++++

Update Without Annual Replacement

No need to buy a whole new book every year to keep abreast of information in the field; the "book within a book" style permits you to update only as needed.

There has never been another manual like it. That's why we undertook to put it together!! Once you have had a chance to put the manual to use, you'll start enjoying electronics as a hobby, with fewer unfinished projects that could have been completed had there not been an information gap!

Electronics Bench Manual

Introductory Price: \$17⁹⁵ Postpaid
In U.S.A.

Send check or money order marked
"EBM" with your name and address
to:

TECHNICAL DOCUMENTATION
BOX 340
CENTREVILLE, VA 22020

703-830-2535

Virginia residents please add 4% sales tax.

S2 and the rf filter (RFC1 and C5) to the meter.

Operation of the unit is similar to most tuners: a matter of getting the unit set up

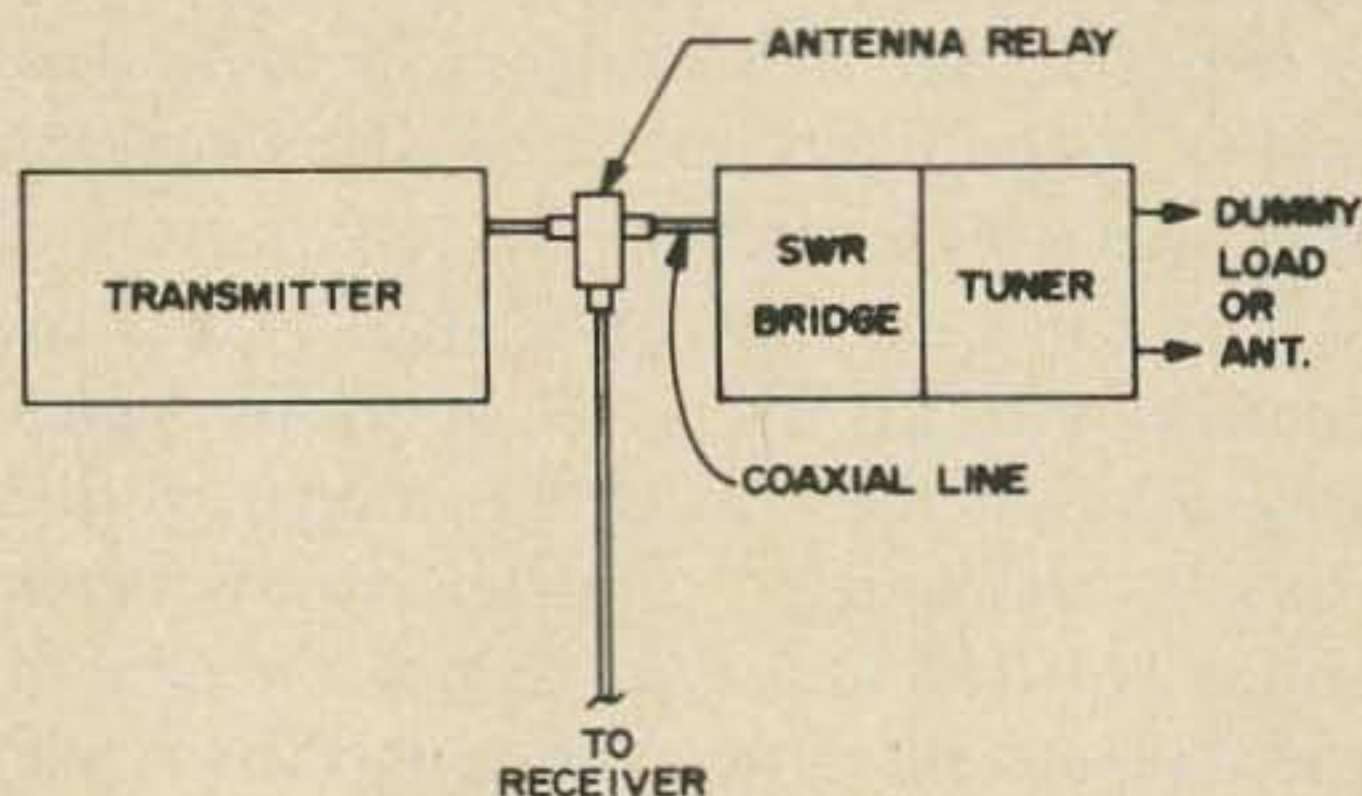


Fig. 3. Proper setup for using the tuner. The coax line to the transmitter may be any reasonable length, and a separate SWR bridge may be used if available.

on each band, and then marking the capacitor dial settings on the panel chart for easy reference. Fig. 3, shows the setup required. With low power fed into the tuner, adjust R4 for full-scale deflection on the meter with S2 in the FORWARD position. Switch S2 to REFLECTED and adjust C1 and C2 to obtain minimum reading on the meter. There is considerable interaction between the capacitors, so make sure they are both set properly and that the SWR is as low as possible. There is also a considerable reaction on the transmitter's plate tuning, so check this often and make sure it is in resonance at all times.

This can be a slow proceeding the first time, so only a small amount of power should be fed into the tuner, and a dummy load should be connected to the output until the settings have been determined. Then a short final adjustment with the antenna connected will suffice. Because there are no bandswitches or coil taps, the setup is very easy to follow and should result in an SWR of 1:1 or very close to it.

The unit was originally built to tune a V-beam feeder, but has also been used on several center-fed 80m dipoles to convert them into all-band antennas, using 300Ω TV ladder-line as the feeder. For the amateur with a space problem, this tuner could be the answer.

...VE1TG■

John J. Schultz W2EEY
 c/o RLC INC.
 30 East 42nd Street
 New York NY 10017

OLD ANTENNAS AND NEW BALUNS

Antenna types rejuvenated by the use of toroid baluns.

Anyone who has been in amateur radio for ten to twenty years will remember the days of elaborate "wire" antennas. Newcomers can also glance in some of the old antenna manuals and find them replete with "wire" antenna designs. Wire antennas as the name indicates, are simply more elaborate antenna forms than a simple dipole which provide some gain and directivity and which were usually constructed from wire hung between the necessary supports. The advantages to such antennas was primarily cost, since relatively high gains could be achieved for the cost of additional antenna wire. All sorts of collinear arrays, broadside arrays, curtains, etc., were developed and used successfully. The problems associated with such antennas were many and one of the primary ones was the often awkward feed point impedances of the antenna and the requirement for a balanced feed. Open wire lines had to be used to feed the antennas at impedances ranging from 150-600Ω and then the balanced open wire line converted via an antenna tuner to an unbalanced coaxial feed. For these and other reasons, elaborate wire antennas have fallen into disuse. Nonetheless, for the amateur who has the necessary space and is primarily interested in working single-band DX, these antennas can provide very good service at minimal cost. Fortunately, the advent of the toroid balun transformers with variable impedance ratios has also eliminated the feed problem once associated with these antennas. The purpose of this article is not to re-present every type of wire antenna array developed. A few examples are given and the use of a toroid balun illustrated. One can,

however, glance back in some of the older antenna manuals and magazines and find any number of elaborate wire arrays to which the same feed techniques illustrated here can be applied.

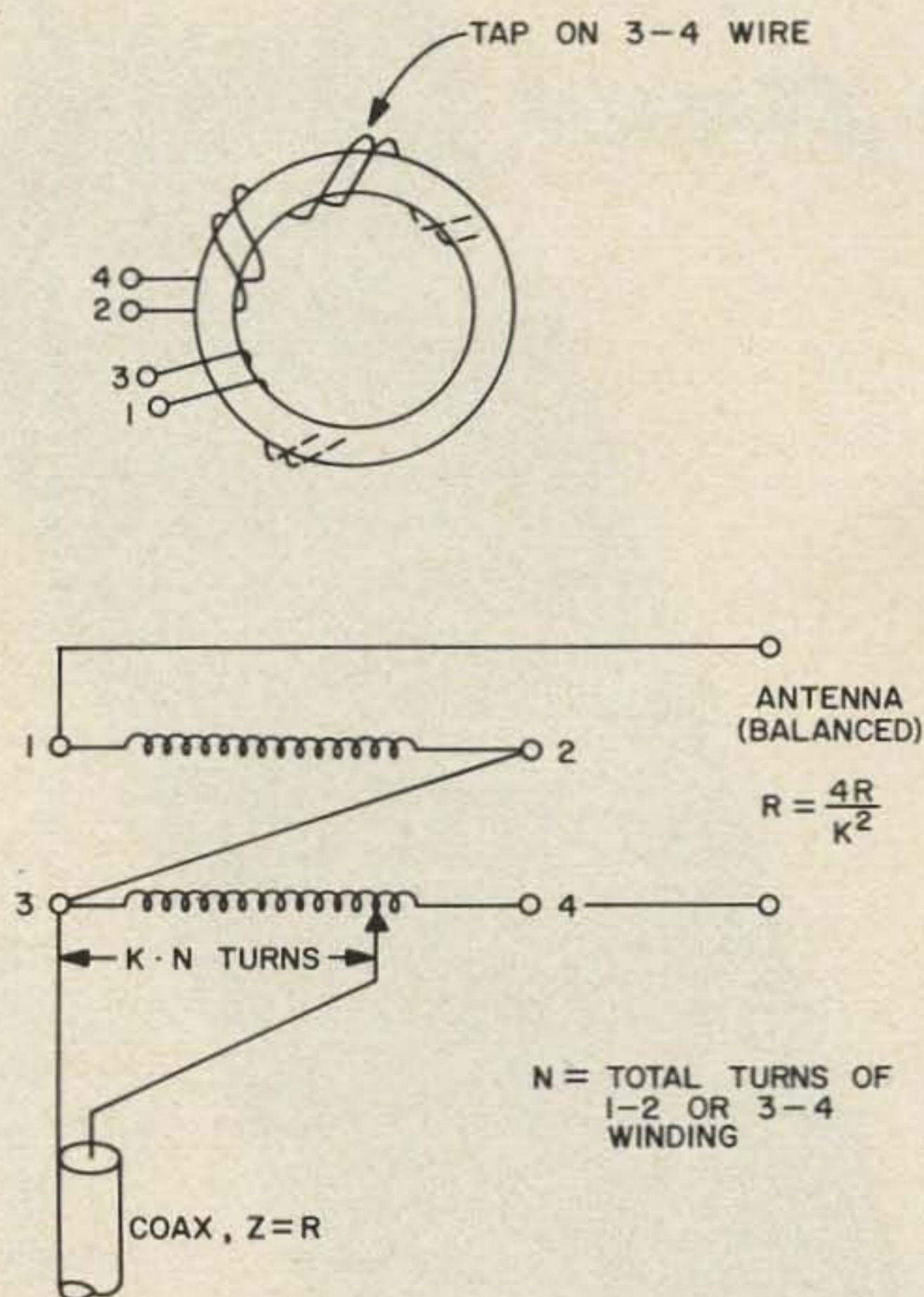


Fig. 1. Variable impedance transformation balun 1:4 to 1:10 or more.

Variable Impedance Toroid Balun

A toroid balun is usually thought of being a 1:1 or 1:4 ratio type unit. That is, going from 50Ω unbalanced to 50Ω balanced or from 75Ω unbalanced to 300Ω balanced. But any toroid balun kit can also be used as a variable impedance balun with transfor-

ESCORT

2 METER TRANSCEIVER

uhf/fm

* *solid state*

* *portable*

* *versatile*

* *mobile*

* *fixed*



- 2 1/2 WATTS OUTPUT
 - UP TO 6 CHANNELS
 - SIGNAL SAMPLER POWER CIRCUIT, SAVES BATTERIES
- OR-
- OPERATES FROM 12V EXTERNAL POWER SOURCE
 - FACTORY SUPPLIED WITH 146.94 SIMPLEX AND 34/94.
 - SENSITIVITY 0.3 UV FOR 12DB SINAD
 - ADJ CHANNEL REJECTION 60 DB, SPURIOUS SIGNAL REJECTION 60 DB

NEW

\$249.00

WARRANTED AGAINST DEFECTS IN MATERIAL OR WORKMANSHIP FOR ONE YEAR FROM DATE OF SALE BY PACIFICOM. BUY DIRECT FROM PACIFICOM AND OWN COMMERCIAL QUALITY. FROM THE MAKERS OF QUALITY MARINE AND COMMERCIAL GEAR, COMES A TWO METER RIG OF THE SAME STANDARDS.

MANUFACTURED IN THE U.S.A. BY

PACIFICOM

3939 Ruffin Rd, San Diego, Ca 92123

(714) 565-7945

Mail to: P.O. Box 80845, San Diego, Ca. 92138

mation ratios greater than 1:4 possible up to about 1:10. Fig. 1, shows a typical toroid balun winding. The instructions contained in any balun kit can be used to place the initial windings on the toroid core for a 1:4 balun. Note that if the coil tap on the 3-4 winding is placed at point 4, one has a normal 1:4 balun. If, however, this tap is moved closer to the 3 terminals, the transformation ratio of the balun increases according to the formula shown. For instance, if the tap were placed at the quarter way winding point between 3 and 4, that is one quarter of the turns from 3 to 4 away from 4, the transformation ratio would be approximately 1:10. A 50Ω unbalanced input would be transformed to a 500Ω balanced output. In a similar manner, the other tap points can be figured out for any impedance transformation ratio.

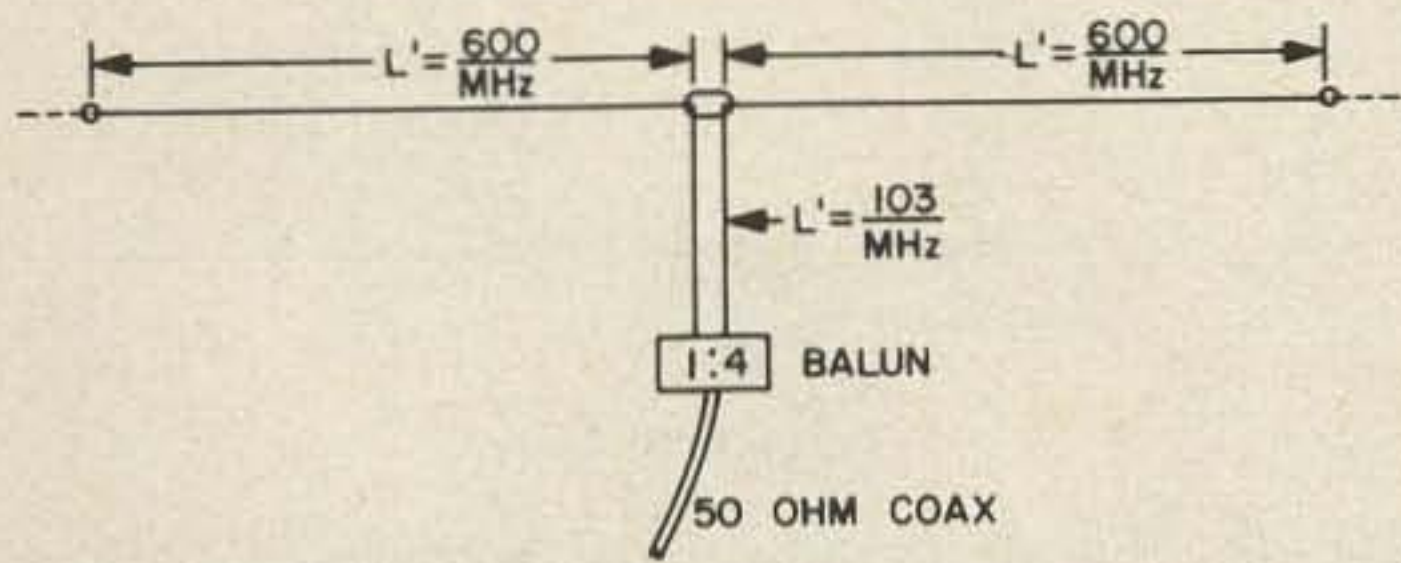


Fig. 2. Extended Double Zepp with balun feed.

Double-Zepp Antenna

The Double-Zepp antenna is a form of extended dipole as shown in Fig. 2, where the dipole elements are made as long as they can be while still having the radiation pattern of the antenna not split up and remain at right angles to the line of the antenna (in

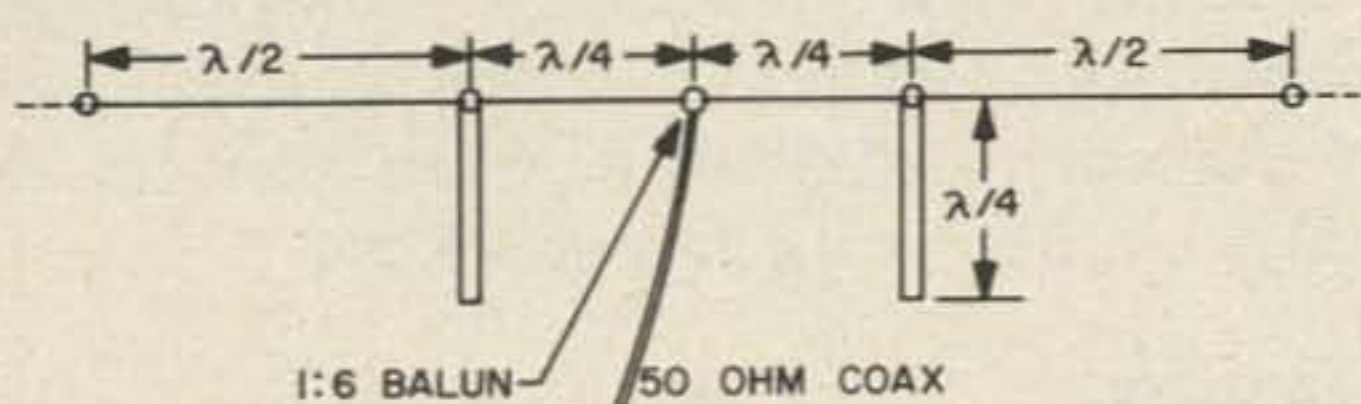


Fig. 3. Classic collinear array balun feed. See text for extending antenna to increase gain.

and out of the page). The gain achieved is an easy 3 dB. A small phasing section is still required at the center of the antenna, as shown, before the connection of a 1:4 balun.

3/4λ Dipole

The 3/4λ dipole of Fig. 3, also has its main radiation at right angles to the line of the wire and produces 3-4 dB gain. This form of antenna may be somewhat easier to construct than the Double-Zepp since the balun (a 1:6 unit in this case) may be connected directly at the center of the antenna. The phase reversal stubs between the 1/2λ elements can be made of simple 300Ω twinlead shorted at the far end. The antenna can be extended with another 1/2λ

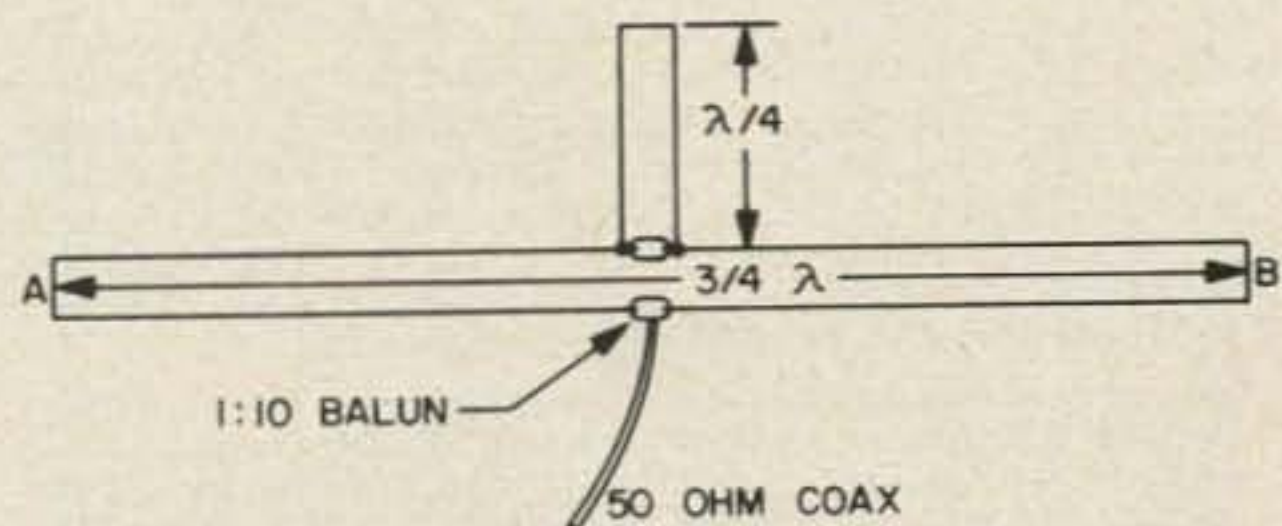


Fig. 4. 3/4λ folded dipole may be operated on two bands if desired by using stub switch.

element on each end (and a 1/4λ stub to connect to the adjacent 1/2λ element) to raise the gain another dB or more. In this case, a 1:10 balun has to be used to feed the antenna.

Dual Band 3/4λ Dipole

The 3/4λ dipole shown in Fig. 4, can be used either as a single band or dual band antenna. Its total length is 3/4λ long at the lowest frequency band used. If used as a single band antenna, the shorted 1/4λ stub shown is not required. If it is to be used as a dual band antenna, the stub is made 1/4λ long

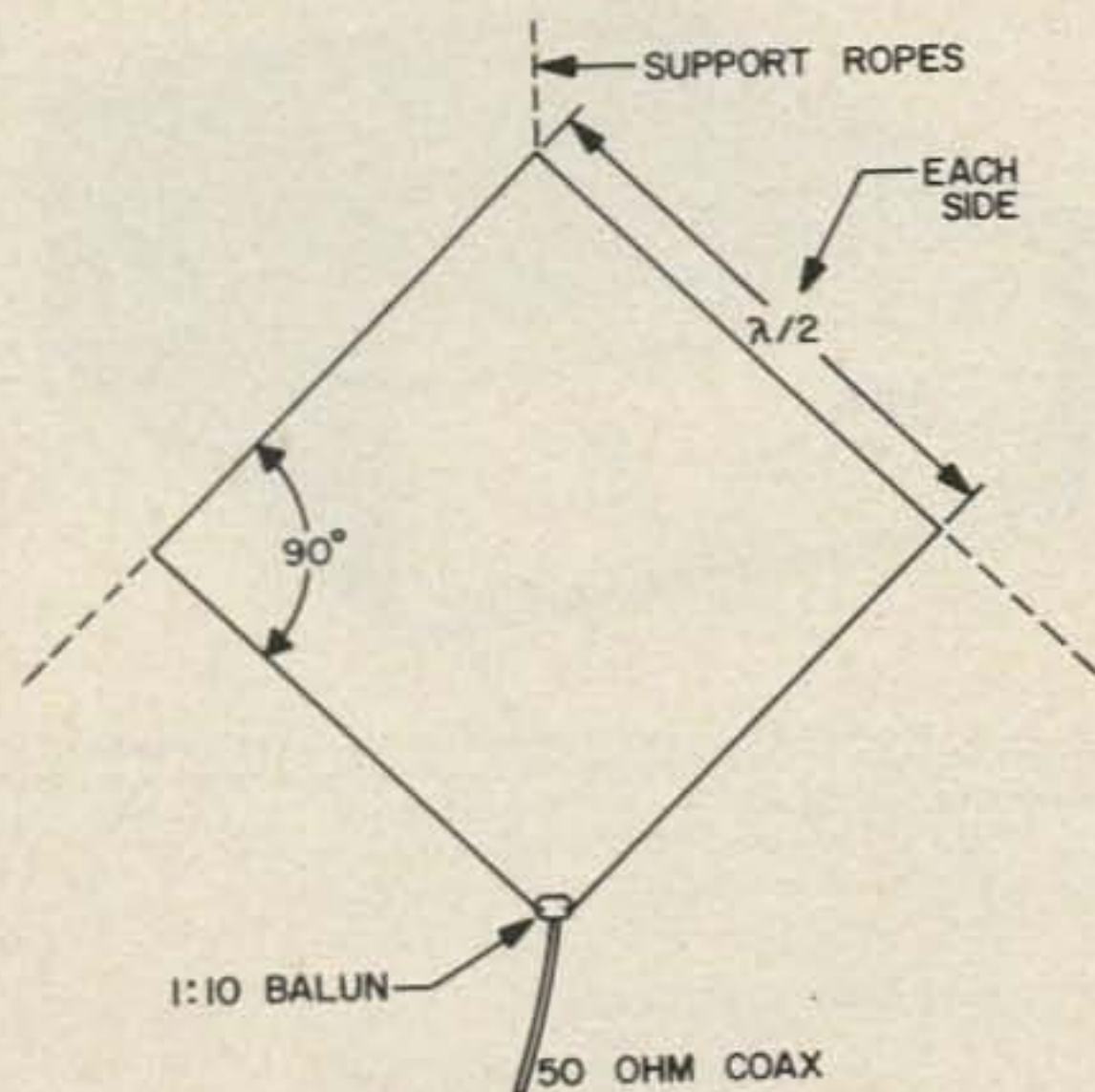


Fig. 5. Super loop or bi-square requires only single support and produces easy 4 dB gain.



GLADE VALLEY SCHOOL RADIO SESSION

15th year — July 27—August 9, 1974

Courses Taught: General Theory and Code
Advanced Theory and Code
Amateur Extra Theory and Code

Golf privileges at New River Country Club; also fishing

TRULY A VACATION WITH A PURPOSE!!!

People attended from the following states and areas:

North Carolina, South Carolina, Missouri, Tennessee, Utah, Florida, Oklahoma, West Virginia, Alabama, New Hampshire, Iowa, District of Columbia, Vermont, Arizona, Indiana, Ohio, New Jersey, New York, Massachusetts, Maryland, Virginia, Illinois, Michigan, Georgia, Kansas, Mississippi, Nebraska, Maine, Kentucky, California, New Mexico, Arkansas, Texas, Wisconsin, Louisiana, Oregon, Connecticut, Minnesota, Pennsylvania.

We have changed our name from Camp Albert Butler to Glade Valley School Radio Session. We are now located on the campus here in Glade Valley, North Carolina. Same good food, same fine instructors — in fact, nothing has changed but the name and location.

C.L. Peters K4DNJ *DIRECTOR*
Box 770 Elkin, North Carolina 28621

Please send me the booklet and application blank for the Glade Valley School Radio Session.

Name _____ Call _____

Address _____

City/State/Zip _____

—Touch-Call—

DECODER

A KIT DESIGNED TO PROVIDE INEXPENSIVE SELECTIVE CALLING

- Detects one 4-digit TOUCH-TONE® sequence selected by internal strapping
- Uses audio from discriminator or speaker output
- Speaker switching relay included — SPDT
- Latest integrated circuit technology — PLL Tone detection
- Easy construction and installation
- Power input 12 vdc negative ground



PCB KIT # T10 4.75 x 5.5 Board and all board mounted components \$39.95
COMPLETE KIT # T10-C PCB Kit with cabinet, switch, LED, and terminal block \$44.95
ASSEMBLED T10-C Specify an initial code preference \$59.95

Prices effective April 15, 1974 supersede all others

Shipping wt. 2 lbs. Add sufficient funds for handling
Texas residents add 5% state tax

ORDER FROM: **CEPCO**
P.O. BOX 189
DUNCANVILLE, TEXAS 75116

© TOUCH-TONE IS A REGISTERED TRADEMARK OF AT&T

at the lowest frequency band. On the next higher harmonically related band, the stub will act as a short circuit, since it becomes $\frac{1}{2}\lambda$ long, and allow the antenna flat-top to properly resonate. Whether used as a single band or dual band antenna, it can be fed via a 1:10 balun.

Super Loop

The large loop antenna shown in Fig. 5, can be mounted from a tower or other support. Its radiation is horizontally polarized and broadside to the plane of the array (in and out of the page). The gain is about 4 dB in both directions. It can be fed directly from a coaxial line via a 1:10 balun at the base as shown.

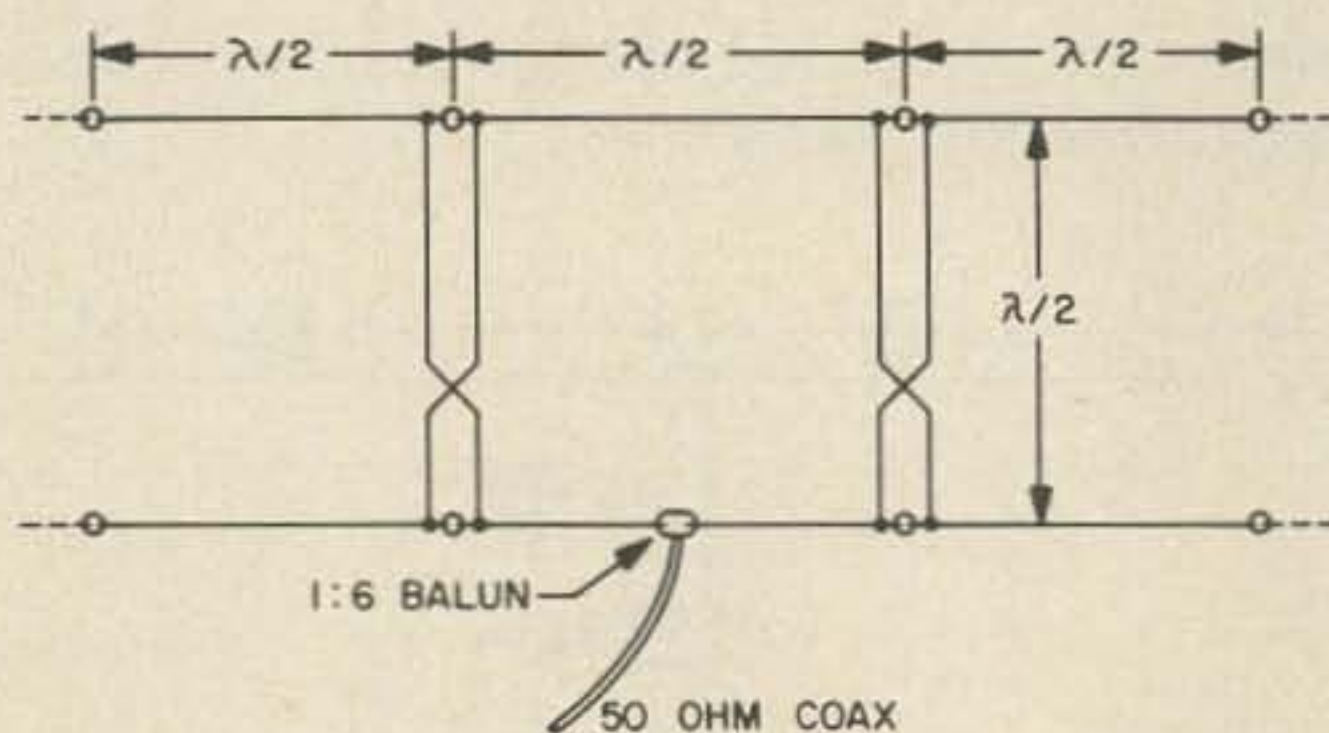


Fig. 6. The six-shooter array provides 7.5 dB of gain. Lower elements should be $\frac{1}{4}\lambda$ high.

Super Loop

The array of Fig. 6, is just one small example of a curtain array including such types as Sterba, Bruce Arrays, etc. The gain that such arrays can provide become quite significant if one has the space to extend them one to two wavelengths. In this case, the array will provide a broadside gain of 7.5 dB in both directions. The antenna can be fed at the point shown via a 1:6 balun. The phasing line between the upper and lower set of elements can either be open wire line or 300Ω twinlead with a single twist.

Summary

Many other antenna forms which present a resistive impedance on a single band but of an awkward value can be fed via a properly constructed balun. Other antenna types which suggest themselves are V beams, rhombics, half rhombics and single tilted wire antennas.

...W2EEY

Thomas Niedermier WA8IYL
Box 163
New Washington OH 44854

A MULTIBAND GROUND PLANE

The last time strong winds turned my homemade beam and removed the teeth from the rotor gears, I decided it was the last time. My financial situation would not permit procuring a good rotor, so an inexpensive homemade multiband ground plane seemed like the answer. Having had good luck with a water pipe as an antenna element and a dielectric pipe union as an insulator, I tried my luck at a plumber's ground plane.


The antenna is simple to construct, with a little plumbing ability or help. The top section is an old CB whip antenna. These are

easy to come by. The whip is bolted to a one-half inch pipe cap by drilling a 3/8 inch hole in the center of the cap. This assembly is installed on an 86 inch section of one-half inch pipe. A coupler from one-half inch to one inch pipe is used to add the remaining 12 inch section of one inch pipe. The overall length of the vertical section is about 16 feet, but length is not critical.

Prepare the dielectric union by welding four 3/16 inch eye bolts to it for attachment of the ground radials. I also added small eyes to solder the ends of the radials. Another small eye is welded or soldered to the base of the vertical section for the other side of the 450Ω feed line.

The mast itself is 1 1/4 inch pipe. The higher it is the better. The plane of the radials must be at least 1/4 wave length above ground to be a true ground plane. The radials serve as guy wires and should be at a 45° angle to the mast. TV mast brackets were used to hold the mast to the house. The bottom end of the mast is buried and set on a steel plate. If you add some good all-weather paint, the antenna will stand for years.

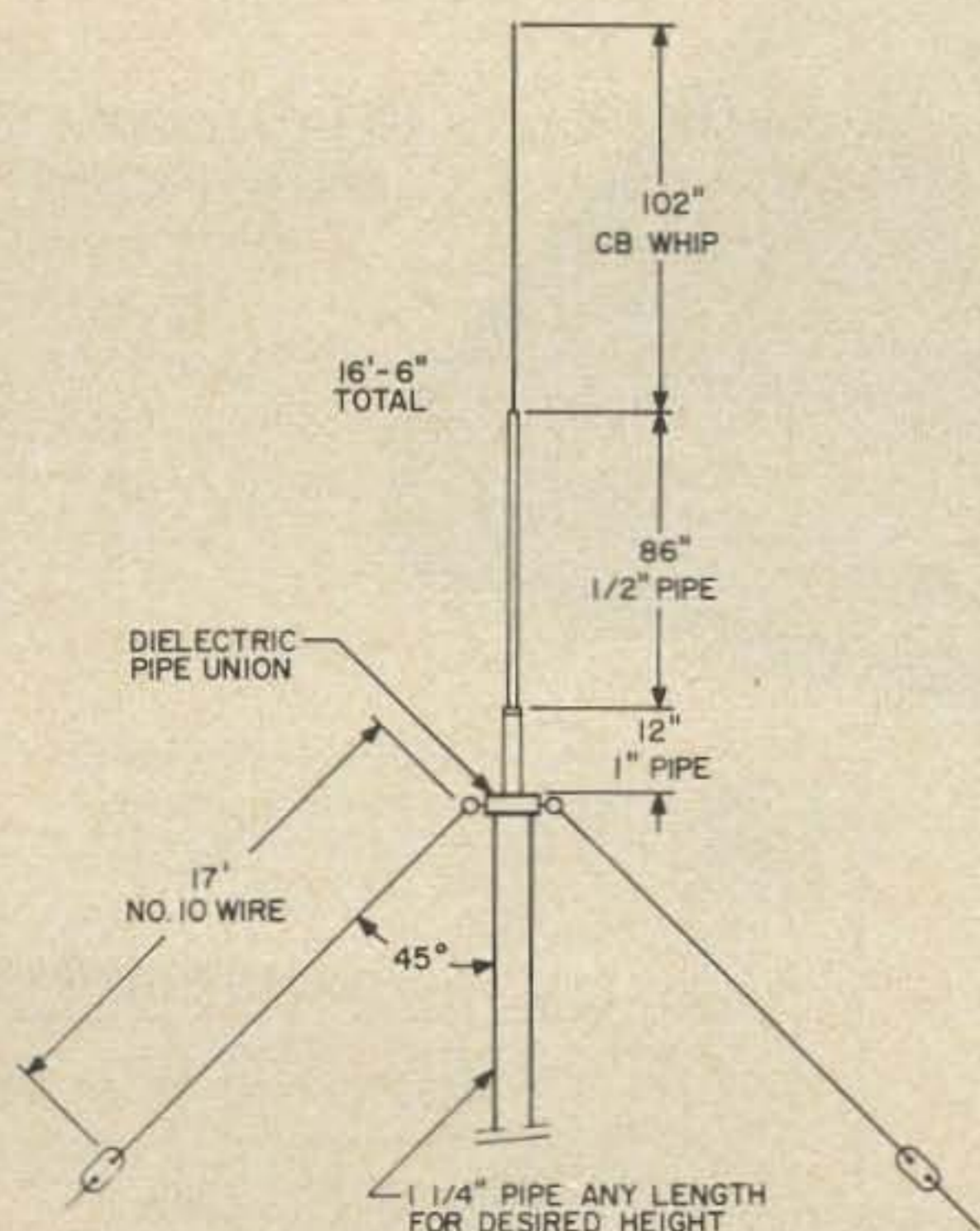By feeding the antenna with 450Ω open wire and using a match box and a SWR indicator, this antenna will do a fine job on 15, 10 and 20 meters. My SWR is less than 1.3 to 1 on these bands and the antenna can be used on 40 meters with an SWR of only 3 to 1.



LENGTH OF ELEMENTS NOT CRITICAL.
FEED WITH 450 OHM OPEN WIRE FOR
USE ON 10, 15, 20 METERS.

...WA8IYL

The ID-1A isn't much to look at.



Until you look into it.

The HAL ID-1A repeater identifier was designed and engineered for commercial service, in compliance with FCC identification requirements. But its price is so attractive that radio amateurs interested in FM are buying it, too.

The heart of any repeater identifier is its Read-Only-Memory. And inside the HAL ID-1A is a unique ROM — one you can easily re-program yourself, should you need to change the call sign. The ID-1A's ROM capacity holds 39 dots, dashes and spaces — enough for "DE" plus the call sign. But there's a lot more inside the ID-1A than that. TTL IC's are used for high noise and temperature immunity. Accurate timing is assured from the 60 Hz VAC line

source, or an internal oscillator — when the unit is operating on 12 VDC. And there's a wide selection of ID time intervals available to you (the factory-assembled set is programmed for 3, 6, 12 or 24-minute ID intervals). Code speed is adjustable. The keyed audio oscillator includes volume and tone controls, with a low-impedance output for driving the transmitter microphone line and a 2" monitor speaker. And there's a rugged transistor switch to actuate the transmitter keying relay or other controller.

The HAL ID-1A is available factory assembled for \$115 or as an assembled board/kit, including all parts external to the board except the cabinet for \$75. Look

into it. Better yet, order yours today.



HAL Communications Corp.
Box 365, Urbana, Ill. 61801
Telephone: (217) 359-7373

- Enclosed is \$ _____ (Assembled)
\$ _____ (PC Board/Parts)
Call letters _____ I.D. Interval _____ min.
 Charge Master Charge # _____
 Charge BankAmericard # _____
M/C Interbank # _____
Card Exp. date _____
 Please send me the HAL catalog.

Name _____

Address _____

City/State/Zip _____

All prices include U.S.A. shipping.
Add \$3 for air shipment.
Illinois res. add 5% sales tax. **L**

Now is the time for all good hams to come to the aid of their code.

With the HAL MKB-1, you can send perfect CW as easily as using a typewriter. The all solid-state MKB-1 is a complete Morse keyboard codetyper, with code speed variable from 10 — 60 WPM. Dot-to-space (weight) ratio is also variable.

The MKB-1 is full of features, like a variable volume/tone oscillator with internal speaker. Plus its own power supply. Computer-grade key switches. And it drives cathode or grid-block keyed transmitters.

An available option is the HAL KB-ID automatic identifier. Touch a button and "DE," followed by your call is automatically transmitted. And you can add two 2-letter characters of your own, e.g., "73 OM."

Assembled, the MKB-1 costs \$250; with the KB-ID option, add \$40. (We'll program your call into the



KB-ID for you.) The MKB-1 kit is \$170; with the KB-ID kit, add \$29. Come to the aid of your code today — and enjoy CW like never before.



HAL Communications Corp.
Box 365, Urbana, Illinois 61801
Telephone: (217) 359-7373

- Enclosed is \$ _____ (MKB-1)
\$ _____ (KB-ID option)
Call letters _____
 Charge to my Master Charge # _____
 Charge to my BankAmericard # _____
 M/C Interbank # _____
Card exp. date _____
 Please send me the HAL catalog.

Name _____

Address _____

City/State/Zip _____

All prices include U.S.A. shipping. Add \$5 for air shipment. Ill. res. add 5% sales tax. **L**

Frederick H. Vogel WN3QBK
500 23rd Street, NW #B-401
Washington, D.C. 20037

MOD QUAD FOR FRUSTRATED CLIFF DWELLERS

If your landlord won't believe that that tower is actually a priceless Picasso sculpture — then read on . . .

This is another answer for the ham who has a luxury apartment complete with everything except permission to erect antennas on the roof or to run wires on the building exterior. The idea was born when I saw my clandestinely mounted mobile whip hauled down from the roof of my 12-story building, and 100 feet of my RG-58/AU feedline tossed to the sidewalk with a warning from the apartment manager. It was almost enough to drive a reborn ham off the air, but not quite enough.

I already knew that most makeshift antennas inside steel-reinforced concrete buildings are pretty poor rf radiators, and they are difficult to load without a good antenna matching unit. Even a shortened helical groundplane on a veranda suffers from inductance and capacitance effects of steel reinforcing and iron railings. At least, I couldn't make it work acceptably in my apartment.


My experience with quad antennas in South America and Asia, however, had



impressed me with the quad's ability to perform well near obstructions, so I decided to try some kind of modified quad on my balcony within the physical space limitations, the building regulations, and the XYL house rules.

Many unsuccessful experiments and trials led me finally to the happy answer: a one-element rectangular quad using the metal porch door frame for a reflector. Its worth is attested by more than 200 CW novice contacts up to 5000 miles in distance, including 30 states and 22 foreign countries, all on the 15 meter novice band with my NCX-5 throttled back to a legal 70 watts input.


I am unable to explain the radiation pattern of my Mod Quad. While my balcony faces east and the quad loop is wholly or partially shielded in other directions, nevertheless I get good reports from almost all around the azimuth circle, as if the radiator were a half-wave vertical in the clear. Several hams have told me of similar radiation

Schematic Of The Month REGENCY HR-6

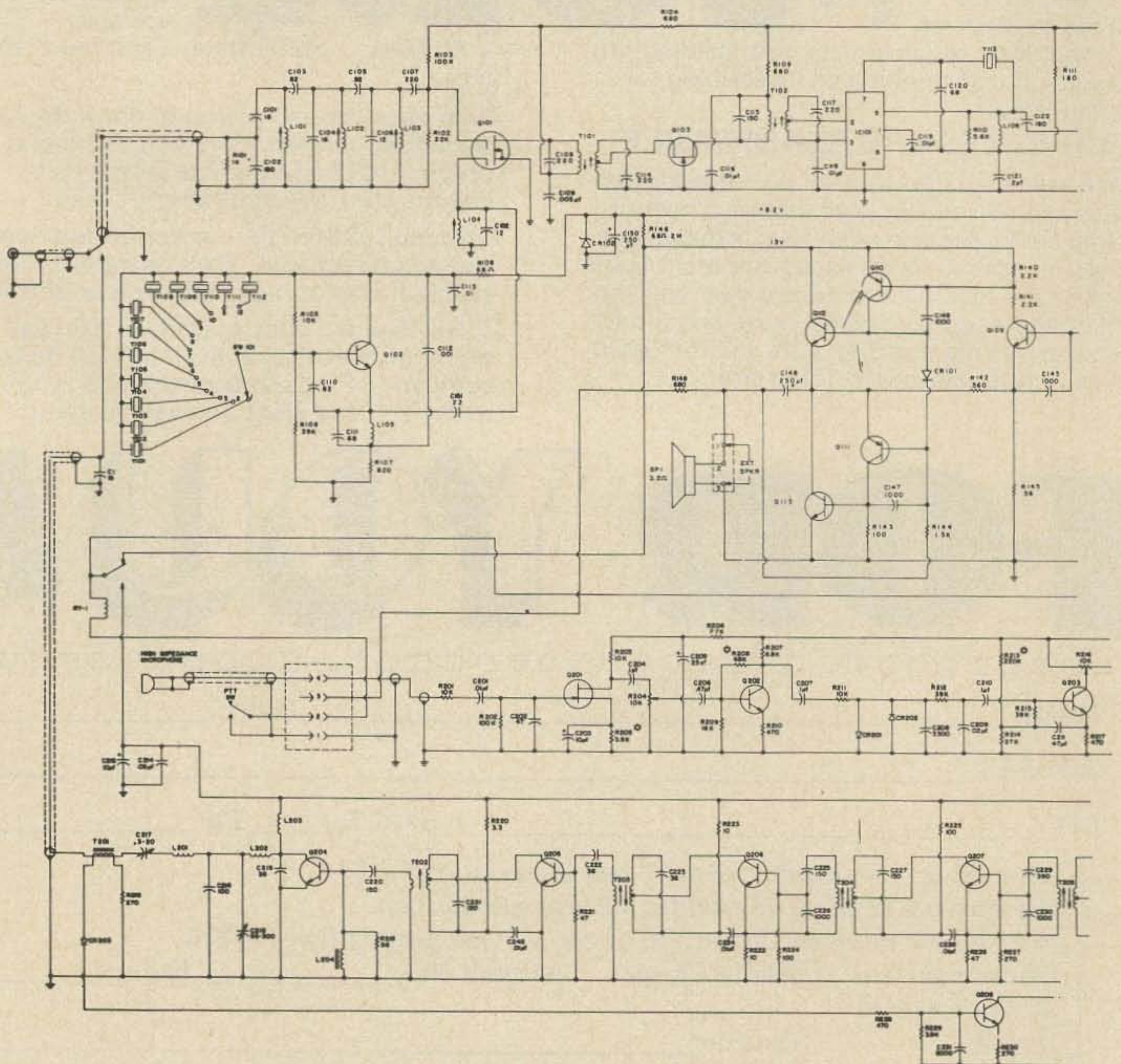

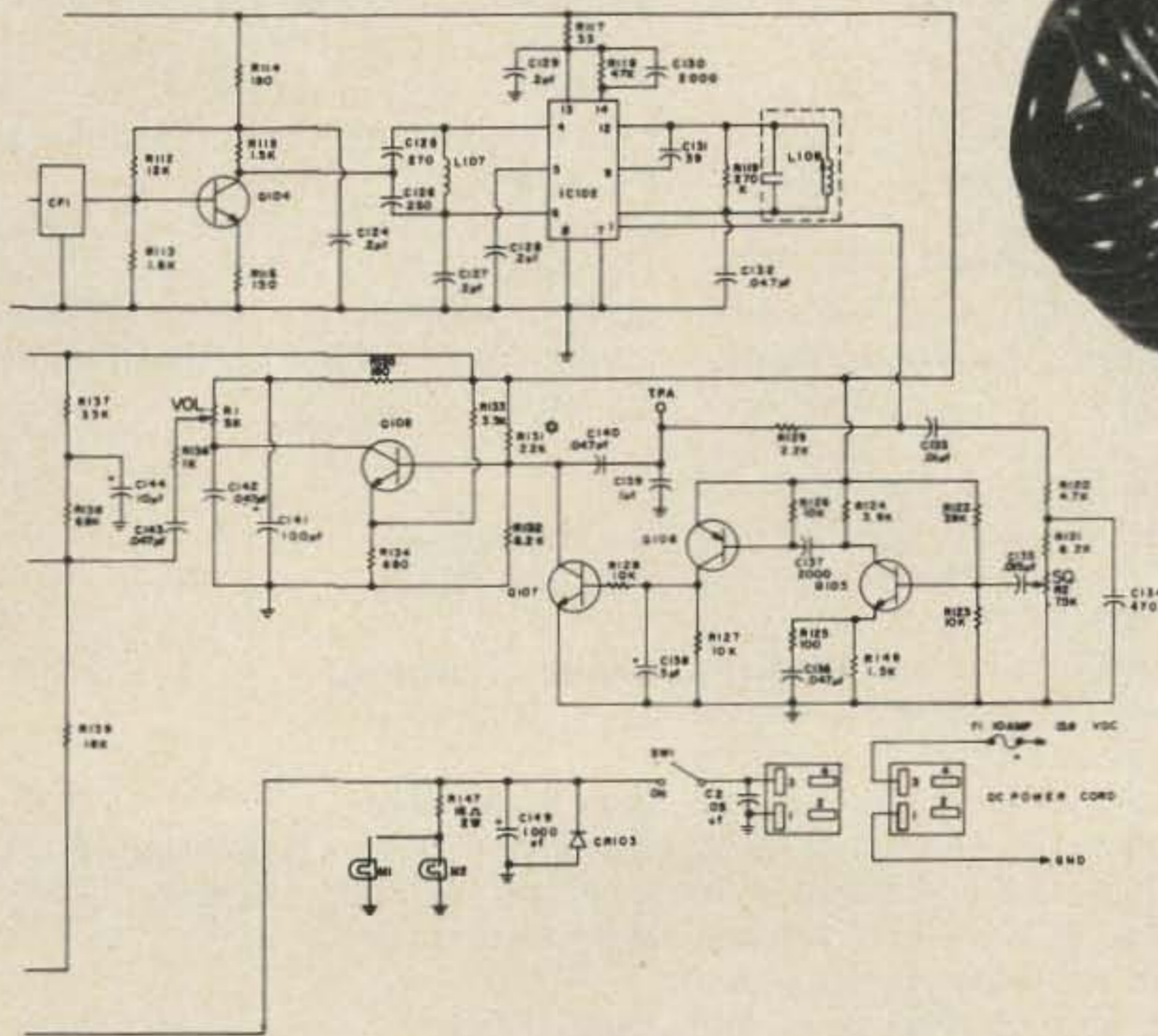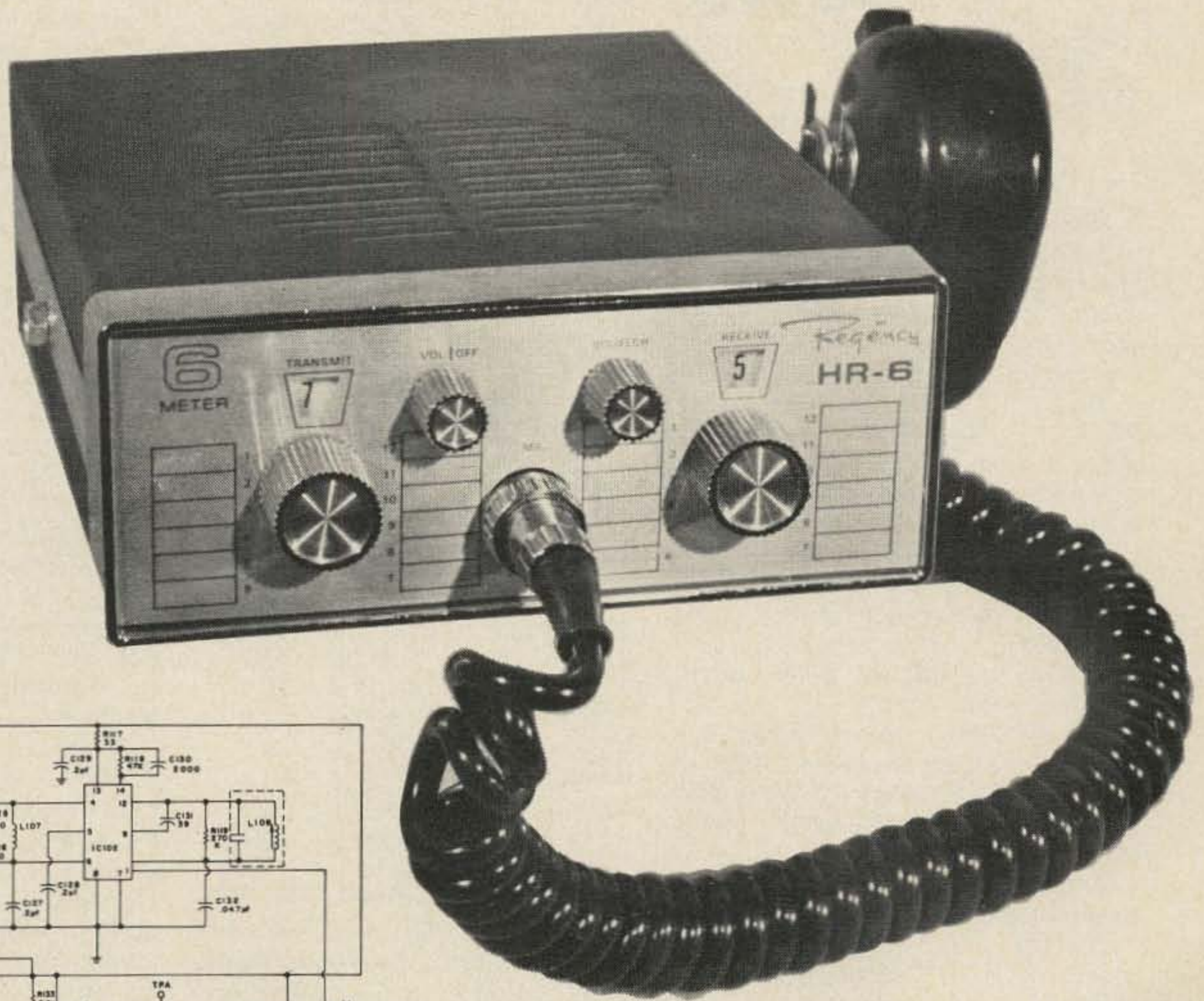

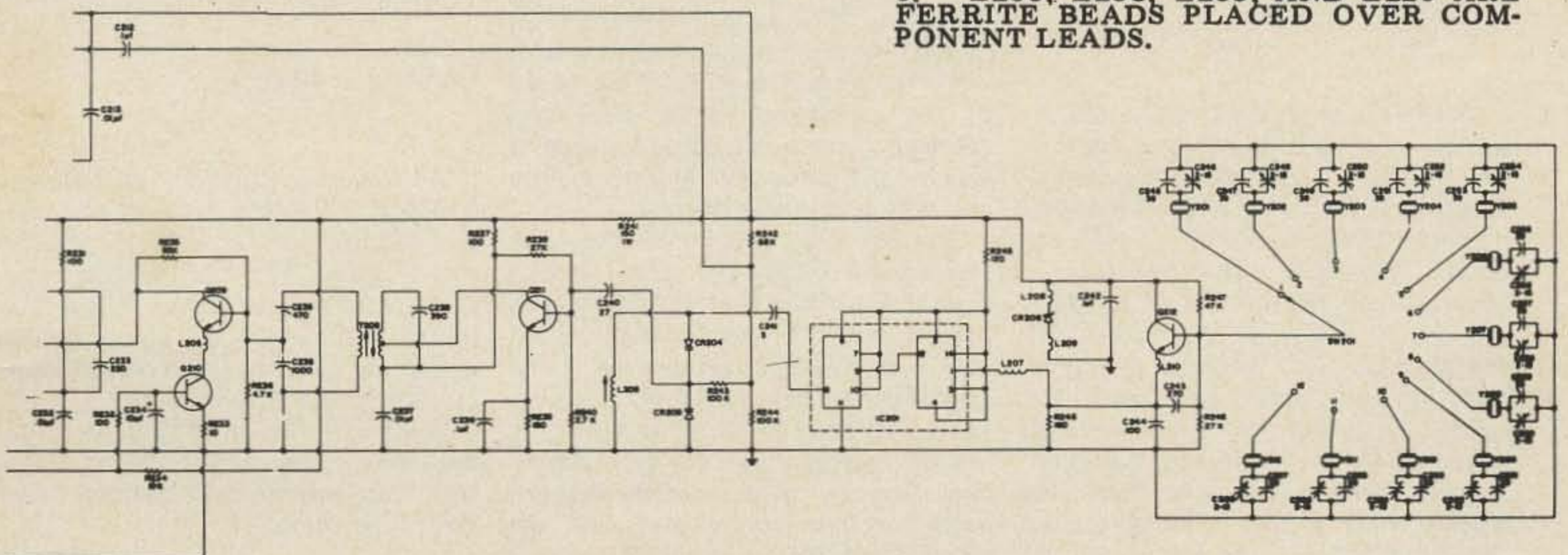NOTES:
 1. ALL CAPACITOR VALUES NOT SPECIFIED ARE PICO-FARAD.
 ALL RESISTOR VALUES NOT SPECIFIED ARE OHMS, 1/4 WATT.
 2. * NOTED VALUES ARE FACTORY SELECTED. NOMINAL VALUES SHOWN.
 3. L205, L208, L209, AND L210 ARE FERRITE BEADS PLACED OVER COMPONENT LEADS.



AMSAT NEWS



Michael Frye WB8LBP
640 Deauville Dr.
Dayton OH 45429

"Space Science Involvement" a 64-page curriculum supplement intended for secondary school teachers, is now available from ARRL Headquarters. Produced by educators at the Talcott Mountain Science Center, Avon CN under contract from AMSAT, this curriculum source material illustrates how AMSAT-OSCAR 6 can be used as a classroom instructional tool.

For your free copy of the book write: Bill Dunkerley, c/o ARRL, 225 Main Street, Newington CN 06111. Be sure to specify how and where you expect to use OSCAR 6 for educational purposes.

The OSCAR 7, two 10m repeater passbands (± 3 dB points) are: UPLINK 145.850-145.950 MHz DOWNLINK 29.40-29.50 MHz, BEACON 29.50 MHz.

Amateurs who have qualified for AMSAT-OSCAR 6 W.A.S. Award are:

W3TMZ	W0LER
K4TI	DJ6RD/W9
W9OII	K2GUG
W8DX	W6EJJ
W5VY	W0NQQ



Joe Kasser G3ZCZ
1701 East West Highway, Apt. 205
Silver Spring MD 20910

When I was writing about the repeaters in the Pittsburgh area, back in the February column, I apparently forgot to mention the 22/82 Repeater. K3ISO wrote in to tell me about WR3ACH. This repeater is accessible on the turnpike from mile marker 30 (west of Warrendale) to mile marker 100 (between Somerset and Donegal). Mobile coverage of the greater Pittsburgh area lies within a 35 mile radius of Churchill Borough, however when driving in that area, one is either in the valley or on the top of a hill so that signals can get

Orbit	Orbital Information		
	Date (Jun)	Time (GMT)	Longitude of Eq. Crossing °W
7430	1	0039.2	57.6
7443	2	0134.1	71.3
7455	3	0034.1	56.3
7468	4	0129.0	70.0
7480	5	0028.9	55.0
7493	6	0123.9	68.8
7505	7	0023.8	53.7
7518	8	0118.7	67.5
7530	9	0018.7	52.5
7543	10	0113.6	66.2
7555	11	0013.5	51.2
7568	12	0108.4	64.9
7580	13	0008.4	49.9
7593	14	0103.3	63.6
7605	15	0003.2	48.6
7618	16	0058.2	62.3
7631	17	0153.1	76.1
7643	18	0053.0	61.1
7656	19	0148.0	74.8
7668	20	0047.9	59.8
7681	21	0142.8	73.5
7693	22	0042.8	58.5
7706	23	0137.7	72.2
7718	24	0037.6	57.2
7731	25	0132.6	70.9
7743	26	0032.5	55.9
7756	27	0127.4	69.7
7768	28	0027.4	54.6
7781	29	0122.3	68.4
7793	30	0022.2	53.4

noisy at times. The equipment consists of Motorola Sensicon Receiver and Transmitter Strips with homebrew power supplies. The I Der, timer and six cavity duplexer are also homebrew. 25W of rf is fed to the four pole antenna for about 100W of erp. The reason that WR3ACH did not get a mention in the column was probably because I didn't have 22/82 in the rig at the time, after all there is a limit to how many pairs of crystals one can put into any one rig at any one time.

A few miles from Pittsburgh in Philadelphia there is a 19/79 repeater. The repeater has wide coverage over the southern part of New Jersey and features a free autopatch or local calls. Access to the autopatch is by the use of the * button on the touchtone pad, while disconnect is achieved by means of the # button. Since everything between * and # is recorded, please, if you use the autopatch, identify before and after and during the call.

Mobile VHF activity in the USA seems to be 99.9% FM. That is not so over in England. There, 2m SSB is also popular and is helped by readily available commercial Japanese rigs. These rigs feature channelized communications (10 kHz) with VFO tuning to get in between the 10 kHz points. Commercially made transverters also exist for base station use, and the resulting simplex range well exceeds

that of FM. The rig is called the Liner 2. A somewhat similar rig is advertised in the USA for 6m use. That does not mean that FM is not popular, one repeater has been on the air for over a year now, and more are planned. There is a lot of simplex activity as well as I found when I was in London for a very brief stay in January.

Prices of ham equipment in England are very different to those in the USA, for example: Yaesu FT 101B \$649, in the US. It is \$760 in the UK. 2m FM crystals, \$3.75 in US, \$8.20 in the UK. Robot SSTV monitor - \$295 as compared to \$506 over there, and so on. One day it will be interesting to compare the cost of ten popular pieces of ham gear in different countries, then compare salaries, and see for example how many hours of work are required to purchase a Flibber 450 DX special.

VK3ZML wrote in with some up-to-date information on the Australian scene. For the latest information write: Wireless Institute of Australia, P.O. Box 150, Toorak, Victoria 3142, or telephone (03)-248-6521 in Melbourne, (02)-435-7951 in Sydney, (08)-261-4814 in Adelaide or (072)-48-6142 in Brisbane. He also passes on a list of repeaters as follows:

Victoria
Bendigo 20/80; Geelong 40/00;
Horsham 10/70; Labrobe Valley
20/80; Melbourne 10/70; Mildura
40/00; Mount Macedon (Melbourne)
30/90.

South Australia
Adelaide 40/00;

Western Australia
Perth 10/70;

New South Wales
Gosford 10/70; Newcastle 40/00;
Orange 10/70; Sydney 40/00;
Woolongong 10/70;

Queensland
Brisbane 40/00; Gold Coast 10/70;

Tasmania
Launceston 40/00;

All repeater channels lie between 146 and 147 MHz. Simplex channels are 145.85, 146.00, 146.15, 146.50 and 146.55 MHz. If you wish to order such nonstandard US channels, I've found that Savoy can supply them within two weeks and that was without any special rush request.

Well, this month we've gone round the world. Keep those letters coming and this column will become even more interesting.

G3ZCZ



NEW FOR 20m

IF YOU WANT TO BE SURE THE SIGNAL GETS THERE.....

GO MONOBAND BEAM

NOW AVAILABLE FROM ANTECH..

\$114.95

FOB ST. LOUIS

With all the 20 meter activity today, there is only one way to get your signal in there. .on top, a beam. That means a monoband beam. If you want DX, 20 meters has it, and you won't have time for any other band. Get your signal in there to be heard just a little bit better with the all new ANTECH 20-3, monoband, 20 meter 3 element beam.


With a gain of 8.5 d/B, and made with only top quality aluminum, here is the way to make a big noise on 20. . . .and the price is right.

(Coming soon, beams for 6 thru 40)

Write: ANTECH
7750 KINGSBURY
CLAYTON, MO 63105

BankAmericard and Master Charge welcomed

CIRCUITS...

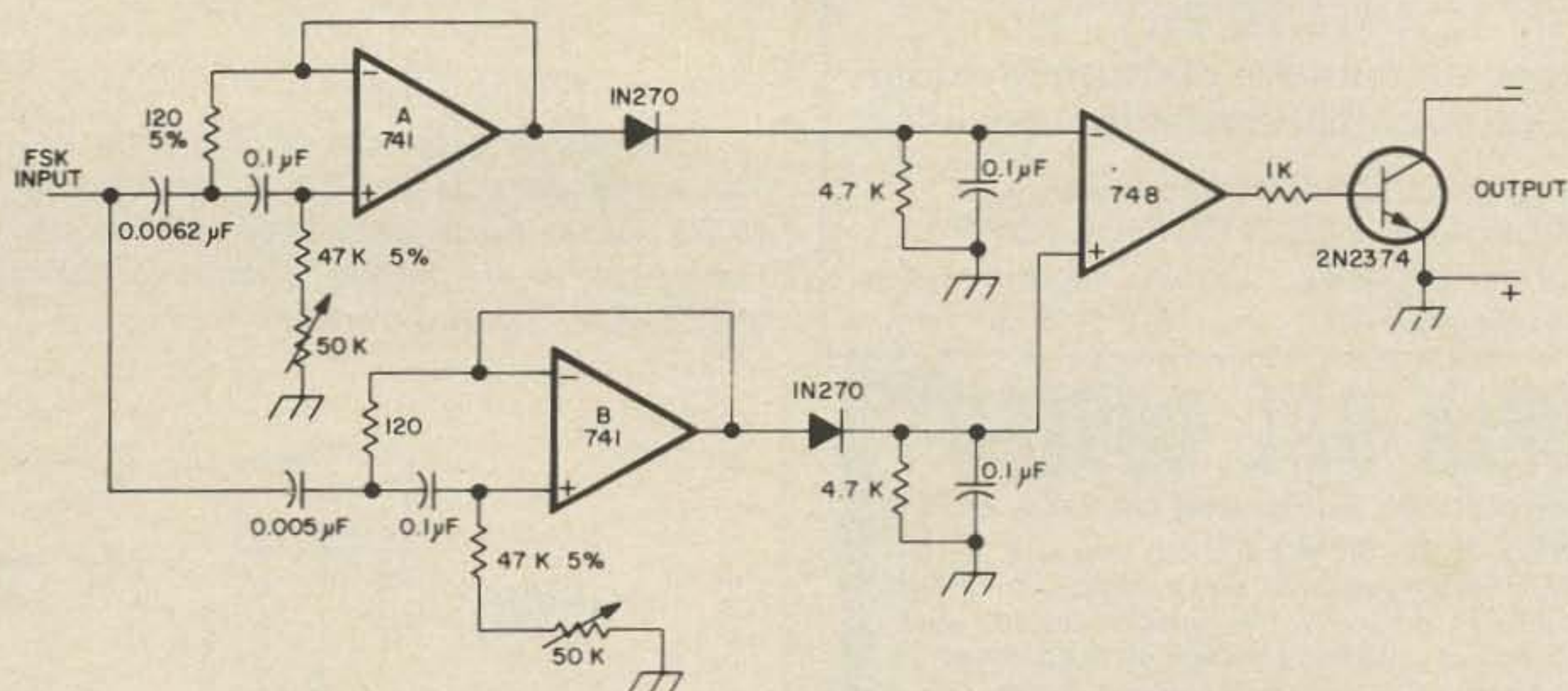

MARK/SPACE DEMODULATOR

FSK demodulator contains 2 active filters, saving space and improving performance over designs that use conventional LC-tuned circuits. Filter A passes the space frequency of 2,025 Hz, while filter B passes the mark frequency of 2,225 Hz. The op amp operates open loop, summing the filter outputs. For a mark input, the output transistor saturates so that circuit loop closes. This circuit works fine on a breadboard. Thanks to F. C. Hervey K4ETZ, for submitting this circuit from the July 19, 1973 issue of Electronics Magazine.

THE ATLANTA HAMFEST and GEORGIA STATE CONVENTION

June 8 - 9
ATLANTA TOWNHOUSE
10th STREET & I - 85
PRIZES

COLLINS KWM2A	ROBOT SLOW SCAN
HEATH SB102 & 200	DRAKE TR4C
GALAXY GT 550A	SWAN 700 CX
HAL ST-6	GLEGG FM27B
(3) HY GAIN ANTENNAS	HALLICRAFTERS FPM 300

& more, Hourly Door Prizes

Mars Meeting Technical Sessions

Tickets to Braves Baseball Friday, June 7th

ATLANTA RADIO CLUB
P.O. BOX 11555
ATLANTA, GEORGIA 30305

PARTS! CORNELL TUBES!
FREE Send For FREE
CORNELL'S New Color Catalog
48 Pgs. New Items IN LOTS OF 100
33¢ per tube
36¢ per tube
ORDER FREE IF NOT SHIPPED IN 24 HOURS!
4215 S University Ave. San Diego, Calif. 92105

WANTS TO BUY

All types of military electronics equipment and parts. Call collect for cash offer.

SPACE ELECTRONICS division of
MILITARY ELECTRONICS CORP.


76 Brookside Drive, Upper Saddle River
New Jersey 07458 / (201) 327-7640.

WORLD QSL BUREAU

5200 Panama Ave., Richmond CA USA 94804
THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next county, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 6¢ each.


5 Channel, 2.2 watt
\$179.00
AMERICAN MADE QUALITY - IMPORT PRICE
Amateur Net
Model HRT-2
by Regency
555 WOODLAWN ROAD
LINCOLN IL 62656 (217)735-1265
A-A-A SALES

CIRCUITS...

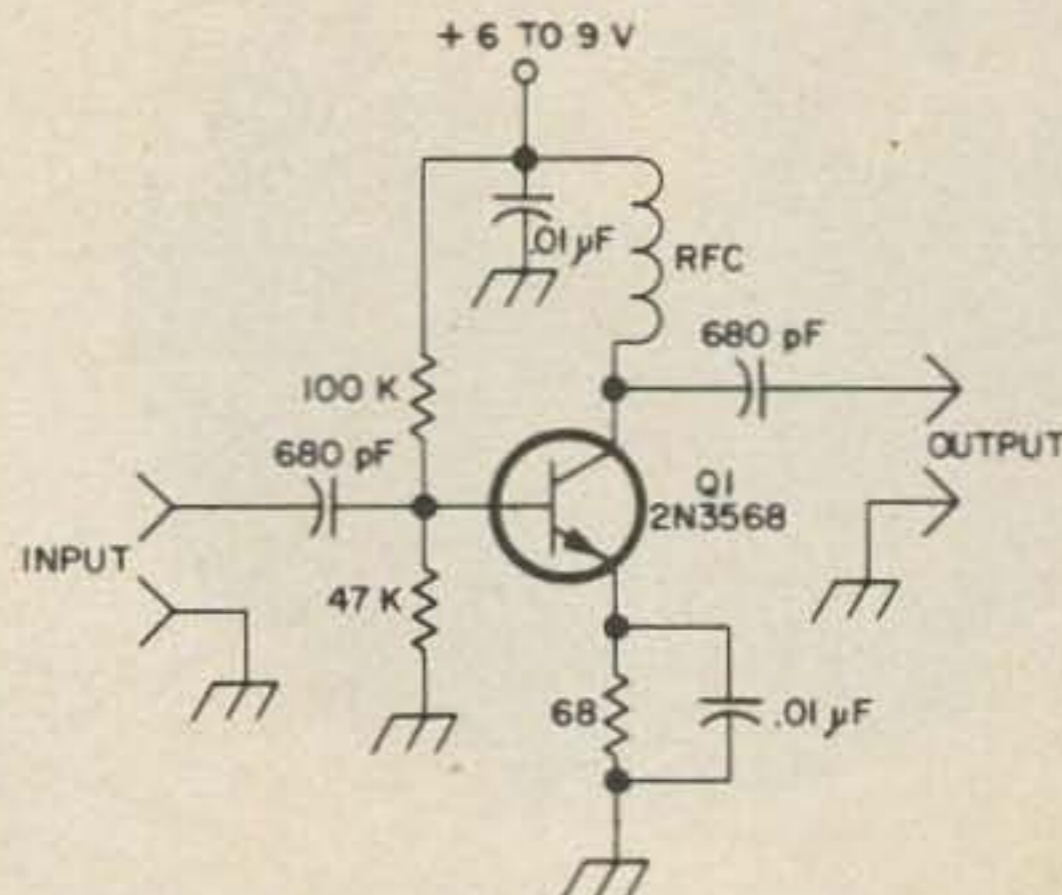


RF PREAMPLIFIER

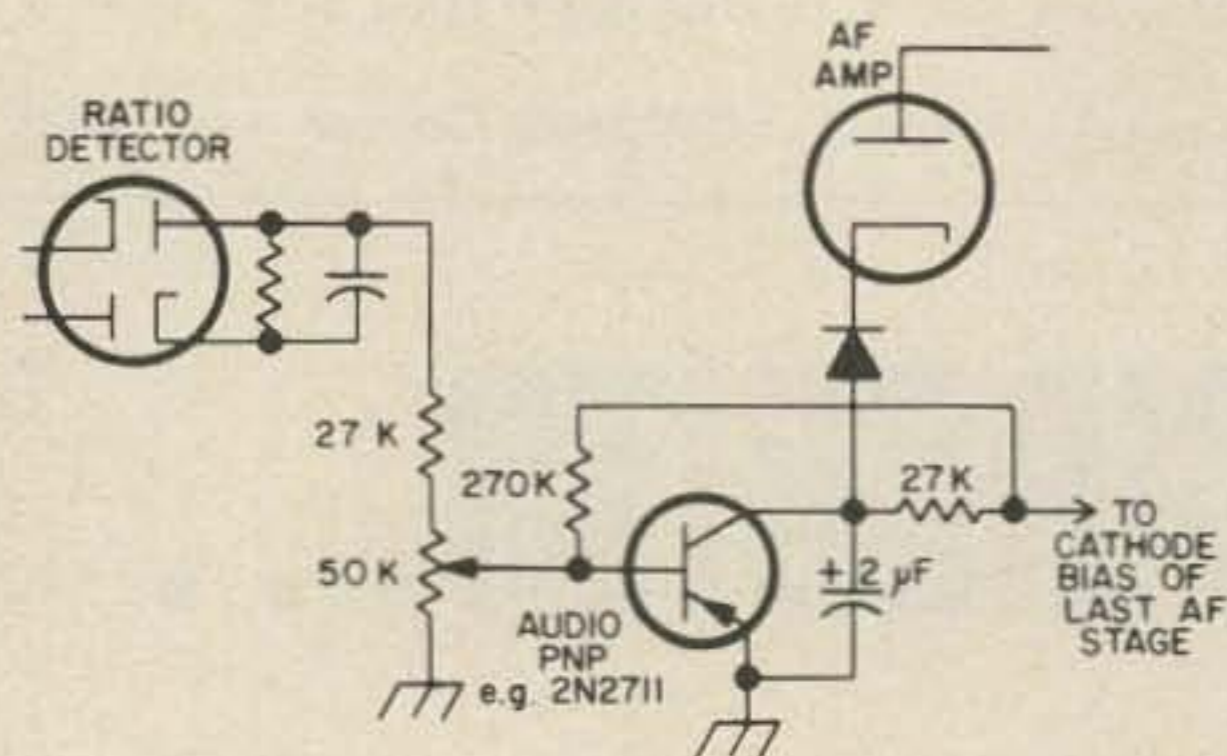This unit offers 12 - 15 dB gain on 10m, and about 20dB or more from 15m and down. All leads should be as short as possible. Building it on a PC board should give good results. Q1 can be any type of transistor. The Beta should be around 150+. f_t should be 60MHz or better. Thanks to Mark Chun KH6HPQ, for this circuit.



SIMPLE SQUELCH CIRCUIT

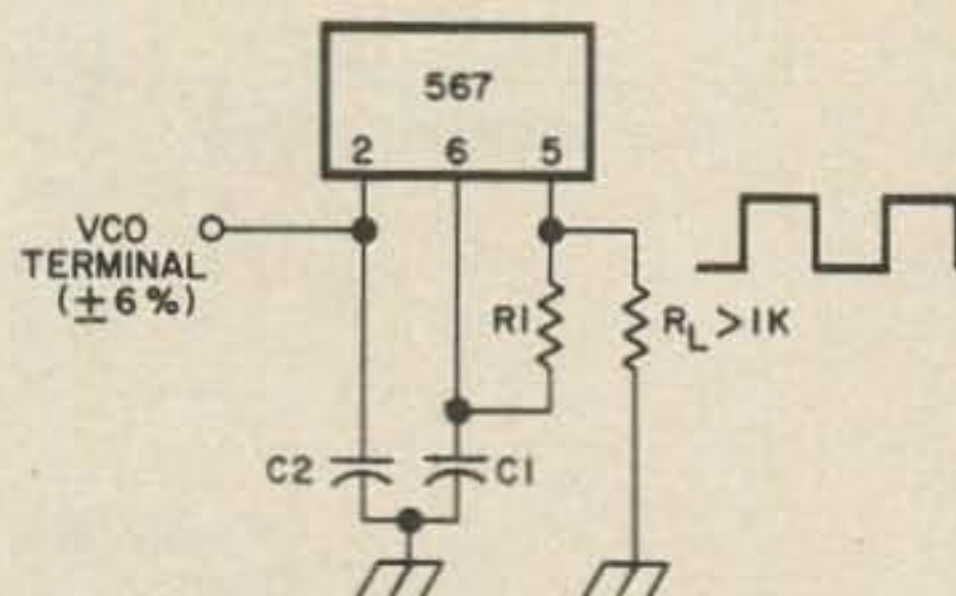
This circuit is for use with a tube FM receiver. The transistor acts as a switch to turn on the first audio stage. Parts not listed are in the receiver. Labeled parts are added. Thanks to Lael Nagurney WA3EEC/1, for this circuit.



PRECISION OSCILLATOR
with 20 nsec SWITCHING

Courtesy of Signetics Catalog

CIRCUITS...

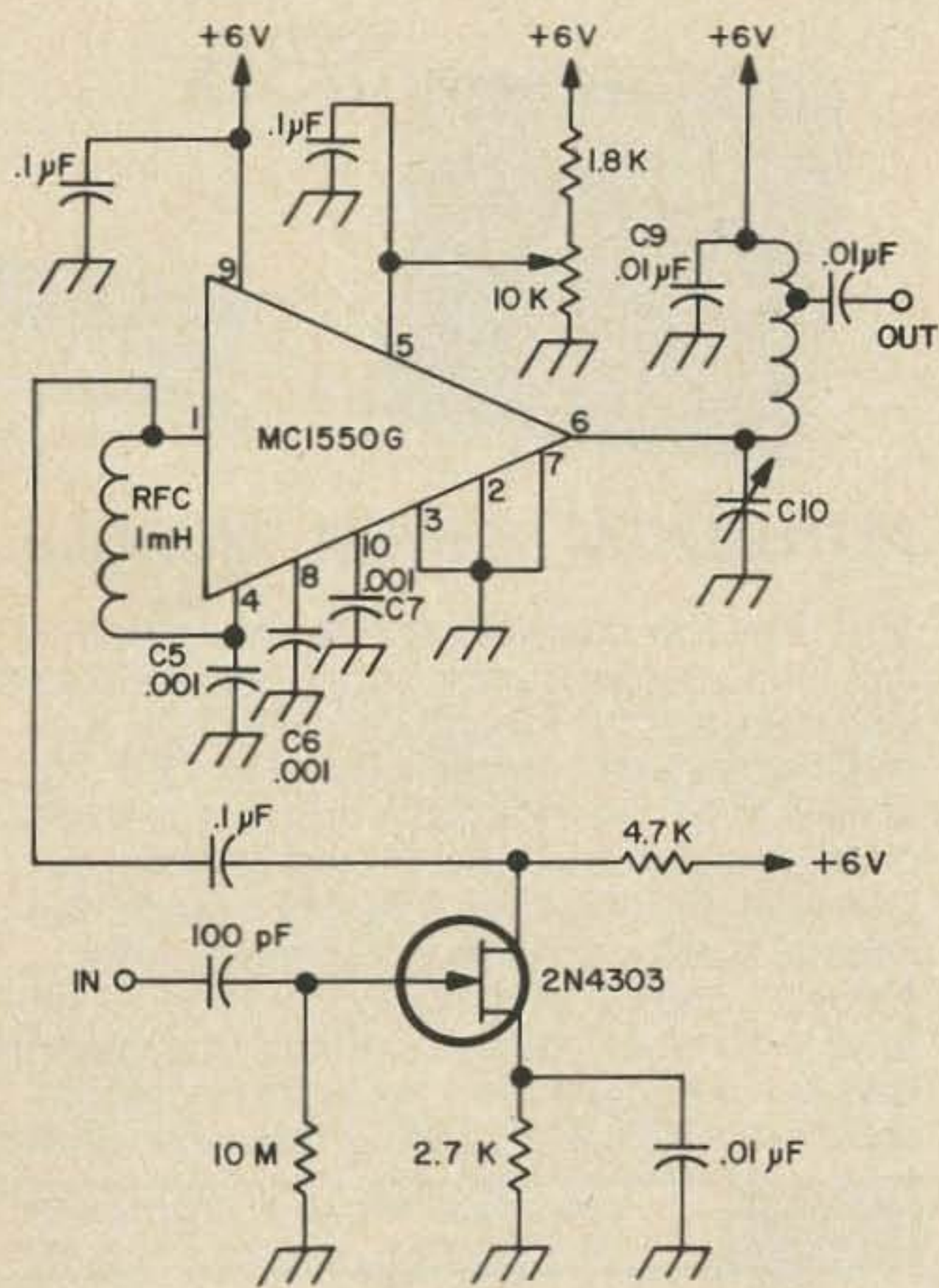

RINGO RANGER

4.5 db Gain (re 1/2 wave dipole)
6 db Gain (re 1/4 wave whip)

THIS IS AN EXTENDED MODEL
OF THE WORLD'S BEST
VHF FM ANTENNA

ARX-2 146-148 MHz \$22.50
ARX-450 435-450 MHz \$22.50
ARX-220 220-225 MHz \$22.50


Conversion Kit to make your
AR-2 into a Ranger
ARX-2K - \$8.95

IN STOCK AT YOUR
LOCAL DISTRIBUTOR

Cush
Craft
CORPORATION

621 HAYWARD STREET
MANCHESTER, N.H. 03103

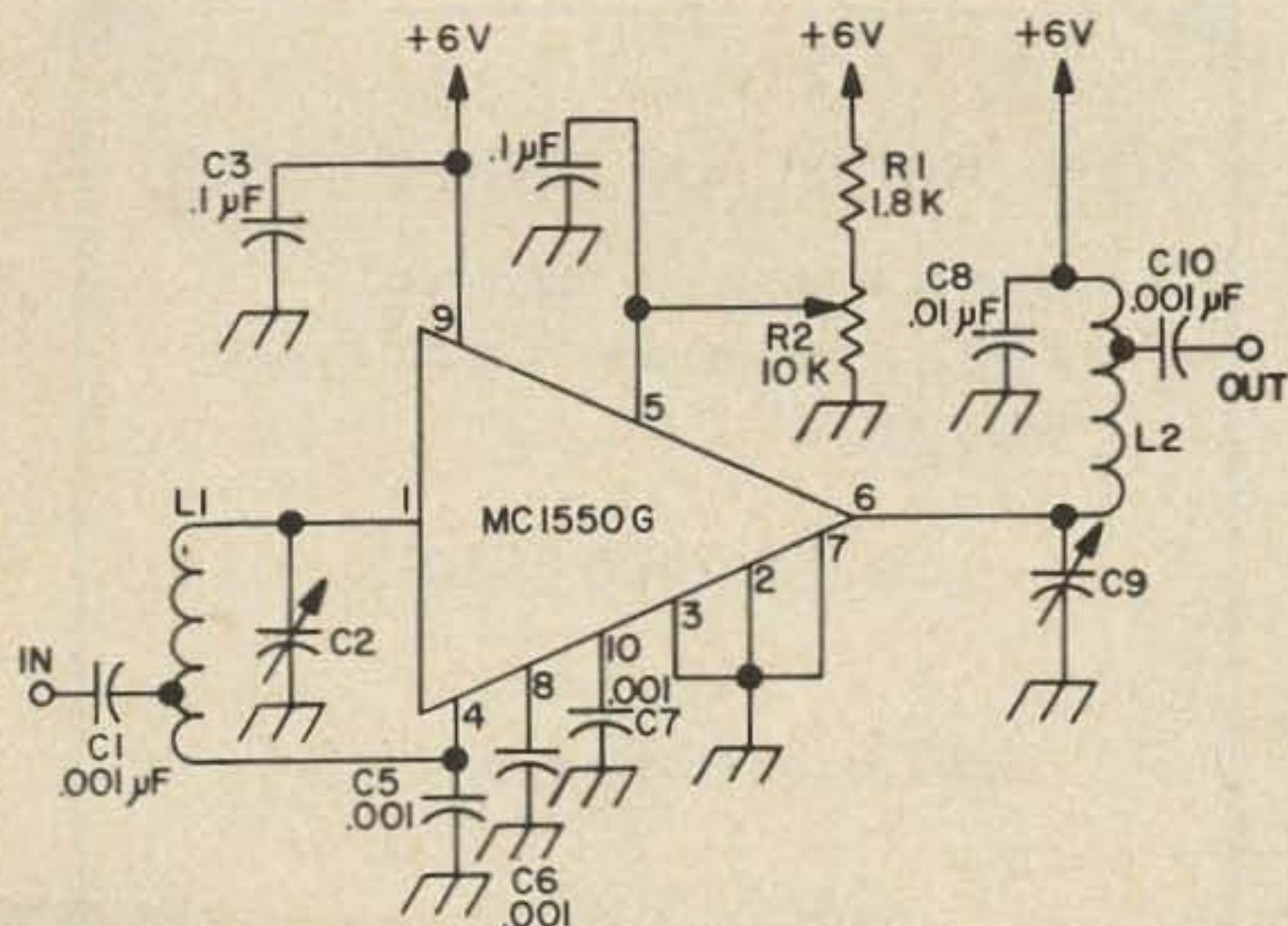
If you cannot install a good big receiving antenna, try this substitute. It adapts the very weak signal from a piece of wire, a lamp post, or a mattress to the common 50-ohm receiver input terminal.



This rf preamplifier is easily adapted to any range under 30 MHz simply by choosing appropriate input and output tuned circuits.

vhf uhf CONVERTERS

START
HEARING the
WEAK ONES

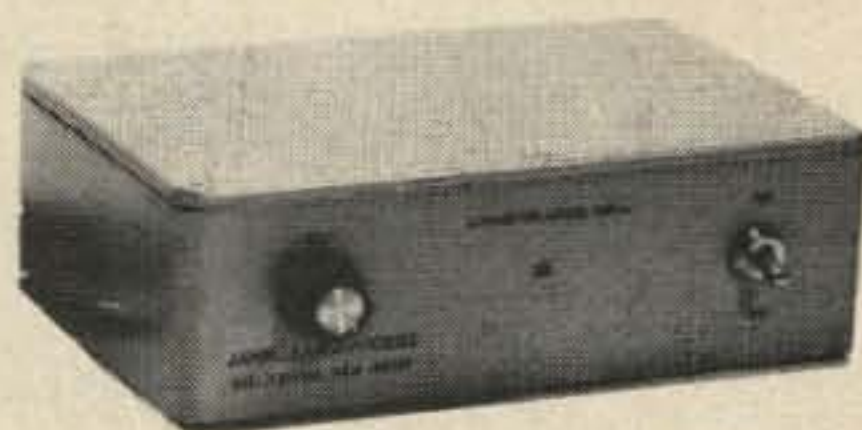

Very sensitive crystal controlled converters for receiving the VHF bands with your present receiver or transceiver. Ideal for DX, FM, Satellite reception or for just talking to the gang. All have built-in supplies for operation from either 117 VAC or 12 VDC. 10 Meter output is standard. Beautifully built and carefully tested with modern equipment.

50 CA, 50 - 52 MHz	\$85.00
144 CA, 144 - 148 MHz	\$85.00
220 CA, 220 - 225 MHz	\$85.00
432 CA, 432 - 436 MHz	\$85.00

JANEL can also supply a wide variety of receiving equipment for industrial applications. Write or call for details.

All items are postpaid and guaranteed. Please order direct or write for our free catalog.

ALSO - We stock a full line of sensitive PREAMPS!



JANEL laboratories

BOX 112, SUCCASUNNA, NJ 07876

Telephone: 201-584-6521

HERE IS A FIST FULL
of 2 METER POWER



NEW

American Made
Quality at Import Price

Model HRT-2 5 Channel, Narrow Band 2.2 watt FM Transceiver

This light weight, "take anywhere" transceiver has the "Regency-type" interior componentry to give you what others are looking for in portable communications. You get a heavyweight 2.2 watt signal . . . or if you want, flip the HI/LO switch to 1 watt and the receiver gives you 0.7 uv sensitivity and 0.5 watts audio. Both transmitter and receiver employ band-pass circuitry so that power and sensitivity are maintained across the entire band. Get one to go . . . only

\$179⁰⁰

Amateur Net

Regency ELECTRONICS, INC.
7707 Records Street
Indianapolis, Indiana 46226


An FM Model For Every Purpose . . .
Every Purse



HR-2MS
8 Channel Transcan
2 Meter FM Transceiver



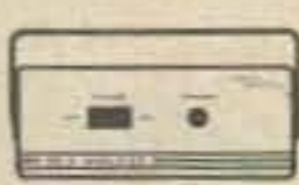HR-212
12 Channel-20 Watt
2 Meter FM Transceiver



AR-2
2 Meter FM
Power Amplifier

Key to the power squeeze.



AUTOMATIC KEYER MODULE

This new, low cost, two-ounce keyer module has full squeeze (iambic) operation yet draws less than one ma., key down! Attach 9v transistor battery and forget it! Great for QRP rigs. The AKM-25 has dot, dash and space memories for self-completion of code elements. Use with any key lever. This tiny module has internal sidetone monitor, transmitter spot function, 6 to 60 wpm speed, and keys + or - lines to common without external components. Use any 4 to 15vdc source. Write or call for brochure. (303)794-7234. Or see your dealer.

CSC

CONTROL SIGNAL COMPANY
5964 W. COLUMBIA PL., DENVER, COLORADO 80227

fantastic buy

1000 ROLLS OF VIDEO TAPE

AMERICAN MADE . . .
PRICED WAY BELOW
RETAIL

1/2" x 2400 FEET

Minimum Order 5 ROLLS

CALL NOW
313-449-4367

COMMUNICATIONS UNLIMITED

9519 MAIN STREET P.O. BOX 463
WHITMORE LAKE, MICHIGAN 48189

IT ONLY HAPPENS ONCE IN A LIFETIME!



NORELCO VIDEO TAPE RE-
CORDER-PLAYBACKS

- *WEIGHS ONLY 26 POUNDS
- *LONG LIFE FERITE HEADS
- *EXTREMELY QUIET
- *USES INEXPENSIVE 1/2" TAPE
- *HORIZ RESPONSE 2½ MHz
- *OPERATES FROM 110 VOLT AC.
- *SOME MODIFIED WITH LIGHT TO INDICATE UNIT IN USE.
- *STANDARD AUDIO-VISUAL SIGNALS

BRAND NEW, AS IS. . . \$399.00

ALSO, SHIBADEN FP-707 VIDICON CAMERA, WITH CRT VIEWFINDER AND LENSES 12 VOLT D.C. REQUIRED AND EXTERNAL SYNC. . . NEW COST \$750.00, NOW **\$325.00**

AC POWER SUPPLY AND SYNC GENERATOR FOR THE ABOVE. . . NEW: **\$65.00**

HUNDREDS OF ADDITIONAL VIDEO ITEMS, WRITE FOR LIST, SASE

COMMUNICATIONS UNLIMITED

9519 MAIN STREET P.O. BOX 463
WHITMORE LAKE, MICHIGAN 48189

Store hours, noon to 6PM, Monday thru Saturday. (313-449-4367)

tape

*YOUR FAVORITE TV
SHOWS. . . .*



build

*AN INEXPENSIVE
LIBRARY OF THE TV
SHOWS YOU LIKE BEST. . .*

INTERNATIONAL ELECTRONICS UNLIMITED

DIGITAL INTEGRATED CIRCUITS

7400	\$.25	7447	\$1.45	74123	\$1.15
7401	.25	7448	1.50	74125	.69
7402	.25	7450	.29	74126	.95
7403	.25	7451	.32	74141	1.25
7404	.29	7453	.32	74145	1.25
7405	.27	7454	.45	74150	1.25
7406	.55	7455	.32	74151	1.05
7407	.53	7460	.30	74153	1.45
7408	.29	7461	.30	74154	1.75
7409	.29	7464	.45	74155	1.35
7410	.25	7465	.45	74156	1.50
7411	.35	7470	.50	74157	1.50
7413	.95	7472	.45	74161	1.65
7415	.50	7473	.55	74163	1.80
7416	.50	7474	.55	74164	2.95
7417	.50	7475	.95	74165	2.95
7420	.25	7476	.55	74166	1.95
7421	.32	7478	.89	74173	1.95
7422	.32	7483	1.25	74175	1.95
7423	.37	7485	1.20	74176	.95
7425	.39	7486	.55	74177	.95
7426	.35	7489	3.25	74180	1.15
7427	.39	7490	1.25	74181	4.25
7430	.25	7491	1.40	74182	1.10
7432	.30	7492	1.05	74190	1.65
7437	.50	7493	1.05	74192	1.65
7438	.55	7494	1.10	74193	1.65
7440	.25	7495	1.05	74194	1.65
7441	1.25	7496	1.05	74195	1.15
7442	1.15	74100	1.65	74196	1.35
7443	1.25	74105	.55	74197	1.15
7444	1.30	74107	.55	74198	2.50
7445	1.25	74121	.65	74199	2.50
7446	1.45	74122	.55		

Low Power TTL

74L00	\$.40	74L51	\$.40	74L90	\$1.75
74L02	.40	74L55	.60	74L91	1.50
74L03	.40	74L71	.60	74L93	1.75
74L04	.40	74L72	.60	74L95	1.75
74L06	.40	74L73	.80	74L164	2.95
74L10	.40	74L74	.80	74L165	2.95
74L20	.40	74L78	.80	85L52	2.95
74L30	.40	74L85	1.25	86L75	2.95
74L42	1.75	74L86	.95		

High Speed TTL

74H00	\$.40	74H21	\$.47	74H60	\$.45
74H01	.40	74H22	.47	74H61	.45
74H02	.40	74H30	.40	74H62	.45
74H04	.45	74H40	.40	74H72	.60
74H08	.45	74H50	.45	74H74	.70
74H10	.40	74H53	.47	74H76	.70
74H20	.40	74H55	.47		

8000 Series TTL

8504	\$.45	8200	\$2.95	8554	\$2.95
8060	.30	8210	3.95	8750	2.95
8091	.69	8214	1.95	8600	1.15
8092	.69	8219	1.95	8810	.95
8093	.69	8220	1.95	8812	1.25
8094	.69	8280	.95	8830	.69
8121	1.05	8288	1.75	8831	2.95
8122	1.05	8520	1.45	8832	2.95
8123	1.75	8551	1.95	8836	.69
8130	2.50	8552	2.95	8830	1.50
8182	1.75				

Please specify which data sheets are required with order. Add \$.50 per data sheet for items priced less than \$1.00 ea. All of above are Dual-In-Line packages.

CMOS

74C00	\$.85	74C76	\$1.70	74C163	\$3.25
74C02	.85	74C107	1.50	74C164	3.50
74C04	.95	74C151	2.90	74C173	2.90
74C10	.85	74C154	3.50	74C192	3.25
74C20	.85	74C157	2.25	74C193	3.25
74C42	2.15	74C160	3.30	74C195	3.00
74C73	1.70	74C161	3.25	80C97	1.50
74C74	1.50	74C162	3.25		

Specify Specs required with order.

4000 Series - RCA Equivalent

CD4001	\$.65	CD4012	\$.65	CD4022	\$2.75
CD4002	.65	CD4013	1.50	CD4023	.65
CD4009	1.00	CD4016	1.50	CD4025	.65
CD4010	.65	CD4017	2.95	CD4027	1.35
CD4011	.65	CD4019	1.35	CD4030	.65
				CD4035	2.85

MEMORIES

1101	256 bit RAM MOS (2501)	\$2.50 ea.
1103	1024 bit RAM MOS	7.50 ea.
5260	1024 bit RAM 16 pin	
	Low power consumption	6.95 ea.
7489	64 bit RAM TTL	3.25 ea.
8223	Programmable ROM	6.50 ea.

JUNE SPECIALS

LED

MAN.3M type			3 or more \$1.25
MAN 5 type Green 7 segment	\$4.75 ea.	4/\$15.75	
MAN 7 type (SLA-1) Red 7 segment	\$2.50 ea.	4/\$7.95	
MAN 8 type Yellow 7 segment	\$5.50 ea.	4/\$18.95	

CMOS

74C00	\$.55 ea.	74C20	\$.65 ea.
74C02	.65 ea.	74C42	1.75 ea.
74C04	.75 ea.	74C73	1.25 ea.
74C10	.65 ea.	74C107	.99 ea.

18-PIN CALCULATOR KIT

- MM5736 - 18 pin calculator chip - four function - 6 digit
- MM5736 - 18 pin calculator - four function - 6 digit
- A pair of 3-in-1 dip paks (6 digits) LED similar to DL-33
- One 75492 Hex Digit Driver

Data supplied on above items. You supply switches, resistor, keyboard and battery for complete calculator. \$11.95/kid

8038 Volt controlled oscillator	DIP	\$7.95 ea.
555 Timer	MINI-DIP	1.15 ea.
7489 64 bit RAM TTL	DIP	2.75 ea.

CALCULATOR CHIPS

- 5001 LSI (40 pin) Add, subtract, multiply & divide 12 digit
- Data supplied with chip \$6.95 ea.
Data only - Refundable w/purchase 1.00 ea.
- 5002 LSI Similar to 5001 except designed for battery power
- Data supplied with chip \$8.95 ea.
Data only - Refundable w/purchase 1.00 ea.
- 5005 LSI (28 pin) Full four function memory. 12 digit display and calc. 7 segment multiplexed output
- Data supplied with chip \$10.95
Data only - Refundable w/purchase 1.00 ea.

DIGITAL CLOCK CHIPS

- MM 5311 (28 pin) Any readout 6 digit BCD with spec. sheet \$11.95 ea.
- MM 5312 (24 pin) Any readout 4 digit 1 pps BCD with spec. sheet 8.95 ea.
- MM 5313 (28 pin) Any readout 6 digit 1 pps BCD with spec. sheet 10.95 ea.
- MM 5314 (24 pin) LED-incandescent readout 6 digit with spec. sheet 10.95 ea.
- MM 5316 (40 pin) Normal alarm, snooze alarm, sleep timer 12 or 24 hr. operation with spec. sheet 15.95 ea.

LED

- MV108 Visible red SUPER SPECIAL \$.25 ea.
- MV50 type red emitting25 ea. 5/\$1.00
- MV5020 type large red35 ea. 3/\$1.00
- AE 4 Infra red TO1869 ea.
- MAN 1 The original 3.95 ea.
- MAN 3 type 1.95 ea. 3 or more 1.49 ea.
- MAN 4 type 2.75 ea. 3 or more 2.50 ea.
- Data-Lite 707 (MAN 1 repl) 3.25 ea.

OPTO ISOLATORS

MCA 2-30 Darlingtr		\$.95 ea.
MCD 2 Diodes		1.95 ea.
MCT 2 Transistor		1.45 ea.

UNTESTED IC's

- MOS Shift Registers 2500 Series
2502 2506 2509 2510 2511 2518 2519 2521 2522
- Untested seconds 4/1.00
- Grab Bag Specials
15 Assorted TTL's (dips) \$1.00/bag
25 Assorted DTL's (dips) \$1.00/bag

LINEAR INTEGRATED CIRCUITS

- 300 Pos V Reg (super 723) TO-5 \$.95 ea.
- 301 Hi performance AMPL MINI-DIP .45 ea.
- 302 Voltage Follower TO-5 .95 ea.
- 304 Negative Voltage Regulator TO-5 1.25 ea.
- 305 Positive Voltage Regulator TO-5 1.25 ea.
- 307 Op AMP (super 741) MINI-DIP .45 ea.
- 308 Micro-Power Op Amp MINI-DIP 1.25 ea.
- 309H 5 V Regulator TO-5 1.25 ea.
- 309K 5 V 1A Regulator TO-3 1.95 ea.
- 310 Voltage Follower Op Amp TO-5 1.45 ea.
- 311 Hi perf. Voltage Comparator MINI-DIP 1.25 ea.
- 319 Hi Speed Dual Comparator DIP 1.65 ea.
- 320 -5.2 V Negative Regulator TO-3 1.95 ea.
- 320 -12 V Negative Regulator TO-3 1.95 ea.
- 320 -15 V Negative Regulator TO-3 1.95 ea.
- 324 Quad Op Amp DIP \$2.25 ea.
- 339 Quad Comparator DIP 2.50 ea.
- 340T Positive Voltage Regulator (6V, 8V, 15V or 24V) TO-220 2.25 ea.
- 370 AGC/Squelch AMPL TO-5 or DIP 1.29 ea.
- 372 AF-IF Strip-detector DIP .85 ea.
- 373 AM/FM/SSB Strip DIP 3.60 ea.
- 376 Pos. Volt Regulator MINI-DIP .65 ea.
- 377 2W Stereo amp DIP 2.75 ea.
- 380 2 Watt Audio Regulator DIP 1.75 ea.
- 380-8 8W Audio amp MINI-DIP 1.75 ea.
- 382 Low Noise Dual Pre-Amp DIP 2.25 ea.
- 550 Precision Voltage Regulator DIP .95 ea.
- 703 RF-IF Amp MINI-DIP .59 ea.
- 709 Operational AMPL TO-5 or DIP .39 ea.
- 711 Dual Differential Comparator DIP .39 ea.
- 723 Voltage Regulator DIP .75 ea.
- 739 Dual Hi Perf. Op AMP DIP 1.25 ea.
- 741 Comp. Op AMP MINI-DIP .45 ea.
- 747 Dual 741 Op AMP TO-5 or DIP .95 ea.
- 748 Freq Adj 741 MINI-DIP .45 ea.
- 1303 Stereo Pre-Amp DIP .95 ea.
- 1304 FM Multiplex Stereo Demod. DIP 1.50 ea.
- 1307 FM Multiplex Stereo Demod. DIP .95 ea.
- 1458 Dual Comp. Op. Amp. MINI-DIP .75 ea.
- 2111 Dual LM211 Volt. Comp. DIP 2.95 ea.
- 30x5 TV-FM Sound System DIP .75 ea.
- 3075 FM Det. - LMT and Audio Pre-Amp. DIP .85 ea.
- 3900 Quad Amplifier DIP .75 ea.
- 3905 Precision Timer MINI-DIP .75 ea.
- 7524 Core Memory Sense AMPL DIP 1.95 ea.
- 7525 Core Memory Sense AMPL DIP .95 ea.
- 7534 Core memorysense amp DIP 2.75 ea.
- 7535 Core memory sense amp DIP 1.25 ea.
- 9601 Retriggerable One Shot DIP .95 ea.
- 75451 Dual Peripheral Driver MINI-DIP .49 ea.
- 75452 Dual Peripheral Driver MINI-DIP .49 ea.
- 75453 (351) Dual Peripheral Driver MINI-DIP .69 ea.
- 75491 Quad seg. driver for LED readout DIP 1.60 ea.
- 75492 Hex digit driver DIP 1.75 ea.

Please specify which data sheets are required with order. Add \$.50 per data sheet for items priced less than \$1.00 each

PHASE LOCKED LOOPS

- | | | |
|------------------------|----------|----------|
| 560 Phase Locked Loop | DIP | 2.95 ea. |
| 561 Phase Locked Loop | DIP | 2.95 ea. |
| 562 Phase Locked Loop | DIP | 2.95 ea. |
| 565 Phase Locked Loop | DIP | 2.95 ea. |
| 566 Function Generator | MINI-DIP | 2.95 ea. |
| 567 Tone Generator | MINI-DIP | 2.95 ea. |

ON ORDERS OVER \$25.00 DEDUCT 10%

All items are new, unused surplus parts - tested functional. Satisfaction is guaranteed. Shipment will be made via first class mail-postage paid-in U.S., Canada and Mexico within three days from receipt of order. Minimum order-\$5.00. California residents add sales tax.

INTERNATIONAL ELECTRONICS UNLIMITED
P. O. Box 1708, Monterey, Calif. 93940 USA

GODBOUT

JUNE SPECIAL

BILL GODBOUT ELECTRONICS

BOX 2673, OAKLAND AIRPORT, CA 94614

Adjustable dual tracking regulated power supply parts kit. Output $\pm 1v$ to greater than $\pm 17v$. Regulation better than 0.5%. Output current up to 215 mA back side. Kit includes line filter and internally shielded transformer to provide excellent rf and line noise rejection. Output is short-circuit protected. For June only — \$9.95. Orders placed after June 30 — \$10.95

- TTL SPECIAL 9601 Monostable — \$.65. 9602 Dual Monostable — \$.90
- DTL SPECIAL Type 988 Monostable similar to 74121 4/\$1.00
- LINEAR SPECIAL "Dime Op—Amp" is here — dual 709 DIP . 5/\$1.00
- MOS DYNAMIC MEMORY 1 x 1024 bit MM5260 \$5.00
- 12 Volt Power Supply \$17.95
- LM 309K 5V 1A REG \$2.00
- LM 320K NEG Reg available in 5V 12V & 15V \$2.25
- LM 340K POS Reg available in 6V, 8V, 12V, 15V, 24V \$2.25
- 4194 TK adjustable dual tracking reg TO66 \$3.90
- 4195 TK dual tracking reg $\pm 15V$ TO66 \$3.40
- SUPER MEMORY Static N MOS 1 x 1024 bit. Runs on single 5 Volt supply, with data sheet, type 2102 \$16.50
- 8008 PROCESSOR 8 bit on a chip \$50.00

CMOS DIGITAL *ICs, most TTL & LINEAR in stock — Send stamp for FREE catalog*

74C00	.60	CD4011	.60	CD4042	2.95	741M	.45
74C02	.60	CD4012	.60	CD4044	2.95	741T	.50
74C04	.85	CD4013	1.25	CD4049	1.25	741 Mini	.45
74C10	.60	CD4014	4.00	CD4050	1.25	747D	.90
74C20	.60	CD4015	4.00	CD4116	1.50	748M	.65
74C73	1.65	CD4016	1.25	LINEAR		1595	1.50
74C74	1.25	CD4017	3.20	LM318	1.75	1596	1.75
74C76	1.75	CD4018	5.00	LM339	2.00	3900	.75
74C107	1.75	CD4019	1.35	LM370	1.25	4136	4/2.00
74C151	3.30	CD4020	5.50	LM371	1.25	4250T	2.25
74C160	3.25	CD4021	4.00	LM372	1.25	CA3028	.75
74C161	3.25	CD4023	.60	LM374	2.00	CA3065	.75
74C162	3.25	CD4024	3.00	LM380	1.75	CA3086	.45
74C163	3.25	CD4025	.60	LM381	2.00	5558	.90
74C195	3.15	CD4027	1.75	LM382	1.75		
CD4001	.60	CD4029	6.00	555	1.00		
CD4002	.60	CD4030	1.20	556	1.60		
CD4008	4.00	CD4035	2.95	723T	.95		
CD4009	.95	CD4037	2.95	723D	.75		
CD4010	.95	CD4040	5.00				

ALL ITEMS IN STOCK and will be shipped within 24 working hours of receipt of order!

Include 50¢ postage and handling on orders under \$10.00

Sorry, NO C.O.D.'s. CALIFORNIA RESIDENTS ADD sales tax.

The most powerful signals under the sun!



hy-gain

Redesigned

HAMCAT


Out-hustles them all!

The famous HAMCAT... now redesigned for greater performance...*equals* or *exceeds* the performance of any other Amateur Mobile antenna. *We guarantee it!* And you need buy only one mast...whether you mount it on fender, deck or bumper. There's just one set of coils and tip rods...and they all stand up to maximum legal power. That's performance, that's value...*THAT'S HY-GAIN!*

Original Hy-Q "quick changer" coils wound on tough fiberglass coil forms for greater heat resistance, less RF absorption / Fiberglass shielded coils can't burn up, impervious to weather / Shake-proof, rattle-proof, positive lock hinge now even stronger...eliminates radio noise / All stainless steel tip rods won't bend or break / Full 5' mast gives you 10% more radiating area than the competition / Rugged swivel-lock stainless steel base for quick band changes, easy garaging.

Get the Hamcat...from Hy-Gain

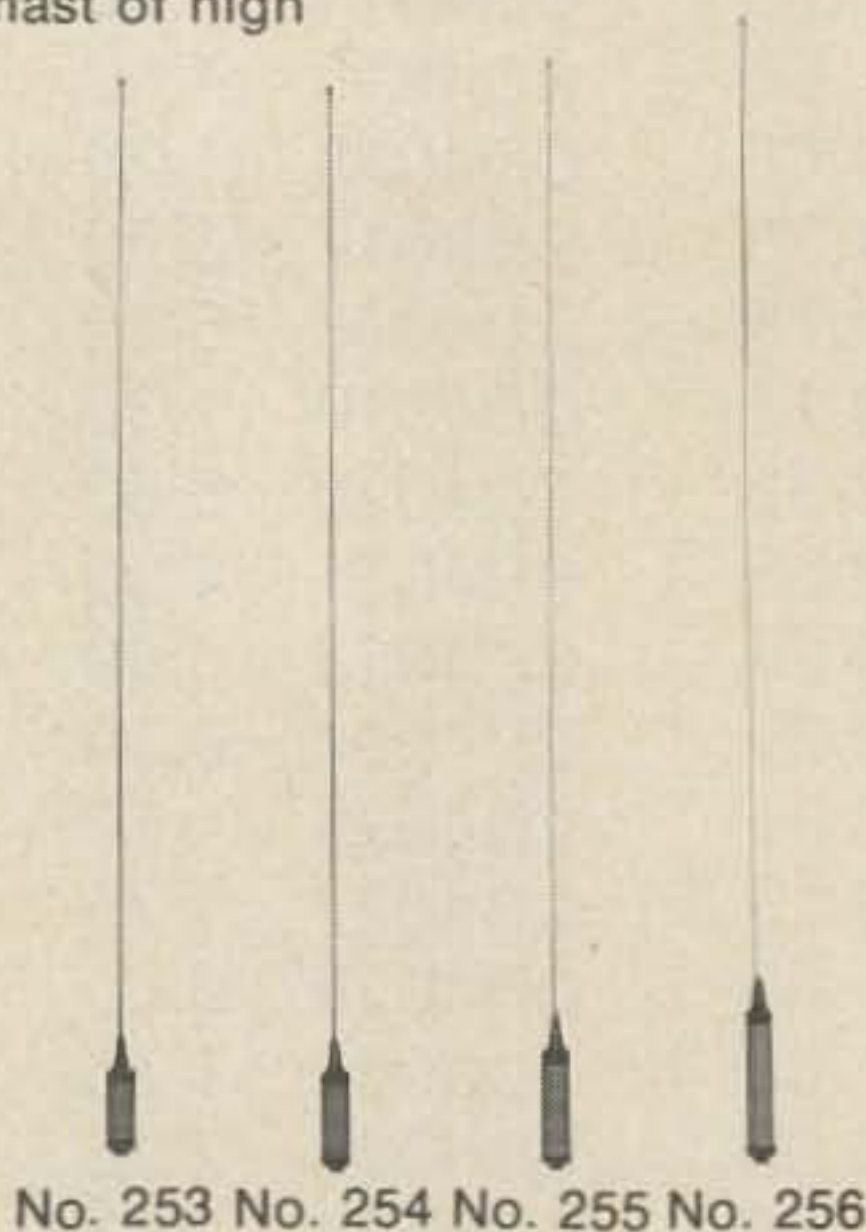- Order No. 257 All new design 5' long heavy duty mast of high strength heavy wall tubing **\$18.95**
- Order No. 252 75 meter mobile coil **\$24.95**
- Order No. 256 40 meter mobile coil **\$19.95**
- Order No. 255 20 meter mobile coil **\$16.95**
- Order No. 254 15 meter mobile coil **\$14.95**
- Order No. 253 10 meter mobile coil **\$12.95**
- Order No. 499 Flush body mount **\$ 9.95**




HY-GAIN ELECTRONICS CORPORATION

8601 Northeast Highway Six
402/434-9151

Lincoln, NE 68507
Telex 48-6424


The most popular three
band beam in the world!

hy-gain TH3Mk3

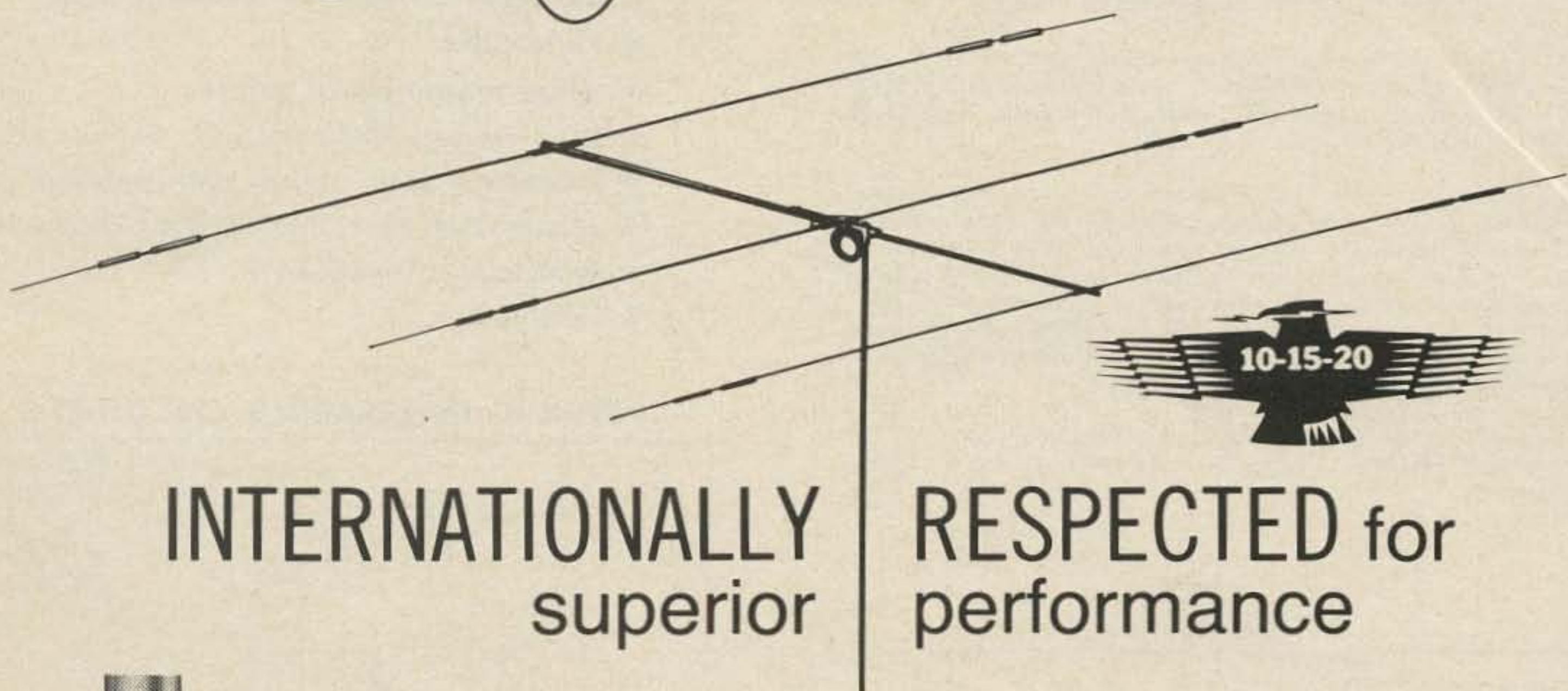

INTERNATIONALLY
superior

RESPECTED for
performance

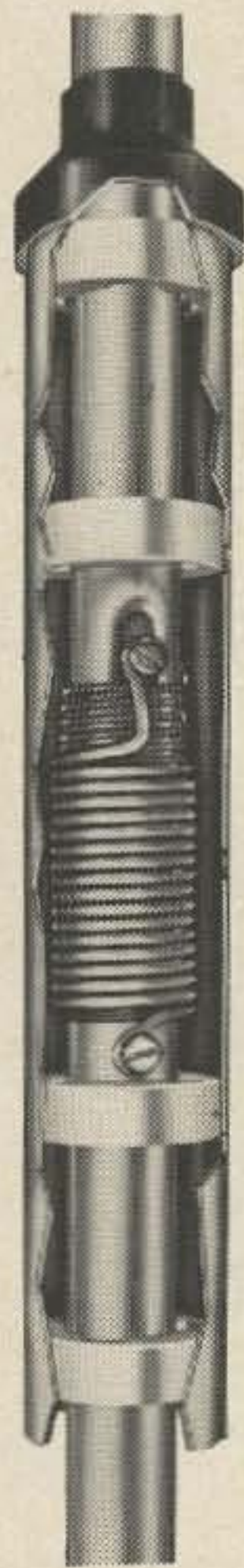

Superior construction and performance make the difference in Hy-Gain's popular 3-element Thunderbird.

- Thunderbird's "Hy-Q" traps provide separate traps for each band. "Hy-Q" traps are electronically tuned at the factory to perform better at any frequency in the band—either phone or CW. And you can tune the antenna, using charts supplied in the manual, to substantially outperform any other antennas made.
- Thunderbird's superior construction includes a new, cast aluminum, tilt-head universal boom-to-mast bracket that accommodates masts from 1¼" to 2½". Allows easy tilting for installation, maintenance and tuning and provides mast feed-thru for beam stacking.

Taper swaged, slotted tubing on all elements allows easy adjustment and re-adjustment. Taper swaged to permit larger diameter tubing where it counts! And less wind loading. Full circumference compression clamps are mechanically and electrically superior to self-tapping metal screws.

- Thunderbird's exclusive Beta Match achieves balanced input, optimum matching on all 3 bands and provides DC ground to eliminate precipitation static.
- Up to 8 db gain
- 25 db front to back ratio
- Power capability 1Kw AM, 2Kw PEP
- SWR less than 2:1
- Extra heavy gauge, machine formed, element to boom brackets with plastic sleeves used only for insulation. Bracket design allows full mechanical support.

Model 388 \$169.95

Other tri-band beams to choose from:

- | | |
|--------------------------------------|---------------------------|
| • 6-element Super Thunderbird TH6DXX | Model 389 \$199.95 |
| • 3-element Thunderbird Jr. TH3JR | Model 221 \$119.95 |
| • 2-element Thunderbird TH2Mk3 | Model 390 \$109.95 |

AVAILABLE FROM AMATEUR DEALERS THROUGHOUT THE WORLD



ELECTRONICS CORPORATION

8601 Northeast Highway Six
402/464-9151

Lincoln, NE 68507
Telex 48-6424

Distributed in Canada by: LECTRON RADIO SALES, LTD. 211 Hunter Street West, Peterborough, Ontario

NOW AVAILABLE FROM SOLID STATE SYSTEMS, INC. LOW-COST FIELD EFFECT TRANSMISSIVE AND/OR REFLECTIVE LIQUID CRYSTAL AC DISPLAY

DESCRIPTION


Only one liquid crystal display provides excellent contrast and readability in diffused light: FELIX. Field Effect Liquid Crystal from Ilixco.

FELIX liquid crystal displays produce superior optical properties than other liquid crystal systems because of their bi-level characteristic. The Felix display system has two distinct optical states, so that display segments are fully off at 3 volts and completely on at 7 volts.

Bi-level refers to the two levels of optical activity present in specially organized liquid crystals. In the quiescent state, the level is referred to as a 90° rotation of the plane of polarized light. That is, when a liquid crystal organized in this manner is inserted between a polarizer and an analyzer which are parallel, the light transmission will be at a minimum. The other level of the bi-level system is zero degrees rotation of the plane of polarized light, which occurs upon the application of a well defined voltage, giving maximum transmission.

Extremely low voltage threshold provides full compatibility with TTL and MOS devices. The power consumption of the ON segment is less than 1/2 microwatt.

DIMENSIONS

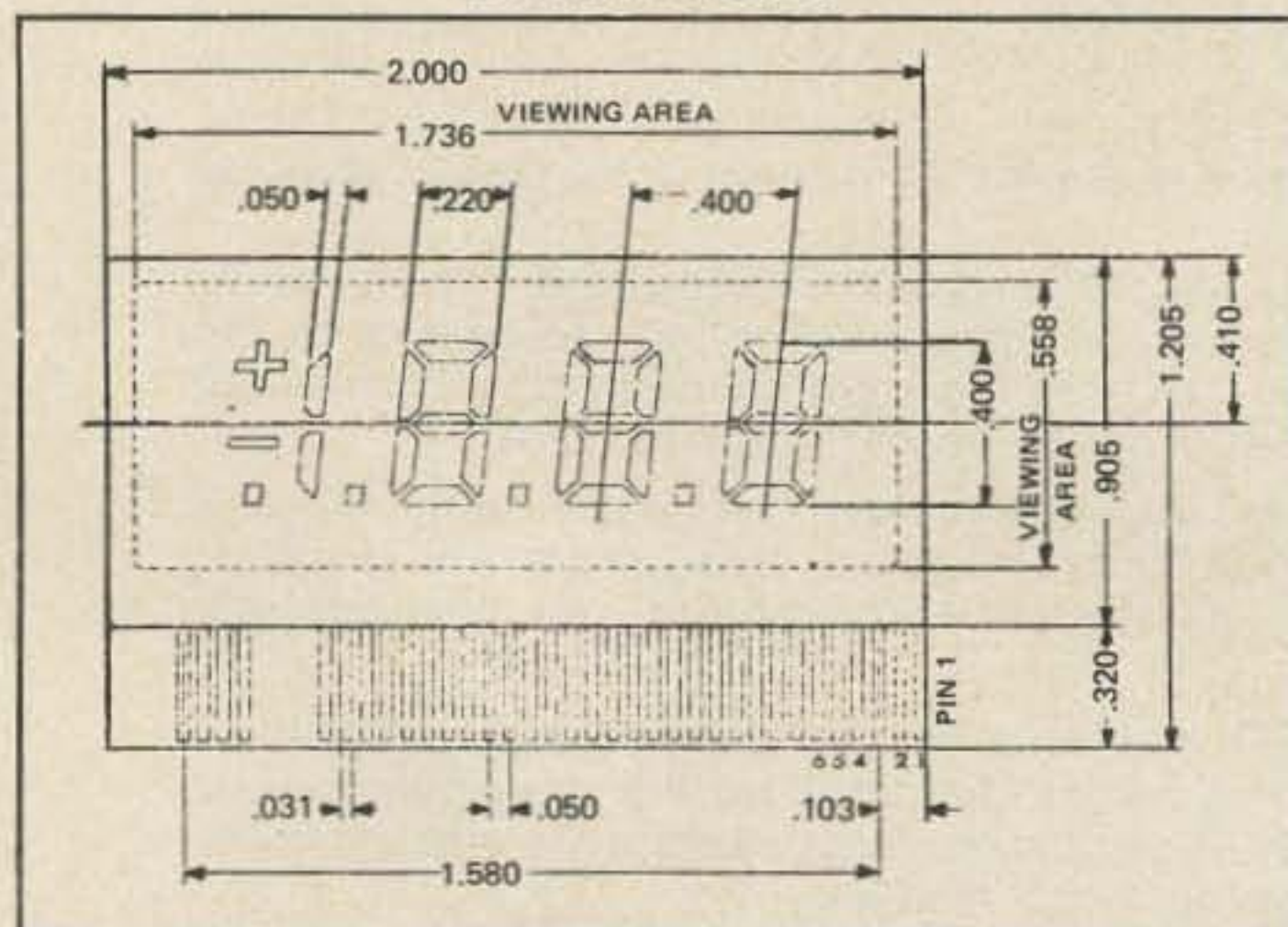

ASSEMBLED COUNTING BOARDS

Completely assembled and tested counting board, consisting of above display and connector, three decade to 7-segment decoder (7448), seven AC pulse drive generators (7486), and tin plated glass-epoxy PC board with edge connector pattern is available as part number 94-06051.


PRICES

Catalog Number	Description	1-4	5-9	10-24	25 Up
94-06051	Complete Assembly	15.50	14.50	13.50	12.50
84-06051	Display & Connector Only	9.75	9.00	8.25	7.50

FEATURES

- ★ Excellent contrast in ambient light
- ★ Field effect
- ★ Wide temperature range
- ★ Low voltage operation (7 volts)
- ★ Extremely low power consumption
- ★ Transmitted or reflected light displays
- ★ Operates 60-10 KHz
- ★ Plugable

TYPICAL INTERFACING CIRCUITRY

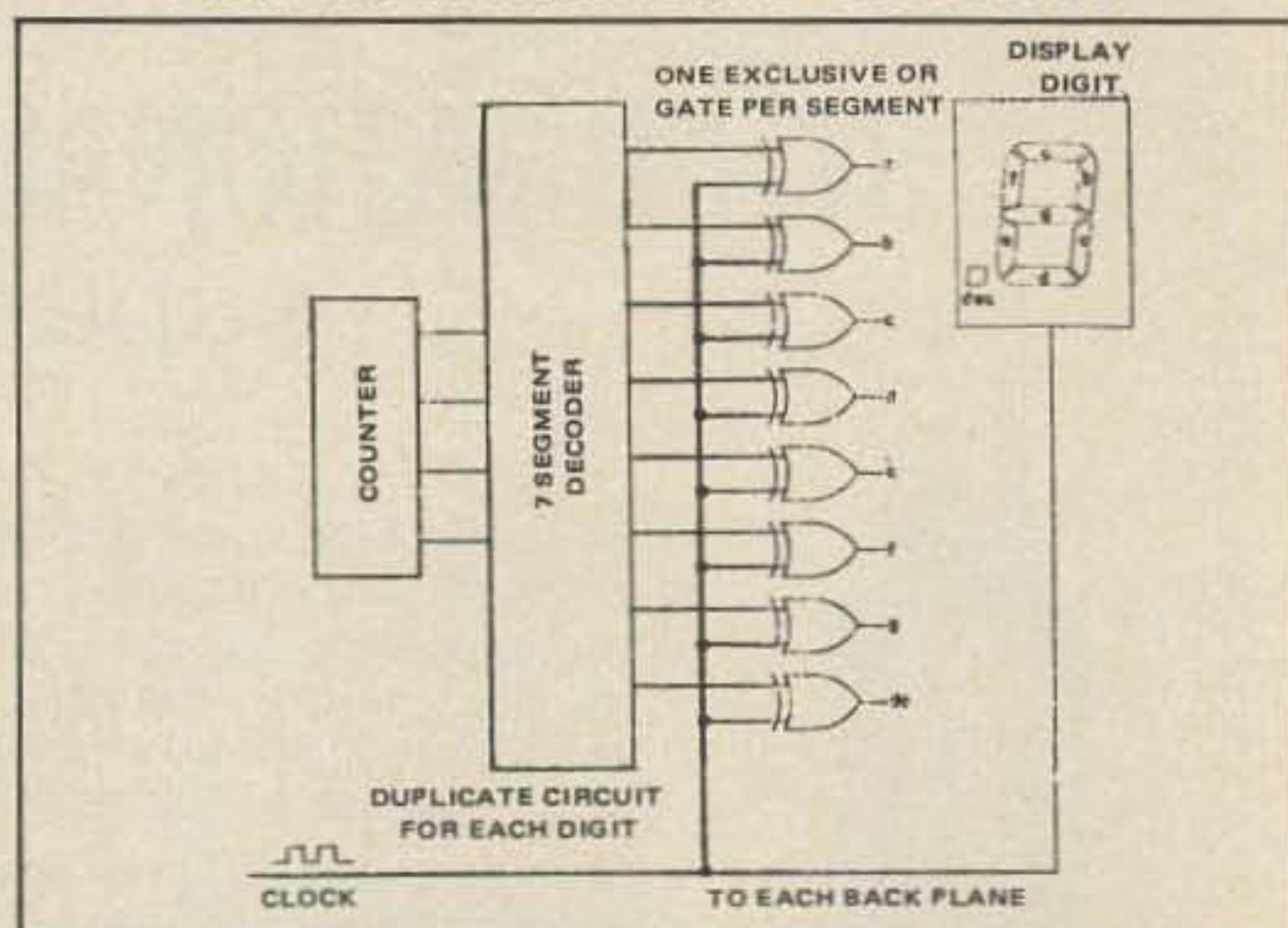


PIN CONNECTIONS

PIN	SEGMENT	PIN	SEGMENT
1.	---	21.	b
2.	---	22.	g
3.	b	23.	c
4.	g	24.	d
5.	c	25.	B.P.
6.	d	26.	e
7.	B.P.	27.	f
8.	e	28.	a
9.	f	29.	DEC.
10.	a	30.	1
11.	DEC.	31.	DEC.
12.	b	32.	-
13.	g	33.	+
14.	c	34.	B.P.
15.	d	35.	---
16.	B.P.	36.	---
17.	e	37.	---
18.	f	38.	---
19.	a	39.	---
20.	DEC.	40.	---

SEND YOUR ORDER TO:

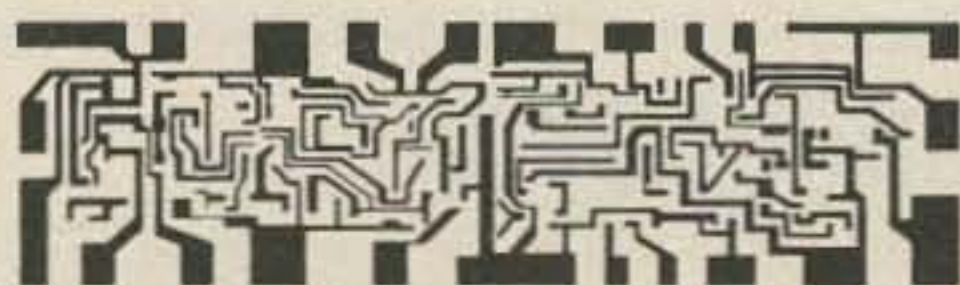SOLID STATE SYSTEMS, INC.
P. O. BOX 617
COLUMBIA, MISSOURI 65201



SOLID STATE SYSTEMS, INC.

OR PHONE (TOLL FREE):

800-325-2595 & 800-325-2981

RGS ELECTRONICS

7400 S	.25	7440	.25	7496	1.00
7401	.25	7442	1.10	74107	.60
7402	.25	7446	1.45	74121	.60
7403	.25	7447	1.45	74122	.60
7404	.30	7448	1.45	74123	1.10
7405	.30	7450	.25	74125	.65
7406	.50	7451	.25	74126	.65
7407	.50	7453	.25	74141	1.25
7408	.30	7454	.25	74151	1.10
7409	.30	7473	.50	74153	1.40
7410	.25	7474	.50	74154	1.70
7411	.30	7475	1.00	74157	1.40
7413	.90	7476	.65	74164	2.00
7416	.50	7483	1.25	74165	2.00
7417	.50	7485	1.40	74166	2.00
7420	.25	7486	.50	74181	4.50
7430	.25	7489	3.25	74192	1.75
7432	.30	7490	1.00	74193	1.50
7437	.50	7492	1.00	74195	1.15
7438	.50	7493	1.00	74200	9.00
		7495	1.00		

DIGITAL LOGIC TESTER

Will test CMOS, TTL, DTL; check out your digital ICs before you solder them in. Find out what that stuff you order through the mail really is! Needs 5V power supply similar to our PS 5-1 kit.

Kit of parts with schematic

\$19.95

FEEL AMBITIOUS THIS MONTH? BUILD A COMPUTER!

8008 CPU chip **\$50.00**
2102 1024-bit static RAM, NMOS +5V supply **\$16.50**
1702A Reprogrammable ROM, 256 x 8 **\$40.00**
Data sheets included.

SPECIAL OFFER - THIS MONTH ONLY:

Buy the basis of a minicomputer with 1024 8-bit words of RAM and 256 8-bit words of ROM, and get 10% off regular price.

One 8008, eight 2102s, and one 1702A, with data sheets - **THIS MONTH ONLY - \$199.80**

1N914 EQUIVALENT DIODES - \$.10 or \$8/100

1/4 WATT RESISTORS - \$.05, \$4/100

We have many 10% values . . .

WIRE WRAP SOCKETS

14 pin	\$.50
16 pin	.60
24 pin	1.25
28 pin	1.35
40 pin	1.80
wire-wrap socket pins	.05
100 or more,	.04

LEDS

LED 10R - Pack of 10 discrete red lens LEDs, various MV5020-series types. **\$1.50**
LED 10C - Pack of 10 discrete clear lens LEDs, various MV5020-series types. **\$1.50**
Application note included.

JUNCTION FETs, TO-18 case

N-CHANNEL: SIMILAR TO:
NJF10 2N4416, MPF102 3/\$1.00
NJF11 2N4091-93 4/\$1.00
NJF12 2N4338-41 4/\$1.00
NJF13 2N3089 3/\$1.00
NJF14 2N4221-22 4/\$1.00

P-CHANNEL:
PJF11 2N3382-86 4/\$1.00
PJF14 2N2608 4/\$1.00

All FETs come with data sheets.

OP AMPS

301T	\$.40	709T	\$.20	748M	\$.40
301M	\$.45	709M	\$.25	747/	
307T	\$.40	739D	\$1.00	5558T	\$.90
307M	\$.45	741D	\$.35	5558M	\$1.00
318T	\$1.50	741T	\$.35	4131M	\$1.25
709D	\$.20	741M	\$.45	4132M	\$1.25

LEGEND

T = TO-5
D = DIP
M = miniDIP

TRANSISTORS

NPN TO-18 general purpose
silicon .15
10 or more, .10
PNP TO-18 general purpose
silicon .15
10 or more, .10
2N2222 (NPN) TO-18 .25
10 or more, .20
2N2907 (PNP) TO-18 .25
10 or more, .20

POWER SUPPLY KIT PS5-1

5 volt 1 amp regulated power supply kit with p/c board and instructions. Board measures 2" x 6"; completed kit is 2" high. Transformer has internal rf shield. **\$8.00**

RGS ELECTRONICS (408) 247-0158
3650 Charles St., Suite K, Santa Clara, CA 95050

We sell many ICs and components not listed in this ad. Send a stamp for our free flyer. **TERMS OF SALE:** All orders prepaid; we pay postage. \$1.00 for handling charge on orders under \$10.00. California residents add sales tax. Please include name, address and zip code on all orders and flyer requests.

TABLE TOP CALCULATOR CASE & KEYBOARD ONLY

Attractively designed! Excellent craftsmanship. Case and keyboard (designed as one unit). Cabinet is made of high-impact plastic beige color with black bezel and amber window. Keyboard consists of a 3-position slide switch and 25 keys, 5 of which are used for memory function. 20 keys gray, 5 keys orange. All keys mounted on one printed circuit board. This modular unit is well suited for our calculator chips. Ideal for the CT5005. Case and Keyboard Complete: ONLY \$15.95



RCA NUMITRON

EACH.....\$ 5.00

SPECIAL: 5 FOR \$20.00

DR2010



Potter & Brumfield

TYPE KHP RELAY 4 PDT 3A CONTACTS



24 VDC (650 coil)....\$1.50

120 VAC (10.5 MA coil).... 1.75

CMOS

CD4001	\$.75	CD4011	\$.75
CD4002	.75	74C20	.75
CD4010	1.00	74C160	3.25

CT5005 CALCULATOR

This calculator chip has a full four-function memory, which is controlled by four keys, **+**M (adds entry into memory), **-**M (subtracts entry from memory), **C**M (clear memory, without clearing rest of registers), **R**M (read memory or use as entry).

12-Digit display and calculate

Fixed decimal at 0, 1, 2, 3, 4, or 5

Leading zero suppression

7-Segment multiplexed output

True credit sign display

Single 28-pin chip

CHIP AND DATA.....ONLY \$14.95

DATA ONLY (Refundable)..... 1.00

5001 CALCULATOR

40-Pin calculator chip will add, subtract, multiply, and divide. 12-Digit display and calculate. Chain calculations. True credit balance sign output. Automatic over-flow indication. Fixed decimal point at 1, 2, 3, or 4. Leading zero suppression. Complete data supplied with chip.

CHIP AND DATA.....ONLY \$9.95

DATA ONLY (Refundable).... 1.00

All ICs are new and fully-tested; leads are plated with gold or solder. Orders for \$5 or more will be shipped prepaid. Add 35c for handling and postage for smaller orders; residents of California add sales tax. IC orders are shipped within 2 workdays--kits are shipped within 10 days of receipt of order. \$10.00 minimum on C.O.D.s (phone in).

MAIL ORDERS:

P. O. Box J 4811 Myrtle Ave.
Carmichael, CA Sacramento, CA
95608 (916) 334-2161

MONEY BACK GUARANTEE ON ALL GOODS!

SEND FOR FREE FLYER LISTING 100's OF MONEY-SAVING BARGAINS!

BABYLON ELECTRONICS

LED's

MV50 red emitting \$.20
10-4 ma @ 2V 10 FOR 1.25

MV5024 red TO-18 \$.35
high dome 10 FOR 2.95

MV10B visible red \$.30
5-7 ma @ 2V 10 FOR 2.50

Memory IC 74S206


1x256 Bipolar TTL RAM (45 ns). One bit wide by 256 deep random access memory. Three-chip enable lines. Output is complement. Complete data supplied.

\$3.95 ea. 10 for \$32.00

3-Amp Power Silicon Rectifiers Marked Epoxy Axial Package

PRV	PRICE	PRV	PRICE
100.....	\$.10	800.....	\$.30
200.....	.15	1000....	.40
400.....	.18	1200....	.50
600.....	.23	1500....	.65

MAN 1

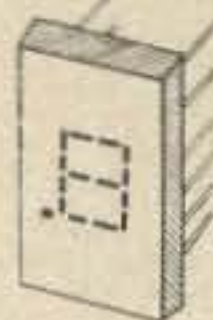

7-Segment, 0-9 plus letters. Snaps in 14-pin DIP socket or Molex. Operates with IC voltage requirements. Long operating life. **ONLY \$3.25**

7400	\$.25	74L51	\$.30
74H00	.35	74H51	.35
7401	.20	7453	.20
74H01	.35	7454	.25
7402	.35	74L54	.35
7403	.30	74L55	.35
7404	.28	7460	.20
74H04	.35	74L71	.30
7405	.28	7472	.40
7406	.70	74L72	.50
7408	.35	7473	.60
74H08	.35	74L73	.75
7410	.25	7474	.65
74H11	.35	74H74	.80
7413	1.25	7475	1.40
7417	.40	7476	.60
7420	.25	74L78	.80
74L20	.35	7480	.65
74H20	.35	7483	1.00
74H22	.35	7489	4.00
7430	.25	7490	1.20
74H30	.35	7492	.90
74L30	.40	7493	1.15
7440	.25	7495	1.15
74H40	.35	74L95	2.00
7441	1.25	74107	.70
7442	1.20	74121	1.25
7446	1.75	74154	2.30
7447	1.50	74163	2.00
7448	1.50	74192	2.50
7450	.25	74193	1.50
74H50	.35	74195	1.00
7451	.25		

7400 Series DIP



RECTIFIERS

VARO FULL-WAVE BRIDGES

V5447	2A	400V	\$.90
V5647	2A	600V	1.10
MR810 Rect.	50V	1A	.10

Special 811: Hex Inverter

TTL DIP Hex Inverter; pin interchangeable with SN 7404. Parts are brand new and are branded Signetics and marked "811."


Data Sheet Supplied

EACH.....	\$.30
10 FOR.....	2.50
100 FOR....	23.00
1000 FOR...	220.00



0-9 plus letters. MAN 3


Right-hand decimal point. Flat-pack type case. Long operating life. IC voltage requirements. Ideal for pocket calculators! **EACH \$1.25 10 OR MORE 1.00**

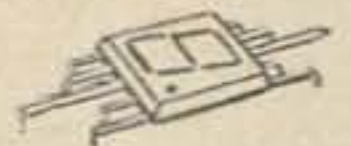

MAN4

Seven-segment, 0-9 plus letters. Right-hand decimal point. Snaps in 14-pin DIP socket or Molex. IC voltage requirements. Ideal for desk or pocket calculators!

EACH.....\$2.75
TEN OR MORE 2.50 EACH

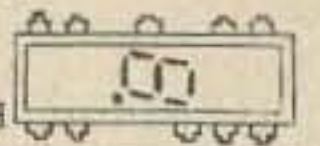


CD-2 Counter Kit

This kit provides a highly sophisticated display section module for clocks, counters, or other numerical display needs. The unit is .8" wide and 4 3/8" long. A single 5-volt power source powers both the ICs and the display tube. It can attain typical count rates of up to 30 MHz and also has a lamp test, causing all 7 segments to light. Kit includes a 2-sided (with plated thru holes) fiberglass printed circuit board, a 7490, a 7475, a 7447, a DR 2010 RCA Numitron display tube, complete instructions, and enough Molex pins for the ICs. . NOTE: boards can be supplied in a single panel of up to 10 digits (with all interconnects); therefore, when ordering, please specify whether you want them in single panels or in one multiple digit board. Not specifying will result in shipping delay.

COMPLETE KIT, ONLY \$11.95

FULLY-ASSEMBLED UNIT \$15.00

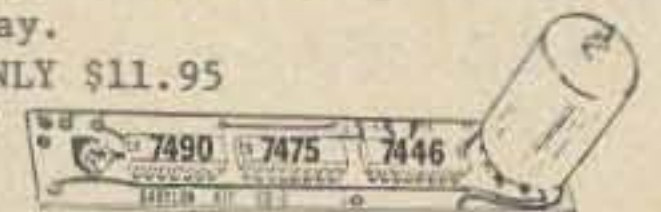

Boards supplied separately @ \$2.50 per digit.

LINEARS

NE540	70-Watt power driver amp.....	\$2.00
NE555	Precision timer.....	1.50
NE560	Phase lock loop DIP.....	3.25
NE561	Phase lock loop DIP.....	3.25
NE565	Phase lock loop TO-5.....	3.25
NE566	Function generator TO-5.....	4.00
NE567	Tone decoder MINI DIP.....	4.00
NE567	Tone decoder TO-5.....	3.00
NE5558	Dual 741 op amp MINI DIP.....	1.00
709	Popular Op Amp DIP.....	.45
710	Voltage comparator DIP.....	.75
711	Dual comparator DIP.....	.40
723	Precision voltage regulator DIP.	1.00
739	Low noise op amp DIP unmarked...	1.00
741	Op amp TO-5/MINI DIP.....	.55
747	Dual 741 op amp DIP.....	1.00
748	Op Amp TO-5.....	1.00
CA3018	2 Isolated transistors and a Darling- ton-connected transistor pair...	1.00
CA3026	Dual differential amp.....	1.00
CA3045	5 NPN transistor array.....	1.00
LM100	Positive DC regulator TO-5.....	1.00
LM105	Voltage regulator.....	1.25
LM302	Op amp voltage follower TO-5....	1.25
LM308	Op Amp TO-5.....	2.00
LM309H	5V 200 MA power supply TO-5....	1.00
LM309K	5V 1A power supply module TO-3..	2.00
LM311	Comparator TO-5.....	1.75
LM370	AGC amplifier.....	2.00
LM380	2-Watt Audio Amp.....	1.75
LM1595	4-Quadrant multiplier.....	2.00
8038	Sine square triangle function gen- erator.....	4.95
MC1536T	Op Amp.....	2.00



GENERAL INFORMATION:

- Anodized aluminum case 1½ x 2½ x 9¼
- All tunable coils are prewound
- Transceiver is on one G-10 predrilled board
- Parts layout silk-screened on boards for easy construction
- Crystal deck is separate predrilled board
- Weight less batteries — approximately 15 oz.
- Battery case is AA size — accepts alkaline or nicad
- External battery charging/power supply jack furnished
- 1 dual gate mosfet 1 I.C. 18 transistors 7 diodes
- Antenna — collapsible 17" whip
- Can be tuned to any 2 MHz segment between 140 and 170 MHz
- Plenty of room in case for add ons (PL and tone)


HT-144 TRANSMITTER SPECIFICATIONS: OUTPUT 2 watts minimum. 3 dB BANDWIDTH 2 MHz typical. STABILITY .002 typical (depends on crystal). SPURIOUS outputs down 30 dB or better. MODULATION true FM with varactor in crystal circuit. NETTING separate trimmers for each channel. DEVIATION adjustable to 5 kHz. AUDIO limiter and active low pass filter. MICROPHONE speaker type. CRYSTAL 18 MHz parallel at 20 pF. MULTIPLICATION FACTOR frequency times 8. CURRENT DRAIN 500 mA typical.

HT-144 RECEIVER SPECIFICATIONS: SENSITIVITY better than .5µV for 20 dB quieting. SQUELCH THRESHOLD better than .3µV. STABILITY .002 typical (depends on crystal). ADJACENT CHANNEL REJECTION 60 dB. SPURIOUS RESPONSES down 70 dB. FIRST IF 10.7 MHz. SECOND IF 455 kHz. BANDWIDTH 15 kHz at 3 dB points. CRYSTAL 45 MHz parallel at 20 pF. CRYSTAL FORMULA receive frequency minus 10.7 divided by 3. HC25U crystal holders, wire leads. AUDIO OUTPUT .5w typical. CURRENT DRAIN 15 mA squelched, 100 mA on voice peaks.

Battery charger \$4.95
 "Rubber Duckie" antenna with
 male & female BNC connectors
 \$12.95

ORDER YOURS NOW !

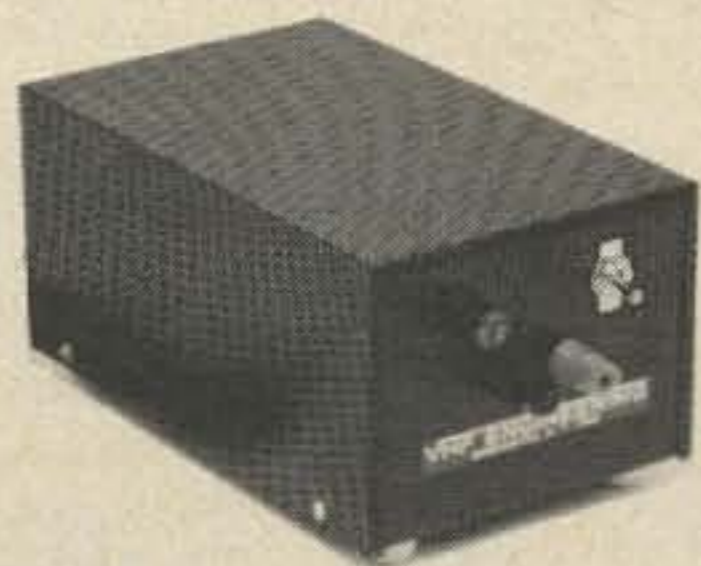HT-144 KIT only \$99.95
 complete less batteries & crystals




PS-12

12 Amp regulated 2%
 50 mV Ripple Max.
 Adjustable 11-15 VDC

WIRED \$79.95

KIT \$59.95

Shipping Weight 12 lbs.

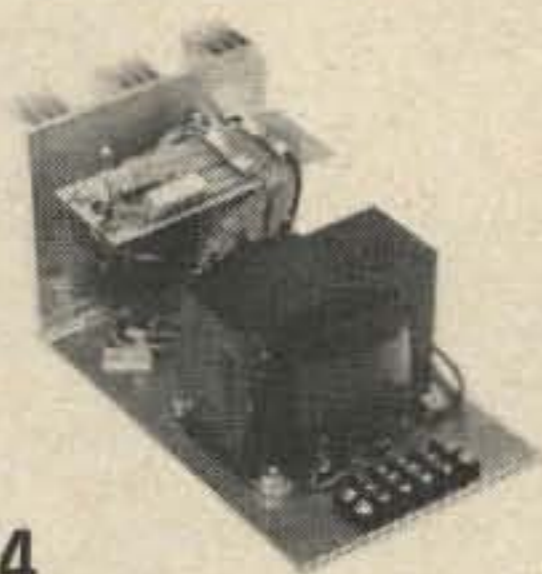

PS-24

24 Amp regulated 2%
 50 mV Ripple Max.
 Adjustable 11-15 VDC

WIRED \$89.95*

KIT \$69.95*

Shipping Weight 21 lbs.

** PS-24 SHIPPED with BASE PLATE — LESS CASE, AS SHOWN*



VHF ENGINEERING

— DIV. of BROWNIAN ELECT. CORP. —

320 WATER ST. POB 1921 BINGHAMTON, NY 13902 607-723-9574

See you at the New York Hamfest — METRO NEW YORK — July 19, 20, 21



RT-70/GRC \$20 each, 3/\$50


Latest government release. Transmitter-Receiver RT-70/GRC covers 47 to 58.4 mc FM. Requires only 90 Volts dc and 6 volts dc. Used, visually OK, supplied with schematic. **1 MC crystal used for calibration . . . \$4.00**
116 page maintenance manual for GRC \$2.00

TRANSFORMERS

BRAND NEW, 115 volt AC input. OP - AMP XFMR, out puts: 16 VCT 1/2 amp, 17 VCT 1/2 amp. **\$3.50**


FILAMENT or BTRY CHARGER XFMR

output of 18 volts at 4.5 amp **\$3.50**

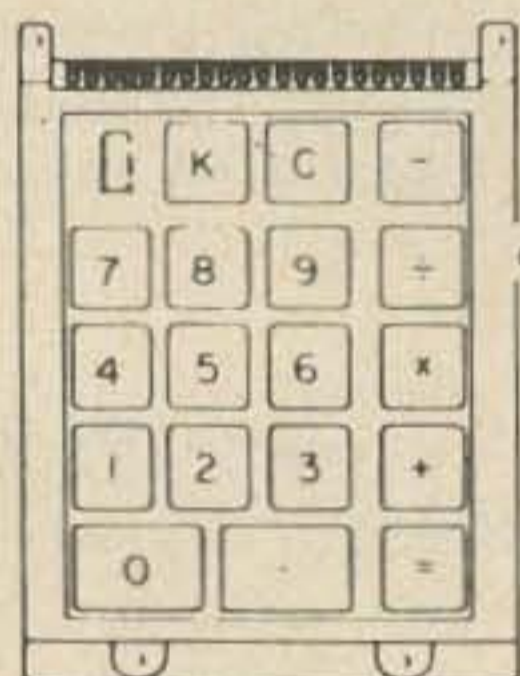

CALCULATOR KEYBOARD

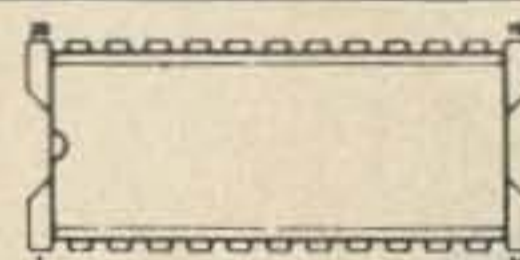\$5.00 Brand new keyboards for hand held calculators. Two styles available. One for use with calculator chip CAL TEX 5001-5002-5012 or MOSTEK 5010-5012. Another for use with Gen. Inst. chip C500. Priced at ~~\$8.00~~ each or two for ~~\$15.00~~. **2/\$9.00**



CT 5005 CALCULATOR CHIP

Single MOS chip with all logic required for 12 digit 4 function desk top calculator with extra storage register for memory or constant. Multiplexed 7 segment outputs for LED, Incandescent, Fluorescent, or Gas Discharge displays. Brand new, bargain priced, with specs. **\$8.00 each, 2 for \$15.00**


AM-FM RADIO \$5.50

Due to the West Coast ship strike they came in too late for the customer. Now it's your bargain. Use it as is or build it into your own cabinet, desk, wall, etc. All built, ready to use, with AC supply. To make it portable all you do is power it with a couple of "D" cells. Fully assembled solid state chassis with AC power supply, less speakers. Covers full AM as well as FM broadcast. The price. . . an astounding meager \$5.50

313,344 CORE MEMORY \$125.00

From SPECTRA computer, visually OK. 64 x 68 x 4 x 18 core stack. Figures out to 35K Byte.

CLOCK/CALENDAR ALARM CHIP

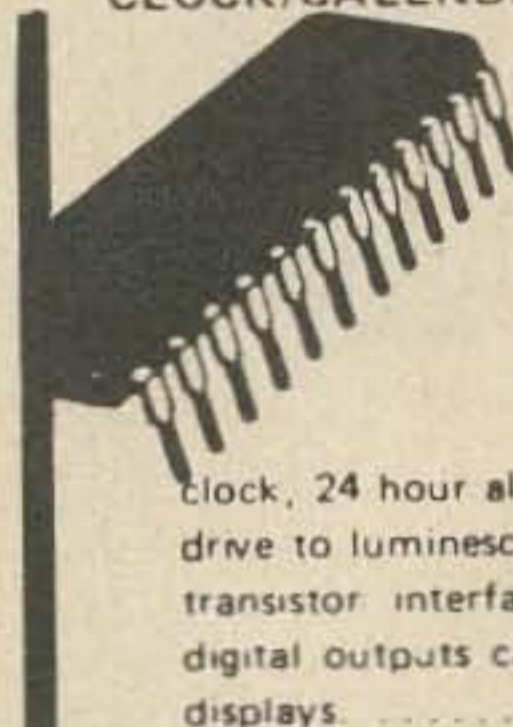

These large scale integrated (LSI) chips eliminate literally thousands of components or hundreds of chips in the construction of a clock. For most applications only a single supply and a minimum of components are required. 7001 Chip - Features 28/30/31 day calendar, 12/24 hour clock, 24 hour clock, 24 hour alarm, snooze alarm, 6 digit display, direct drive to luminescent anode tubes or LED segments, single transistor interface with Sperry displays. Segment and digital outputs can be "wire or 'D'" to share calculator displays. **\$9.95 each, 2/\$18.00**

IC SALE YOUR CHOICE 3 for \$1.00

- μl 900 BUFFER TO-5
- μl 914 DUAL 2 INPUT GATE TO-5
- μl 923 JK FLIP FLOP TO-5
- μl 926 Hi speed JK FLIP FLOP TO-5
- μl 931 JK/RS FLIP FLOP (DIP)
- 10 pin socket for TO-5 IC **3/1.00**



GIANT NIXIE B7971

Used \$1.00 Brand New \$2.00
 With schematic for GIANT clock.

COMPUTER TAPE DECK \$75.00

Takes 1/2 inch tape, made by Computer Entry Systems. Visually ok, with electronics, no data available.

Calculator Chips

5001 LSI (40 pin) Add, subtract, multiply, divide 12 digit. With data \$6.95
 Data alone 50 cents

CMOS 4814 HEX INVERTER

CMOS HEX INVERTER, dual inline package. 3-18 volt range, dual diode protection against static charge. Dielectrically isolated complimentary MOS. **\$1.00 each 12 for \$10.00**

DUAL 16 BIT MEMORY

Dual 16 bit memory, serial MOS by Philco TO-5 case, brand new with 2 page specs. #PLR 532 **\$1.00 each \$10/12**

2048 BIT MOS MEMORY

2048 bit MOS LSI random access memory NEC 6003. All inputs except clock are TTL compatible. 2048 word by 1 bit. 22 pin ceramic dual-in-line. With specs. **\$5.00 EACH** ~~\$9.00~~ each 2 for **\$9.00**

RCA INJECTION LASER DIODES

Another SUPER SCOOP by Meshna. Brand new RCA packaged, considered obsolete by RCA but what an exotic opto-electronic device for the sophisticated experimenter. Only several hundred on hand. Values shown are approx. as each diode characteristic varies. Each is marked with correct value.
 6 WATT \$10.00
 10 WATT \$15.00

Meshna

Postage extra on above. MESHNA PO Bx 62 E. Lynn Mass. 01904

COMPLETE MEMORY SYSTEM

Measures 12 x 7 x 1 inches. Utilizes TTL ICs. 10240 memory cores. 9 installed sense amps, addressed as 1024 locations. I/O lines include 9 data-in, 9 data-out, 10 address-in, powering status and control. Only 40 systems on hand. Schematics included.

DCU \$150pp

AUTOMOBILE REVERB


Brand new fully assembled, ready to install in your car to give 3rd dimension concert hall effect. Complete with instructions, rear seat speaker, grill, wires, plugs.

05 \$7.00

15 AMP BATTERY CHARGER

Brand new GE transformer, 25 amp fullwave bridge. Output approximately 15 volts up to 15 amps. Ideal battery charger or DC source for general use. With instructions, assembled in minutes.

PK-4 \$10.00

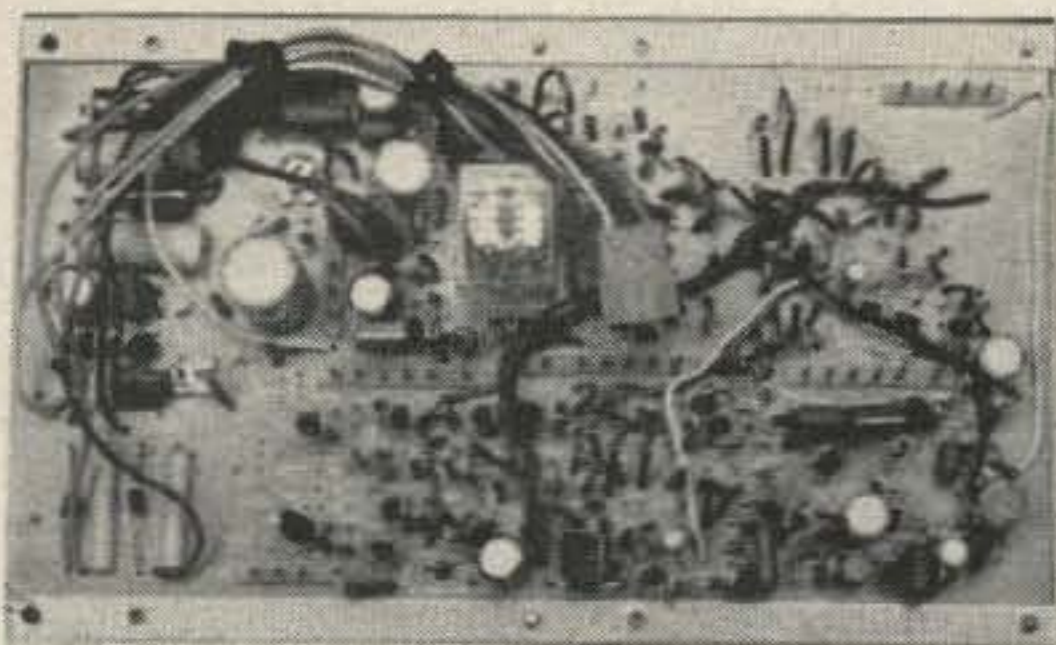

TV POWER SUPPLY & TRANSPORT CIRCUIT

A complete assembled PC board, spares from a video tape machine. Many many fine components to be found. One section of the board used as a 12 volt and 24 volt regulated power supply. You add the transformer and output will be 24 volts transistor regulated as well as another output of 12 volts transistor regulated. 3 amps on the 12 volts and 1 amp on the 24 volt section. Full schematic of the complete board included. These are unused and cost in excess of \$200.

B74-1 \$6 or 3/\$15

8 TRACK STEREO TAPE DECK

With built-in stereo pre-amp, 115 volt drive motor, channel indicator lamps. Unused, original boxed, less cabinet. Customize your stereo music center with one of these tape decks.

46 \$14.00

UNDERWATER LISTENING

Brand new by OLIN. Use it for a swim pool monitor-alarm, use it on lake or ocean listening to underwater noises, fish, etc. Complete with hydrophone, 50 ft. mike cable, speaker-amplifier console. Operates from 115 volts AC or 15 volt dry cells. 12 lbs.

\$25.00

RCA TD-2 TUNNEL DIODE

Original packaged, each factory marked, with spec sheet.

\$1.25 each, 5/\$5.00.

CALCULATOR KIT

Includes 8 digit LED readout, Keyboard, Calculator Chip - all for \$15.00

RCA INJECTION LASER DIODES

Another SUPER SCOOP by Meshna. Brand new RCA packaged, considered obsolete by RCA but what an exotic opto-electronic device for the sophisticated experimenter. Only several hundred on hand. Values shown are approx. as each diode characteristic varies. Each is marked with correct value.

6 WATT \$10.00

10 WATT \$15.00

2N2152	45 volt	170 watt	PNP-G	\$1.00
*2N3713	80	170	NPN-S	1.00
*2N3789	60	150	PNP-S	.75
2N5301	40	200	NPN-S	1.25
*2N5301	40	200	NPN-S	1.00

*Removed from used equipment

Postage extra on above. MESHNA PO Bx 62 E. Lynn Mass. 01904

NEW 96 PAGE CATALOG NOW READY

Meshna

CALCULATOR KIT

Kit contains NORTEC calculator chip 4024, 21 driver transistors, 8 LEDs, 7 segment readout by EXITON, 3 LED for overflow, low btry, over-range, a keyboard by FLEX KEY. \$45 value.

\$16.50 each, 2/\$27

BASIC CLOCK KIT

We furnish clock chip CT 7001 and 4 first line LED readouts .3 inch hgt. You furnish the misc. minor parts. \$35 value.

\$19.95


LIQUID CRYSTAL WATCH

Build a wrist watch or desk clock with this liquid crystal display. Recently written up in several magazines. Display with special socket reads hours and minutes.

\$15.00 each, 2/\$25.00

HP LED DISPLAYS

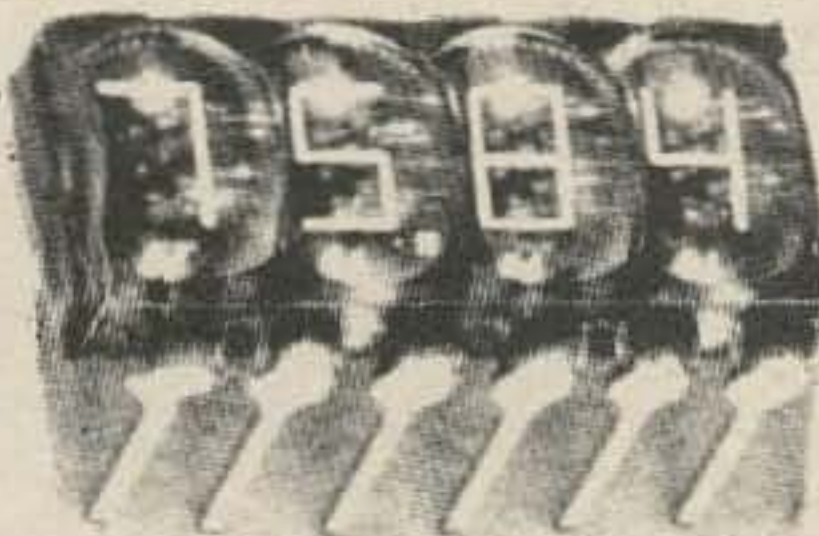Brand new 4-on-strip LED display. End butt two strips and come up with 8 digit readout. An unheard of SUPER VALUE at \$5.00 per strip of 4 digits. Two strips (8 digits)



\$9.00. Another strip . . . this one a clock readout. The strip has 2 digits . . . space . . . 2 digits. Perfect for reading hours & minutes.

\$5.00 per strip, 2/\$9.00

CMOS 4814 HEX INVERTER

DIP with operation 3-18 Volts. Dual diode protection against static charge destruction. Dielectrically isolated complimentary MOS.

\$.50 each, 12/\$5.00

DUAL 16 BIT MEMORY

Serial MOS by PHILCO in TO-5 case. Brand new with 2 page specs.

#PLR 532

\$1.00 each, 12/\$1.00

PHONE PATCH KIT

Includes all parts, instructions, cabinet.

AM PATCH - \$5.00

SSB PATCH - \$9.00

2048 BIT MOS MEMORY

MOS LSI random access memory NEC 6003. All inputs except clock are TTL compatible. 2048 word by 1 bit. 22 pin ceramic DIP. With specs.

\$9.00 each, 2/\$17.00

VOLTAGE CONTROLLED OSCILLATOR

Rare item. See Pop. Elect. Mag. Oct. 1973 for uses. In 14 pin DIP package.

#8038C


\$5.00 each, 2/\$9.00



ASCII KEYBOARDS W/ENCODER

From Raytheon, new or like new. 5 extra function buttons each side. Open faced, no cabinet. Schematic provided. Price is postpaid world wide.

\$46.00

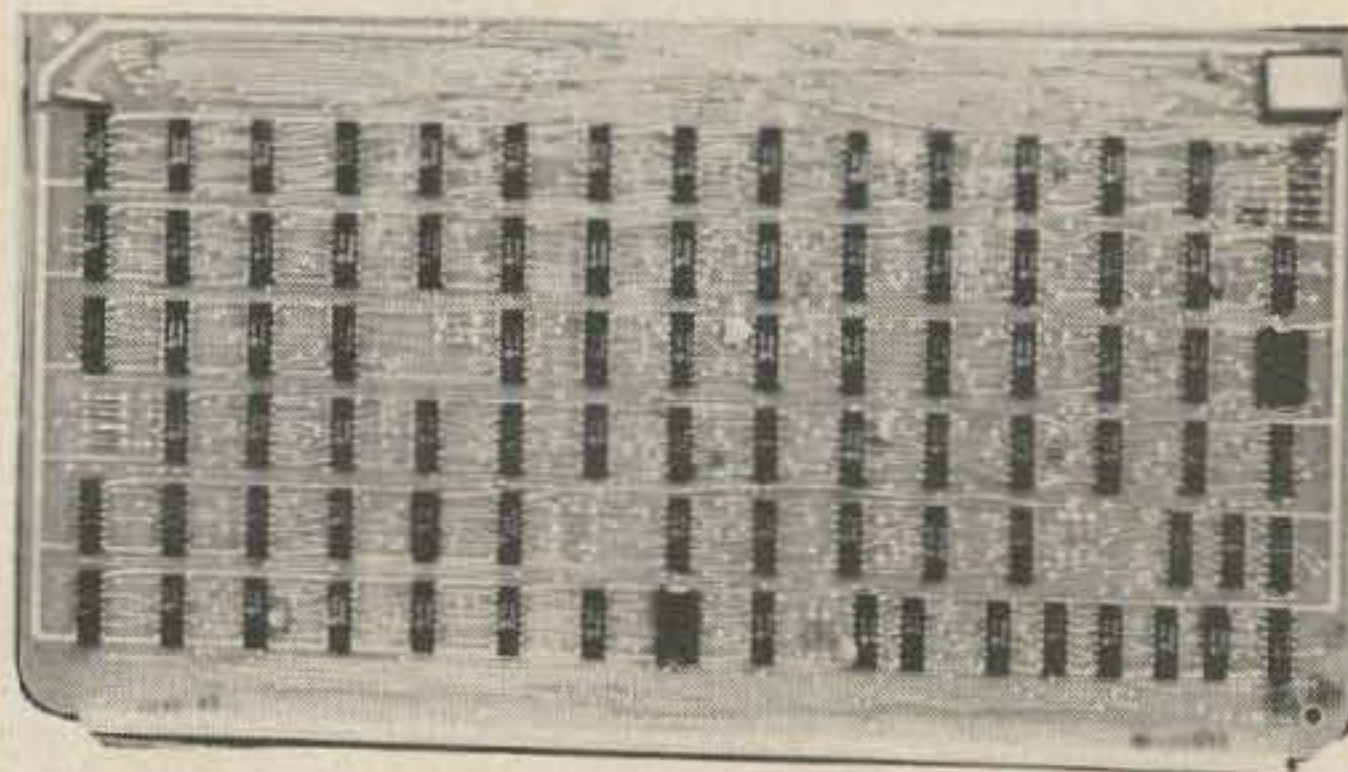

DTL SERIES ICs




Talk about bargains . . . this is a whopper. Due to quantity on hand, we are reducing this item to a new MESHNA MESHU GINA deal. About 100 devices, all marked and easily removed. With shrinking supplies and upward direction of prices, this makes it well worth going into the salvage business. This Super Mother Board can be stolen for \$6.00 each or 6 for \$25.00. We have these in ST 600 series DTL.

#SAN-D

\$6.00 each, 6/\$25.00

Meshna

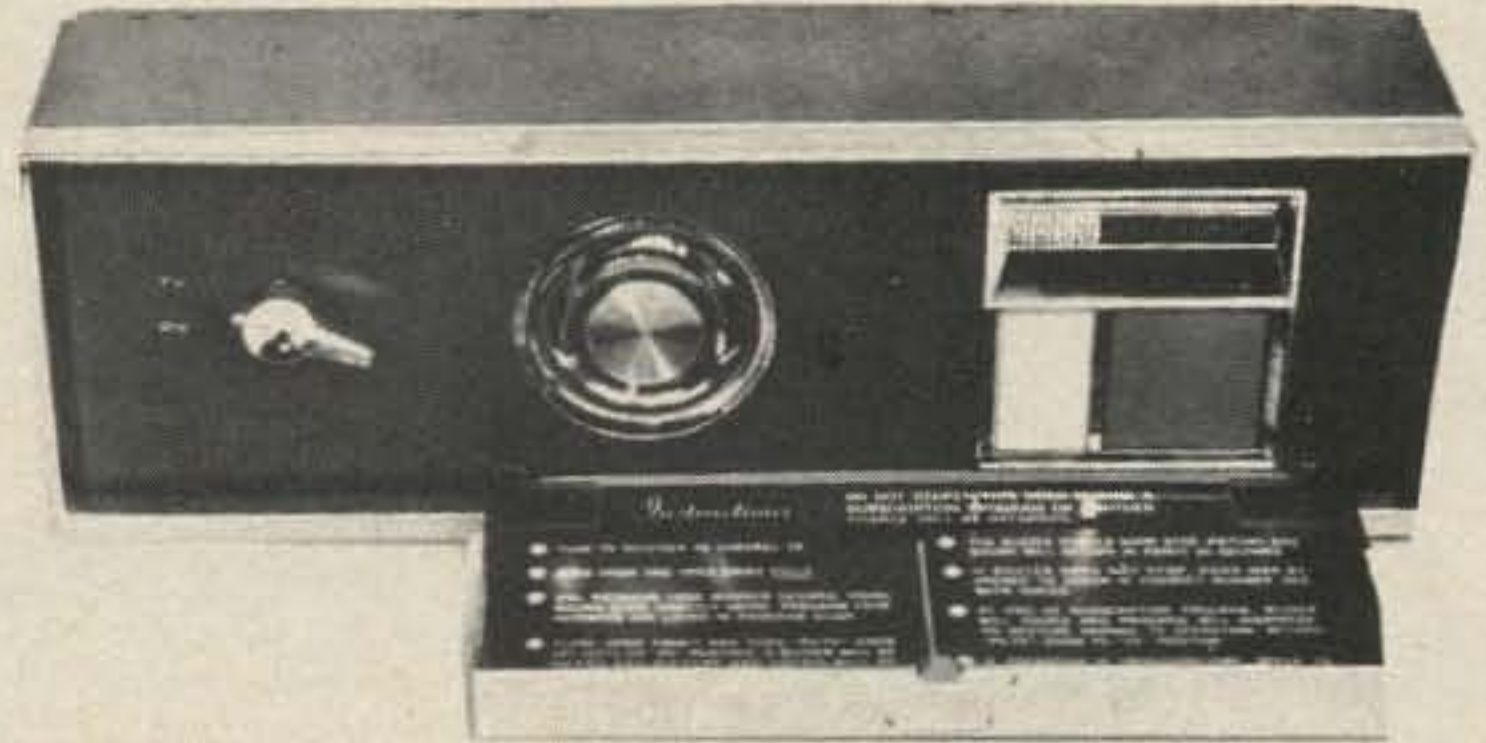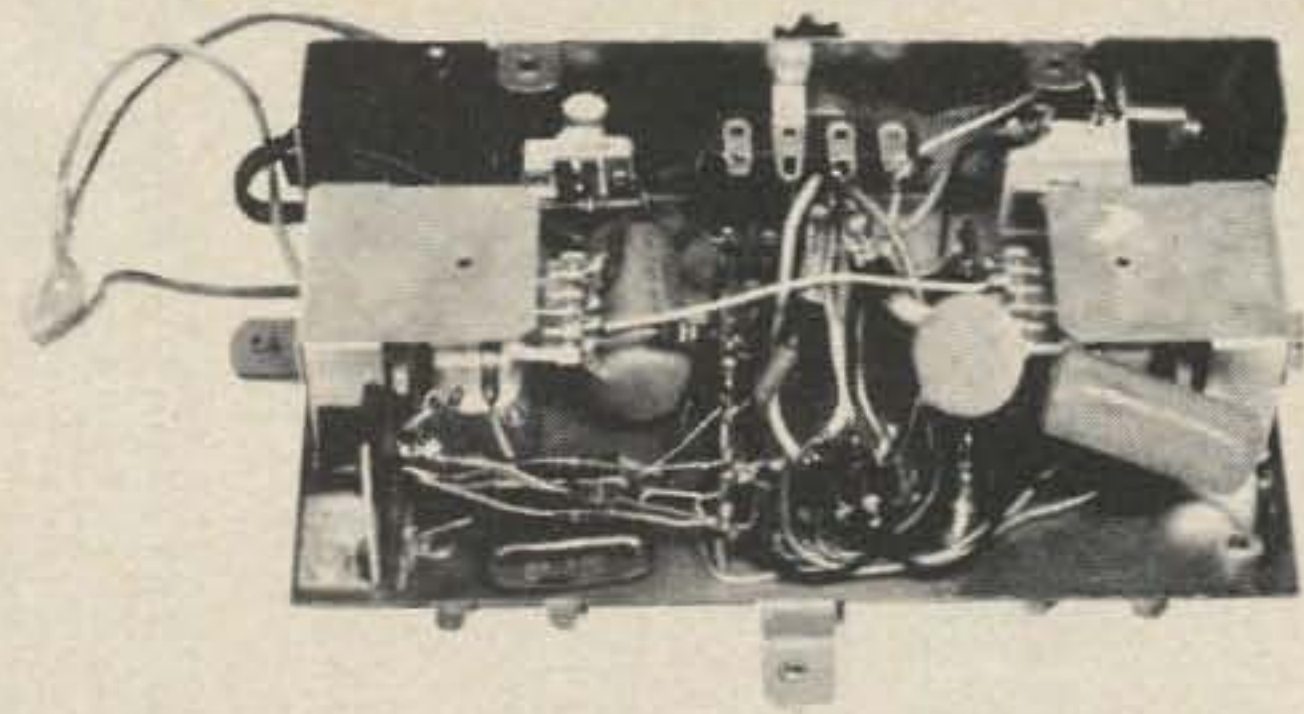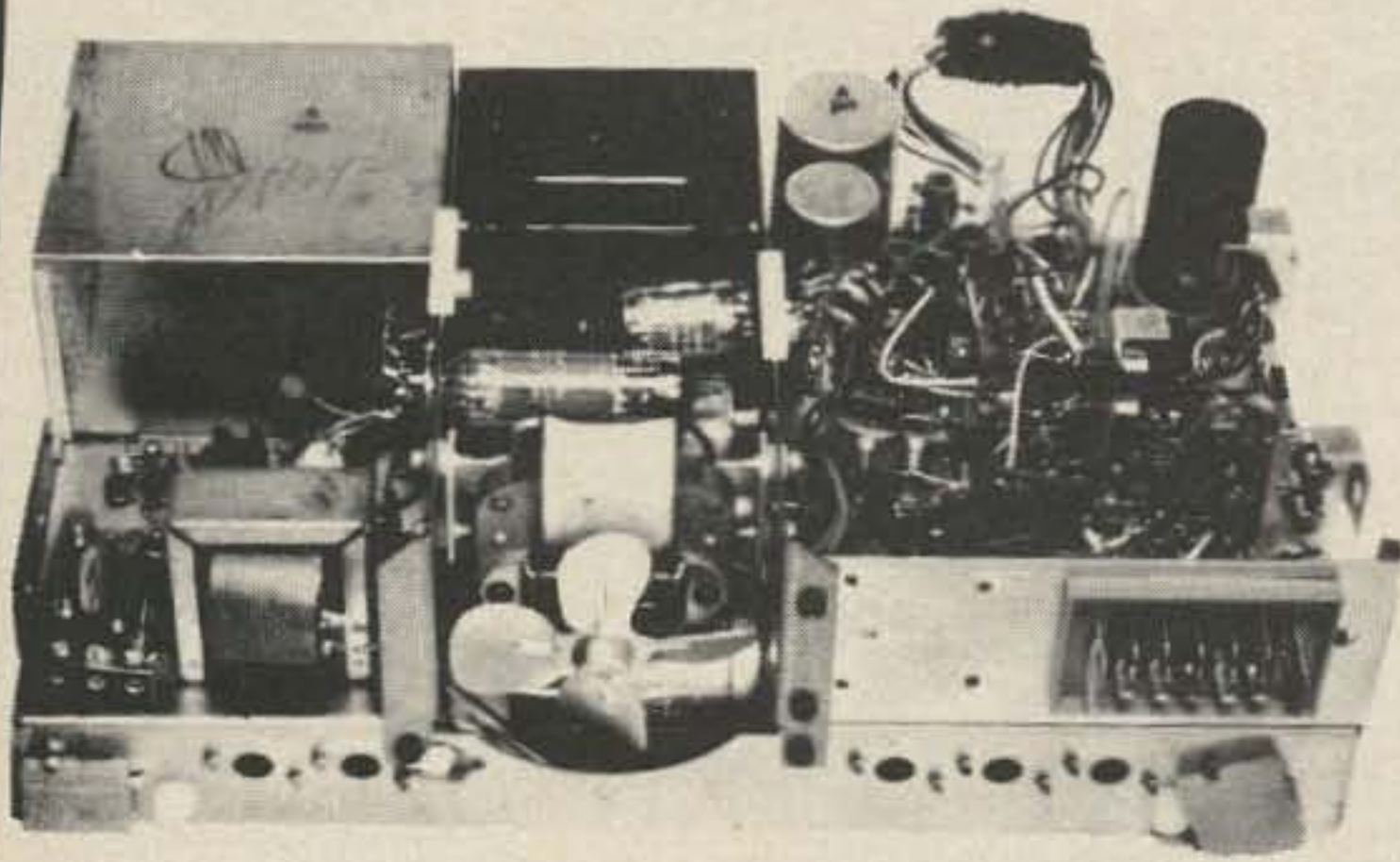Postage extra on above. MESHNA PO Bx 62 E. Lynn Mass. 01904



PAY TV ASSEMBLY \$15.00

A "Super Value" for the gadgeteer. A complete Pay TV installation made for ZENITH and all in original packing (3 cartons - wgt 36 lbs) and all unused. Operates on regular 115 volt 60 cycle power. A wealth of parts, easily removed due to long leads on components, most over one inch long. The 3 units consist of Translator, Adapter, Decoder. Transistors, tubes, solid state bridge power supply, geared clock motor, 35mm geared transport, time recorder, solenoid, relays, hundreds of small parts such as resistors, caps, etc. Our estimate as to cost to Zenith, approx \$1,000 per set. Schematics with each purchase. One set of 3 units \$15.00 wgt of 36 lbs. Special . . . 3 sets \$30 wgt of 108 lbs. All unused, original boxed.

AUDIO OSCILLATOR TS-382

Military surplus. 20-200,000 CPS in 4 bands. Amplitude variable 0-10 volts. Freq. response 20 CPS to 150,000 CPS. Operation from regular 115 volts. Ship wgt. 75 pounds.

Government cost\$224
Our low price\$49
Buy three for\$125

TELETYPE CONVERTER CV 278/GR

From the military. Standard 455 kc IF. A rare item. Power input 24-28 volts DC. Ship wgt. approx 20 lbs.

Government cost\$496
Our low price\$49
Buy three for\$125

RECEIVER BC 348

An old friend amongst the surplus buyers, but long gone from the market. Once again available as surplus. Covers 1.5-18 MHz tuneable in 6 bands. Also covers 200 kHz-500 kHz. Crystal phasing, MVC, AVC, BFO, etc. 60 lbs.

#348\$55

RECEIVER BC 312

Similar to BC 348, this is the Army version. A little heavier in construction. Covers 1.5 MHz-18 MHz. Ship wgt. approx. 60 lbs.

#312\$49

TWO COLOR LED RED/GREEN

Bidirectional, reversing polarity reverses color, the same diode emits red or green depending on polarity. Limited quantity.

Two color LED\$1.50 each, 12/\$15

UNBELIEVABLE?????

Silicon diode stacks at amazing ratings. Good for 50 Ma.

45,000 PIV	\$4.00
37,500	\$3.50
30,000	\$3.00
22,500	\$2.75
15,000	\$2.00

Postage extra on above. MESHNA PO Bx 62 E. Lynn Mass. 01904

Meshna



Brand New
"DIP" Packages

POLY PAKS SMASHES IC PRICES

Buy 3
or more,
10%
discount

LIMITED
OFFER!

Buy 100 — Take 20%

• Factory Marked


Order by type number! Spec sheets on request "ONLY"

Type	Sale	SN7432	.55	SN7471	.55	SN74108	.95	SN74161	1.95
SN7400	\$0.30	SN7437	.55	SN7472	.50	SN74112	.95	SN74163	1.95
SN7401	.30	SN7438	.55	SN7473	.55	SN74113	.95	SN74164	2.95
SN7402	.30	SN7440	.30	SN7474	.55	SN74114	.95	SN74165	2.10
SN7403	.30	SN7441	1.40	SN7475	1.00	SN74121	.60	SN74166	2.05
SN7404	.35	SN7442	1.50	SN7476	.65	SN74122	.95	SN74173	2.50
SN7405	.35	SN7443	1.50	SN7477	.95	SN74123	1.20	SN74174	3.20
SN7406	.45	SN7444	1.50	SN7478	.95	SN74125	.71	SN74175	3.20
SN7407	.55	SN7445	1.50	SN7480	.65	SN74126	.71	SN74176	2.10
SN7408	.35	SN7446	1.65	SN7481	1.25	SN74139	4.50	SN74177	2.10
SN7409	.35	SN7447	1.45	SN7482	.99	SN74140	1.25	SN74179	2.10
SN7410	.30	SN7448	1.50	SN7483	1.25	SN74145	1.55	SN74180	1.20
SN7411	.35	SN7449	1.50	SN7485	1.41	SN74148	4.50	SN74181	3.95
SN7413	.95	SN7450	.30	SN7486	.55	SN74150	1.61	SN74182	1.20
SN7415	.55	SN7451	.30	SN7489	3.50	SN74151	1.25	SN74185	2.50
SN7416	.55	SN7453	.30	SN7490	1.49	SN74152	4.95	SN74192	1.95
SN7417	.55	SN7454	.30	SN7491	1.35	SN74153	1.60	SN74193	1.95
SN7420	.30	SN7455	.55	SN7492	1.35	SN74154	2.10	SN74194	1.95
SN7421	.55	SN7460	.30	SN7493	1.35	SN74155	1.55	SN74195	1.25
SN7422	.35	SN7461	.35	SN7494	1.35	SN74156	1.45	SN74196	2.50
SN7425	.50	SN7462	.35	SN7495	1.35	SN74157	1.55	SN74197	2.50
SN7426	.55	SN7464	.30	SN7496	1.35	SN74158	1.55	SN74198	2.65
SN7430	.30	SN7465	.50	SN7497	.95	SN74160	1.95	SN74200	9.95
		SN7470	.50	SN74107	.70				

OVER 1,000,000-PC INVENTORY

HIGH POWER TRANSISTOR WITH HEAT SINK

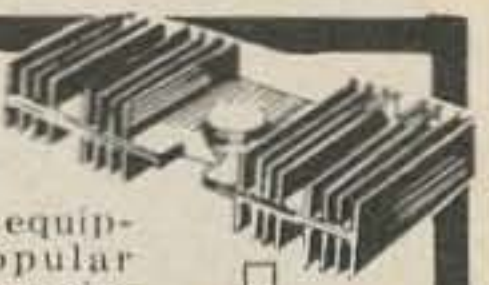Removed from new equipment! Includes popular 2N174 'doorknob' transistor TO-36, germanium, PNP, 150 watts, VCBO 80V, 15 amps, 40 hfe. For ignition, high power transmitters, etc. Mounted on heat sink 5 x 2 1/2 x 1 1/4".



\$1.49
3 for \$3

POCKET CALCULATOR KEYBOARD Only

3 for \$18. \$6.95


For hand-held units, properly multiplexed for chip CT-5001, 2, 12 or Mostek 5010-12, 18 feather-touch keys, by FLEX-KEY.



CALCULATOR CHIPS ON A "DIP"

CT5001	12-digits 40-Pin	\$6.95
CT5002-9	Volt version of 5001	8.88
CT5005	12-digits 28-Pin with 3-function memory.	9.95

7-SEGMENT LED Readouts

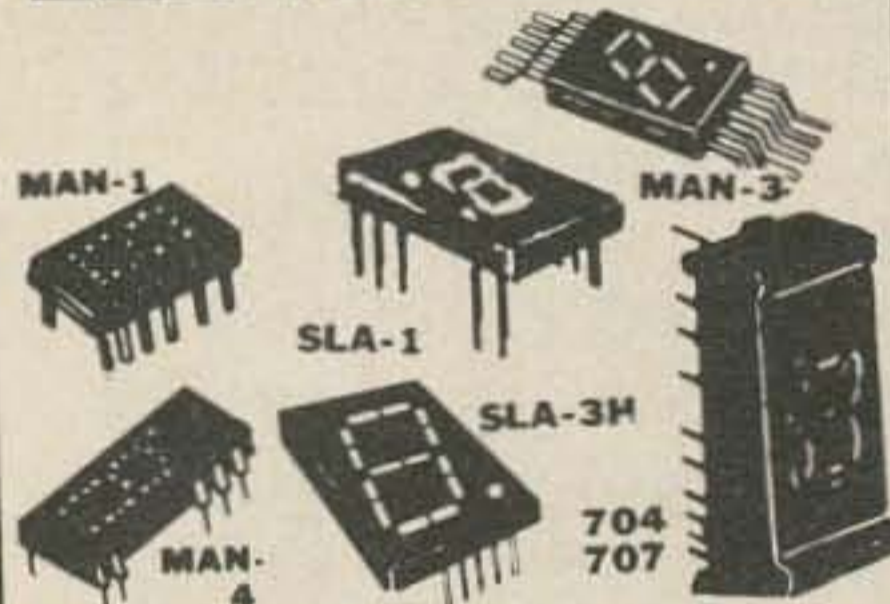

(All "LED" TYPES)

Type	Char.	Each	Special
MAN-1	.27	\$3.75	3 for \$9.
MAN-3	.12	1.49	3 for \$3.
MAN-4	.19	2.50	3 for \$6.

REFLECTIVE BAR TYPES

707*	.33	2.50	3 for \$6.
704*	.33	2.50	3 for \$6.
SLA-1**	.33	2.10	3 for \$5.
SLA-3**	.70	4.95	3 for \$13.
SLA-11**	.33†	3.50	3 for \$10.
SLA-21**	.33†	3.95	3 for \$10.

*By Litronix. **By Opcoa, equal to MAN-1 or MAN-4 specs. Color - RED.
†Green. ††Yellow

LINEAR Op Amps

531	Hi slew rate op-amp (TO-5)	\$2.50
532	Micro power 741 (TO-5)	2.50
533	Micro power 709 (TO-5)	2.50
536	FET Input op amp (TO-5)	2.95
550	Precision 723 voltage reg. (DIP)	1.17
555	Timer 2 u Seconds to 1-hr. (A)	1.25
556	5 Times faster than 741C	2.10
558	Dual 741 (A)	1.00
560	Phase lock loops (DIP)	2.95
561	Phase lock loops (DIP)	2.95
562	Phase lock loops (DIP)	2.95
565	Phase lock loops (A)	2.95
566	Function generator (TO-5)	2.95
567	Tone decoder (A)	2.95
702C	Hi-grain, DC amp (TO-5)	.49
704	TV sound IF system	1.50
711C	Dual diff. comp (A)	.33
723C	Voltage regulator (A)	.69
741CV	Freq. comp 709 (Mini DIP)	.44
748C	Freq. adj. 741C (A)	.44
753	Gain Block	1.75
739-739	Dual stereo preamp	1.98
741-741	Dual 741C (TO-5)	.89
PA265	5-Watt voltage regulator	1.00
ULN2300M	Op amp with SCR	1.00
CA3065	Video Audio system	1.00
4136	Quad 741's (DIP)	1.95

(A) TO-5 or DIP dual in line pak

EPOXY	PIV	2 Amp	6 Amp
FULL	50	\$5.69	\$8.88
WAVE	100	.79	.99
SILICON	200	.95	1.25
BRIDGE	400	1.19	1.50
RECTIFIERS	600	1.35	1.75
	800	1.59	1.95
	1000	1.79	2.25

Code: 2 amp TO-5 case
6 Amp 1/2 x 1/2 x 1/16 sq

CLOCK CHIPS ON A "DIP" as Low as 8.88

MM5311	6-digit 28-Pin	\$ 8.88
MM5312	4-digit 24-Pin	8.88
MM5313	6-digit 28-Pin	8.88
MM5314	6-digit 24-Pin	8.88
MM5316	4-digit 40-Pin, Alarm	13.50

NATIONAL Buy any 3 — Take 10% LINEAR OP AMPS

LM-300	POS V.R. (super 723) TO-5	.91
LM-301	Hi-performance op amp (A)	.41
LM-302	Voltage follower TO-5	.91
LM-304	Neg. Voltage Regulator TO-5	1.19
LM-305	Pos. Voltage Reg. TO-5	1.19
LM-307	Super 741 op amp (A)	.41
LM-308	Hi-Q fet type op amp TO-5	1.19
LM-309H	5V Volt-Regulator TO-5	1.19
LM-309K	5V Volt.-Reg. 1 Amp TO-3	1.85
LM-310	Voltage-Follower TO-5	1.25
LM-311	Hi-perf. Volt. Comp. (A)	1.19
LM-319	Hi-speed Dual Comp. DIP	1.50
LM-320	MINUS 5, 12 or 24V V.R. TO-3	1.50
LM-322	Precision Timer	1.75
LM-339	Quad Comparator. DIP	1.75
LM-324	Quad (4-741's in DIP)	2.50
LM-350	Dual peripheral driver	.41
LM-370	AGC Squelch op amp, TO-5	1.19
LM-371	RF, IF op amp, TO-5	1.25
LM-373	AM-FM SSB I.A.D. TO-5	3.50
LM-374	AM-FM SS IVAD TO-5	3.50
LM-377	Dual 2-watt audio amp	3.00
LM-380	2-watt audio amplifier TO-5	1.69
LM-381	Low noise dual pre amp DIP	1.95
LM-382	Low noise dual pre amp DIP	1.95
LM-703	RF-IF amp, TO-5	.55
LM-709	Operational amplifier (A)	.36
LM-710	Differential amplifier (A)	.45
LM-711	Dual Differential Amp (A)	.36
LM-723	Voltage Regulator (A)	.69
LM-725	Instrument Op Amp	.95
LM-733	Differential Video	1.75
LM-741	Freq. Comp. 709 (A)	.41
LM-741CV	Mini DIP 741C	.45
LM-747	Dual 741 (A)	.89
LM-748	Freq. adjustable 741C (A)	.44
LM-1303	Stereo pre amp DIP	.95
LM-1305	FM Multi. Stereo Dem. DIP	1.25
LM-1307	FM Multi. Stereo Dem. DIP	.91
LM-3028	Differential RF/IF amp	1.50
LM-3900	Quad "current mirror" amp	.95
LM-4250C	Programmable op amp	2.50
LM-75451	Dual peripheral driver	.44
LM-75453	Dual peripheral driver	.44
LM-75492	Quad seg. driver, LED (DIP)	1.65
LM-75492	Hex digit driver, 250ma, DIP	1.85

(A) TO-5, Dip or mini Dip

SANKEN HYBRID AUDIO POWER AMPS

Mfg's Type	Watts	Sale
SI-1010Y	10	\$ 8.88
SI-1025E	25	18.88
SI-1050E	50	29.95

Used extensively in hi-fi systems, tape decks, FM tuners, record players, stereo components, musical instruments, P.A., etc. All amplifiers, flat within 1/2 db from hz to 100,000. Each unit properly heat-sinked, with heavy-duty connecting tie lug connections. Single-ended pushpull output. Power supply required 24VDC. Output to 8 ohms. Order by Stock No.

Terms: add postage Rated: net 30
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

15¢ CATALOG on Fiber Optics, 'IC's', Semi's, Parts

POLY PAKS

P.O. BOX 942A LYNNFIELD, MASS. 01940



WRIST WATCH only \$19.95 LIQUID CRYSTAL DISPLAY

*3-1/2 digit. 7 segment
*Only 1-1/16 x 11/16 x 1/4"


See POPULAR ELECTRONICS (Jan., 1974) for building your own electronic digital wristwatch using the Liquid Crystal Display (LCD) as its basic. Easy to see, 3 1/2 digit display, requires less than 1/1000 of power as LED'S. Visibility increases with ambient light. Difficult reading of LED'S in light. Pulsates SECONDS in center of display. NO NEED OF TRANSISTOR-RESISTOR interface, as LED'S, thus smaller package. Chip contains holder, tiny connecting terminals, and "slide-in-place chrome spring face plate". Size of display in holder: 1-1/16 x 11/16 x 1/4". Operating freq. 32 hertz. 45-microwatts of power. Operates from 1.5V hearing aid cell. Uses the new and latest C MOS micro-circuitry. We include copy of write up from PE magazine.



CALL BOOK 74

*When you want
an authoritative,
up to date,
complete reference
It's the
CALLBOOK*

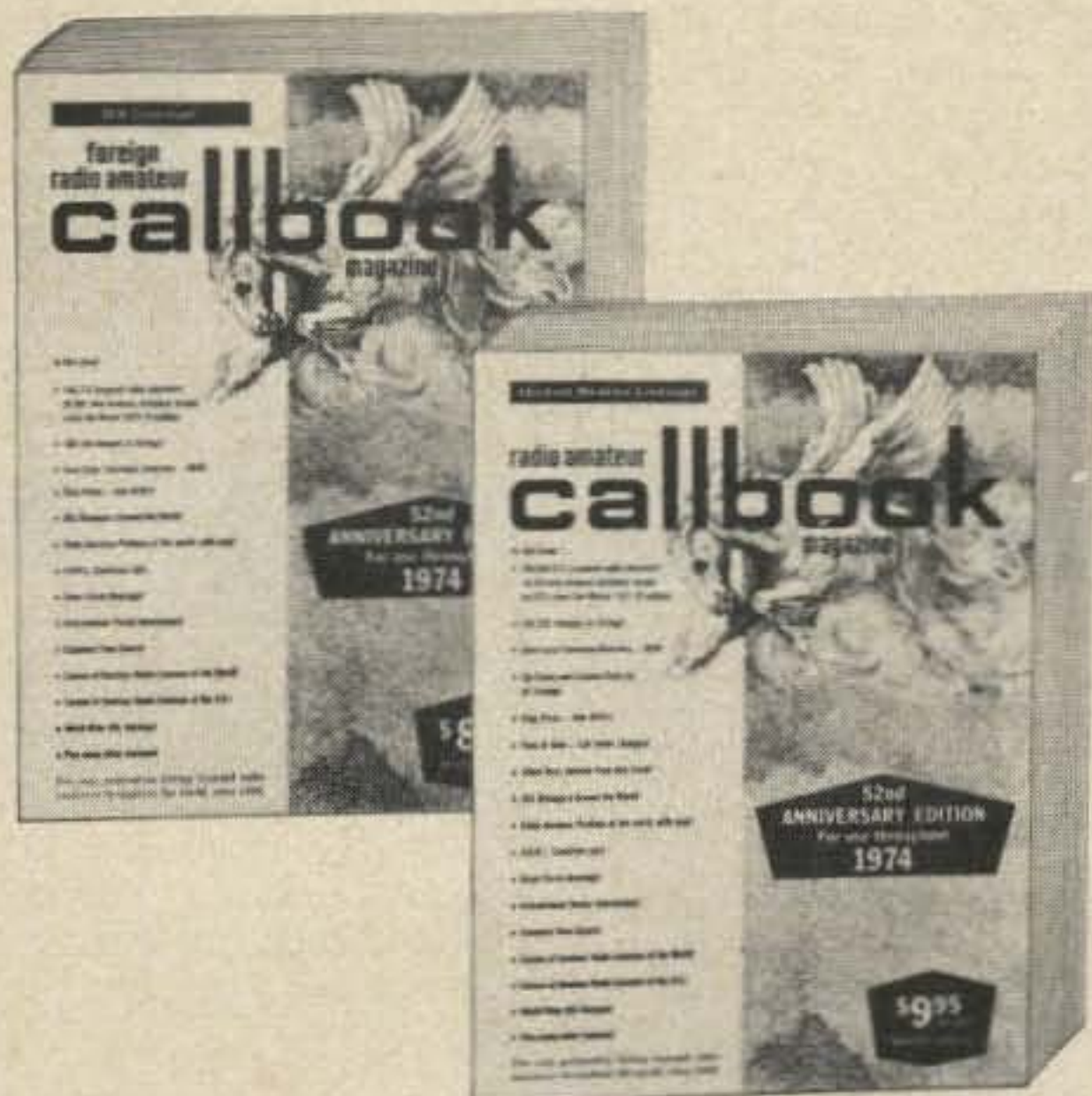Over 210,000 QTH's
in the DX edition
DX CALLBOOK for 1974
\$8.95



Over 285,000 QTH's
in the U.S. edition
U.S. CALLBOOK for 1974
\$9.95

See your favorite dealer or Send today to
(Mail orders add 50¢ per CALLBOOK
for postage and handling)

WRITE FOR FREE BROCHURE
RADIO AMATEUR **callbook** INC.
Dept. B 925 Sherwood Drive
Lake Bluff, Ill. 60044

FREE

 Windjammer

CRUISE

— from Reader Service —



73 will be giving away a Windjammer cruise each month absolutely free! It's a vacation of a lifetime — 10 Windjammin' days of swimming, snorkeling and prowling uninhabited beaches. They'll take you to funny little places with funny little names . . . Mustique, Bequia, Saba, Carriacou. Or, to Guadaloupe, St. Lucia, Grenada and Martinique. And the only thing better than a Windjammer day is a Windjammer night. Soak up a golden moon, limbo to a steel band and fall asleep under a star-spangled Carribean sky. No stuffed shirts, no plush resorts, just a bunch of congenial shipmates heading for adventure.

All you have to do to win is check off the advertisers you are interested in, on the Reader Service coupon and send it in to 73. We'll do the rest. Each month a winner will be drawn from all the Reader Service inquiries received.
Mail today!!!!

READER SERVICE

Please either tear out this list of advertisers and send it in to 73 with as many boxes checked off as you would like to see brochures, data sheets or catalogs. . . or else make a copy and send that in. Include your zip code, please. Send money directly to advertisers.

ADVERTISER INDEX

- | | |
|--|---|
| <input type="checkbox"/> AAA 78 | <input type="checkbox"/> Juge 32 |
| <input type="checkbox"/> ADVA 47 | <input type="checkbox"/> K-Enterprises 21 |
| <input type="checkbox"/> Am. Whisle. 69 | <input type="checkbox"/> Meshna 90,91,92,93 |
| <input type="checkbox"/> ANTECH 77 | <input type="checkbox"/> MFJ 41 |
| <input type="checkbox"/> Atlanta Hamfest 78 | <input type="checkbox"/> Newtronics CII |
| <input type="checkbox"/> ATLAS 42 | <input type="checkbox"/> Nurmi 40 |
| <input type="checkbox"/> ATV 69 | <input type="checkbox"/> Pacificom 60 |
| <input type="checkbox"/> Autek 30 | <input type="checkbox"/> Palomar 30 |
| <input type="checkbox"/> Babylon 88 | <input type="checkbox"/> PEMCO 66 |
| <input type="checkbox"/> CEPCO 62 | <input type="checkbox"/> Polypaks PolyPaks |
| <input type="checkbox"/> CFP 46 | <input type="checkbox"/> Qument 46 94 |
| <input type="checkbox"/> Columbia 46 | <input type="checkbox"/> Radio Am. Callbook |
| <input type="checkbox"/> Comm. Spec. 30 | <input type="checkbox"/> Regency 80 95 |
| <input type="checkbox"/> Comm. Unlimited 80,81 | <input type="checkbox"/> RGS 87 |
| <input type="checkbox"/> Control Signal 80 | <input type="checkbox"/> Robot 25 |
| <input type="checkbox"/> Cornell 78 | <input type="checkbox"/> Rohn 36 |
| <input type="checkbox"/> Cushcraft 79 | <input type="checkbox"/> RP Elec. 68 |
| <input type="checkbox"/> DA Products 68 | <input type="checkbox"/> SBE 18 |
| <input type="checkbox"/> Data Eng. 44 | <input type="checkbox"/> Scelbi 49 |
| <input type="checkbox"/> ECM 66 | <input type="checkbox"/> SEMEX 48 |
| <input type="checkbox"/> Emergency Beacon 28 | <input type="checkbox"/> Sentry 11 |
| <input type="checkbox"/> Erickson 54 | <input type="checkbox"/> Slep 49 |
| <input type="checkbox"/> Freck 49 | <input type="checkbox"/> Solid State 86 |
| <input type="checkbox"/> Gateway 31 | <input type="checkbox"/> Space 78 |
| <input type="checkbox"/> Glade Valley 62 | <input type="checkbox"/> Stahler 66 |
| <input type="checkbox"/> Global 66 | <input type="checkbox"/> Standard 5 |
| <input type="checkbox"/> Godbout 83 | <input type="checkbox"/> Tech. Doc. 58 |
| <input type="checkbox"/> HAL 64 | <input type="checkbox"/> Tri-Tek 20 |
| <input type="checkbox"/> Ham Radio Center 43 | <input type="checkbox"/> Tucker 34,35,67 |
| <input type="checkbox"/> Henry 22,38,56 | <input type="checkbox"/> VHF Eng. 89 |
| <input type="checkbox"/> Hobby Ind. 24 | <input type="checkbox"/> Wilson 19 |
| <input type="checkbox"/> HyGain 84,85 | <input type="checkbox"/> Windjammer 95 |
| <input type="checkbox"/> ICOM 52,53 | <input type="checkbox"/> Wolf 49 |
| <input type="checkbox"/> Int. Electronics 82 | <input type="checkbox"/> World QSL 78 |
| <input type="checkbox"/> Jan 41 | <input type="checkbox"/> Yaesu CIV |
| <input type="checkbox"/> Janel 79 | |

73 STUFF
QSLs CIII

Bookshop 70,71,72
Subs 73

Hotline 69

NEWSSTAND

SUBSCRIPTION

*Reader service inquiries not solicited. Correspond directly to company.

JUNE 1974

Reader's Service
73 Inc., Peterborough NH 03458
Please Print or Type

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

Coupon expires in 60 days

PROPAGATION CHART

J.H. Nelson

Good (open) Fair (□) Poor (O)

June 1974

Sun	Mon	Tue	Wed	Thu	Fri	Sat
						I
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29
30						

EASTERN UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	7	7	7	7	7	7	7	7	7	7	7A
ARGENTINA	14	14	14	7A	7	7	14	14	14	14	14	14A	14
AUSTRALIA	14	14	7A	7B	7	7	7	7	7	7B	14	14	
CANAL ZONE	14	14	14	7	7	7	7A	14	14	14	14	14	
ENGLAND	14	7	7	7	7	7	14	14	14	14	14	14	
HAWAII	14	14	7A	7B	7	7	7	7	7A	14	14	14	
INDIA	7	7B	7B	7B	7B	7B	14	14	14	14	14	14	7A
JAPAN	14	14	7	7	7	7	7	7	7	7	7	7	14
MEXICO	14	14	7A	7	7	7	7	14	14	14	14	14	
PHILIPPINES	14	7	7B	7B	7B	7B	7B	7	7	7	7	7	14
PUERTO RICO	14	7	7	7	7	7	7	7	7A	14	14	14	
SOUTH AFRICA	7	7	3A	7	7B	14	14	14	14	14	7B	7B	
U. S. S. R.	7	7	7	7	7	7	7	7	14	14	14	14	7A
WEST COAST	14	14	7A	7	7	7	7	7	7A	14	14	14	

CENTRAL UNITED STATES TO:

ALASKA	14	14	14	7	7	7	7	7	7	7	7	7	14
ARGENTINA	14	14	14	14	7	7	7A	14	14	14	14A	14	
AUSTRALIA	14	14	14	7A	7	7	7	7	7	7B	14	14	
CANAL ZONE	14	14	14	7	7	7	7	14	14	14	14	14	
ENGLAND	7A	7	7	7	7	7	7	7	7	7A	14	14	
HAWAII	14	14	14	7A	7	7	7	7	7A	14	14	14	
INDIA	7A	7	7	7	7B	7B	7B	7	14	14	14	14	
JAPAN	14	14	14	7	7	7	7	7	7	7	7	7	14
MEXICO	14	14	7	7	7	7	7	7	7	7	14	14	
PHILIPPINES	14	14	14	7B	7B	7B	7B	7	7	7	7	7	14
PUERTO RICO	14	14	14	7	7	7	7	14	14	14	14	14	
SOUTH AFRICA	7	7	3A	7	7B	7B	7B	7A	14	14	7	7	
U. S. S. R.	7	7	7	7	7	7	7	7	7A	7A	7	7	

WESTERN UNITED STATES TO:

ALASKA	14	14	14	7	7	7	7	7	7	7	7	7	7
ARGENTINA	14	14	14	14	7	7	7	7A	14	14	14	14	
AUSTRALIA	21	14A	14A	14	14	7	7	7	7	7B	14	14	
CANAL ZONE	14	14	14	7	7	7	7	14	14	14	14	14	
ENGLAND	7A	7	7	7	7	7	7	7	7	7A	14	14	
HAWAII	14	14A	14A	14	14	7A	7	7	7	14	14	14	
INDIA	14	14	14	7B	7B	7B	7B	7	7	7	7	7	14
JAPAN	14	14	14	14	14	7	7	7	7	14	14	14	
MEXICO	14	14	7	7	7	7	7	7	7	14	14	14	
PHILIPPINES	14	14	14	14	14	7B	7B	7	7	14	14	14	
PUERTO RICO	14	14	14	7	7	7	7	14	14	14	14	14	
SOUTH AFRICA	7	7	3A	7	7B	7B	7B	7B	7A	14	7A	7	
U. S. S. R.	7	7	7	7	7	7	7	7	7A	7	7	7	
EAST COAST	14	14	7A	7	7	7	7	7	7A	14	14	14	

A = Next higher frequency may be useful also.
B = Difficult circuit this period.

ADVANCED
AMATEUR
TECHNOLOGY from



YAESU

YOUR ASSURANCE OF PERFORMANCE
AND QUALITY

JOIN THE ACTION ON 2M FM

THE WORLD'S LEADER IN AMATEUR COMMUNICATIONS
NOW OFFERS YOU "TOTAL SPECTRUM COVERAGE"
FROM 160 THROUGH 2 METERS



SIGMASIZER 200R

200 CHANNEL

SYNTHESIZED 2M FM TRANSCEIVER

*NO CRYSTALS TO BUY. GET TOTAL REPEATER
AND SIMPLEX OPERATION OVER THE ENTIRE
FM BAND

*FEATURES

- Complete 146-148 MHz coverage
- 200 channels in 10 KHz increments
- Selectable ± 600 KHz repeater offset
- Built-in repeater tone burst
- Selectable repeater or simplex operation
- Priority channel provision
- Automatic final protection
- Plus many more exciting features

Amateur Net \$449

Available soon from your dealer



FT-2 AUTO

AUTO-SCAN WITH PRIORITY CHANNEL
2M FM TRANSCEIVER

*AUTOMATIC SCANNING ALLOWS YOU TO
CONTINUOUSLY MONITOR ALL OF YOUR
FAVORITE CHANNELS

*FEATURES

- Automatic scan of all 8 channels
- Hi/Low power: 10 Watts or 1 Watt
- Selectable scan of priority channel
- Individual channel lockout
- Automatic channel lock with mike
- Built-in AC & DC power supplies
- Built-in repeater tone burst
- Complete with three channels,
cables, and microphone

Amateur Net \$379

COMING SOON!

NEW FT-224 23 CHANNEL 2M FM TRANSCEIVER
WITH PRIORITY CHANNEL FEATURE

Watch for price announcement and further information on this new, low cost FM Radio

Prices and specifications subject to change without notice

Full dealer warranty with factory service available for continued after warranty service backup

For further information on these, the complete Yaesu line, and a current dealer list, write:



YAESU MUSEN USA INC.

7625 E. Rosecrans Ave., Unit #29, Paramount, CA. 90723
(213) 633-4007