

# HOME BREW

## 7MHz SSB TRANSCEIVER


The transceiver described here is remarkably simple based on popular communication building block MC1496. It is fairly simple to build because most of the functions are performed by MC1496.

The emphasis during the design of the project was on repeatability, minimum number of switching and ability to modify for multi band operation.

In the beginning I would like to say that none of these circuit ideas are totally original and are taken from various books and magazines.

The circuit uses easily available components. Most of the coils are wound on low cost balun core. The circuit uses a ladder filter. Filter is build around four numbers of 4.43 MHz crystals. I used ladder filter because it is cheap and getting reasonably good reports.

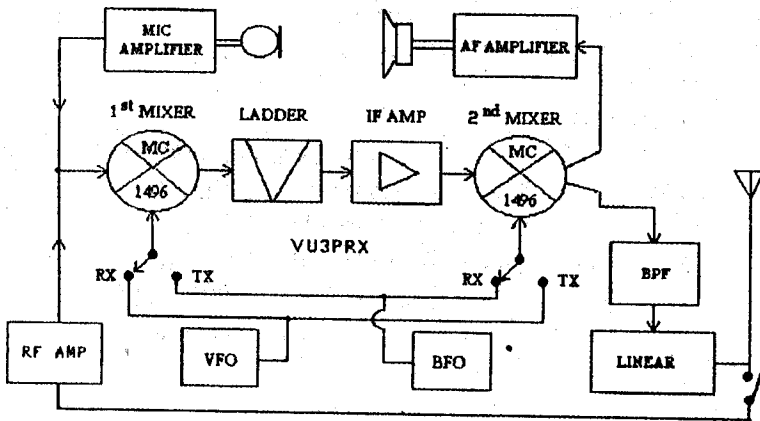The circuit uses two numbers of MC1496. First MC1496 functions as receiver mixer cum balanced modulator. Second MC1496 works as product detector cum transmit mixer. The block diagram of the transceiver is given below.



Presently the circuit is only for 7 MHz SSB operation. It can be modified for other bands by suitably changing VFO, transmit band pass filter and receiver band pass filter. I had avoided CW and AM provision for simplicity. CW and AM can be implemented by making some carrier to leak through balanced modulator. This can be done by offsetting balanced modulator by applying some external voltage to pin 4 of MC1496.

Before you start heating your soldering iron, here is some advice for beginners.

1. Avoid dry soldering- Many of the problems with unsuccessful project are dry soldering. Dry soldering is due to dirt in soldering surface Clean legs of the component and pcb surface before soldering. Use good quality soldering plaster and lead.

2. Before placing components- confirms the value of resistance, legs of transistors; pin configuration of IC. etc.

3. Assemble stage by stage- Never put all the components in the board expecting it will work perfectly when you switch on. It is highly recommended to follow some divide and conquer method. Divide your project into small modules that can be easily assembled and tested. Test each module thoroughly before going for next stage.

### MC1496 DBM

A mixer is a nonlinear element that combines two signals. A mixer has three ports: F1 receives low level signal; F2 is high level signal (local oscillator) and F3 is the resultant mixer product.


The output of the mixer contains number of different frequencies that obey the relationship  $F3 = mF1 + nF2$ . Where m and n are integers 0, 1, 2, 3.....

There are three types of mixers: single-ended, single balanced and double balanced. Double Balanced Mixer (DBM) suppresses F1 and F2 components of the output signal leaving only the sum and difference frequencies. Double Balanced Mixer provides superior suppression of the local oscillator and RF signals in the output leaving only the sum and difference frequencies. This is known as port to port isolation.

MC1496 is an active double balanced mixer made from bipolar silicon transistors formed into Gilbert transconductance cell.

The transceiver is designed around two numbers of MC1496. The first MC1496 performs the function of Receiver mixer and balanced modulator. Second MC1496 works as Product detector cum Transmit mixer.

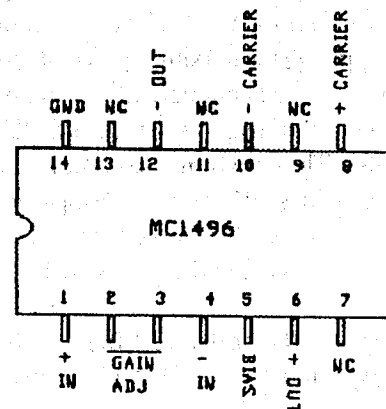MC1496 is available in 14-pin DIP package. Brief descriptions of various pins are given below.



Pin 1 and pin 4 are balanced low-level inputs. Pin 8 and pin 10 are balanced high-level inputs. Pin 6 and pin 12 are outputs. Pin 5 is bias usually connected to Vcc through a resistor (normally 10k). Pin 2 and pin 3 determines gain of the mixer. The gain will be maximum when pin 2 and pin 3 are shorted. Gain can be adjusted by connecting some resistance between pin 2 and pin 3. Pin 7, pin 9, and pin 11 and pin 13 are not used.

DC Voltage measured at various pins of MC1496 given below. There may be slight variation in these voltages due to accuracy of measuring equipment or components used.

PIN	VOLTAGE	PIN	VOLTAGE
1	3.58V	8	6.51V
2	2.96V	9	NC
3	2.91V	10	6.51V
4	3.58V	11	NC
5	1.25V	12	11.8V *
6	11.81V	13	NC
7	NC	14	0V [GND]

**TEST EQUIPMENT'S**

Assembling will be easy if you use proper test equipments. Average hobbyists can't go for sophisticated test equipments. In this project I had used multimeter and RF voltmeter for measurement. Using RF probe you can use multimeter as RF voltmeter. RF probe is essential test equipment for ham shack. It can be used as an FSM also.

To work as RF voltmeter put multimeter in volt range. For FSM I used multimeter in 0.25 ma range and connect a long wire to the probe. If you won't have a multimeter a vu meter can be used.


**WINDING COILS**

Most of the coils used are wound on balun core. They can work up to VHF range, normally used in TV boosters. A single balun core can handle up to 10 Watts. Band pass coils and coils used in IF amplifiers are wound on IFT former. Wind both primary and secondary in the same direction. If the start end of the primary is cold end, the start end of the secondary should also be a cold end.

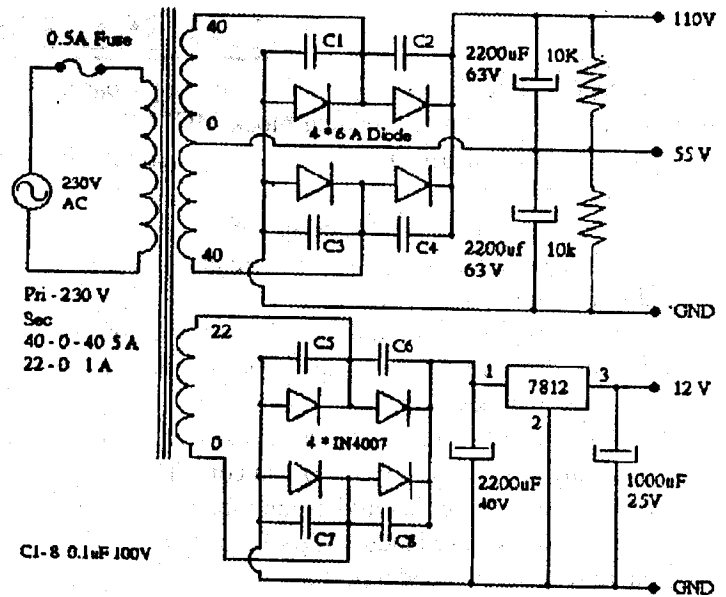**POWER SUPPLY**

The transceiver requires 12 volt for most of the circuitry and 120 V for the final. The power supply should be capable of supplying the maximum current required with good stabilization. I used commercially available 40-0-40 5A transformer. The transformer have 6V, 9V, 12V, and 22V windings also. The transformer cost me around Rs:370. Power supply provides 110 Volt 2.5 Amps or 55 Volt 5 Amps. Three-pin regulator IC is used for regulating 12-volt supply. Good heat sink should be provided for regulator IC.

All diodes in the bridge rectifier are shunted with 0.1 uF 100 V capacitor (C1 to C8) to keep the diode pro-



ected from high voltage transients on the AC line as well as reduce inter-carrier hum modulation of RF that may be picked up by the mains. Always use fuse in 120 V supply line. This can avoid hand full of burned IRF. It also protects the power supply itself. My final consumes around 1 A at peak. I used to 0.5 A fuse; it won't go QRT with 1 A peak current. It is better to use a fuse that can just withstand the peak current.

**LADDER FILTER**

The circuit uses ladder filter builds around 4.43 MHz crystals. I selected 4.43 MHz crystals for the filter because they are cheap and easily available.

By terminating input & output with a 1000E resistor, pass band ripple can be reduced. For R = 1000E and F = 4.43 MHz, the value of C0, C1, C2 are given below.

- C0 = 101 PF (use 100 PF)
- C1 = 65 PF (use 68 PF)
- C2 = 14 PF (use 15 PF)

Ladder filter is assembled on a small PCB. The metal enclosures of all crystals are connected to ground through thick copper wire. For ladder filter you need four crystals and one crystal for carrier oscillator. Collect all crystals of same make and with same serial number.

**AF AMPLIFIER**

The receiver audio amplifier uses popular low noise IC LM386. Operational amplifier IC 741 is used as preamplifier. Both LM386 and 741 are available in 8 pin DIP.

LM386 is designed for operation with power supplies in the 4 V to 15 V range. Quiescent current is about 4 ma. It's input impedance is 50 K. Output automatically centers on a quiescent half supply voltage value. It provides 250 mw to 8 E speaker, which will be sufficient for



I used 2-wire shield wire for connecting microphone. One wire is used for condenser microphone and the other for PTT switch. Shield serves common ground to both.

**LINEAR AMPLIFIER**

The linear amplifier consists of 2N2222, SL100 and BD139. Heat sink should be provided for SL100 and BD139. All coils are wound on balun core. Some of the DC voltages measured are given below. These voltages are measured without any input using digital multimeter.

*DC	Emitter	Base	Collector
2N2222A	2.79 V	4.43V	9.54 V
SL100B	1.078 V	1.69V	12.05 V
BD139	7.5 mV	0.67V	12.01 V

Some of the RF voltages measured are given below. For measuring RF voltage, I had connected a crystal oscillator to input of the linear. These voltages are measured using digital multimeter and RF probe.

*RF	Emitter	Base	Collector
2N2222A	0.44 V	2.3V	0.82 V
SL100B	0.76 V	0.78V	4.87 V
BD139	0.55 V	1.3V	23.0 V

**POWER AMPLIFIER**

In my prototype I used IRF840 in the final. Most of the power FET are designed for high voltage operation. At lower operating voltages they saturate quickly limiting the output power. I had given 120 V for IRF840 it takes 1 Amp at peak. Gate voltage is fixed at 1V. Heavy head sink is essential for IRF. My heat sink measures 30 cm \* 6.5 cm. Use a mica insulator and heat sink compound for fixing IRF. You can directly replace IRF840 with many of the power FET like IRF830, IRF530, IRF540 etc... When using a different IRF, supply voltage should be changed to less than half the maximum drain voltage (Vds). A zener diode rated slightly higher than the twice the supply voltage connected across drain and source can prevent drain source breakdown. Peak to peak gate voltage of magnitude more than 20 Volts can destroy the FET instantaneously. Two numbers of 15 Volt zener diodes are used to keep gate voltage swing below 20 Volts. Specifications for some of IRF series are given below.

FET	POWER	VOLT	CURRENT
IRF530	75 W	100 V	14 Amps
IRF540	125 W	100 V	27 A
IRF830	75 W	500 V	4.5 A
IRF840	125 W	500 V	8 A

**ANTENNA**

Proper antenna is essential for good reception and transmission. Horizontal dipole and Inverted 'V' antenna are popular among hams. I am using horizontal dipole antenna. Horizontal dipole is considered to be a fundamental antenna. Inverted 'V' is a variation of dipole with its center position raised. For inverted 'V' the angle at the center

between the two halves should be between 90 degree to 120 degree for better results. Impedance of horizontal dipole is 70 ohms and a coaxial cable with impedance of 73 ohms like RG59 can be used. The impedance of inverted 'V' is around 50 ohms and a coaxial cable with impedance of 50 ohms like RG58 or RG8 can be used. The length of the dipole is half the wavelength. Any thick copper wire can be used. Cut the wire at the center and connect suitable coaxial cable at the center. For 7.05 MHz the length can be calculated as follows.

\* Horizontal Dipole

$$\text{Length} = 468 / F \text{ (in MHz)}$$

$$= 468 / 7.05 = 66.38 \text{ feet}$$

\* Inverted 'V'

$$\text{Length} = 464 / F \text{ (in MHz)}$$

$$= 464 / 7.05 = 65.81 \text{ feet}$$

**CONCLUSION**

The circuit is for 40 meter band. It can be modified for other bands by making suitable changes in the receiver band pass filter, transmit band pass filter and VFO. I had used 4.43 MHz ladder filter. If you want to use 9 MHz crystal filter or any other filter you need to change IF amplifier frequency, carrier oscillator and VFO. For multi band operation you need to switch VFO and both transmit and receive band pass filters. So go ahead and enjoy home brewing. (For Complete Circuit diagram see pages 15 & 16)

**OPERATING AWARDS**

(ARRL HANDBOOK)

**GERMANY (DL)**



**DLD Award**

The DLD Award is an official award of the German Amateur Radio Club (DARC). It is available to all licensed radio amateurs and shortwave listeners (SWL). The names of new award holders will be published in the DARC magazine *CQ-DL*.


All members of DARC, its associate club VFDB, and club stations of both organizations are issued a *District Location Code* (DOK). To qualify for DLD, applicants must submit QSL cards from licensed radio amateurs showing a certain number of DOKs worked or- for SWLs-heard.

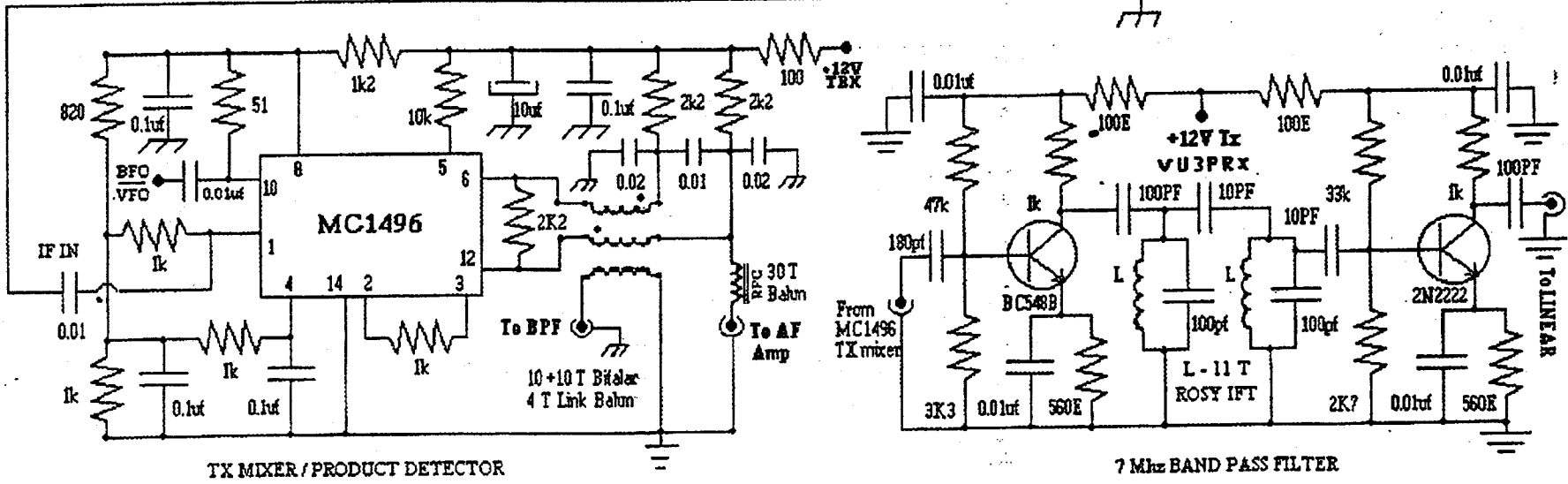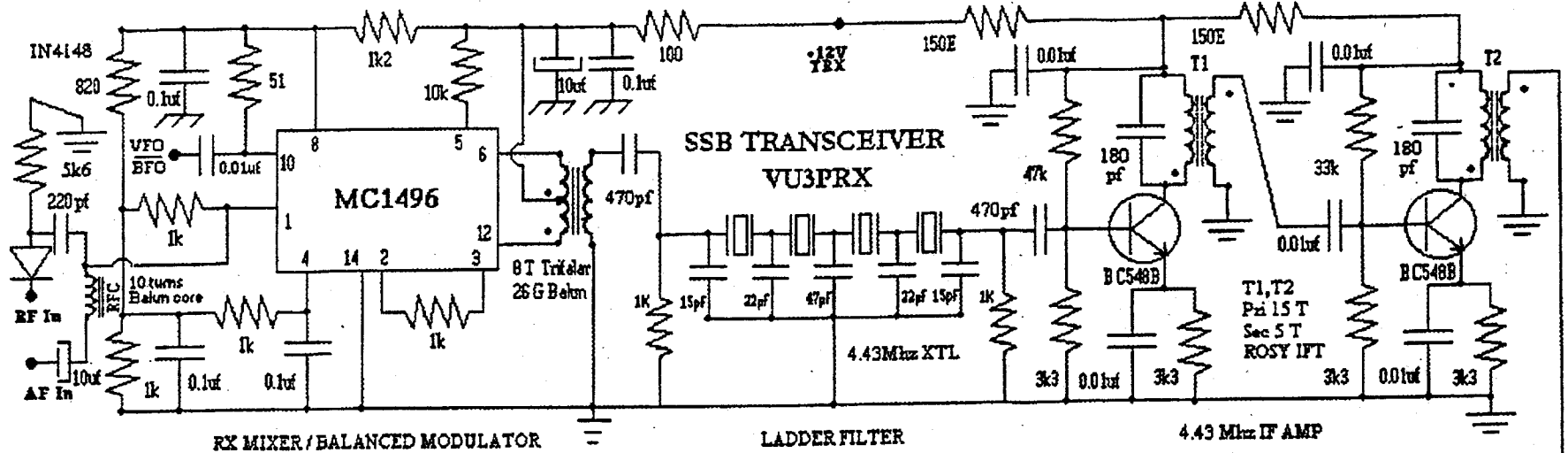**DLD Award Classes and Modes**

- \* DLD is issued separately for each amateur band.
- \* DLD is issued in different classes on each band as follows: DLD 100, DLD 200, DLD 300, DLD 400, DLD 500 (with lapel badge), DLD 600, DLD 700, DLD 800, DLD 900 and DLD 1000 (with engraved badge of honor).
- \* For SWLs, the awards are known as DLD-SWL 100, DLD-SWL 200 and so on up to DLD-SWL 1000.
- \* All DLD Awards may be issued for mixed modes, or may be endorsed for single mode operation, providing that this is supported by QSL cards. (continued on page-20)



15

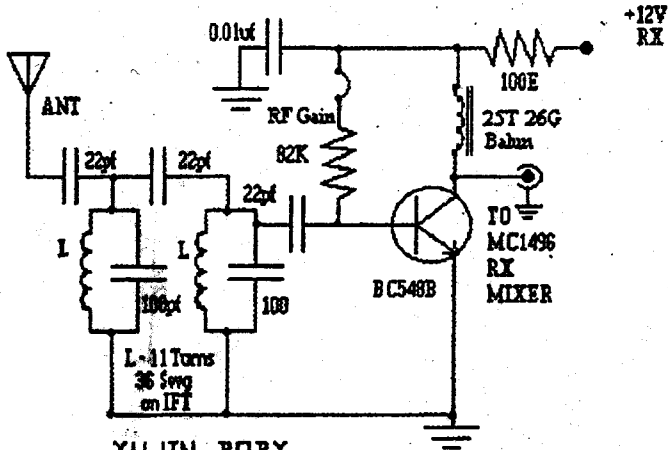

**YUJIN BOBY**  
 Radio VU3PRX  
 KOILPARAMBIL  
 ARTHINKAL PD  
 KERALA - 688 530  
 Ph : 0478-573334

